

Map Layout


	X1'X2'	X1'X2	X1X2	X1X2'
C1'C2'	0	1	3	2
C1'C2	4	5	7	6
C1C2	12	13	15	14
C1C2'	8	9	11	10

Groups

(0,1)	C1'C2'X2
(1,9)	C1'X1'X2
(2,10)	C1'X1X2'
(4,12)	C2X1'X2'
(15)	C1C2X1X2

$$Y = C1'C2'X2 + C1'X1'X2 + C1'X1X2' + C2X1'X2' + C1C2X1X2$$

Implementation using NAND gate

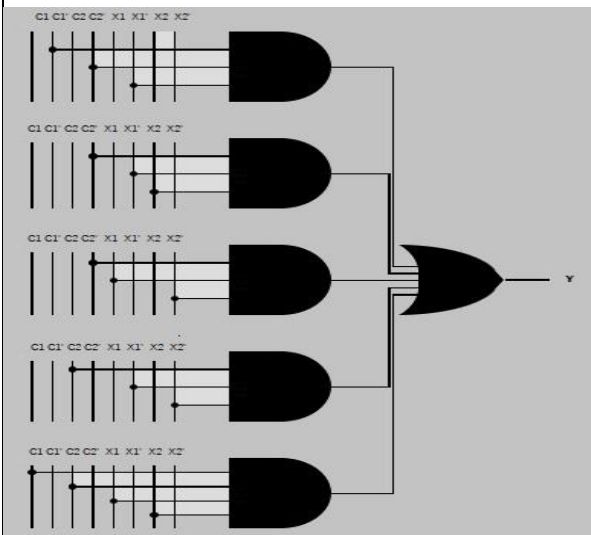

<http://www.32x8.com/var4.html>

2 A Digital system is to be designed in which month of the year is given as input is four bit form. The month January is represented as "0000", February as "0001" and so on. The output of the system is 1 corresponding to the input of the month containing 31 days or otherwise is 0 consider excess number in the input beyond '1011' as don't cares conditions.

- Write truth table ,SOP
- Simplify for SOP using **QM method**
- Realize using Basic Gates

Solution :

Input	First Comparison	Second Comparison
0 m0 0000	(2, 0) 00-0 (4, 0) 0-00	(6, 4, 2, 0) 0-0
1 m2 0010 m4 0100	(6, 2) 0-10 (6, 4) 01-0 (12, 4) -100	(14, 12, 6, 4) -1-0
2 m6 0110 m9 1001 d12 1100	(7, 6) 011- (14, 6) -110 (11, 9) 10-1 (13, 9) 1-01 (13, 12) 110- (14, 12) 11-0	(15, 14, 7, 6) -11- (15, 13, 11, 9) 1-1- (15, 14, 13, 12) 11-
3 m7 0111 m11 1011 d13 1101 d14 1110	(15, 7) -111 (15, 11) 1-11 (15, 13) 11-1 (15, 14) 111-	
4 d15 1111		

[10]

CO2

L2,L3

Prime Implicants

0	1	2	3	4	5
6	7	8	9	10	11
12	13	14	15	16	17
996	997	998	999	1000	1001

Coverage Table

	0-0	1-0	1-1	1-1	1-1
0	x				
2	x				
4	x	x			
6	x	x	x		
7			x		
9				x	
11				x	

Essential Prime Implicants
Using column/row dominance methods.
Tutorial 6
 $AB + BC + AD$

<http://quinemccluskey.com/?min=0%0D%0A2%0D%0A4%0D%0A6+%0D%0A7%0D%0A9%0D%0A11&dont=>

3 (a) Define 1.Implicant 2.Prime Implicant 3.Essential Prime Implicant 4. Selective prime implicant 5.Redundant prime implicant
Solution:

[05] CO2 L1,L2

(b) Design function EX OR gate 1) using NAND gate only 2) using NOR gate only

(e) Ex-OR gate: $Y = A \oplus B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

(e) Ex-NOR gate: $Y = A \odot B = (A \oplus B)'$

0	0	1
0	1	0
1	0	0
1	1	1

[05] CO2 L1,L2

4(a) Using the method of map-entered variables, use four-variable maps to find a minimum sum-of-products expression for $F(A, B, C, D, E) = m(0, 2, 5, 8, 9) + d(6, 10) + E(m7, m12)$ where the m 's represent minterms of the variables $A, B, C,$ and D .

Truth Table

	A	B	C	D	Y
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	X
7	0	1	1	1	E
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	X
11	1	0	1	1	0
12	1	1	0	0	E
13	1	1	0	1	0
14	1	1	1	0	0
15	1	1	1	1	0

Map

	C'D'	C'D	CD	CD'
A'B'	1	0	0	1
A'B	1	1	E	X
AB	E	0	0	0
AB'	1	1	0	X

Map Layout

	C'D'	C'D	CD	CD'
A'B'	0	1	3	2
A'B	4	5	7	6
AB	12	13	15	14
AB'	8	9	11	10

Step 1 : consider 1s and don't cares and E=0

	C'D'	C'D	CD	CD'
A'B'	1	0	0	1

[06]

CO2

L2,L3

A'B	1	1	0	X
AB	0	0	0	0
AB'	1	1	0	X

Groups

(0,2,8,10)	B'D'
(8,9)	AB'C'
(5)	ABC'D

SO $MS1=B'D'+AB'C'+ABC'D$

STEP 2 : consider variable E = 1 and make all 1s don't care and consider all don't care

	C'D'	C'D	CD	CD'
A'B'	X	0	0	X
A'B	X	X	1	X
AB	1	0	0	0
AB'	X	X	0	X

Groups

(5,7)	A'BD
(8,12)	AC'D'

SO $MS2=(A'BD+AC'D')E =A'BDE+AC'D'E$

SO minimum SOP Boolean expression is $=MS1+MS2= B'D'+AB'C'+ABC'D+ A'BDE +AC'D'E$

4(b) What are the benefits of MEV over KM Method.

Solution:

K-map is the best manual technique to solve Boolean equations, but it becomes difficult to manage when number of variables exceed 5 or 6. So, a technique called Variable Entrant Map (VEM) is used to increase the effective size of k-map. It allows a smaller map to handle large number of variables. This is done by writing output in terms of input.

[04]

CO2

L1,L2

5 Consider the following logic function.

$F(A, B, C, D)=m(0, 4, 5, 10, 11, 13, 14, 15)$

(a) Find two different minimum circuits which implement F using AND and OR gates.

Identify two hazards in each circuit

(b) Find an AND-OR circuit for F which has no hazards.(hazard cover)

(c) Find an OR-AND circuit for F which has no hazards. (hazard cover)

Solution :

(a)

Map

	C'D'	C'D	C.D	C.D'
A'B'	1	0	0	0
A'B	1	1	0	0
A.B	0	1	1	1
AB'	0	0	1	1

Map Layout

	C'D'	C'D	C.D	C.D'
--	------	-----	-----	------

[10]

CO2

L3,L2

A'B'	0	1	3	2
A'B	4	5	7	6
A.B	12	13	15	14
AB'	8	9	11	10


Groups

(10,11,14,15)	A.C	
(0,4)	A'.C'.D'	
(5,13)	B.C'.D	
(4,5)	A'BD	STATIC-1 COVER
(15,13)	ABD	STATIC-1 COVER


Minimize SOP expression $Y = AC + A'C'D' + BC'D$

Implement using AND-OR circuit as follows

1.

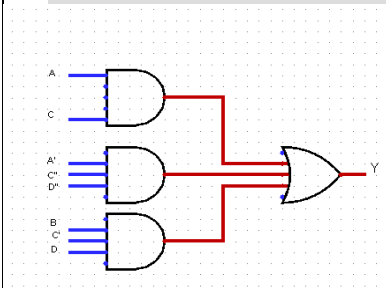

2.

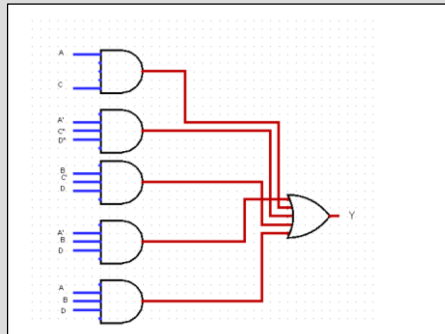

(b) Recover Static -1 in SOP are $= AC + A'C'D' + BC'D + A'BD + ABD$

2.

(a) PRODUCT of SUMS

Map

	C'D'	C'D	C.D	C.D'
A'B'	1	0	0	0
A'B	1	1	0	0
A.B	0	1	1	1
AB'	0	0	1	1

Map Layout

	C'D'	C'D	C.D	C.D'
A'B'	0	1	3	2
A'B	4	5	7	6
A.B	12	13	15	14
AB'	8	9	11	10

Groups

(2,3,6,7)	A.C
-----------	-----

(1,9)	$B'.C'.D$
(8,12)	$A.C'.D'$

$$y = A.C + B'.C'.D + A.C'.D'$$


$$y = A.C + B'.C'.D + A.C'.D'$$

Minimize POS expression $Y = (A + C') (B + C + D') (A' + C + D)$

Implement using OR-AND circuit as follows


1.

2.

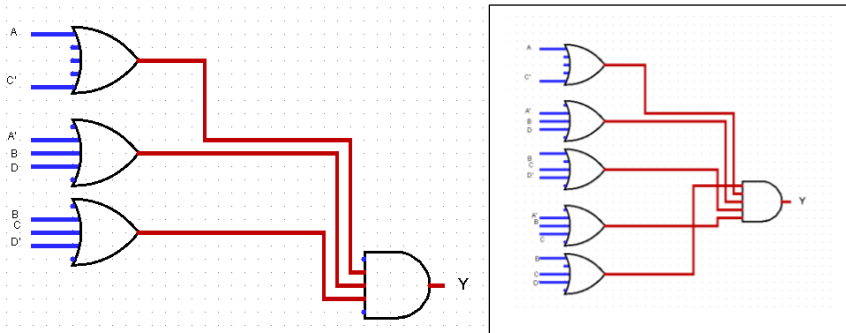

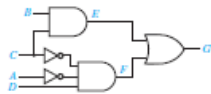2.Recover Static -1 in POS are $(A + C') (B + C + D') (A' + C + D)(A' + B + C)(B + C + D')$

6 What is the use of simulation software? For the following circuit
 (a) Assume that the inverters have a delay of 1 ns and the other gates have a delay of 2 ns. Initially $A = 0$ and $B = C = D = 1$, and C changes to 0 at time =2 ns. Draw a timing diagram and identify the transient that occurs.




(b) Modify the circuit to eliminate the hazard.

Solution :

Simulation is a decision analysis and support tool. Simulation software allows you to evaluate, compare and optimize alternative designs, plans and policies

(a)

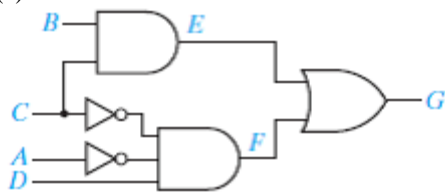

[5+5]

CO2

L1,L2,L3

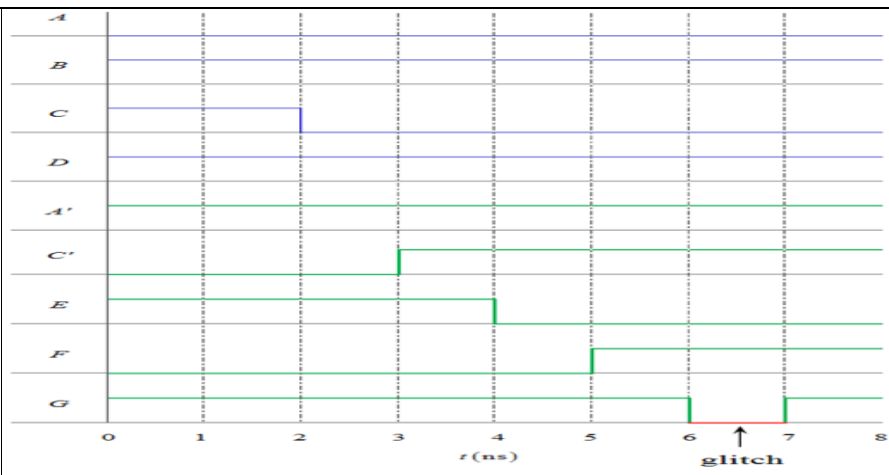


Figure 1

(b) Recover Hazard circuit as below

