

USN

Internal Assessment Test 1 – December 2022

Sub:	Analog and Digital Electronics				Sub Code:	21CS33	Branch:	ISE		
Date:	02/12/2022	Duration:	90 min's	Max Marks:	50	Sem/Sec:	III / A,B and C			OBE
Answer any FIVE FULL Questions								MARKS	CO	RBT
1	With the help of flow chart explain how to determine Minimum Sum of Products using a Karnaugh Map with an Example.						10	CO3	L3	
2	What are the disadvantages of K map? Find the minimum SOP expression using QM method for the following function $f(a, b, c, d) = \sum m(0,1,2,3,10,11,12,13,14,15)$						10	CO3	L3	
3	Minimize the following function for SOP using K map and realize it by using basic gates $f(a,b,c,d) = \pi M(5,7,13,14,15) + d(1,2,3,9)$						10	CO3	L3	
4	Realize basic gates and Ex-Or using NAND and NOR gates only.						10	CO4	L3	
5	What is Hazard? Explain Static 0 and Static 1 hazard with an example and its elimination method.						10	CO4	L2	
6	Implement the following Boolean function using 8:1 Mux $f(a, b, c, d) = \sum m(0,1,2,4,6,9,12,14)$						10	CO3	L3	

Faculty Signature

CCI Signature

HOD Signature

USN

Internal Assessment Test 1 – December 2022

Sub:	Analog and Digital Electronics				Sub Code:	21CS33	Branch:	ISE		
Date:	02/12/2022	Duration:	90 min's	Max Marks:	50	Sem/Sec:	III / A,B and C			OBE
Answer any FIVE FULL Questions								MARKS	CO	RBT
1	With the help of flow chart explain how to determine Minimum Sum of Products using a Karnaugh Map with an Example.						10	CO3	L3	
2	What are the disadvantages of K map? Find the minimum SOP expression using QM method for the following function $f(a, b, c, d) = \sum m(0,1,2,3,10,11,12,13,14,15)$						10	CO3	L3	
3	Minimize the following function for SOP using K map and realize it by using basic gates $f(a,b,c,d) = \pi M(5,7,13,14,15) + d(1,2,3,9)$						10	CO3	L3	
4	Realize basic gates and Ex-Or using NAND and NOR gates only.						10	CO4	L3	
5	What is Hazard? Explain Static 0 and Static 1 hazard with an example and its elimination method.						10	CO4	L2	
6	Implement the following Boolean function using 8:1 Mux $f(a, b, c, d) = \sum m(0,1,2,4,6,9,12,14)$						10	CO3	L3	

Faculty Signature

CCI Signature

HOD Signature




Internal Assessment Test I –December 2022

Sub:	Analog and Digital Electronics			Sub Code:	21CS33	Branch:	ISE
Date:	02/12/2022	Duration:	90 min's	Max Marks:	50	Sem/Sec:	III / A, B and C

Answer any FIVE FULL Questions

MARKS CO RBT

- 1 With the help of flow chart explain how to determine Minimum Sum of Products using a Karnaugh Map with an Example.

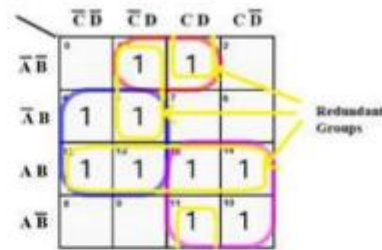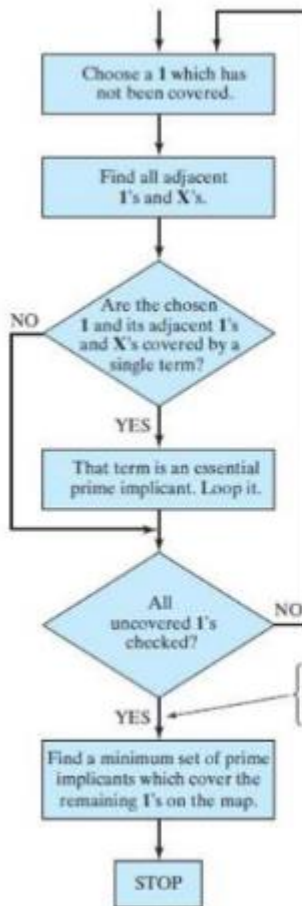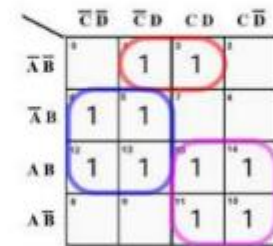Solution:All prime implicants: $A'B'D, BC', AC, A'C'D, AB, B'CD$ Minimum solution: $F = A'B'D + BC' + AC$

- 2 What are the disadvantages of K map? Find the minimum SOP expression using QM method for the following function $f(a, b, c, d) = \sum m(0,1,2,3,10,11,12,13,14,15)$

Solution:

Disadvantages of K map:

The Karnaugh map method is an effective way to simplify switching functions which have a small number of variables. When the number of variables is large or if several functions must be simplified, the use of a digital computer is desirable.

Determination of PI:

10 CO3 L3

Stage 1		Stage 2		Stage 3	
ABCD	minterms	ABCD	minterms	ABCD	minterms
0000	(0)✓	000-	(0,1)✓	00--	(0,1,2,3)
		00-0	(0,2)✓	00--	(0,2,1,3)
0001	(1)✓				
0010	(2)✓	00-1	(1,3)✓	-01-	(2,10,3,11)
		001-	(2,3)✓		
		-010	(2,10)✓	1-1-	(10,11,14,15)
0011	(3)✓			1-1-	(10,14,11,15)
1010	(10)✓	-011	(3,11)✓	11--	(12,13,14,15)
1100	(12)✓	101-	(10,11)✓	11--	(12,14,13,15)
		1-10	(10,14)✓		
		110-	(12,13)✓		
1011	(11)✓	11-0	(12,14)✓		
1101	(13)✓				
1110	(14)✓	1-11	(11,15)✓		
1111	(15)✓	11-1	(13,15)✓		
		111-	(14,15)✓		

Prime implicant charts:

	0	1	2	3	10	11	12	13	14	15
$A'B'$ (0,1,2,3)	✓	✓	✓	✓						
$B'C$ (2,3,10,11)			✓	✓	✓	✓				
AC (10,11,14,15)					✓	✓			✓	✓
AB (12,13,14,15)							✓	✓	✓	✓

$$Y = A'B' + B'C + AB \text{ or } Y = A'B' + AC + AB$$

3 Minimize the following function for SOP using K map and realize it by using basic gates $f(a,b,c,d) = \pi M(5,7,13,14,15) + d(1,2,3,9)$.

Solution:

C D		A B			
		00	01	11	10
00	1	1	1	1*	
01	X	0	0	X	
11	X	0	0	1*	
10	X	1*	0	1*	

$$F = A'D' + B' + C'D'$$

(*) Indicates a minterm that makes the corresponding prime implicant essential.

$$C'D' \rightarrow m_{12}; A'D' \rightarrow m_6; B' \rightarrow m_{10} \text{ or } m_{11}$$

4 Realize basic gates and Ex-Or using NAND and NOR gates only.

Solution:


Ex-Or using NAND

10

CO4


L3

(e) Ex-OR gate: $Y = A \oplus B$


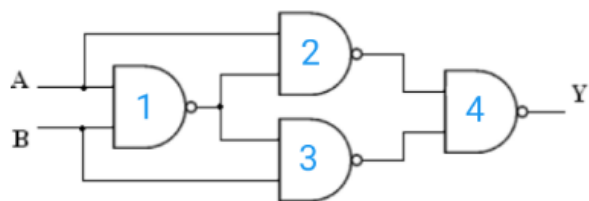


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Ex-Or using NOR

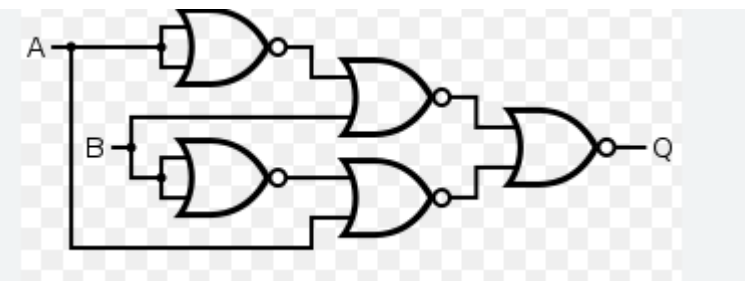

Basic gates using NAND

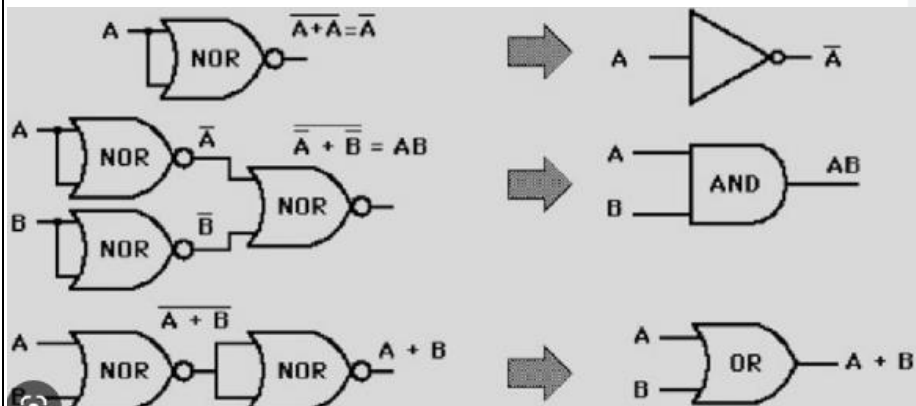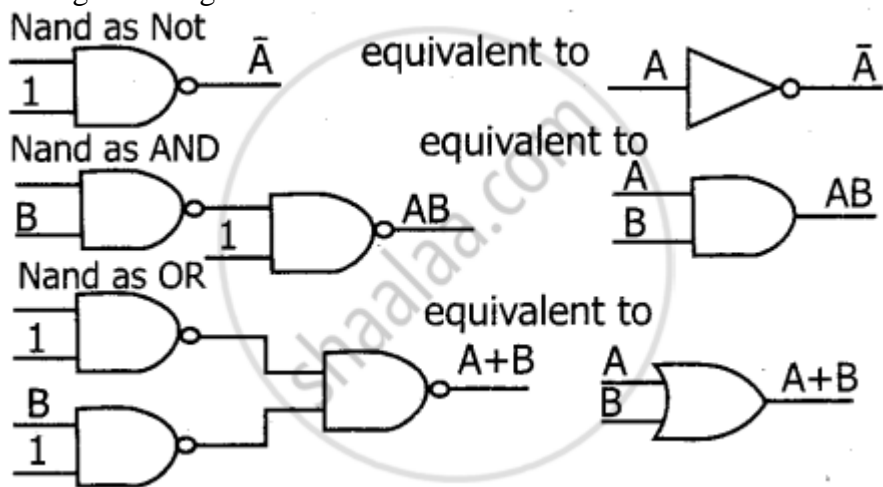

5 What is Hazard? Explain Static 0 and Static 1 hazard with an example and its elimination method.

10


CO4

L2

Solution:

When the input to a combinational circuit changes, unwanted switching transients may appear in the output. These transients occur when different paths from input to output have different propagation delays.

- o If, in response to any single input change and for some combination of propagation delays, a circuit output may momentarily go to 0 when it should remain a constant 1, we say that the circuit has a **static 1-hazard**.
- o Similarly, if the output may momentarily go to 1 when it should remain a 0, we say that the circuit has a **static 0-hazard**.
- o If, when the output is supposed to change from 0 to 1 (or 1 to 0), the output may change three or more times, we say that the circuit has a **dynamic hazard**.

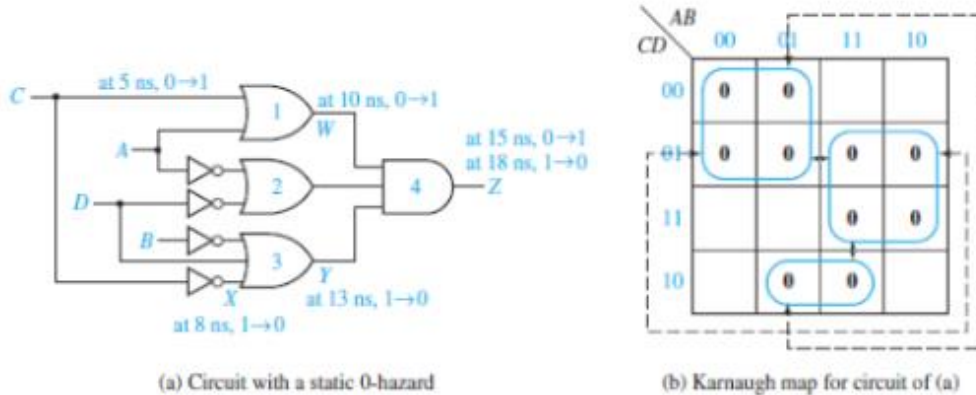


Detection of Static 1 Hazard: Hazards can be detected using a Karnaugh map (see above Figure). As seen on the map, no loop covers both minterms ABC and ABC' . So if $A = C = 1$ and B changes, both terms can momentarily go to 0, resulting in a glitch in F .


We can detect hazards in a two-level AND-OR circuit, using the following procedure:

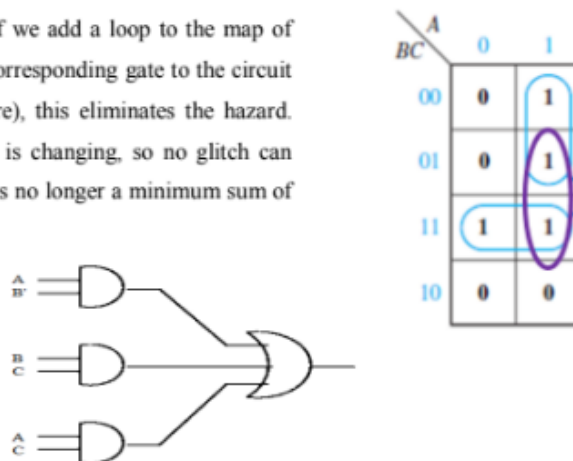1. Write down the sum-of-products expression for the circuit.
2. Plot each term on the map and loop it.
3. If any two adjacent 1's are not covered by the same loop, a 1-hazard exists for the transition between the two 1's. For an n -variable map, this transition occurs when one variable changes and the other $n - 1$ variables are held constant.


To Eliminate Static 1 Hazard: If we add a loop to the map of above Figure and, then, add the corresponding gate to the circuit (as shown in the following Figure), this eliminates the hazard. The term AC remains 1 while B is changing, so no glitch can appear in the output. Note that F is no longer a minimum sum of products.



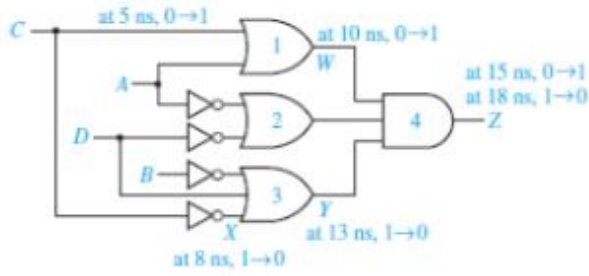Detection of Static 0 Hazard: The following Figure shows a circuit with several 0-hazards. The product-of-sums representation for the circuit output is $F = (A + C)(A' + D')(B' + C' + D)$



(a) Circuit with a static 0-hazard

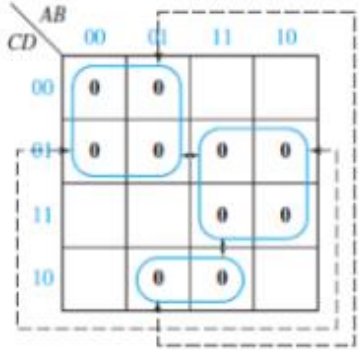

(b) Karnaugh map for circuit of (a)

6 Implement the following Boolean function using 8:1 Mux $f(a, b, c, d) = \sum m(0,1,2,4,6,9,12,14)$

10 CO3 L3

Solution:

