

USN



Internal Assessment Test 2 – December 2022

Sub:	Analog and Digital Electronics				Sub Code:	18CS33	Branch:	ISE		
Date:	27/12/2022	Duration:	90 min's	Max Marks:	50	Sem/Sec:	III / A,B and C			OBE
<b>Answer any FIVE FULL Questions</b>								MARKS	CO	RBT
1	Explain the structure of VHDL Program. Write VHDL Code for 4-bit full subtractor.					10	CO5	L2		
2	Design 7 segment decoder and realize using PLA					10	CO4	L3		
3	Construct and explain SR gate latches using NAND gates and derive the characteristics equation for the same					10	CO4	L2		
4	Differentiate between PAL and PLA. Realize the following functions using PLA. $F(a, b, c, d) = m(1,2,4,5,6, 8,10,12,14)$ and $F(a, b, c, d) = m(1,2,4,6,8,10,11,12,14,15)$					10	CO4	L2		
5	Design full subtractor circuit using decoder and NAND gates					10	CO4	L3		
6	Design 8:1 MUX, using conditional signal assignment statement and selected signal assignment statement.					10	CO4	L3		

Faculty Signature

CCI Signature

HOD Signature

USN



Internal Assessment Test 2 – December 2022

Sub:	Analog and Digital Electronics				Sub Code:	18CS33	Branch:	ISE		
Date:	27/12/2022	Duration:	90 min's	Max Marks:	50	Sem/Sec:	III / A,B and C			OBE
<b>Answer any FIVE FULL Questions</b>								MARKS	CO	RBT
1	Explain the structure of VHDL Program. Write VHDL Code for 4-bit full subtractor.					10	CO5	L2		
2	Design 7 segment decoder and realize using PLA					10	CO4	L3		
3	Construct and explain SR gate latches using NAND gates and derive the characteristics equation for the same					10	CO4	L2		
4	Differentiate between PAL and PLA. Realize the following functions using PLA. $F(a, b, c, d) = m(1,2,4,5,6, 8,10,12,14)$ and $F(a, b, c, d) = m(1,2,4,6,8,10,11,12,14,15)$					10	CO4	L2		
5	Design full subtractor circuit using decoder and NAND gates					10	CO4	L3		
6	Design 8:1 MUX, using conditional signal assignment statement and selected signal assignment statement.					10	CO4	L3		

Faculty Signature


CCI Signature

HOD Signature

USN

**Internal Assessment Test II –December 2022**

Sub:	Analog and Digital Electronics	Sub Code:	21CS33	Branch:	ISE	
Date:	27/12/2022	Duration:	90 min's	Max Marks:	50	
					Sem/Sec:	III / A, B and C
<b>Answer any FIVE FULL Questions</b>						OBE

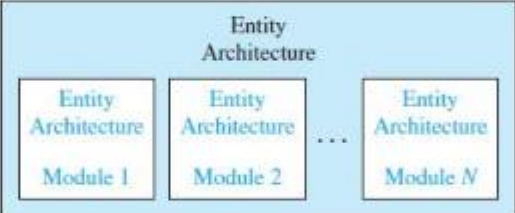		MARKS	CO	RBT
1	<p>Explain the structure of VHDL Program. Write VHDL Code for 4-bit full subtractor.</p> <p><b>Solution:</b></p> <pre> <b>entity</b> entity-name <b>is</b>   [<b>port</b>(interface-signal-declaration);] <b>end</b> [<b>entity</b>] [entity-name];           </pre> <p>The items enclosed in square brackets are optional. The interface-signal-declaration normally has the following form:</p> <pre> list-of-interface-signals: mode type [: _ initial-value] {; list-of-interface-signals: mode type [: _ initial-value]};           </pre> <div style="text-align: center;"> <p><b>FIGURE 10-9</b> VHDL Program Structure</p>  </div> <p>The curly brackets indicate zero or more repetitions of the enclosed clause. Input signals are of mode <b>in</b>, output signals are of mode <b>out</b>, and bi-directional signals are of mode <b>inout</b>.</p> <p>Associated with each entity is one or more architecture declarations of the form</p> <pre> <b>architecture</b> architecture-name <b>of</b> entity-name <b>is</b>   [declarations] <b>begin</b>   architecture body <b>end</b> [<b>architecture</b>] [architecture-name];           </pre> <pre> entity half_sub is port ( a,b : in std_logic;       dif,bo: out std_logic ); end half_sub;  architecture sub_arch of half_sub is begin     dif &lt;= a xor b;     bo &lt;= (not a) and b; end sub_arch;           </pre>	10	CO5	L2

2 Design 7 segment decoder and realize using PLA


10

CO4

L3

**Solution:**

A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

 

3 Construct and explain SR gate latches using NAND gates and derive the characteristics equation for the same.


6

CO4

L2

 **Solution:**

In the SR flip flop we will use the SR latch using NAND gate and two extra NAND gate will be used which are G3 and G4. The input to G3 and G4 will be S and R respectively and clock signal is applied to both gates which will be train of pulses.



$Q_n$	$S_n$	$R_n$	$Q_{n-1}$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	x
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	x

$Q_n S_n$	00	01	11	10
$R_n$				
0	0	1	1	1
1	0	X	X	0

Where X represents don't pair in the K-map table. We will make two group in which one group will consists of four element while other group consist of two elements.  
 For the first group above 1 is common which means  $S_n$  and in the second group again 1 is common which represents  $Q_n$  and as it is in the first row so  $R_n$  will be 0.  
 $Q_{(n+1)} = S_n + Q_n (R_n)^-$   
 So this is the procedure with the help of which we can draw the characteristics equation of the flip flop.

4 Differentiate between PAL and PLA. Realize the following functions using PLA.  
 $F(a, b, c, d) = m(1,2,4,5,6, 8,10,12,14)$  and  $F(a, b, c, d) = m(1,2,4,6,8,10,11,12,14,15)$

10 CO4 L2


**Solution:**


**Programmable Logic Arrays (PLA):**

A PLA with  $n$  inputs and  $m$  outputs can realize  $m$  functions of  $n$  variables. In PLA, the product terms of the input variables is realized by an AND array; and the OR array ORs together the product terms needed to form the output functions. Hence, a PLA implements a sum-of-products expression.

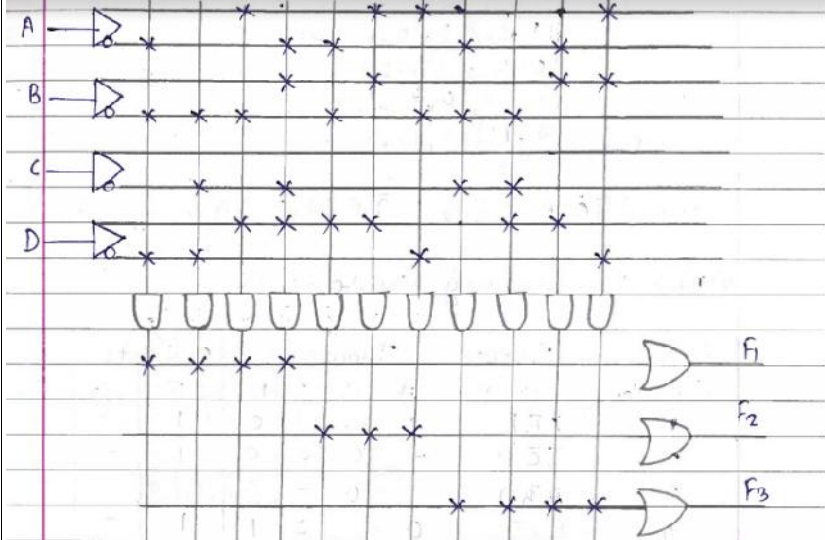**Programmable Array Logic (PAL):**

A PAL is a special case of the programmable logic array (PLA) in which the AND array is programmable and the OR array is fixed. The following Figure represents a segment of an un-programmed PAL.



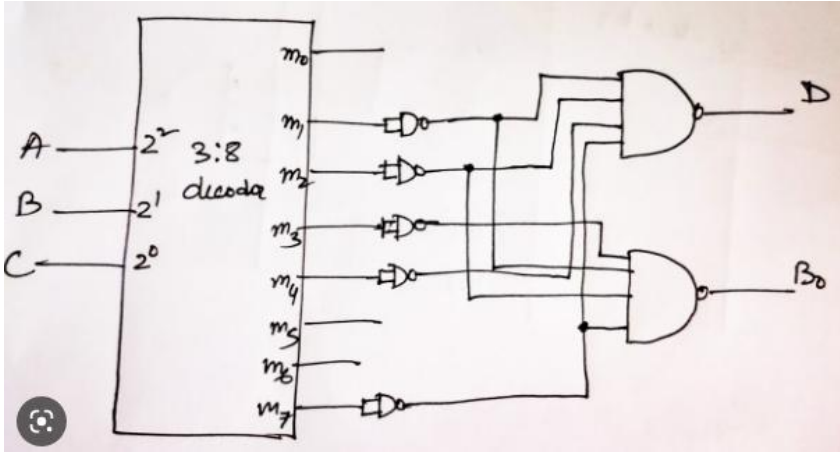5	<p>Design full subtractor circuit using decoder and NAND gates.</p> <p><b>Solution:</b></p> 	10	CO4	L3
6	<p>Design 8:1 MUX, using conditional signal assignment statement and selected signal assignment statement.</p> <p><b>Solution:</b></p> <p><u>conditional signal assignment statement</u></p> <pre> library ieee; use ieee.std_logic_1164.all;  entity demux_1x8 is port (i : in std_logic;       s : in std_logic_vector (0 to 2);       o : out std_logic_vector (0 to 7)); end demux_1x8;  architecture demux_arch of demux_1x8 is begin process (i,s) begin o &lt;= "00000000"; case s is when "000" =&gt; o(0) &lt;= i; when "001" =&gt; o(1) &lt;= i; when "010" =&gt; o(2) &lt;= i; when "011" =&gt; o(3) &lt;= i; when "100" =&gt; o(4) &lt;= i; when "101" =&gt; o(5) &lt;= i; when "110" =&gt; o(6) &lt;= i; when "111" =&gt; o(7) &lt;= i; when others =&gt; o &lt;= "00000000"; end case; end process; end demux_arch; </pre> <p><u>selected signal assignment statement.</u></p> <p>Entity mux ;</p> <p>Port (S0: in STD_LOGIC;</p> <p>S1 :in STD_LOGIC;</p> <p>S2 :in STD_LOGIC;</p> <p>IN0 :in STD_LOGIC;</p> <p>IN1 :in STD_LOGIC;</p> <p>IN2 :in STD_LOGIC;</p> <p>IN3 :in STD_LOGIC;</p> <p>IN4 :in STD_LOGIC;</p>	10	CO4	L3

```
IN5 :in STD_LOGIC;  
IN6 :in STD_LOGIC;  
IN7 :in STD_LOGIC;  
Y :out STD_LOGIC );  
End mux ;
```

Architecture behavioral of mux is

Signal a0,a1,a2,a3,a4,a5,a6,a7:BIT;

begin

a0 <= IN0 and (not s0) and (not s1) and (not s2);

a1 <= IN1 and (not s0) and (not s1) and s2;

a2 <= IN2 and (not s0) and s1 and (not s2);

a3 <= IN3 and (not s0) and s1 and s2;

a4 <= IN4 and s0 and (not s1) and (not s2);

a5 <= IN5 and s0 and (not s1) and s2;

a6 <= IN6 and s0 and s1 and (not s2);

a7 <= IN7 and s0 and s1 and s2;

Y <= a0 or a1 or a2 or a3 or a4 or a5 or a6 or a7

end behavioral;