

Internal Assessment Test - I

Sub:	Power System Analysis II	Code:	18EE71
Date:	20/10/2022	Duration:	90 mins
		Max Marks:	50
		Sem:	7
		Branch:	EEE

Answer Any FIVE FULL Questions. Each question carry 10 marks

	Marks	OBE																																																								
		CO	RBT																																																							
1a	Derive an expression for obtaining the $Y_{bus}$ using singular transformation method	[5]	CO1	L2																																																						
1b	Explain briefly about the primitive network. Obtain the impedance and admittance form of primitive network.	[5]	CO2	L2																																																						
2	With the help of singular transformation method, determine the bus admittance matrix $Y_{bus}$ for the power system whose oriented graph is shown in fig.1 Element no and self impedance of the elements in pu are marked on the diagram. Neglect mutual coupling .Verify the same using direct inspection method.	[10]	CO1	L3																																																						
Fig.1																																																										
3a	The bus incidence matrix A for a network of 8 elements and 5 nodes is as given below. Reconstruct the oriented graph. Hence obtain the one line diagram of the system indicating the generator positions.	[5+5]	CO1	L3																																																						
A=																																																										
<table border="1" style="width: 100%; border-collapse: collapse; text-align: center;"> <thead> <tr> <th style="text-align: left;">Elements ▶</th> <th>1</th> <th>2</th> <th>3</th> <th>4</th> <th>5</th> <th>6</th> <th>7</th> <th>8</th> </tr> </thead> <tbody> <tr> <th style="text-align: left;">Nodes ▼</th> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> </tr> <tr> <th>1</th> <td>1</td> <td>0</td> <td>0</td> <td>0</td> <td>-1</td> <td>0</td> <td>-1</td> <td>0</td> </tr> <tr> <th>2</th> <td>0</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> <td>-1</td> <td>0</td> <td>-1</td> </tr> <tr> <th>3</th> <td>0</td> <td>0</td> <td>1</td> <td>-1</td> <td>0</td> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <th>4</th> <td>0</td> <td>0</td> <td>0</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> </tbody> </table>					Elements ▶	1	2	3	4	5	6	7	8	Nodes ▼									1	1	0	0	0	-1	0	-1	0	2	0	1	0	0	1	-1	0	-1	3	0	0	1	-1	0	1	0	0	4	0	0	0	1	0	0	1	1
Elements ▶	1	2	3	4	5	6	7	8																																																		
Nodes ▼																																																										
1	1	0	0	0	-1	0	-1	0																																																		
2	0	1	0	0	1	-1	0	-1																																																		
3	0	0	1	-1	0	1	0	0																																																		
4	0	0	0	1	0	0	1	1																																																		

3b Consider three passive elements whose data is given in table below. Form the primitive admittance matrix

Element No		
	Self Impedance in pu	Mutual impedance in pu
1	$j0.6$	
2	$j0.5$	$j0.2(\text{element 1})$
3	$j0.7$	

4 For the power system shown in fig.2, Obtain  $Y_{bus}$  using singular transformation method. Verify the obtained  $Y_{bus}$  by inspection method. Line impedance and shunt admittance values are marked in the diagram.

[10] CO1 L3

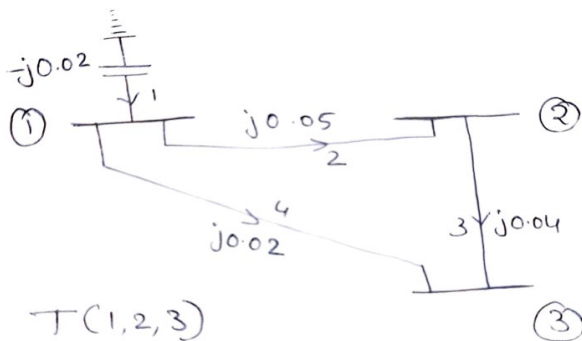


Fig.2

5 Obtain the oriented graph for the system shown in fig.3. Select  $T(1,2,3,4)$  as the tree. Show that  $B_l = A_l K^t$

[10] CO1 L4

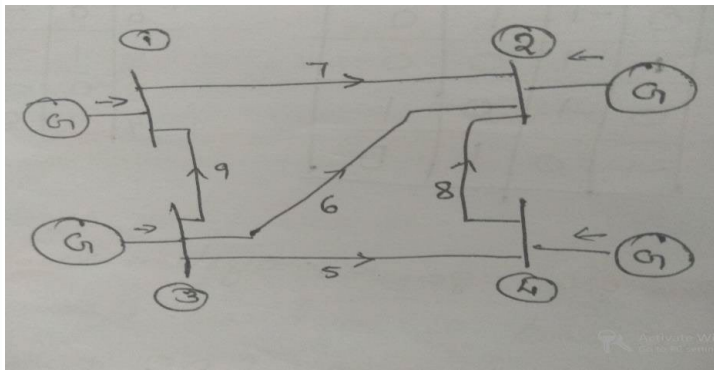


Fig.3

6 For the power system shown in fig.4, choose node 1 as reference &  $T(1,2,3)$  as tree and verify the following relations : 1)  $A_b K^t = U$  2)  $B_l = A_l K^t$

[10] CO1 L4

CO1	L3
CO1	L3
CO1	L4
CO1	L4

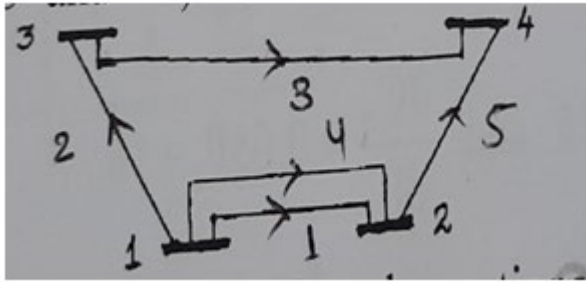


Fig.4

Solutions

1a

Singular Transformation method

The performance equation of the primitive network

$$\bar{i} + \bar{j} = [y] \bar{v}$$

Multiplying by  $A^t$

$$A^t \bar{i} + A^t \bar{j} = A^t [y] \bar{v}$$

According to Kirchhoff's law the algebraic sum of the current at a bus is zero then

$$A^t \bar{i} = 0$$

$A^t \bar{j}$  is the algebraic sum of the source current at each bus and equals the vector of impressed bus currents

$$I_{bus} = A^t \bar{j} \quad \text{--- (1)}$$

$$I_{bus} = A^t [y] \bar{v} \quad \text{--- (2)}$$

We know that  $(\mathbf{I}_{bus}^*)^t E_{bus}$  is the power into the network.

Sum of the powers in the primitive network

$$(\mathbf{I}_{bus}^*)^t E_{bus} = (\mathbf{j}^*)^t \bar{e} \quad \text{--- (2)}$$

Taking the conjugate of  $(\mathbf{I}_{bus}^*)^t$  <sup>transpose</sup>

$$(\mathbf{I}_{bus}^*)^t = (\mathbf{j}^*)^t \cdot \mathbf{A}^*$$

Since  $\mathbf{A}$  is a real matrix  $\mathbf{A}^* = \mathbf{A}$

$$(a) (\mathbf{I}_{bus}^*)^t = (\mathbf{j}^*)^t \cdot \mathbf{A}$$

$$(b) (\mathbf{I}_{bus}^*)^t = (\mathbf{j}^*)^t \cdot \mathbf{A}$$

Substituting this in (2)

$$(j\omega)^t A \cdot \bar{E}_{bus} = (j\omega)^t \bar{V}$$

$$(a) \bar{V} = A \cdot \bar{E}_{bus}$$

Substituting in (3)

$$(a) \bar{I}_{bus} = A^t \cdot [Y] \cdot \bar{V}$$

$$\bar{I}_{bus} = A^t \cdot [Y] \cdot A \cdot \bar{E}_{bus}$$

$$(a) \bar{I}_{bus} = Y_{bus} \cdot \bar{E}_{bus}$$

$$(a) Y_{bus} = A^t \cdot [Y] \cdot A$$

(a)  $A^t \cdot [Y] \cdot A$  is the singular transformation of  $[Y]$



## Primitive network

Network components represented both in impedance form and in admittance form.

$V_{pq}$  is the voltage across the element P-Q

$E_p$  is the source voltage in series with P-Q

$i_{pq}$  is the current through element P-Q

$j_{pq}$  is the source current in parallel with element P-Q

$Z_{pq}$  is the self impedance of element P-Q


$Y_{pq}$  is the self admittance of element P-Q.

Performance equation of an element in impedance form


$$V_{pq} + E_{pq} = Z_{pq} i_{pq}$$

admittance form is

$$i_{pq} + j_{pq} = Y_{pq} V_{pq}$$

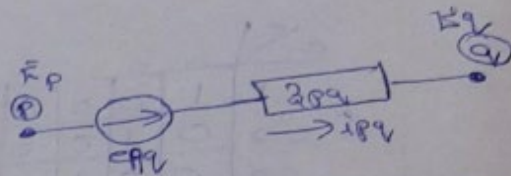

Impedance form

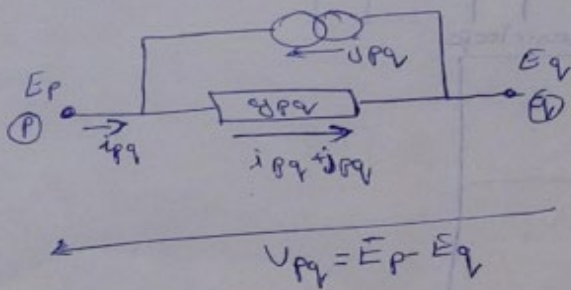

$$V_{pq} + E_{pq} = Z_{pq} i_{pq}$$

$$i_{pq} + j_{pq} = Y_{pq} V_{pq}$$

$$i_{pq} + j_{pq} = y_{pq} v_{pq}$$

$$v_{pq} + e_{pq} = z_{pq} i_{pq}$$

$$\frac{i_{pq} + j_{pq} + e_{pq}}{y_{pq}} = z_{pq} i_{pq}$$

$$i_{pq} + j_{pq} + e_{pq} y_{pq} = i_{pq} z_{pq} y_{pq} \quad | \quad z_{pq} y_{pq} = 1$$

$$j_{pq} = -y_{pq} e_{pq}$$

Parallel source current in admittance form is related to series source voltage in impedance form by

$$j_{pq} = -y_{pq} e_{pq}$$


A set of unconnected elements is defined as Primitive network. The performance equation in impedances is

$$\bar{v} + \bar{e} = [z] \bar{i}$$

$$\text{Admittance form } \bar{i} + \bar{j} = [y] \bar{v}$$

Singular Transformation method.

(b)  
2b

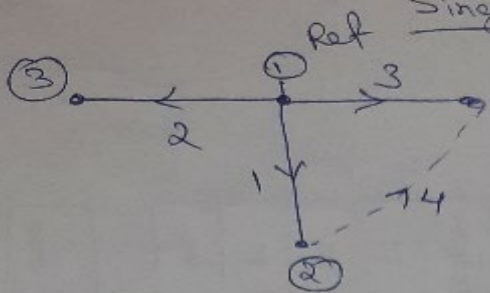

$$Y_{bus} = A^T [Y] A$$

$$A = \begin{array}{c|ccc} & 2 & 3 & 4 \\ \hline 1 & -1 & 0 & 0 \\ 2 & 0 & -1 & 0 \\ 3 & 0 & 0 & -1 \\ 4 & 1 & 0 & -1 \end{array}$$

$$A^T = \begin{bmatrix} -1 & 0 & 0 & 1 \\ 0 & -1 & 0 & 0 \\ 0 & 0 & -1 & -1 \end{bmatrix}$$

$$[Y] = \begin{array}{c|cccc} & 1 & 2 & 3 & 4 \\ \hline 1 & \cancel{j0.33} & 0 & 0 & 0 \\ 2 & 0 & \cancel{j0.1} & 0 & 0 \\ 3 & 0 & 0 & \cancel{j0.2} & 0 \\ 4 & 0 & 0 & 0 & \cancel{j0.5} \end{array}$$

$$Y_{bus} = A^T [Y] A$$


$$= \begin{bmatrix} -1 & 0 & 0 & 1 \\ 0 & -1 & 0 & 0 \\ 0 & 0 & -1 & -1 \end{bmatrix} \begin{bmatrix} \cancel{j0.33} & 0 & 0 & 0 \\ 0 & \cancel{j0.1} & 0 & 0 \\ 0 & 0 & \cancel{j0.2} & 0 \\ 0 & 0 & 0 & \cancel{j0.5} \end{bmatrix} \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 0 & -1 \\ 1 & 0 & -1 \end{bmatrix}$$

$$= \begin{bmatrix} j0.85 & 0 & -j0.5 \\ 0 & j0.1 & 0 \\ -j0.5 & 0 & j0.7 \end{bmatrix}$$

$$= \begin{bmatrix} -j5.03 & 0 & j2 \\ 0 & -j10 & 0 \\ j2 & 0 & j7 \end{bmatrix}$$



Verify using inspection method

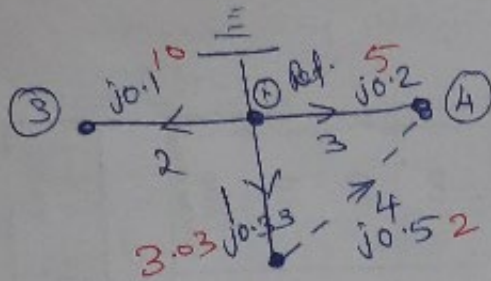

$$Y_{bus} = \begin{matrix} & \begin{matrix} \textcircled{2} & \textcircled{3} & \textcircled{4} \end{matrix} \\ \begin{matrix} \textcircled{2} \\ \textcircled{3} \\ \textcircled{4} \end{matrix} & \begin{bmatrix} j0.83 & 0 & -j0.5 \\ 0 & j0.1 & 0 \\ -j0.5 & 0 & j0.7 \end{bmatrix} \end{matrix}$$


$$= \begin{bmatrix} \textcircled{2} & \textcircled{3} & \textcircled{4} \\ -j5.03 & 0 & +j2 \\ 0 & j10 & 0 \\ +j2 & 0 & -j7 \end{bmatrix}$$

3a

The bus incidence matrix. A power network of 2-ohm and 5 nodes (4-buses) is as given below. Re construct the oriented graph. Hence obtain the one line diagram of the system indicating the generator positions.

$A =$

	1	2	3	4	5	6	7	8
1	1	0	0	0	-1	0	-1	0
2	0	1	0	0	1	-1	0	-1
3	0	0	1	-1	0	1	0	0
4	0	0	0	1	0	0	1	1

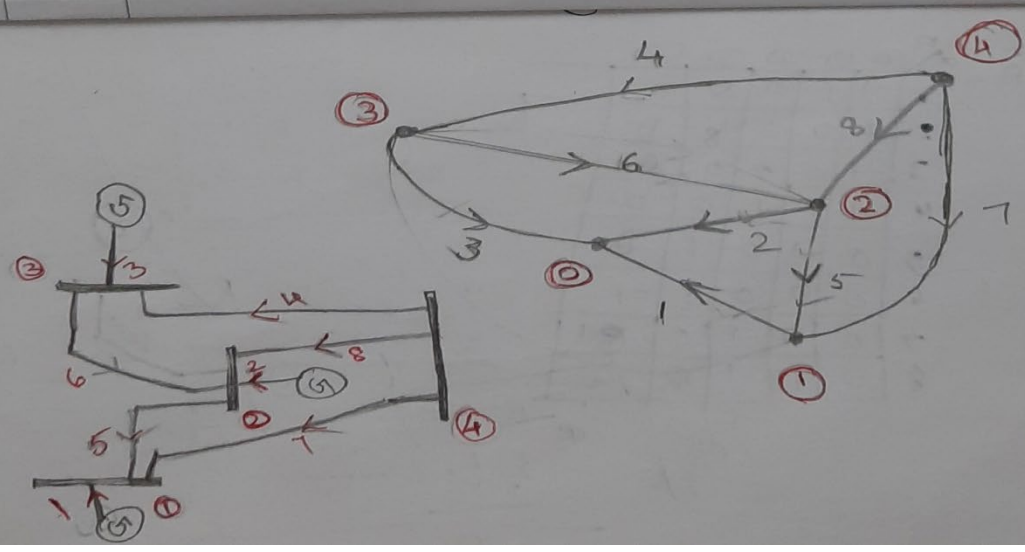


3b

Consider three passive elements whose data is given in table 2.1. Form the primitive impedance matrix.

element	$Z_k(\text{pu})$	Mutual impedance
1	$j0.6$	...
2	$j0.5$	$j0.2$ (element 1)
3	$j0.7$	.

$$[Z] = \begin{bmatrix} j0.6 & j0.2 & 0 \\ j0.2 & j0.5 & 0 \\ 0 & 0 & j0.7 \end{bmatrix}$$
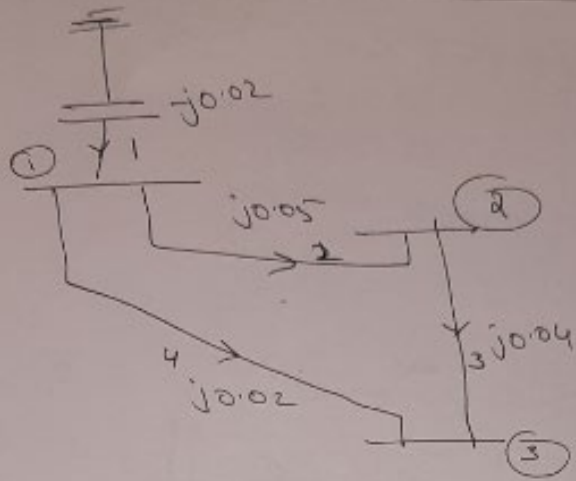
$$y = [Z]^{-1} = \begin{bmatrix} -j1.923 & j0.7692 & 0 \\ j0.7692 & -j2.3077 & 0 \\ 0 & 0 & -j1.4286 \end{bmatrix}$$



$$\textcircled{1} \frac{1}{j0.05} = -j20$$

$$\textcircled{3} \frac{1}{j0.04} = -j25$$

$$\textcircled{4} \frac{1}{j0.02} = -j50$$

$$\begin{bmatrix} -j70.02 & j20 & +j50 \\ j20 & -j45 & +j25 \\ j50 & j25 & -j75 \end{bmatrix}$$

$$A = \begin{array}{c|ccc} & \textcircled{1} & \textcircled{2} & \textcircled{3} \\ \hline 1 & -1 & 0 & 0 \\ \hline 2 & 1 & -1 & 0 \\ \hline 3 & 0 & 1 & -1 \\ \hline 4 & 1 & 0 & -1 \end{array}$$

$$[Y] = \begin{bmatrix} -j0.02 & 0 & 0 & 0 \\ 0 & -j20 & 0 & 0 \\ 0 & 0 & -j25 & 0 \\ 0 & 0 & 0 & -j50 \end{bmatrix}$$

$$\begin{pmatrix} 1 & -1 & 0 & -1 \\ 0 & -1 & -1 & 0 \\ 0 & 0 & -1 & -1 \end{pmatrix} \begin{pmatrix} \times & \times & \times & \times \\ \times & \times & \times & \times \\ \times & \times & \times & \times \\ \times & \times & \times & \times \end{pmatrix} \begin{pmatrix} -j0.02 & 0 & 0 & 0 \\ 0 & -j20 & 0 & 0 \\ 0 & 0 & -j25 & 0 \\ 0 & 0 & 0 & -j50 \end{pmatrix}$$


~~$$j0.02$$~~

$$\begin{pmatrix} j0.02 & -j20 & 0 & -j50 \\ 0 & j20 & -j25 & 0 \\ 0 & 0 & j25 & j50 \end{pmatrix} \begin{pmatrix} -1 & 0 & 0 \\ 1 & -1 & 0 \\ 0 & 1 & -1 \\ 1 & 0 & -1 \end{pmatrix}$$


$$\begin{pmatrix} -j70.02 & j20 & j50 \\ j20 & -j45 = j25 & \\ j50 & j25 & -j75 \end{pmatrix}$$




Oriented graph

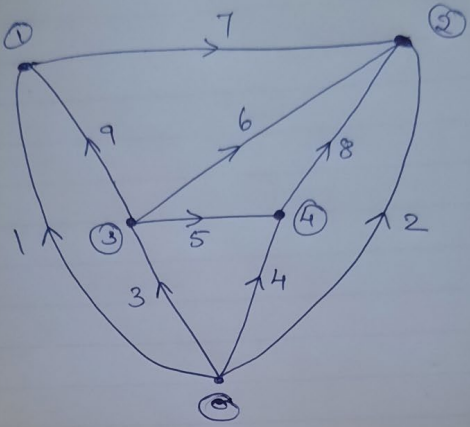


Tree:  $T(1,2,3,4)$

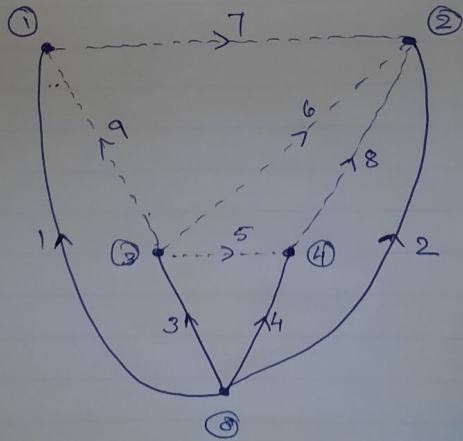

Basic loops

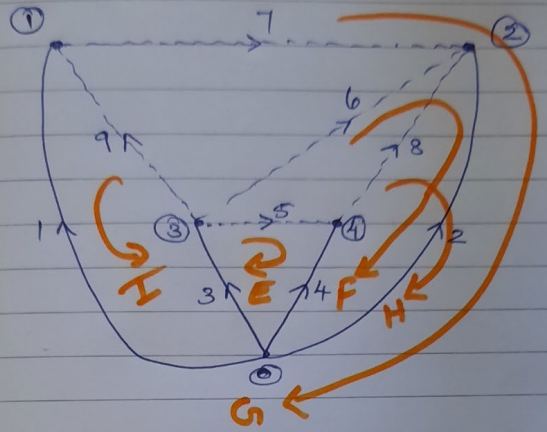

Basic cutsets

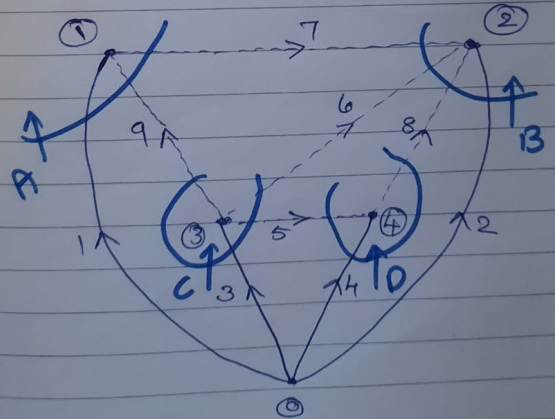

$\vec{A} =$

$c^T$	①	②	③	④	⑤
1	1	-1	0	0	0
2	1	0	-1	0	0
3	1	0	0	-1	0
4	1	0	0	0	-1
5	0	0	0	1	-1
6	0	0	-1	1	0
7	0	0	-1	0	0
8	0	0	-1	0	1
9	0	-1	0	1	0

$D =$

$e^{bw}$	①	②	③	④
1	-1	0	0	0
2	0	-1	0	0
3	0	0	-1	0
4	0	0	0	-1
5	0	0	1	-1
6	0	-1	1	0
7	1	-1	0	0
8	0	-1	0	1
9	-1	0	1	0

$$D_D = \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{pmatrix}$$

~~$$0 \quad 0 \quad 0 \quad 0$$~~
~~$$0 \quad 0 \quad 0 \quad 0$$~~

$$K = \begin{matrix} & \textcircled{1} & \textcircled{2} & \textcircled{3} & \textcircled{4} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \end{matrix} & \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{pmatrix} \end{matrix}$$

$$D_{D^{T^T}} = \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{pmatrix} \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{pmatrix}$$

$$= \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{pmatrix} = I_4$$

$$B = \begin{matrix} & 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 & 9 \\ \begin{matrix} A \\ B \\ C \\ D \\ E \\ F \\ G \\ H \\ I \end{matrix} & \begin{pmatrix} - & 0 & 0 & 0 & 0 & 0 & 1 & 0 & - \\ 0 & - & 0 & 0 & 0 & 0 & - & - & 0 \\ 0 & 0 & - & 0 & 0 & 1 & 0 & 0 & 1 \\ 0 & 0 & 0 & - & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & - & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{pmatrix} \end{matrix}$$

$C_D$   
 $B_D$

$$B_q = A_q \cdot K^t = \begin{bmatrix} 0 & 0 & -1 & -1 \\ 0 & 1 & -1 & 0 \\ -1 & 1 & 0 & 0 \\ 0 & 1 & 0 & -1 \\ 1 & 0 & -1 & 0 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 1 & -1 \\ 0 & -1 & -1 & 0 \\ -1 & -1 & 0 & 0 \\ 1 & 0 & -1 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}$$


6

		(2)	(3)	(4)	
A =	1	-1	0	0	} A <sub>b</sub>
	2	0	-1	0	
	3	0	1	-1	
	4	-1	0	0	} A <sub>d</sub>
	5	1	0	-1	

$K =$

$b$	②	③	④
1	-1	0	0
2	0	-1	-1
3	0	0	-1

Tree

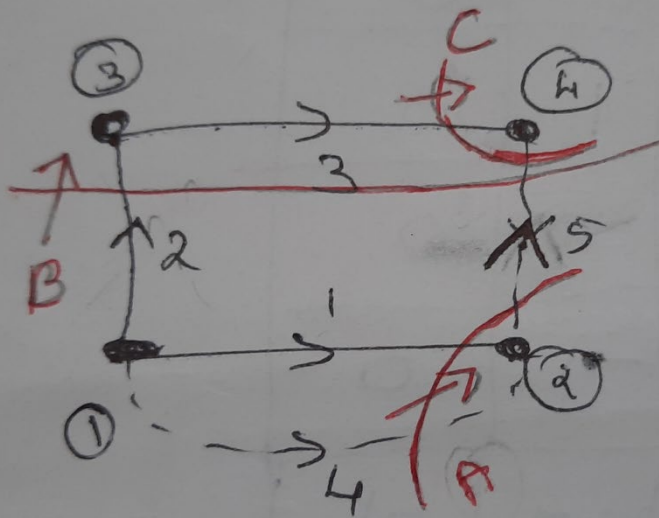



$A_2 K^t =$

$$\begin{bmatrix} -1 & 0 & 0 \\ 1 & 0 & -1 \end{bmatrix} \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & -1 & -1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 0 & 0 \\ -1 & 1 & 1 \end{bmatrix}$$

$B =$

$e/b$	A	B	C
1	1	0	0
2	0	1	0
3	0	0	1
4	1	0	0
5	-1	1	1

$$B_2 = \begin{bmatrix} u_b \\ B_2 \end{bmatrix}$$

$\rightarrow B_2$

$B_2 = A_2 K^t$

$$\begin{bmatrix} 1 & 0 & 0 \\ -1 & 1 & 1 \end{bmatrix}$$