


Internal Assessment Test - I

Sub:	Analog Electronic Circuits and Op-Amps						Code:	21EE32	
Date:	02.12.2022 10.15 – 11.45AM	Duration:	90 mins	Max Marks:	50	Sem:	III	Branch:	EEE
Answer Any FIVE FULL Questions									
							Marks	OBE	
								CO	RBT
1	Explain the operation of double ended clipping circuit with neat circuit diagram and waveforms						10	CO1	L2
2	Derive the expression for stability factors $S(I_{CO})$ and $S(V_{BE})$ for voltage divider biasing circuit.						10	CO2	L3
3	With the help of r_e equivalent model derive an equation for input impedance, output impedance, voltage gain and current gain for emitter follower configuration						10	CO2	L3
4	Design a voltage divider bias circuit using the given parameters: $I_{CQ} = 1\text{mA}$, $S(I_{CO}) = 20$, $\beta = 100$, $V_E = 1\text{V}$, $V_{CE} = 6\text{V}$ and $V_{CC} = 12\text{V}$. Draw its circuit diagram						10	CO2	L6
5	Explain hybrid equivalent model for transistor. Develop h-parameter model for CE, CC and CB configurations.						10	CO2	L2
6	For the transistor connected in CE configuration, determine A_V , A_I , Z_i and Z_o using complete hybrid equivalent model. $R_L = R_S = 1\text{K}\Omega$, $h_{ie} = 1\text{K}\Omega$, $h_{re} = 2 \times 10^{-4}$, $h_{fe} = 100$ and $h_{oe} = 20\mu\text{A/V}$						10	CO2	L3

AEC IAT 1 Solution

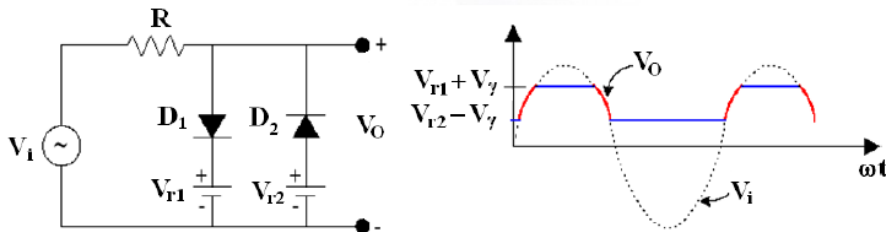1. Double ended clipper

- Two parallel clippers can be combined to form a double-ended clipper:



Input	Diode status	Output
$V_i < (V_{r2} - V_\gamma)$	D ₁ OFF, D ₂ ON	$V_{r2} - V_\gamma$
$(V_{r2} - V_\gamma) \leq V_i \leq (V_{r1} + V_\gamma)$	D ₁ OFF, D ₂ OFF	V_i
$V_i > (V_{r1} + V_\gamma)$	D ₁ ON, D ₂ OFF	$V_{r1} + V_\gamma$

2. Stability factor

$$S(I_{CO}) = \frac{1+\beta}{1-\beta \frac{\partial I_B}{\partial I_C}}$$

$$V_{Th} = R_{Th} I_B + V_{BE} + I_E R_E$$

But $I_E = I_C + I_B$

$$V_{Th} = R_{Th} I_B + V_{BE} + I_C R_E + I_B R_E$$

Differentiating with respect to I_C , keeping V_{BE} constant,

$$0 = (R_E + R_{Th}) \frac{\partial I_B}{\partial I_C} + R_E$$

$$\therefore \frac{\partial I_B}{\partial I_C} = \frac{-R_E}{R_E + R_{Th}}$$

Substituting in the expression for $S(I_{CO})$, we get

$$S(I_{CO}) = \frac{1+\beta}{1+\beta \frac{R_E}{R_E + R_{Th}}} = \frac{1+\beta}{R_E + R_{Th} + \beta R_E} (R_E + R_{Th})$$

$$\therefore S(I_{CO}) = (\beta + 1) \frac{R_E + R_{Th}}{(\beta + 1)R_E + R_{Th}}$$

$$\therefore S(I_{CO}) = (\beta + 1) \frac{\left[1 + \frac{R_{Th}}{R_E} \right]}{(\beta + 1) + \frac{R_{Th}}{R_E}}$$

$$S(V_{BE}) = \frac{\partial I_C}{\partial V_{BE}}$$

$$V_{Th} = R_{Th} I_B + V_{BE} + I_C R_E + I_B R_E$$

$$I_B = \frac{I_C}{\beta}$$

$$\therefore V_{Th} = \left(\frac{R_{Th}}{\beta} + \frac{R_E}{\beta} + R_E \right) I_C + V_{BE}$$

$$= \left(\frac{R_{Th} + R_E + \beta R_E}{\beta} \right) I_C + V_{BE}$$


$$V_{Th} = \left(\frac{(R_{Th} + (\beta + 1)R_E)}{\beta} \right) I_C + V_{BE}$$

Differentiating with respect to V_{BE} ,
keeping β constant

$$0 = \frac{R_{Th} + (\beta + 1)R_E}{\beta} \frac{\partial I_C}{\partial V_{BE}} + 1$$

$$\therefore S(V_{BE}) = \frac{\partial I_C}{\partial V_{BE}} = \frac{-\beta}{R_{Th} + (\beta + 1)R_E}$$

3. Emitter follower re model.

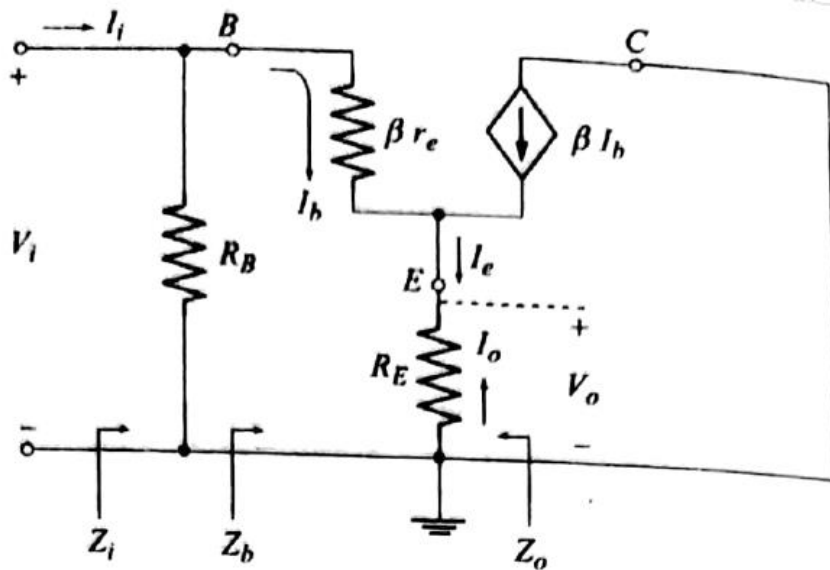

Input Impedance

$$V_i = I_b \beta r_e + I_e R_E \Rightarrow I_b \beta r_e + (1 + \beta) I_b R_E$$

$$Z_b = \frac{V_i}{I_b} = \beta r_e + (1 + \beta) R_E \quad \left[\because (1 + \beta) \approx \beta \right]$$

$$= \beta (r_e + R_E) \quad \left[\because (r_e + R_E) \approx R_E \right]$$

$$= \beta R_E$$

$$Z_i = \frac{V_i}{I_i} = R_B \parallel Z_b$$

Output Impedance

$$Z_b = \frac{V_i}{I_b} \Rightarrow I_b = \frac{V_i}{Z_b}$$

$$I_b = \frac{I_e}{1 + \beta}$$

$$\frac{I_e}{1 + \beta} = \frac{V_i}{Z_b} \Rightarrow I_e = \frac{V_i (1 + \beta)}{Z_b}$$

$$I_e = \frac{V_i \beta}{\beta (r_e + R_E)} \Rightarrow V_i = I_e r_e + I_e R_E$$

To find Z_o , let $V_i = 0$.



$$Z_o = r_e \parallel R_E = \frac{r_e R_E}{r_e + R_E}$$

$$Z_o \approx r_e$$

Voltage Gain $A_v = 1$

Current Gain

$$V_o = I_e R_E = -I_o R_E \quad [\because I_e = -I_o]$$


$$\therefore I_o = -\frac{V_o}{R_E}$$

$$\text{Also } I_i = \frac{V_i}{Z_i}$$

$$\text{Now } A_i = \frac{I_o}{I_i} = \left[-\frac{V_o}{R_E} \right] \div \left[\frac{V_i}{Z_i} \right]$$
$$= -\left[\frac{V_o}{V_i} \right] \left[\frac{Z_i}{R_E} \right]$$

$$A_i = -\frac{A_v Z_i}{R_E}$$

4.

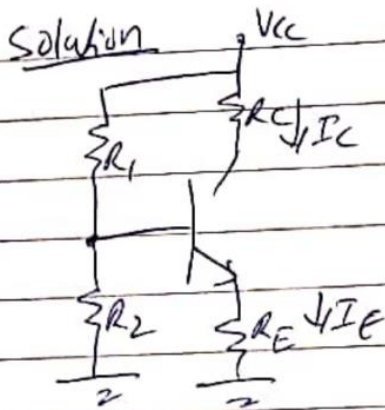

$$I_C \approx I_E = 1 \text{ mA}$$

$$V_E = I_E R_E$$

$$\therefore R_E = \frac{V_E}{I_E} = \underline{\underline{1 \text{ k}\Omega}}$$

$$I_B = \frac{I_C}{\beta} = 0.01 \text{ mA}$$

$$V_{CC} - V_{CE} - I_C(R_C + R_E) = 0$$

$$\therefore R_C = \frac{V_{CC} - V_{CE} - R_E I_C}{I_C} = \underline{\underline{5 \text{ k}\Omega}}$$

$$S_{IC0} = (B+1) \left[\frac{R_E + R_{TH}}{(1+B)R_E + R_{TH}} \right] \Rightarrow \text{Solve to find } R_{TH}$$

$$\rightarrow S_{IC0} [(1+B)R_E + R_{TH}] = (1+B)(R_E + R_{TH})$$

$$V_{TH} = R_{TH} I_B + I_E R_E + V_{BE}$$

$$2020 R_E + 20 R_{TH} = 101 R_E + 101 I_B R_{TH}$$

$$1919 R_E = 81 R_{TH}$$

$$V_{TH} = V_{CC} \frac{R_2}{R_1 + R_2}$$

$$R_{TH} = \frac{1919}{81} \times 1 = 2369 \text{ } \Omega$$

Multiply & Divide by R_1 .

$$V_{TH} = \frac{V_{CC}}{R_1} \frac{R_1 R_2}{R_1 + R_2} \Rightarrow \text{Solve to find } R_1$$

$$\rightarrow V_{TH} = \frac{V_{CC} R_{TH}}{R_1} \Rightarrow R_1 = \frac{V_{CC} R_{TH}}{V_{TH}}$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} \Rightarrow \text{Solve to find } R_2$$

$$\rightarrow R_{TH}(R_1 + R_2) = R_1 R_2$$

$$R_{TH} R_1 = R_1 R_2 - R_{TH} R_2$$

$$= R_2 (R_1 - R_{TH}) \quad \Bigg| \quad R_2 = \frac{R_{TH} R_1}{R_1 - R_{TH}}$$

5.


H-parameter model

Parameters are defined in general terms of any operating conditions.

Hybrid means mixed. Here we have mixed parameters.

In hybrid model, the transistor is modelled based on what is happening at its terminals without regard for the physical process taking place inside the transistor.

CE Configuration

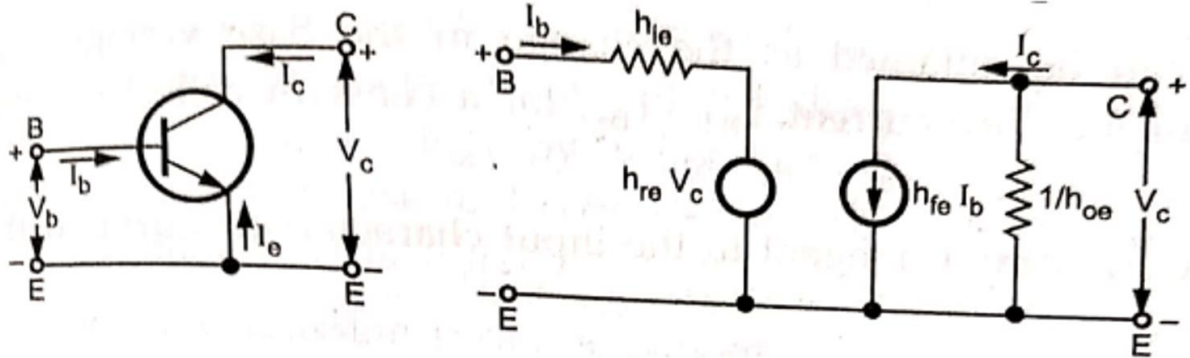

$$v_1 = h_i i_1 + h_r v_2$$


$$i_2 = h_f i_1 + h_o v_2$$



$$V_b = h_{ie} I_b + h_{re} V_c$$

$$I_c = h_{fe} I_b + h_{oe} V_c$$

CC Configuration

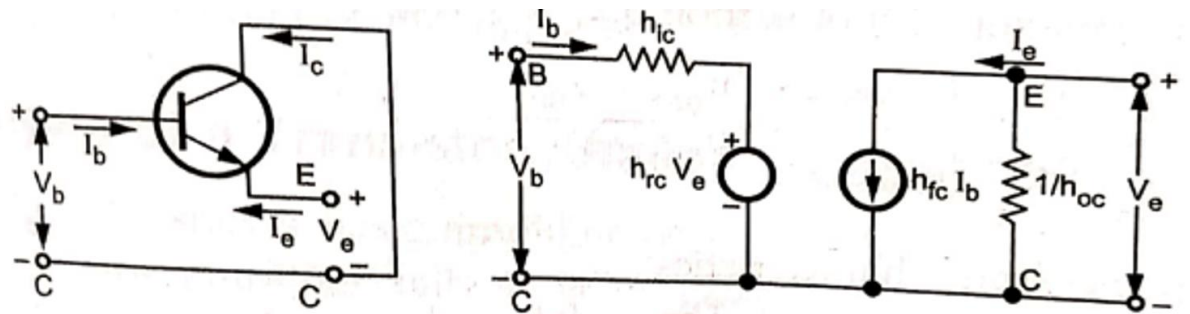

$$v_1 = h_i i_1 + h_r v_2$$


$$i_2 = h_f i_1 + h_o v_2$$



$$V_b = h_{ic} I_b + h_{rc} V_e$$

$$I_e = h_{fc} I_b + h_{oc} V_e$$

CB Configuration

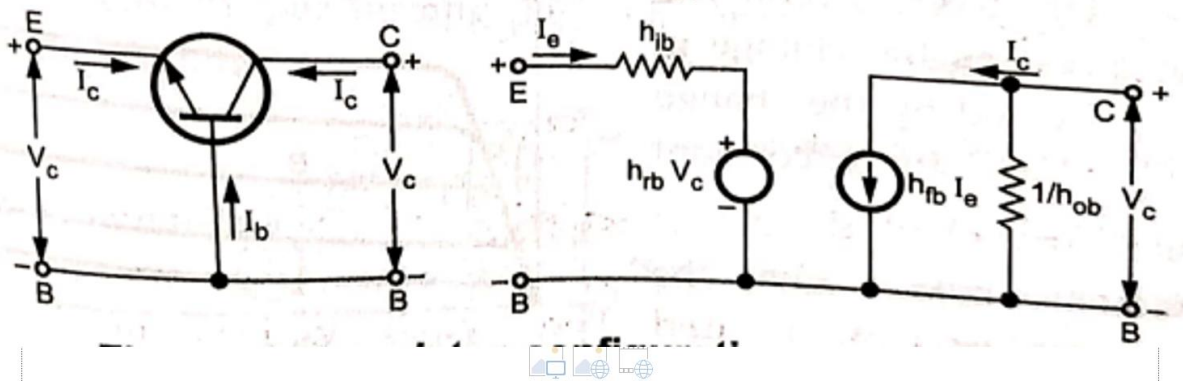

$$\begin{aligned} v_1 &= h_i i_1 + h_r v_2 \\ i_2 &= h_f i_1 + h_o v_2 \end{aligned}$$



$$\begin{aligned} V_e &= h_{ib} I_e + h_{rfb} V_c \\ I_c &= h_{fb} I_e + h_{ob} V_c \end{aligned}$$

6.

$$h_{oe} R_L = 0.02 \angle 0^\circ$$

$$A_I = -h_{fe} = -100$$

$$A_V = \frac{-h_{fe} R_L}{h_{ie}} = \frac{-100 \times 1}{1} = -100$$

$$Z_i = h_{ie} = 1 \text{ k}\Omega$$

$$Z_o \approx 0$$