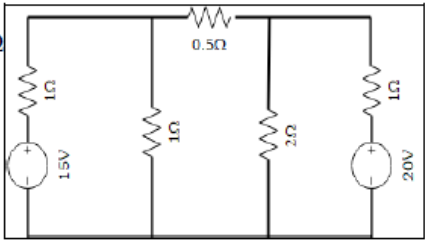
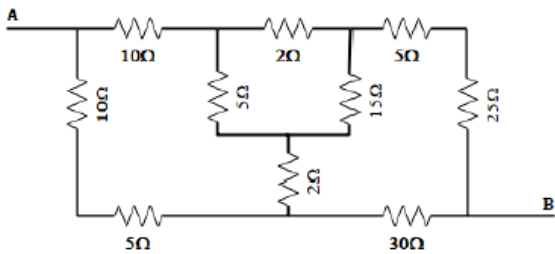



Sub :	Electric Circuits Analysis				Sub Code:	21EE	Branch:	EEE
Date:	03.12.2022	Duration:	90 mins	Max Marks:	50	Sem / Sec:	3	OBE

**Answer any five questions**


MAR KS	CO	RBT
-----------	----	-----

1	Determine the current through $0.5 \Omega$ resistance. Use nodal analysis.		[10]	CO2	L4
2	Determine resistance between 'A' & 'B', use Y-Δ transformation.		[10]	CO2	L4


3	Determine the current 'i' in the circuit, using mesh analysis.	[10]	CO1	L4
4	Determine ' $v_x$ ', in the circuit, using source transformation.	[10]	CO1	L4
5	Use source shifting and transformation to find voltage across 'a' - 'b'.	[10]	CO1	L4
6	For $\Delta ABC$ to be equivalent to Y A'B'C', obtain expression for $R_1$ in terms of $R_{12}$ , $R_{13}$ , and $R_{23}$ .	[10]	CO1	L2

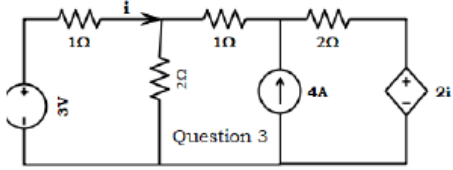


Question 3

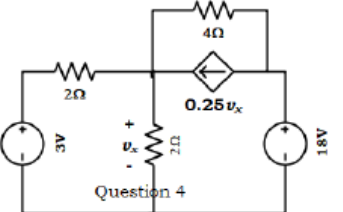

Question 4

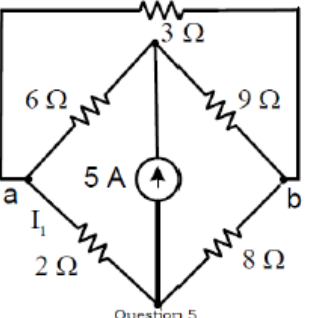

Question 5

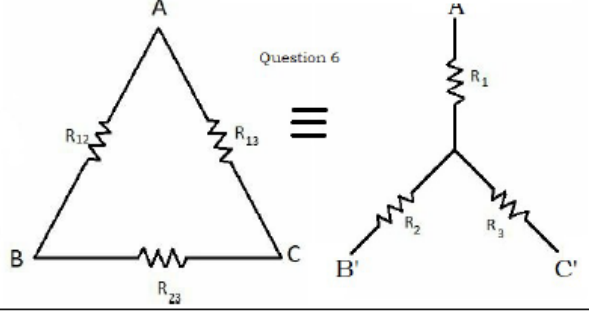


Question 6

Signature of CI

Signature of CCI

Signature of HoD

Solution:

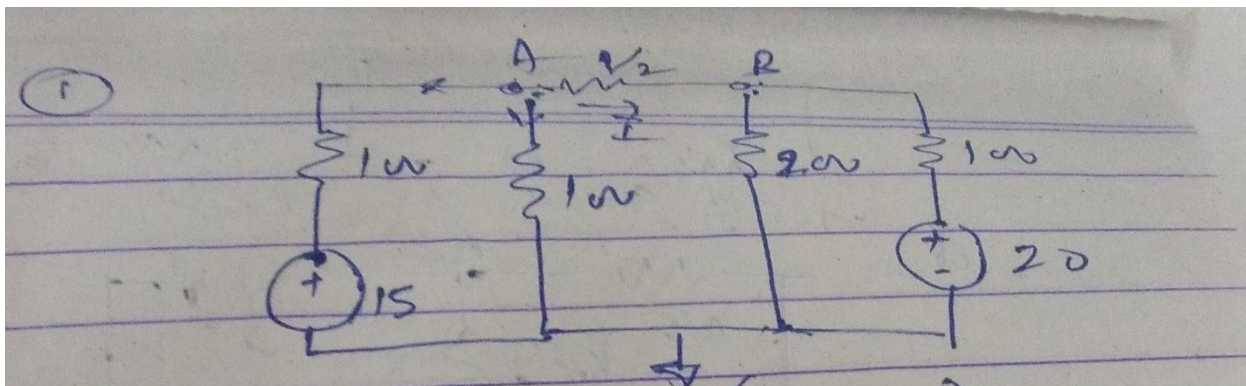

$$-(V_A - 15) + V_A + (V_A - V_B) \times 2 = 0$$

$$2(V_A - V_B) - (V_B/2) = (V_B - 20) = 0$$
$$4V_A - 2V_B = 15$$

$$-4V_A + 7V_B = 40$$

$$5V_B = 55$$

$$V_B = 11$$







$$V_A = 37/4$$


$$I_1 = \frac{V_A - V_B}{1/2}$$

$$= \frac{37/4 - 11}{1/2}$$

$$= \frac{-7/4 \cdot 2}{1/2} = -7/2 \text{ A}$$

2

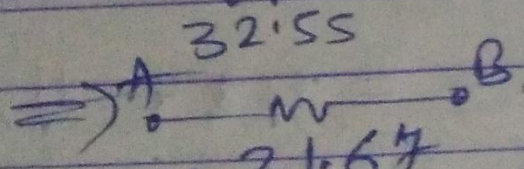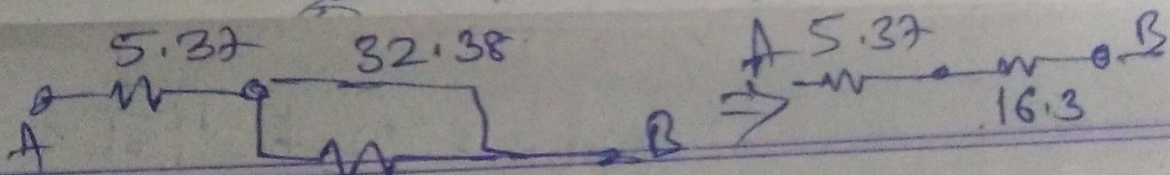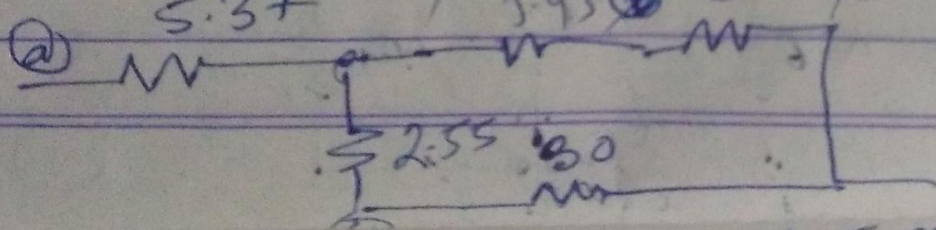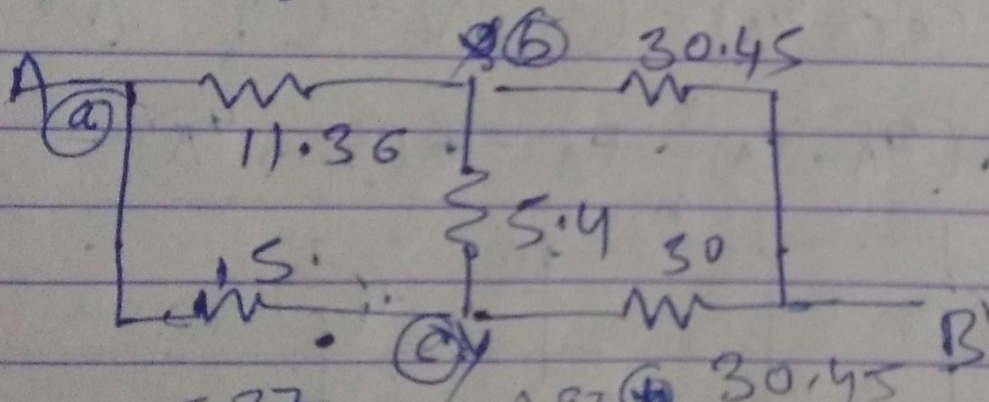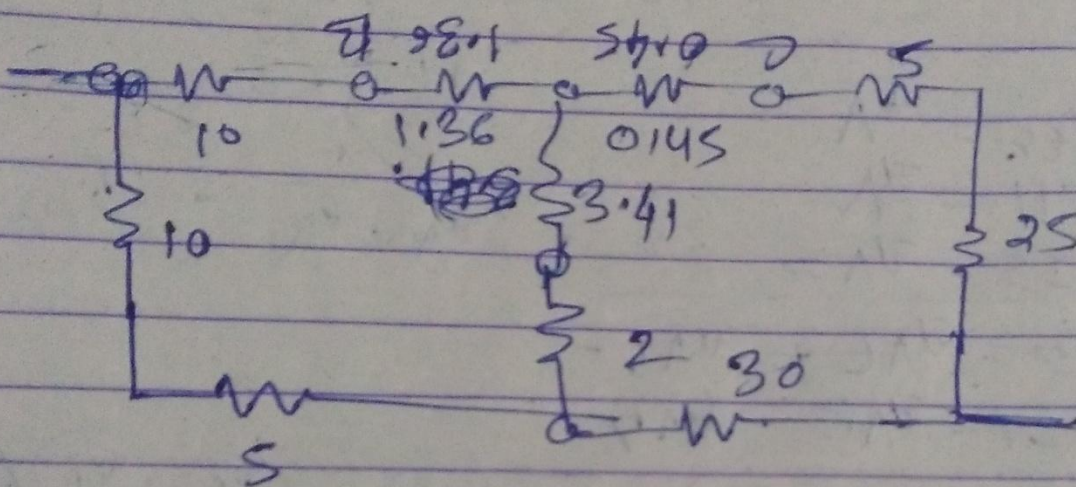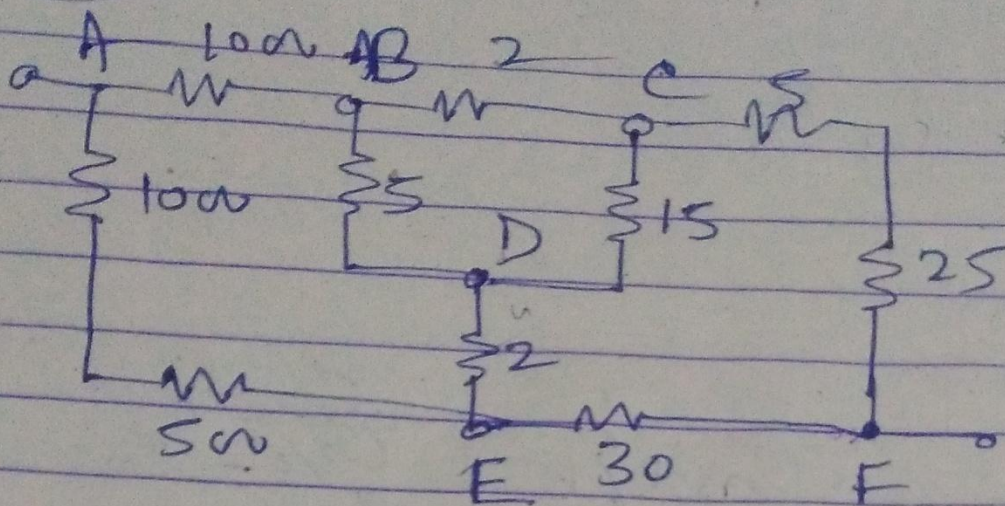

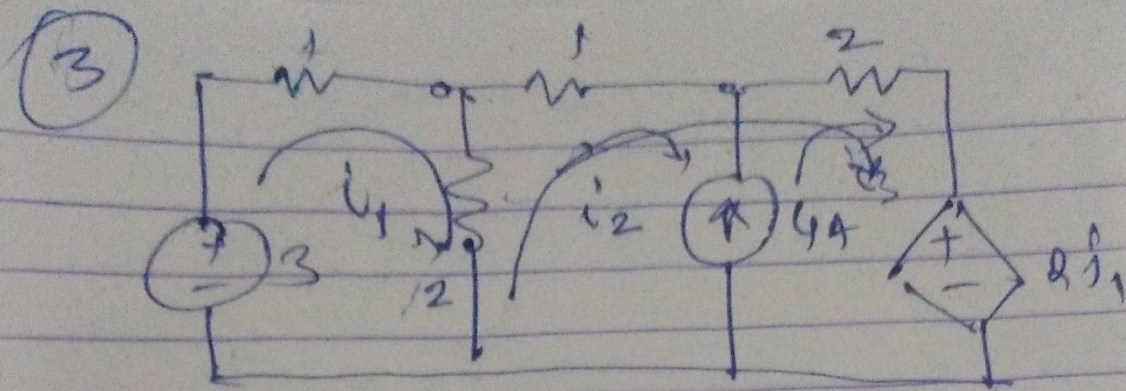

(1)  $3 - i_1 - (i_1 - i_2) \cdot 2 = 0$

$3 - 3i_1 + 2i_2 = 0 \quad \dots (1)$

Substituting (2)

(2)  $-(i_2 - i_1) \cdot 2 - i_2 - 2i_3 - 2i_1 = 0$

$2i_1 - 2i_2 - i_2 - 2i_3 - 2i_1 = 0$

$-i_2 - 3i_2 - 2i_3 = 0 \quad \dots (1')$

$-3i_1 + 2i_2 + 0i_3 = -3$

$-2i_2 + 2i_3 = 3$

$-i_1 - 5i_2 = 4$

$\frac{-3i_1 + 2i_2}{2} = -\frac{3}{2}$




$-\frac{15}{2}i_1 + 5i_2 = -15/2$

$-4.5i_1 = -3.5$

$i_1 = +3.5/4.5 = 7/9 \text{ A}$



$\frac{7}{9} \text{ A}$

4

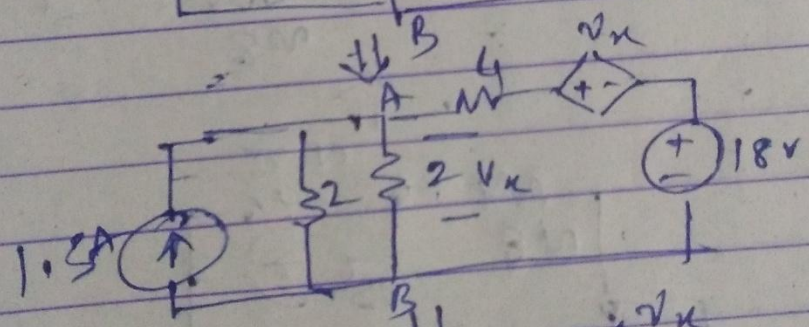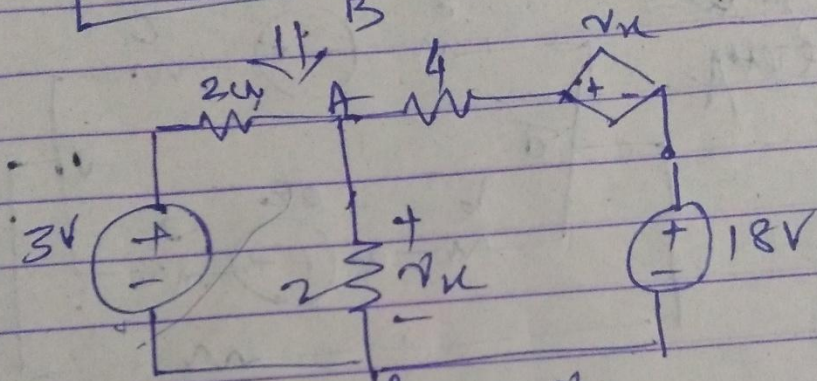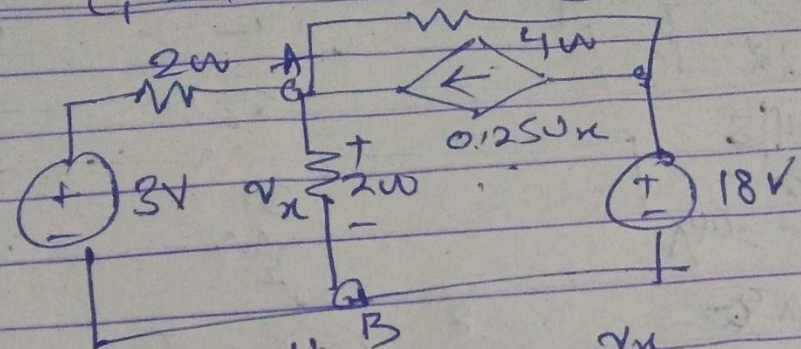

$1.5 + 4.5 = 6V$   
 $1.5 - I = 0$   
 $1.5 - I - 4I - 18 = 0$   
 $1.5 - I - 4I - 18 = 0$   
 $1.5 - 5I - 18 = 0$   
 $-16.5 - 5I = 0$   
 $-5I = 16.5$   
 $I = -16.5 / 5 = -3.3$

5

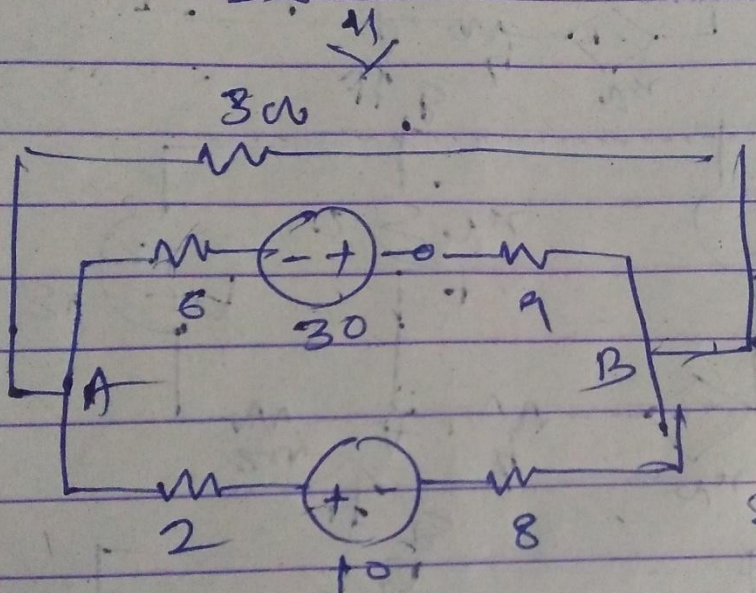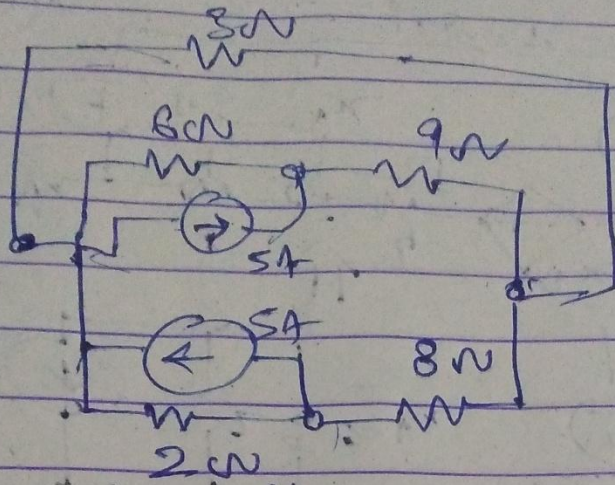

~~V<sub>AB</sub> = 3V~~  
~~3V~~

$$V_{AB} = -R_{eq}(I)$$

$$= -2V \cdot \frac{3 \parallel 15 \parallel 10}{10}$$

