

CBCS SCHEME

17EE32

Third Semester B.E. Degree Examination, Jan./Feb. 2023 Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Differentiate between:
- Active and passive elements
 - Unilateral and bilateral elements
 - Linear and non-linear elements
 - Lumped and distributed elements
 - Independent and dependent sources.
- (10 Marks)
- b. Find the current flowing through the 10Ω resistor using source transformation technique for the circuit given in Fig.Q.1(b).
- (10 Marks)

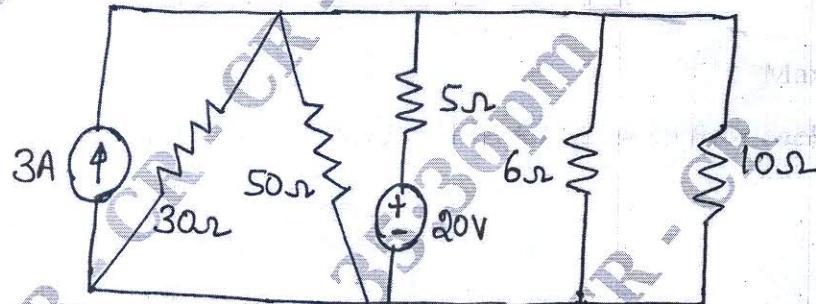


Fig.Q.1(b)

Max. Marks: 100

- 2 a. Define and explain supernode.
b. Find the equivalent resistance between the terminals A and B using star-delta transformation technique for the circuit given in Fig.Q.2(b).
- (04 Marks)
- (08 Marks)

OR

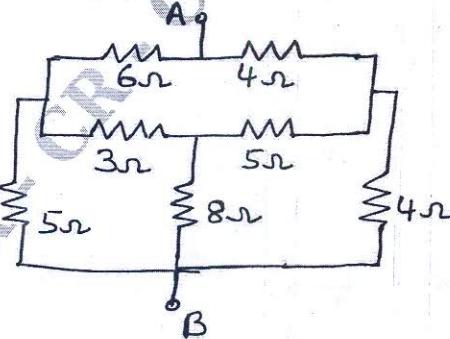


Fig.Q.2(b)

- a. State and explain superposition theorem.
 b. Find the current through the 10Ω resistor using
 c. For the circuit shown in the Fig.Q.2(c), find the current through the 5Ω resistor using mesh analysis. (08 Marks)

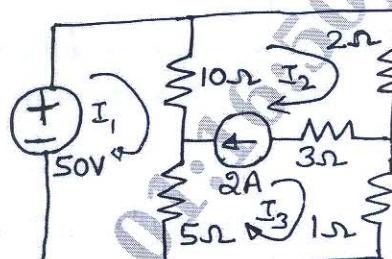


Fig.Q.2(c)

Module-2

- 3 a. State and explain superposition theorem.
 b. Find the current through the 10Ω resistor using Thevenin's theorem for the circuit shown in Fig.Q.3(b). (05 Marks) (08 Marks)

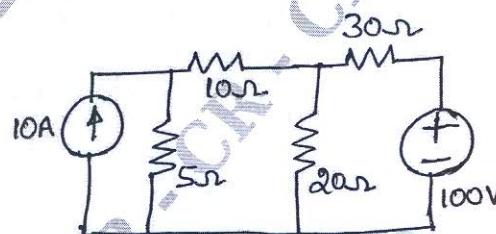


Fig.Q.3(b)

- c. For the circuit given in Fig.Q.3(c), find the value of load impedance Z_L for which power transferred is maximum. (07 Marks)

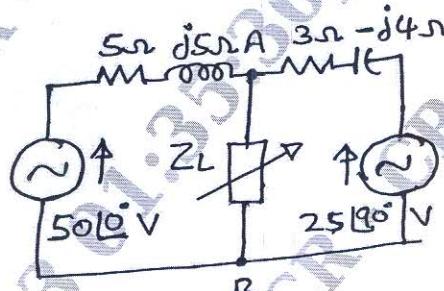


Fig.Q.3(c)

CMRIT LIBRARY
BANGALORE - 560 037

OR

- 4 a. Use Norton's theorem for the circuit of Fig.Q.4(a) to determine the power absorbed by the 9Ω resistor. (10 Marks)

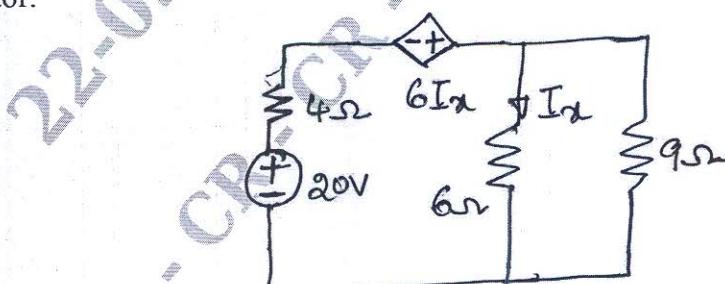


Fig.Q.4(a)

- b. In the circuit shown in Fig.Q.4(b), verify reciprocity theorem.

(10 Marks)

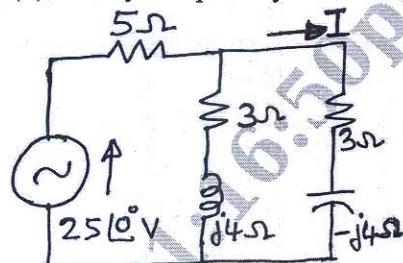


Fig.Q.4(b)

Module-3

- 5 a. An R-L-C series circuit with a resistance of 10Ω , inductance of $0.2H$ and a capacitance of $40\mu F$ is supplied with a 100-V supply at variable frequency. Find: i) Resonant frequency ii) Current at resonance iii) Quality factor iv) Half power frequencies v) Voltage at resonance across R-L-C. Draw the resonance curve. (10 Marks)
- b. Derive an expression for the band width of series R-L-C circuit. (10 Marks)

OR

- 6 a. In the circuit shown in Fig.Q.6(a), the switch is changed from the position a to the position b at $t = 0$, steady state condition having reached before switching. Find the value of $i(t)$, $\frac{di(t)}{dt}$ and $\frac{d^2i(t)}{dt^2}$ at $t = 0^+$. (10 Marks)

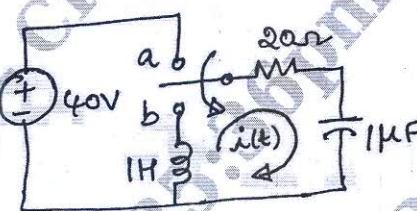


Fig.Q.6(a)

- b. Explain the behavior of R, L and C elements for transients. Write the procedure for evaluating initial conditions. (10 Marks)

Module-4

- 7 a. State and explain initial value theorem. (06 Marks)
- b. Find the Laplace transform of i) e^{at} ii) $\sin wt$. (06 Marks)
- c. Find the Laplace transform of the function given in Fig.Q.7(c). (08 Marks)

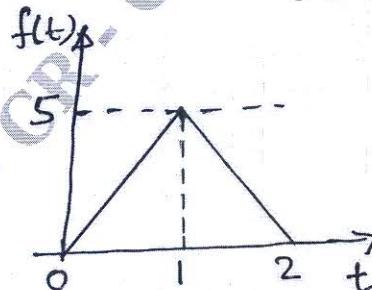


Fig.Q.7(c)

9 a. A $400V, 3$ phase supply feeds an unbalanced 3 wire star connected load consisting of impedances $Z_R = 7[10^\circ]\Omega$, $Z_Y = 8[30^\circ]\Omega$ and $Z_B = 8[50^\circ]\Omega$. The phase sequence is RYB.

- b. Verify initial and final value theorem to i) $10e^{5t}$ ii) $5 \sin 3t$. (10 Marks)
- Module-5**
- 9 a. A $400V, 3$ phase supply feeds an unbalanced 3 wire star connected load consisting of impedances $Z_R = 7[10^\circ]\Omega$, $Z_Y = 8[30^\circ]\Omega$ and $Z_B = 8[50^\circ]\Omega$. The phase sequence is RYB. Determine the line currents and power taken by the load. (10 Marks)
- b. Define Z-parameters. Express Y-parameters in terms of Z-parameters. (10 Marks)

OR

- 10 a. Find the Y and Z parameters for the network shown in the Fig.Q.10(a). (10 Marks)

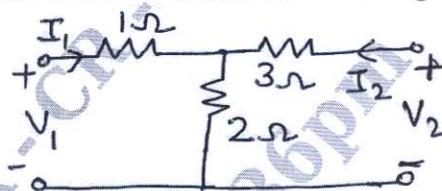


Fig.Q.10(a)

- b. Determine the transmission parameters for the circuit shown in the Fig.Q.10(b). Verify for reciprocity. (10 Marks)

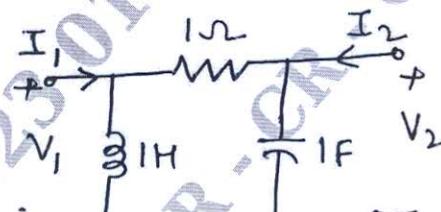


Fig.Q.10(b)
