

CBCS SCHEME



18EC42

Fourth Semester B.E. Degree Examination, Jan./Feb. 2023 Analog Circuits

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain the working of classical discrete circuit Bias – voltage divider bias. (10 Marks)
- b. Design a collector – to – base bias circuit for the specified conditions. Given :
 $V_{CC} = 15V$, $V_{CE} = 5V$, $I_C = 5mA$, $\beta = 100$. (10 Marks)

OR

- 2 a. Draw and explain the MOSFET biasing circuit using Fixed V_G . (10 Marks)
- b. Derive the expression for g_m and A_V for the MOSFET amplifier circuit. (10 Marks)

Module-2

- 3 a. Write a note on three basic configuration of a MOSFET amplifier. Derive expression for characterizing parameters of MOSFET amplifier. (10 Marks)
- b. Draw the high frequency equivalent circuit of a MOSFET and explain the significance of the different elements of the circuit. (10 Marks)

OR

- 4 a. Explain the working of RC – phase shift oscillator using FET. (10 Marks)
- b. In Hartley oscillator $L_1 = 20\mu H$, $L_2 = 2mH$ and C variable. Find the range of C , if frequency is to be varied from 1 MHz to 2.5 MHz. Neglect the mutual inductance. (10 Marks)

Module-3

- 5 a. Draw the block diagram of current series feedback amplifier and derive an expression for input resistance, voltage gain, and output resistance. (10 Marks)
- b. How power amplifiers are classified? Explain them briefly. (10 Marks)

OR

- 6 a. Explain the working of class B push pull amplifier with relevant waveforms. Show that maximum conversion efficiency is 78.5%. (10 Marks)
- b. Explain series – shunt (voltage series) feedback amplifier. Determine input and output resistance of the amplifier. (10 Marks)

Module-4

- 7 a. Explain the working of inverting schmitt trigger. Derive the equation for the trigger points. (10 Marks)
- b. Derive an expression for the output of an inverting summing amplifier with 3 inputs and hence prove the circuit can act averaging amplifier. (10 Marks)

OR

- 8 a. Explain the working of instrumentation amplifier. Mention its applications. (10 Marks)
- b. Explain the working of practical non-inverting amplifier. (10 Marks)

Module-5

- 9 a. Explain Successive – Approximation type – ADC with neat block diagram. (10 Marks)
b. Explain the working of precision full wave rectifier with relevant circuit and waveforms. (10 Marks)

OR

- 10 a. Explain the working of a monostable multivibrator with relevant circuit and wave forms. Mention few applications of this circuit. (10 Marks)
b. Design a second order low-pass Butterworth filter having high cut-off frequency of 1 KHz. Draw its frequency response. (10 Marks)

* * * * *