



Fourth Semester B.E. Degree Examination, Jan./Feb. 2023

Linear Integrated Circuits

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Draw the basic op-amp internal circuit diagram. Identify the terminals and explain the circuit operation. (06 Marks)
- b. Sketch the op-amp voltage follower circuit with voltage divider providing bias to one input terminal. Show the various currents and explain how the resistor values are selected. (06 Marks)
- c. An op-amp circuit with closed loop gain of 100 has common mode output of $5\mu\text{V}$ when the common mode input is 5mV . Calculate the common mode rejection ratio. (04 Marks)

OR

- 2 a. Explain the following parameters of op-amp and give its ideal and typical values :
i) PSRR ii) Input offset voltage iii) Slew rate. (06 Marks)
- b. Sketch a two-input op-amp inverting summing amplifier, and explain its operation. Derive the equation for output voltage in terms of the inputs. Design a summing amplifier to give the direct sum of two inputs, each ranging from 0.1 to 1V. (06 Marks)
- c. A simple inverting amplifier has $R_1 = 8.2\text{K}\Omega$ and $R_2 = 270\Omega$. Determine the voltage gain calculate the new resistance value for R_2 to give gain of -60 . (04 Marks)

Module-2

- 3 a. Sketch the circuit of a high input impedance capacitor coupled non-inverting amplifier, and explain its operation. (06 Marks)
- b. Draw the circuit of adjustable positive voltage source using op-amp and zener diode. Explain the circuit operation and derive the expression for output voltage. (06 Marks)
- c. Design a capacitor coupled voltage follower using 741 op-amp. The lower cut off frequency should be 50Hz, and the load resistance is $3.9\text{K}\Omega$. (04 Marks)

OR

- 4 a. Draw the circuit of capacitor coupled difference amplifier, and explain its operation. Also explain how to determine the values of the capacitors. (06 Marks)
- b. Sketch the circuit of non-saturating half-wave precision rectifier. Draw the input and output waveforms and explain the operation of the circuit. (06 Marks)
- c. Design a current amplifier to have a gain of 10. The maximum input current is 1mA , the load resistance is 100Ω , and the supply voltage is $\pm 15\text{V}$. (04 Marks)

Module-3

- 5 a. Draw the circuit of inverting op-amp Schmitt trigger, and explain its operation. Define UTP and LTP, and sketch the typical input and output waveforms. (06 Marks)
- b. Sketch the Zener diode peak clipper circuit with adjustable output voltage limit. Explain the circuit operation and write the equations for the upper and lower limits of output voltage. (06 Marks)
- c. Design an op-amp differentiator to produce 5V output when the input changes by 1V in $100\mu\text{s}$. (04 Marks)

OR

- 6 a. Draw the circuit diagram of op-amp sample and hold circuit. Sketch the signal, control and output voltage waveforms, and explain the circuit operation. (06 Marks)
- b. Draw and explain the circuit of logarithmic amplifier using single op-amp. Derive the expression for output voltages. (06 Marks)
- c. Design a practical integrator circuit to produce a triangular output waveform having 4V peak-to-peak amplitude, and input of $\pm 5V$, 500Hz square wave. Use $c = 0.1\mu F$. (04 Marks)

Module-4

- 7 a. Draw the circuit of a first order low-pass filter and explain the circuit operation with frequency response curve. Discuss the role of op-amp in the circuit. Choosing $R = 120K\Omega$, design a first-order low-pass filter to have cutoff frequency of 1.2KHz. (08 Marks)
- b. What is a voltage regulator? Draw the circuit of series regulated power supply using discrete components and explain the working. Design a regulator using IC7805 to supply a current of 1A to a 10Ω load. (08 Marks)

OR

- 8 a. Draw the circuit of single stage band-pass active filter and explain its operation. Design a band-pass filter to have unity voltage gain and pass-band from 300Hz to 30KHz. Select $C_2 = 1000pF$. (08 Marks)
- b. Draw the functional block diagram of IC723 general purpose regulator and explain its working. Show how a simple low positive voltage regulator can be constructed using this IC. (08 Marks)

Module-5

- 9 a. Draw the functional diagram of 555 Timer and explain its operation as monostable vibrator. (08 Marks)
- b. Draw the circuit of 3-bit R-2R ladder DAC, and explain its operation. Derive the expression for output voltage, by drawing its equivalent circuit, and taking the binary inputs as 100 and 001. (08 Marks)

OR

- 10 a. With a neat block schematic, explain the different blocks of a PLL. Explain lock-in range, capture range and pull-in time. (08 Marks)
- b. Draw the functional block diagram of successive approximation ADC and explain its operation with an example. Suppose the clock frequency is 4 MHz, what is the conversion time for an 8-bit ADC? (08 Marks)

* * * * *