



CBGS SCHEME

15EC35

Third Semester B.E. Degree Examination, Jan./Feb. 2023

Electronic Instrumentation

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define i) Accuracy ii) Precision iii) Resolution iv) Significant figures. (06 Marks)
- b. Explain different types of Static Errors. (06 Marks)
- c. A basic D'Arsonval movement with a full scale deflection of $50 \mu\text{A}$ and internal resistance of 500Ω is used as a voltmeter. Determine the value of multiplier resistance needed to measure a voltage range of $0 - 10\text{V}$. (04 Marks)

OR

- 2 a. With a neat block diagram, explain true RMS reading voltmeter. (08 Marks)
- b. Explain AC voltmeter using full wave rectifier. (04 Marks)
- c. What are the limitations of thermocouple? (04 Marks)

Module-2

- 3 a. Explain Ramp type DVM, with a neat block diagram. (08 Marks)
- b. Explain successive approximation DVM, with neat block diagram. (08 Marks)

OR

- 4 a. A $4\frac{1}{2}$ digit voltmeter is used for Voltage measurement i) Find its resolution. ii) How would 12.98V be displayed on a 10V range? iii) How would 0.6973 be displayed on 1V and 10V ranges? (06 Marks)
- b. Explain the working of digital frequency meter with neat block diagram. (06 Marks)
- c. What are the advantages of digital meters over analog meters? (04 Marks)

Module-3

- 5 a. Explain Simple CRO, with neat block diagram. (08 Marks)
- b. Explain the working of storage oscilloscope. (08 Marks)

OR

- 6 a. Explain the working of laboratory type single generator, with neat diagram. (08 Marks)
- b. Explain the working of function generator, with neat block diagram. (08 Marks)

Module-4

- 7 a. Explain the working of field strength meter. (06 Marks)
- b. Explain the Q meter, with neat diagram. (06 Marks)
- c. Explain Analog pH meter. (04 Marks)

OR

- 8 a. Explain unbalanced wheat stone bridge and derive the expression for galvanometer current. (08 Marks)
- b. Explain Wagner's Earth connection. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, $42+8 = 50$, will be treated as malpractice.

15EC35

Module-5

- 9 a. Define Transducer. What are the types of transducer? (04 Marks)
b. Explain Resistance thermometer, with neat diagram. (06 Marks)
c. Explain Resistive Position transducer. (06 Marks)
- OR
- 10 a. Explain the construction and working of LVDT. (08 Marks)
b. Explain Photovoltaic transducer. (08 Marks)
