

Third Semester B.E. Degree Examination, Jan./Feb. 2023
Digital Electronics

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Construct a truth table and write a Boolean expression for the problem statement: An output variable Y is true when the value of the inputs exceeds 3. Design the logic circuit for the obtained expression. (10 Marks)
- b. What do you mean by canonical SOP a POS? Explain with an example. (04 Marks)
- c. Simplify $s = f(a, b, c) = \sum m(0, 1, 3, 4, 5, 6)$ using K-map and draw the logic diagram using NAND gates for obtained expression. (06 Marks)

OR

- 2 a. Simplify using K-map method. $K = f(w, x, y, z) = \sum(0, 1, 3, 4, 5, 7, 9, 12, 13) + \sum d(2, 8, 10, 11, 14)$ and draw the logic circuit for obtained expression. (10 Marks)
- b. Simplify using QM-method. $D = f(a, b, c, d) = \sum(0, 1, 2, 5, 7, 8, 9, 14, 15)$. Verify the same using K-map method. (10 Marks)

Module-2

- 3 a. Implement $f_1(a, b, c) = \sum(0, 2, 6)$ and $f_2(a, b, c) = \sum(1, 3, 7)$ using 74138, 3:8 decoder IC. (06 Marks)
- b. With a neat circuit diagram, explain the carry look ahead adder with relevant expressions. (06 Marks)
- c. Design 2-bit comparator using suitable gates. (08 Marks)

OR

- 4 a. Realize the function $y = f(a, b, c, d) = \sum(0, 1, 3, 5, 6, 7, 9, 10, 11, 13, 15)$ using 8:1 Mux. (10 Marks)
- b. What is an Encoder? Design and explain 4:2 priority encoder. (10 Marks)

Module-3

- 5 a. Explain the working of Master-Slave JK-FF with the help of logic diagram. (08 Marks)
- b. Obtain the characteristic equations for J-K and T-Flip-Flops (FF). (06 Marks)
- c. What is race around condition and how it is overcome? Explain with the help of logic diagram. (06 Marks)

OR

- 6 a. Explain the working of gated SR-latch with the help of logic circuit. Draw the timing diagrams also. (10 Marks)
- b. Explain the working of +ve edge triggered D-flip-flop with functional table. Draw the timing diagrams of the same. (10 Marks)

Module-4

- 7 a. Design 4-bit ripple up counter using positive edge triggered T-flip-flops and draw the truth table and timing diagram of the same. (10 Marks)
- b. Explain the working of 4-bit of twisted ring counter with necessary logic diagram, truth table and timing diagrams. (10 Marks)

OR

- 8 a. What is register? Explain 4-bit serial-in, serial-out unidirectional shift register with the help of diagram. (10 Marks)
- b. Design MOD-6 synchronous counter using SR flip-flops. (10 Marks)

Module-5

- 9 a. What are Mealy and Moore Models? Explain. (08 Marks)
- b. Design 3-bit synchronous up counter. (12 Marks)

OR

- 10 a. Analyze the following sequential circuit of Fig.Q.10(a), by writing input and output equations, state table and state diagram. (12 Marks)

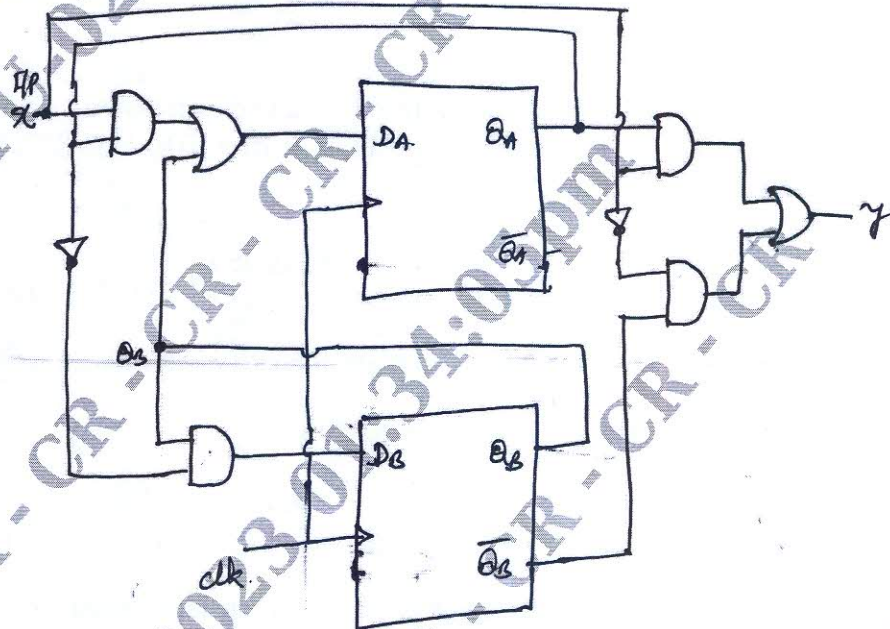


Fig.Q.10(a)

- b. Draw a state table and state diagram with an example. (08 Marks)
