

CBCS SCHEME

18EC72



Seventh Semester B.E. Degree Examination, June/July 2023

VLSI Design

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Implement a 4 : 1 multiplexer using :
 - i) Transmission gate
 - ii) Tristate inverters

(08 Marks)
- b. Realize CMOS compound gate for the function : $Y = D + A(B + C)$.

(04 Marks)
- c. With necessary circuit diagram and timing diagram explain the operation of positive edge triggered D flip-flop.

(08 Marks)

OR

- 2 a. Draw the circuit diagram of a CMOS inverter and its DC transfer characteristics. Explain various region of operation and indicate the voltage levels. Derive the equation for switching threshold.

(10 Marks)
- b. Derive the equation for drain current of a MOSFET in non-saturated and saturated region of operation.

(06 Marks)
- c. Explain the following non-ideal effects of a MOSFET –channel length modulation mobility degradation.

(04 Marks)

Module-2

- 3 a. With necessary diagrams explain CMOS n-well fabrication process.

(12 Marks)
- b. Draw the layout of $Y = ABC + D$ and estimate the area.

(08 Marks)

OR

- 4 a. With necessary diagrams explain lambda based design rules for wires, contact cuts and transistors.

(08 Marks)
- b. Explain MOSFET capacitances in three different regions of operation with necessary diagrams and equations.

(06 Marks)
- c. What is Scaling? Compute drain current, power, current density, power density, Cox for constant field scaling.

(06 Marks)

Module-3

- 5 a. Explain the RC delay model to compute the delay of the logic circuit. Also calculate the delay of unit size inverter driving another unit size inverter.

(08 Marks)
- b. With necessary circuit example explain :
 - i) Pseudo nMOS
 - ii) Ganged CMOS,

(06 Marks)
- c. Explain the following CMOS optimization techniques with necessary examples :
 - i) Input ordering
 - ii) Asymmetric gates.

(06 Marks)

OR

- 6 a. Analyze the three input NAND gate using Elmore's delay and compute the falling and rising propagation delays if the output is loaded with 'h' identical gates. (08 Marks)
- b. Compute and compare the logical effort and parasitic delay of the following gates with the help of schematic diagram :
- 2 input NOR gate
 - Input NAND gate.
- (06 Marks)
- c. Explain Cascade voltage switch logic (CVSL) implement two input OR/NOR gate using CVSL. (06 Marks)

Module-4

- 7 a. Compute the output voltage V_{out} in the following pass transistor circuits. Assume $V_{tn} = 0.7V$.

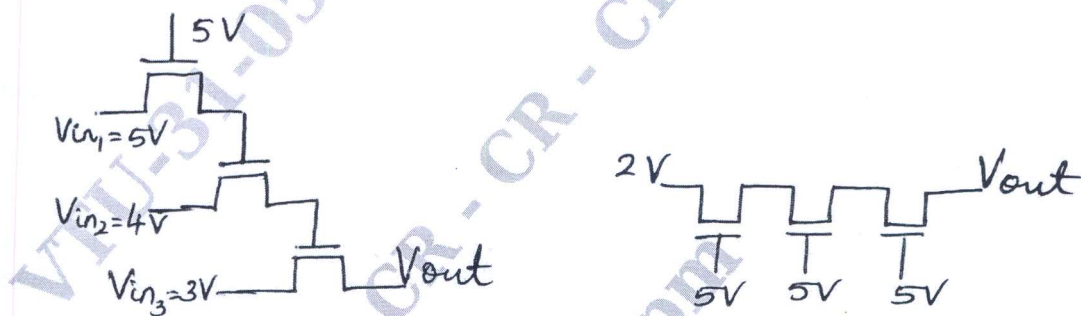


Fig.Q7(a)

- (08 Marks)
- b. With necessary diagrams and equations explain charge storage and charge leakage in dynamic logic. (06 Marks)
- c. With necessary circuit diagrams explain resettable latches with :
- synchronous reset
 - asynchronous reset.
- (06 Marks)
- OR
- 8 a. Explain dynamic logic with an example. Also explain the advantage and limitations of dynamic logic. (08 Marks)
- b. With necessary circuit diagram explain 3 bit dynamic shift register with enhancement load (radio less). (08 Marks)
- c. Explain dynamic synchronous CMOS transmission gate logic with necessary diagrams. (04 Marks)

Module-5

CMRIT LIBRARY
BANGALORE - 560 037

- 9 a. With necessary circuit diagram explain the operation of four transistor DRAM cell. (06 Marks)
- b. Explain the terms : i) controllability ii) observability iii) repeatability iv) survivability. (08 Marks)
- c. Explain full CMOS SRAM cell with necessary circuit topology. (06 Marks)

OR

- 10 a. Explain CMOS bridging fault with necessary example. (06 Marks)
- b. What is a fault model? Explain stuck at fault model with examples. (08 Marks)
- c. Draw the circuit of 3 bit BILBO register and explain. (06 Marks)
