

# CBCS SCHEME

USN

BESCK104B /BESCKB104

First Semester B.E./B.Tech. Degree Examination, Jan./Feb. 2023

## Introduction to Electrical Engineering


Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

2. VTU Formula Hand Book is permitted.

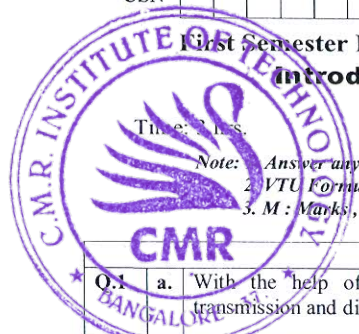3. M: Marks, L: Bloom's level, C: Course outcomes.



Module – 1			M	L	C
Q.1	a.	With the help of single line diagram, explain the electrical power transmission and distribution system.	6	L2	CO2
	b.	Explain the working of hydro power generation using relevant block diagram.	8	L2	CO1
	c.	A resistance R is connected in series with a parallel circuit comprising of two resistance $12\Omega$ and $8\Omega$ . The total power in the circuit is $70W$ , when the applied voltage is $20V$ . Calculate R.	6	L3	CO1
<b>OR</b>					
Q.2	a.	State Kirchhoff's law for DC circuits. Illustrate with an example.	6	L2	CO1
	b.	With the help of block diagram, explain the working of Solar power generation.	8	L2	CO1
	c.	For the circuit shown in Fig. Q2(c), find the current supplied by each battery and power dissipated in $1\Omega$ resistor.	6	L3	CO2
		Fig. Q2(c)			
<b>Module – 2</b>					
Q.3	a.	A pure inductor excited by sinusoidal varying AC voltage, show that the average power consumed by inductor is zero.	8	L2	CO1
	b.	Define i) Real power ii) Reactive power iii) Apparent power iv) Power factor.	6	L1	CO1
	c.	The current in a circuit is $(8 - j10)A$ , when the applied voltage is $(50 + j25)$ volts. Determine i) The magnitude of the current ii) Impedance iii) The circuit elements iv) Power factor v) Power.	6	L3	CO2
<b>OR</b>					
Q.4	a.	Develop an equation for the power consumed by a R – C series circuit. Draw the waveform of voltage, current and power.	8	L2	CO3
	b.	With relevant diagrams, explain the concept of line values of voltage and current and phase values of voltage and currents in $3\phi$ star and delta connections.	6	L2	CO3

BESCK104B/BESCKB104

	c.	A circuit having a resistance of $12\Omega$ on inductors of $0.15H$ and a capacitance of $100\mu F$ in series is connected across a $100V$ , $50Hz$ supply. Calculate i) Impedance ii) Current iii) Power factor iv) Phase difference between the current and supply voltage v) Power.	6	L3	CO3
<b>Module – 3</b>					
Q.5	a.	With the help of neat diagram, explain the construction of DC generator.	8	L2	CO4
	b.	With usual notations, derive the torque equation of a DC motor.	6	L2	CO4
	c.	A d.c. shunt generator has a shunt field winding resistance of $100\Omega$ , it is supplying a load of $5kW$ at a voltage of $250V$ . If its armature resistance is $0.22\Omega$ and per brush voltage drop is $1$ volt. Calculate the induced e.m.f of generator.	6	L3	CO4
<b>OR</b>					
Q.6	a.	Give the classification of DC generator. Obtain the expression for EMF equation of a DC generator.	8	L2	CO4
	b.	With neat diagrams, explain the speed control of DC shunt motor.	6	L2	CO4
	c.	A 4 pole dc shunt motor takes $22 A$ from $220V$ supply. the armature and field resistances are respectively $0.5\Omega$ and $100\Omega$ . The armature is lap connected with $300$ conductors. If the flux per pole is $20$ mwb, calculate i) Speed ii) Gross torque.	6	L3	CO4
<b>Module – 4</b>					
Q.7	a.	Explain the working principle of single phase transformer and its necessity in power system.	8	L1	CO1
	b.	Explain the concept of rotating magnetic field in a 3 – phase induction motor with neat vector diagrams.	6	L2	CO2
	c.	The maximum efficiency at full load and unity power factor of a single – phase $25KVA$ , $500V/1000V$ , $50Hz$ , transformer is $98\%$ . Determine its efficiency at i) $75\%$ load, $0.9$ p.f. ii) $50\%$ load, $0.8$ p.f.	6	L3	CO2
<b>OR</b>					
Q.8	a.	With relevant diagrams, explain the construction of 3 – phase induction motors.	8	L2	CO2
	b.	Derive an EMF equation of single phase transformer with usual notation.	6	L2	CO2
	c.	A 3 – phase, $50Hz$ , 4 pole induction motor, its rotor induced e.m.f is $1.5$ Hz frequency. Calculate i) Synchronous speed ii) Full load slip iii) Actual speed.	6	L3	CO3
<b>Module – 5</b>					
Q.9	a.	List the types of wiring system used for domestic / industry. Explain suitable wiring used for staircase, give the schematic / circuit diagram.	6	L1	CO5
	b.	What is Earthing? With a neat diagram, explain plate earthing.	8	L2	CO5
	c.	Define Unit and Tariff. Explain the two port tariff with its merits and demerits.	6	L2	CO5

BESCK104B/BESCKB104

OR

Q.10	a.	What is Fuse? With neat diagram, explain the working principle of fuse.	6	L2	CO5
	b.	Define Electric shock. What are the safety precaution to be taken against to avoid electric shock?	8	L2	CO5
	c.	An electric boiler draws 6A current at 230V for 4 hrs. The electricity costs Rs 3/- per unit. Determine the total cost.	6	L3	CO5

\*\*\*\*\*

CMRIT LIBRARY  
BANGALORE - 560 037