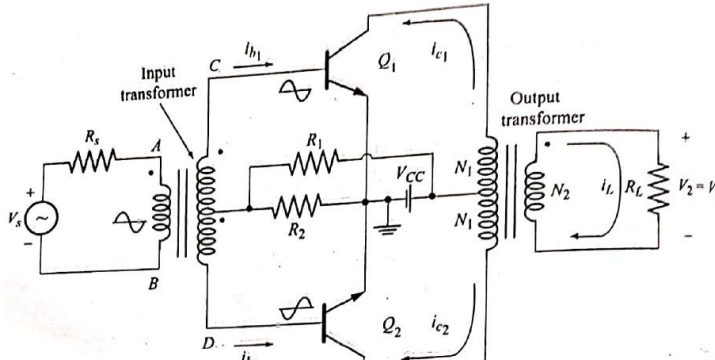
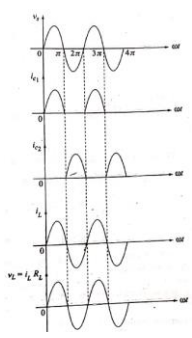


Internal Assessment Test - III

Sub:	Analog Electronic Circuits and Op-Amps	Code:	21EE32
Date:	07.02.2023 8.30am – 10am	Duration:	90 mins
		Max Marks:	50
		Sem:	III
		Branch:	EEE

Answer Any FIVE FULL Questions

		Marks	OBE	
			CO	RBT
1	<p>Explain the operation of Class B push pull amplifier. Prove that the maximum efficiency of Class B amplifier is 78.5%</p> <p>Solution:</p>  <p>During Positive half cycle - Q₁ conducts and Q₂ is off.</p> $i_L = \frac{N_1}{N_2} i_{c1}$ <p>During Negative half cycle – Q₁ is off and Q₂ conducts.</p> $i_L = -\frac{N_1}{N_2} i_{c2}$ <p>Combining both equations</p> $i_L = \begin{cases} \frac{N_1}{N_2} i_{c1} & \text{for } 0 \leq \omega t \leq \pi \\ -\frac{N_1}{N_2} i_{c2} & \text{for } \pi \leq \omega t \leq 2\pi \end{cases}$ <p>or</p> $i_L = \frac{N_1}{N_2} [i_{c1} - i_{c2}]$ 	2	CO4	L3
		2		
		2		

$$\% \eta = \frac{P_{o(ac)}}{P_{i(dc)}} \times 100\%$$

AC output power

$$P_{o(ac)} = \frac{V_{CE(p)} I_{C(p)}}{2}$$

DC input power

$$P_{i(dc)} = V_{CC} I_{dc}$$

average current in each transistor is $\frac{I_{C(p)}}{\pi}$

$$\therefore I_{dc} = 2 [\text{average current in each transistor}]$$

$$= \frac{2I_{C(p)}}{\pi}$$

$$P_{i(dc)} = \frac{2}{\pi} V_{CC} I_{C(p)}$$

$$\% \eta = \frac{\left(\frac{V_{CE(p)} I_{C(p)}}{2} \right)}{\frac{2}{\pi} V_{CC} I_{C(p)}} \times 100\%$$

$$\% \eta = \frac{\pi}{4} \frac{V_{CE(p)}}{V_{CC}} \times 100\%$$

$$V_{CE(p)} = V_{CC}$$

$$\% \eta_{\max} = \frac{\pi}{4} \times 100\% = 78.54\%$$

4


2 With the help of neat diagrams, explain the construction, working and characteristics of N-channel depletion type MOSFET.

CO5 L2

Solution:

- Metal Oxide Semiconductor Field Effect Transistor (or) Metal Oxide Silicon Field Effect Transistor.
- Also called as IGFET (Insulated Gate Field Effect Transistor).
- Operated in both Depletion mode and Enhancement modes of operation.
- ✓ D-MOSFET
- ✓ E-MOSFET

2

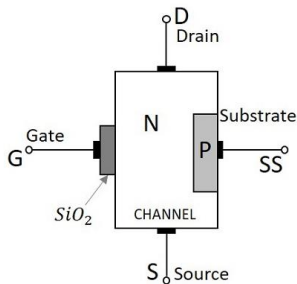

2

- An oxide layer is deposited on the substrate to which the gate terminal is connected.
- This oxide layer acts as an insulator (SiO₂ insulates from the substrate), and hence the MOSFET has another name as IGFET


In the construction of MOSFET, a lightly doped substrate, is diffused with a heavily doped region. Depending upon the substrate used, they are called as **P-type** and **N-type** MOSFETs.

2

- The voltage at gate controls the operation of the MOSFET.
- In this case, both positive and negative voltages can be applied on the gate as it is insulated from the channel.


With negative gate bias voltage, it acts as **Depletion mode** while with positive gate bias voltage it acts as an **Enhancement mode**.

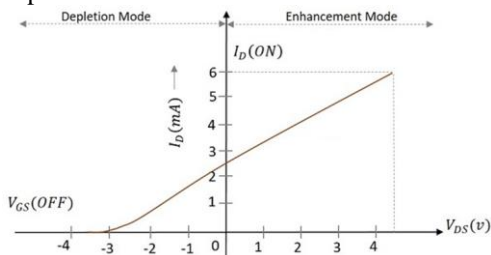Transfer characteristics define the change in the value of **V_{DS}** with the change in **I_D** and **V_{GS}** in both depletion and enhancement modes



2

Symbol of N-Channel D-MOSFET

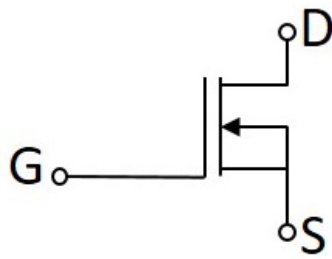

2

3 A series fed Class A amplifier operates from dc source and applied sinusoidal input signal generates peak base current 9mA, Calculate I_{CQ} , V_{CEQ} , P_{dc} , P_{ac} and efficiency. Given values are $R_B = 1.5K\Omega$, $R_L = 16\Omega$, $\beta = 50$, $V_{BE} = 0.7V$, $V_{CC} = 20V$.

Solution:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{20 - 0.7}{1.5K\Omega} = 12.8mA$$

$$I_{CQ} = \beta I_B = 50 \times 12.8 = 640mA$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_L = 20 - (640 \times 16\Omega) = 9.76V$$

$$P_{dc} = V_{CC} \times I_{CQ} = 20 \times 640 = 12800mW$$

$$P_{ac} = \frac{(I_{CP})^2 R_L}{2}$$

$$I_{CP} = \beta I_{B(P)} = 50 \times 9 = 450mA$$

$$P_{ac} = \frac{(450)^2 (16\Omega)}{2} = 1620mW$$

$$\% \eta = \frac{P_{ac}}{P_{dc}} \times 100 = \frac{1620}{12800} \times 100 = 12.66\%$$

2

2

2


2

2

4 Explain the 3 Op-Amp instrumentation amplifier and derive the expression for output voltage.

Solution:

Instrumentation amplifier is a high gain differential amplifier with high CMRR value and also allows to adjust the gain of the amplifier circuit without having to change more than one resistor value. The op-amps A1 & A2 are the non-inverting amplifier forming the first stage of the Instrumentation Amplifier. The op-amp A3 is the normal difference amplifier forming the output stage of the Instrumentation Amplifier.

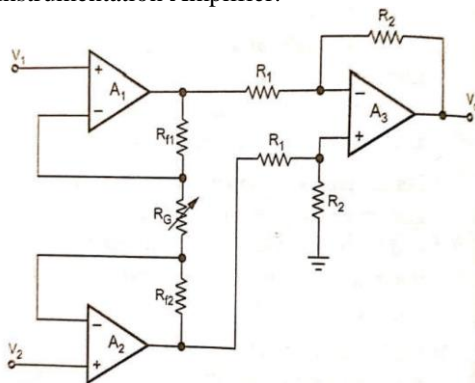

$$V_o = \frac{R_2}{R_1} (V_{o2} - V_{o1})$$

2

2

1

CO4

L3

CO6

L2

Applying Ohm's law between the nodes E and F we get,

$$I = \frac{V_{o1} - V_{o2}}{R_{f1} + R_G + R_{f2}}$$

Let $R_{f1} = R_{f2} = R_f$

$$\therefore I = \frac{V_{o1} - V_{o2}}{2R_f + R_G}$$

Now from the observation of nodes G and H,

$$I = \frac{V_G - V_H}{R_G} = \frac{V_1 - V_2}{R_G}$$

Equating the two equations (1.30.4) and (1.30.5),

$$\frac{V_{o1} - V_{o2}}{2R_f + R_G} = \frac{V_2 - V_1}{R_G}$$

$$\therefore \frac{V_{o2} - V_{o1}}{2R_f + R_G} = \frac{V_1 - V_2}{R_G}$$

$$\therefore V_{o2} - V_{o1} = \frac{(2R_f + R_G)(V_2 - V_1)}{R_G}$$

Substituting the $V_{o2} - V_{o1}$ in the equation (1.30.1),

$$V_o = \frac{R_2}{R_1} \left[\frac{2R_f + R_G}{R_G} \right] (V_2 - V_1)$$

$$\therefore V_o = \frac{R_2}{R_1} \left(1 + \frac{2R_f}{R_G} \right) (V_2 - V_1)$$

2

3

5 Design a first order low pass Butterworth filter at a cutoff frequency of 1KHz with pass band gain of 2 and also draw its circuit diagram.

Solution:

Solution : Step 1 : Cut-off frequency $f_H = 1 \text{ kHz}$

Step 2 : Choose $C = 0.001 \mu\text{F}$

Step 3 : $f_H = \frac{1}{2\pi RC}$ i.e. $R = \frac{1}{2\pi \times 0.001 \times 10^{-6} \times 1 \times 10^3}$


$\therefore R = 159.15 \text{ k}\Omega$ (Use $150 \text{ k}\Omega$)

Step 4 : $A_F = 2$ but $A_F = 1 + \frac{R_f}{R_1}$

$\therefore \frac{R_f}{R_1} = 1$ i.e. $R_f = R_1$

Choose $R_f = R_1 = 10 \text{ k}\Omega$

The designed circuit is shown in the

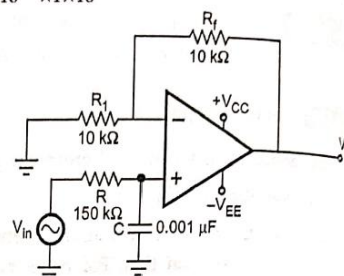

2

2


2

2

2

6 Explain the op-amp series voltage regulator with neat circuit diagram. Define Line regulation and Load regulation with respect to voltage regulator.

Solution:

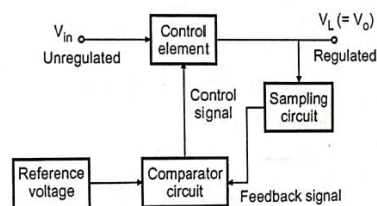

3

CO6

L6

CO6

L2

The unregulated d.c. voltage is the input to the circuit.

The control element, controls the amount of the input voltage, that gets to the output. The sampling circuit provides the necessary feedback signal. The comparator circuit compares the feedback with the reference voltage to generate the appropriate control signal.

For example, if the load voltage tries to increase, the comparator generates a control signal based on the feedback information. This control signal causes the control element to decrease the amount of the output voltage. Thus the output voltage is maintained constant.

Two basic categories of voltage regulation are:

❖ **Line regulation and**

❖ **Load regulation**

The purpose of line regulation is to maintain a constant output voltage when the **input voltage changes**.

The purpose of load regulation is to maintain a nearly constant output voltage when the **load varies**

3

2

2