

USN

--	--	--	--	--	--	--	--	--	--	--



Internal Assessment Test 3 – Feb. 2023

Sub:	Digital System Design using Verilog				Sub Code:	21EC32	Branch:	ECE	
Date:	08-02-2023	Duration:	90 Minutes	Max Marks:	50	Sem / Sec:	3/A,B,C,D		OBE
<u>Answer any FIVE FULL Questions</u>							MARKS	CO	RBT
1 (a)	Write the characteristics equation for SR flip-flop & T flip –flop, and draw the excitation table for the JK flip-flop.					[04]	CO3	L1	
1 (b)	Design a Mod-6 synchronous counter using T Flip-flop.					[06]	CO3	L2	
2	Design a 4-bit universal shift register using positive edge triggered D-flip-flop and multiplexers to operate as indicated below:					[10]	CO3	L3	
		Mode select		Operation					
		00		Hold					
		01		Right Shift					
		10		Left Shift					
		11		Parallel Load					
3	Design a 4-bit ripple counter using JK flip-flop along with the waveforms. Compare the counters based shift register.					[10]	CO3	L2	
4	Illustrate with examples the data types used to define nets, registers, vectors and arrays.					[10]	CO4	L2	
5	Write the Verilog code for the Half Adder using the data-flow description, assign a delay time to the signal assignment statement with the timing waveform.					[10]	CO4	L3	
6	Illustrate the IF statement, IF as ELSE-IF, signal and variable assignment with an example.					[10]	CO4	L3	
7	Explain the behavioral description of a Positive Edge-Triggered JK flip-flop using the CASE statement with the timing waveform.					[10]	CO4	L2	

COURSE INSTRUCTOR

CCI

HOD

21EC32 - Digital System Design using Verilog

Internal Assessment Test 3

Answer Key

1. a) Characteristic Equation

SR Flip-Flop: $Q^+ = S + R'Q$

T Flip-Flop: $Q^+ = TQ' + T'Q$

(1 Mark)

(1 Mark)

Excitation Table:

Q	Q ⁺	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

(2 Marks)

1. b) Mod-6 synchronous counter using

Q _A	Q _B	Q _C	Q _A ⁺	Q _B ⁺	Q _C ⁺	T _A	T _B	T _C
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	0	0	0	1	0	1

T-Flip-Flop

A	BC	00	01	11	10
0				1	
1		1	X		X

$T_A = BC + AC$


$T_C = C(A+B)$

A	BC	00	01	11	10
0		1	1		
1			X	X	

$T_B = \bar{A}C$

$T_C = 1$ (2 Marks)


(2 Marks)

 

(2 Marks)


2. 4-bit Universal Shift Register

Mode select	Operation
00	Hold
01	Right shift
10	Left shift
11	parallel Load

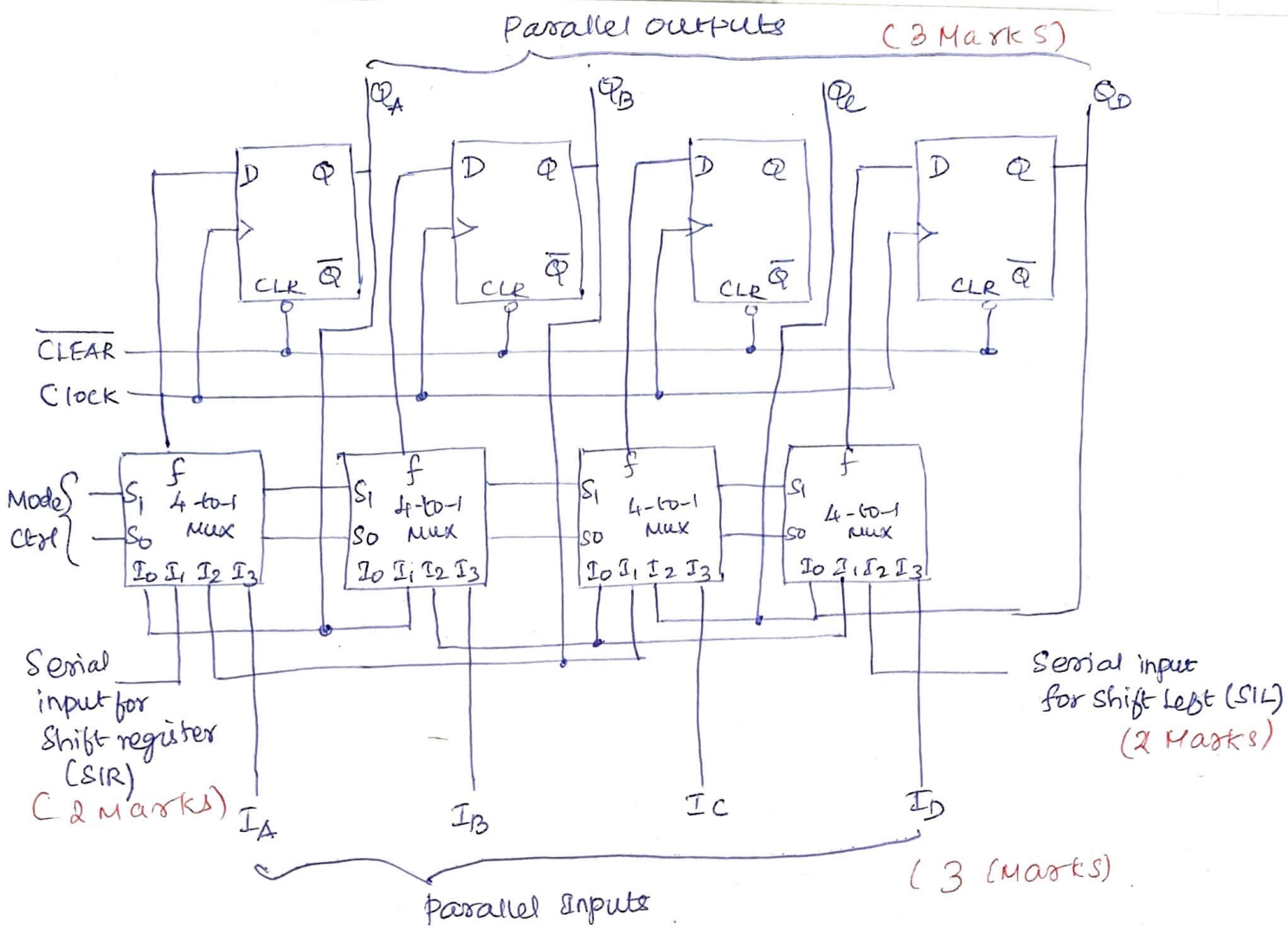

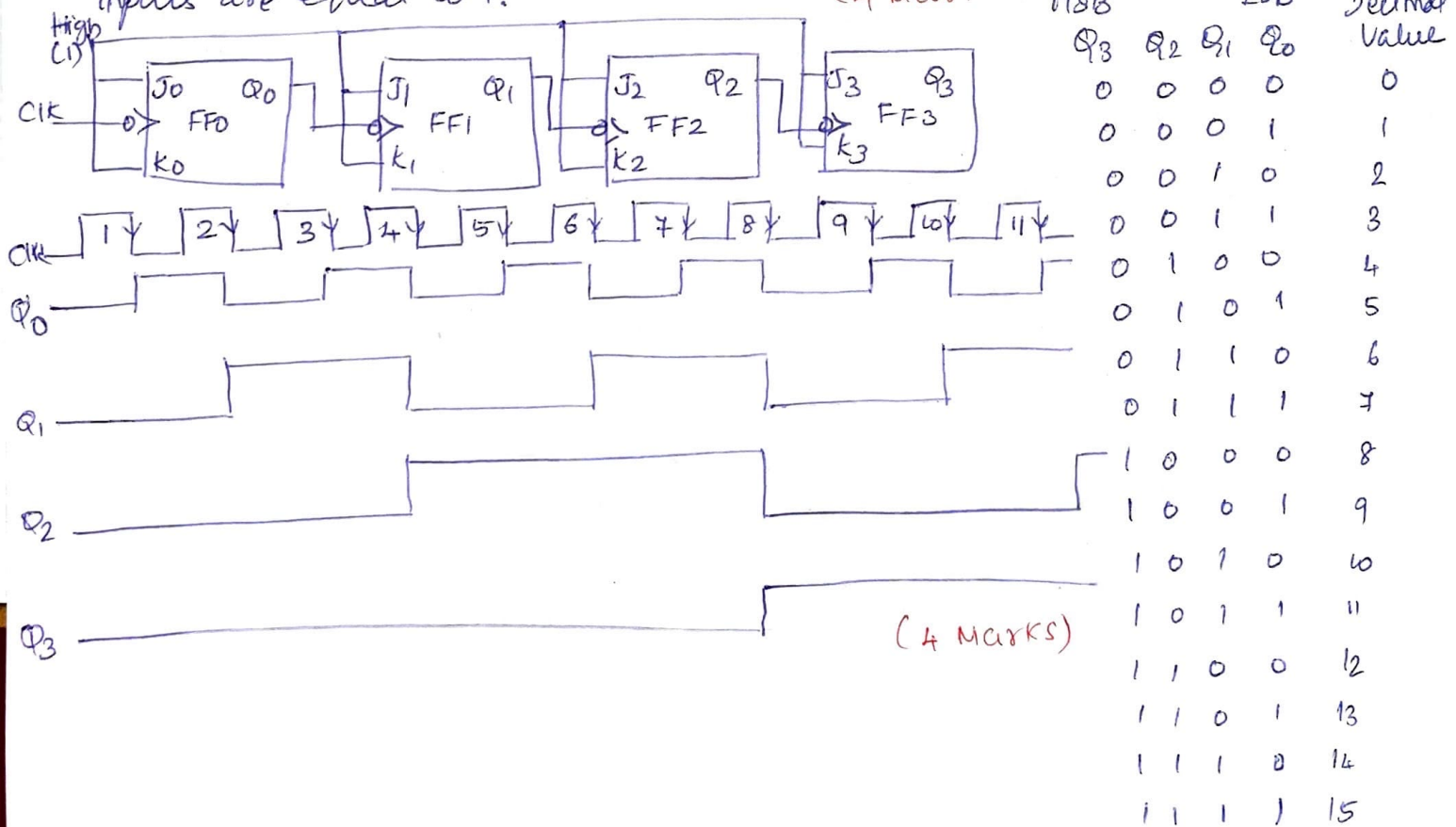3. 4-bit Ripple counter using JK Flip-Flops. (2 Marks)

A binary ripple counter consists of a series connection of complementing flip-flops, with the output of each flip-flop connected to the clock-pulse input of the next-higher order flip flop. All J and K inputs are equal to 1. (4 Marks)



4. Verilog Data Types

Verilog supports several data types, including: nets, registers, vectors, integers, real, parameters and arrays.

Nets: It is declared by the predefined word `wire`. Nets have value that change continuously by the circuits that are driving them.

(2 marks)

Verilog Net Values

Value	Definition
0	logic 0 (false)
1	logic 1 (true)
x	unknown
z	High impedance

Example:

```
wire sum; (Declares a net by name sum)
wire s1 = 1'b0; (initial value of s1 is declared).
```

Registers: It stores the value until they are updated. It is defined by the predefined word `reg`.

(4 marks)

Verilog Register Values

Value	Definition
0	Logic 0 (false)
1	logic 1 (true)
x	unknown
z	High impedance

Example:

```
reg sum_total;
The statement declares a register by the name sum_total.
```

Vectors: Vectors are multiple bits. A register or a net can be declared as a vector. Vectors are declared by brackets `[]`.

(2 marks)

Example:

```
wire [3:0] a = 4'b1010;
reg [7:0] total = 8'd12;
```

The statement declares net `a`. It has 4-bits and its initial value is 1010. The second statement describes a register `total`. Its size is 8 bits and decimal value is 12.

(2 marks)

Arrays: It does not have a predefined word for array.

Registers and integers can be written as arrays.

Example:


```
parameter N = 4;
parameter M = 3;
reg signed [M:0] carry[0:N];
reg [M:0] b[0:N];
integer sum[0:N];
```

5. Verilog Half Adder Description - Dataflow

```

module half-adder(a,b,s,c);
input a,b;
output s,c;
assign #10 s = a ^ b;
assign #10 c = a & b;
endmodule
    
```

(6 marks)

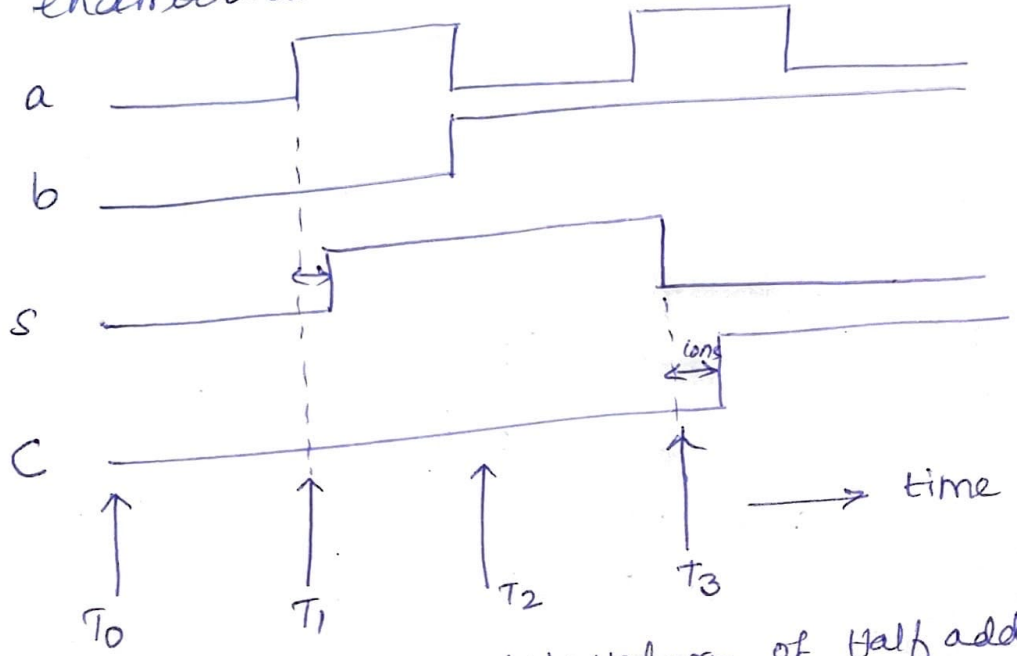

(4 marks)

Simulation Waveform of Half adder

(6 marks)

6. IF statement

Execution of IF as else-IF.

```

Verilog code
if (Boolean Expression)
begin
    statement 1;
    statement 2;
    ...
end
else
begin
    statement a;
    statement b;
    ...
end
    
```

```

Verilog code
if (Boolean Expression 1) then
statement 1; statement 2; ...
elseif (Boolean Expression 2) then
statement i; statement ii; ...
else
statement a; statement b; ...
end if
    
```

Example

```

Eg: if (CLK == 1)
begin
temp = S1;
end
    
```

```

if (signal 1 == 1)
temp = S1;
else if (signal 2 == 1)
temp = S2;
else
temp = S3;
    
```



Signal and Variable Assignment

(4 marks)

```
Example: module D_latch (d, E, Q, Qb);  
input d, E;  
output Q, Qb;  
reg Q, Qb;  
always @ (d, E)  
begin  
if (E == 1)  
begin Q = d;  
Qb = ~Q;  
end  
end  
endmodule
```

  7. Positive-Edge Triggered JK Flip-flop

positive edge Flip-Flops sample the input only at the positive edges of the clock; any change in the input that does not occur at the edges is not sampled by the output. (4 marks)



State diagram

Verilog Positive Edge-Triggered JK Flip-Flop using case

```
module JK-FF (JK, clk, q, qb);
```

(6 marks)

```
input [1:0] JK;
```

```
input clk;
```

```
output reg q, qb;
```

```
always @ (posedge clk)
```

```
begin
```

```
case (JK)
```

```
2'd0: q = q;
```

```
2'd1: q = 0;
```

```
2'd2: q = 1;
```

```
2'd3: q = ~q;
```

```
endcase
```

```
qb = ~q;
```

```
end
```

```
endmodule
```