 


# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EC56



**Fifth Semester B.E. Degree Examination, June/July 2023**

## Verilog HDL

Time: 3 hrs

Max. Marks: 100

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

### Module-1

- Explain typical design flow for designing VLSI IC circuits with a neat flow chart. (10 Marks)
  - Explain top-down design methodology and bottom-up design methodology. (06 Marks)
  - Explain trends in HDL's. (04 Marks)

OR

- Explain design hierarchy by taking 4-bit ripple carry counter. (08 Marks)
  - Define the following terms with examples "
    - Module
    - Instances
    - Instance name. (06 Marks)
  - Explain the different levels of abstraction used for programming in verilog. (06 Marks)

### Module-2

- With a neat block diagram, explain the components of verilog module. (08 Marks)
  - Explain \$display, \$monitor, \$finish and \$stop system tasks with examples. (08 Marks)
  - How to write comments in verilog HDL, explain with examples. (04 Marks)

OR

- Explain the following data types of with an examples :
    - Nets
    - Registers
    - Integers
    - Parameters. (08 Marks)
  - Write verilog description of SR latch. Also write stimulus code. (08 Marks)
  - With an example, explain hierarchical names. (04 Marks)

### Module-3

- What are Rise, Fall and Turn-off delays? How they are specified in verilog. (06 Marks)
  - Write a verilog dataflow level of abstraction for 4 to 1 multiplexer using conditional operator. Also write stimulus code. (08 Marks)
  - Design a gate level module according to the logic diagram given Fig.Q5(c). Write stimulus code delay. (06 Marks)

 


Fig.Q5(c)

1 of 2

(06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 6 a. Develop a gate-level verilog code for 4-bit ripple carry adder from 1-bit full adder. What is the output if  $A = 1010$ ,  $B = 1100$  and  $c_{in} = 0$  at  $t = 0$ . (10 Marks)
- b. What would be the output of the following :  
 $a = 4'b0111$ ,  $b = 4'b1001$
- $\&b$
  - $a \ll 2$
  - $\{a, b\}$
  - $\{2\{b\}\}$
  - $a \wedge b$
  - $a|b$
  - $a \& b$
  - $\sim a$ .
- (08 Marks)
- c. Declare following variables in Verilog,  
 i) A 8-bit vector called a – in  
 ii) An integer called count. (02 Marks)

Module-4

- 7 a. Discuss sequential and parallel blocks with examples. (08 Marks)
- b. Write a verilog behavioral description of 8 : 1 multiplexer using case statement. (06 Marks)
- c. Illustrate the use while loop and repeat loop with examples. (06 Marks)

OR

- 8 a. Explain blocking and non-blocking assignment statements with relevant examples. (08 Marks)
- b. Write verilog behavioral description of 4-bit binary counter. (06 Marks)
- c. Write the verilog behavioral description of Dflip – flip. (06 Marks)

Module-5

- 9 a. Define the term logic synthesis. With a neat flow-chart explain computer – Aided logic synthesis process. (10 Marks)
- b. What will the following statement translate to when run on a logic synthesis tool,  
 i)  $assign\ y = (a\&b) | (c\&b)$  where y, a, b, c and d are 3 – bit vectors  
 ii) `if(s)  
     out = i1 ;  
 else  
     out = i0 ;`

**CMRIT LIBRARY**  
 BANGALORE - 560 037

(10 Marks)

OR

- 10 a. With neat flow diagram explain synthesis design flow. (10 Marks)
- b. Write a notes on :  
 i) Assign and deassign  
 ii) Overriding parameters. (10 Marks)

\*\*\*\*\*