



Fourth Semester B.E. Degree Examination, June/July 2023
Linear Integrated Circuits

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain the basic circuit of operational amplifier. (08 Marks)
- b. Sketch an illustration to show the effect of op-amp slew rate and explain. (04 Marks)
- c. Define the following op-amp parameters and write their typical values for op-amp 741 : (04 Marks)
(i) CMRR (ii) PSRR

OR

- 2 a. Design a non-inverting amplifier to provide a gain of 100 for an input of 50 mV. Draw the circuit diagram of the same. Use op-amp 741. $I_{Bmax} = 500$ nA (08 Marks)
- b. Sketch an op-amp difference amplifier circuit. Derive an equation for the output voltage and explain the operation. (08 Marks)

Module-2

- 3 a. Explain the operation of a high Z_{in} voltage follower based AC amplifier. Prove that its Z_{in} is very large, ideally. (08 Marks)
- b. Using a LF 353 BIFET op-amp design a high Z_{in} capacitor coupled non inverting amplifier to have a low cut off frequency of 200 Hz. The input and output voltages are 15 mV and 3 V respectively. The minimum load resistance is 12 K Ω . Draw the circuit diagram. (08 Marks)

OR

- 4 a. Using op-amp 741, design a constant voltage source to provide 6 V. The load resistance is 100 Ω and the available supply voltage is ± 12 V. Use zener diode IN.753 transistor 2N 718, $V_2 = 6.3$ V, $I_2 = 20$ mA, $h_{fe(min)} = 20$ (08 Marks)
- b. Sketch the complete circuit of an instrumentation amplifier and explain its operation. (08 Marks)

Module-3

- 5 a. Draw the op-amp sample and hold circuit and explain its operation with relevant waveforms. (08 Marks)
- b. Using a 741 op-amp with a supply of ± 12 V, design a RC phase shift oscillator to have an output frequency of 3.5 kHz. $I_{B(max)} = 500$ nA ($A_v \geq 29$) (08 Marks)

OR

- 6 a. Sketch the circuit of a capacitor coupled zero-crossing detector. Show the waveforms at various points in the circuit and explain its operation. (08 Marks)
- b. Draw the circuit diagram of logarithmic amplifier. Derive the expression for output voltage. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-4

- 7 a. Design a second order low pass filter using op-amp 741, for a cut off frequency of 2 kHz. Draw the circuit diagram. $I_{B(max)} = 500 \text{ nA}$ (08 Marks)
- b. Using 741, op-amp, design a single stage bandpass filter for a center frequency of 2 kHz and the pass band is to be approximately $\pm 100 \text{ Hz}$ on each side of 2 kHz. ($I_{B(max)} = 500 \text{ nA}$). (08 Marks)

OR

- 8 a. With neat diagram, explain the working of series op-amp regulator. (08 Marks)
- b. Design a voltage regulator using IC723 to get a O/P voltage of 5 V. Draw the circuit diagram. (08 Marks)

Module-5

- 9 a. Draw the block diagram of PLL and explain its operation. (08 Marks)
- b. Briefly explain the working of 3-bit binary weighed DAC. (08 Marks)

CMRIT LIBRARY
BANGALORE - 560 037

- 10 a. Explain 555 timer as monostable multivibrator with relevant circuit diagram and waveforms. (08 Marks)
- b. For an astable multivibrator, given $R_A = 6.8 \text{ K}\Omega$, $R_B = 3.3 \text{ K}\Omega$, $C = 0.1 \mu\text{f}$. Calculate
- t_{High}
 - t_{low}
 - Duty cycle
 - Free running frequency f.
- Draw the circuit diagram. (08 Marks)
