



CBCS SCHEME

15EC33

Third Semester B.E. Degree Examination, June/July 2023 Digital Electronics

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. A digital system has three inputs A, B and C and one output Y. If $A = B$ then Y is complement of C. If $A \neq B$ then Y is same as C. Draw the truth table of the system and express the output as sum of minterms and product of maxterms in decimal notation. (06 Marks)
- b. Simplify the function $F(w, x, y, z) = \pi(3, 4, 6, 7, 11, 12, 13, 14, 15)$ using K-map and write the simplified expression as product of sums. (05 Marks)
- c. Simplify the function $F(a, b, c, d) = \Sigma(3, 5, 7, 10, 11, 13, 14) + \Sigma_d(1, 9, 12, 15)$ using K-map and write the simplified expression as sum of products. (05 Marks)

OR

- 2 a. Simplify $F(a, b, c, d) = \Sigma_m(0, 1, 5, 6, 8, 9, 11, 13) + \Sigma_d(7, 10, 12)$ using QM method. Identify the essential prime implicants and write the final expression. (10 Marks)
- b. Realize $F = \overline{xz} + x\overline{z} + y$ using only NAND gates, and then using only NOR gates. (06 Marks)

Module-2

- 3 a. Design a full subtractor and implement the same using two half subtractors and an additional gate. (08 Marks)
- b. Explain 4-bit carry look-ahead adder with block diagram and logic diagrams. (08 Marks)

OR

- 4 a. Design a 2-bit magnitude comparator to compare two 2-bit numbers, and realize the same using any logic gates. (08 Marks)
- b. Give the truth table of full-adder, and implement the same using one 3 : 8 decoder with active-two outputs and additional gates. (08 Marks)

Module-3

- 5 a. With a neat diagram, explain the operation of negative edge triggered master slave D flip-flop. Draw sample waveforms to support the exploration. (06 Marks)
- b. With diagram and neat waveforms, explain how SR latch can be used as switch debouncer. (06 Marks)
- c. With a neat diagram, show how JK flip-flop can be converted into D flip-flop and T flip-flop. (04 Marks)

OR

- 6 a. Draw Q and \overline{A} output waveforms of a negative edge triggered JK flip-flop if the inputs are as indicated in Fig.Q6(a). (04 Marks)

 


Fig.Q6(a)

- b. Using K-map simplification, obtain the characteristics equations of SR, JK and T flip-flops. (06 Marks)
- c. Draw the circuit of positive edge triggered D-flip-flop using NAND gates and explain its operation. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8=50, will be treated as malpractice.

CMRIT LIBRARY
REFERENCE

Module-4

- 7 a. Construct 3-bit ripple up counter using negative edge-triggered T-flip-flops, and draw the waveforms showing all the states. (08 Marks)
 b. Construct 3-bit parallel-in serial-out shift register using positive edge-triggered D-flip-flops and example the operation. (08 Marks)

OR

- 8 a. Design a synchronous counter having the count sequence 0, 2, 3, 5, 6 using D-flip-flops. (08 Marks)
 b. Design mod-6 ripple counter using negative edge triggered JK flip-flops having clear inputs. Draw the waveform showing all the states. (08 Marks)

Module-5

- 9 a. With block diagrams, explain the Moore and Mealy models of synchronous sequential circuits. (08 Marks)
 b. Analyze the sequential circuit given in Fig.Q9(b) and obtain the transition and state tables. (08 Marks)

 


Fig.Q9(b)

(08 Marks)

OR

- 10 a. Design a sequential circuit for the state diagram shown in Fig.Q10(a) using D flip-flops. Assume $S_1 = 00$, $S_2 = 01$, $S_3 = 10$.

 


Fig.Q10(a)

(12 Marks)

- b. Give the application tables or excitation tables of D, T, SR and JK T-flip-flops. (04 Marks)
