

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

18CS33



Third Semester B.E. Degree Examination, Jan./Feb. 2023

**Analog and Digital Electronics**

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

SOLUTION

**Sub: Analog and Digital Electronics**

**Sub Code: 18CS33**

**Session: July 2022/ Jan 2023**

**Branch: CSE**

**Course Instructor:**

**Prof. Pratham Majumder**

**&**

**Prof. Paramita Mitra**

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

**Module-1**

- 1 a. Explain the construction and working principle of LED. (05 Marks)
- b. List the types of transistor biasing. Explain Fixed Bias Circuit with necessary analysis. (06 Marks)
- c. Explain the operation of astable multivibrator using IC555 and derive the expression for time period, frequency and duty cycle. (09 Marks)

OR

- 2 a. Explain the operation of peak detector circuit with neat diagram. (05 Marks)
- b. List and explain the performance parameters of regulated power supply. (06 Marks)
- c. Explain the 3 bit flash type ADC with necessary circuit and truth table. (09 Marks)

**Module-2**

- 3 a. Find the minimum sum of products using K-map and identify prime implicants.  
 $f(a, b, c, d) = \sum m(0,2,6,10,11,12,13) + d(3,4,5,14,15)$  (06 Marks)
- b. Find the minimum SOP and POS using K-map.  
 $f(a, b, c, d) = \sum m(6,7,9,10,13) + d(1,4,5,11)$  (08 Marks)
- c. List the steps for Petrick's method. (06 Marks)

OR

- 4 a. Find all the prime implicants using Quine Mc Cluskey method. Verify the result using K-map.  
 $f(w, x, y, z) = \sum m(7,9,12,13,14,15) + d(4,11)$  (12 Marks)
- b. Using Prime implication chart, find all the minimum SOP of the function using Quine McCluskey method.  
 $f(a, b, c, d) = \sum m(0,1,2,3,10,11,12,13,14,15)$  (08 Marks)

**Module-3**

- 5 a. Realize the function using only two input NAND gate and inverters.  
 $f_1 = \sum m(0,2,3,4,5)$ ,  $f_2 = \sum m(0,2,3,4,7)$ ,  $f_3 = \sum m(1,2,6,7)$  (06 Marks)
- b. Draw the timing diagram of the circuit. Assume propagation delay of each gate is 20 ns. (05 Marks)

 


Fig. Q5 (b) - (i)

Fig. Q5 (b) - (ii)

- c. List the types of hazards. Explain how static 1 hazard can be detected and removed with suitable example. (09 Marks)

OR

- 6 a. Write short notes on three state buffers. (06 Marks)  
b. Design 7-segment decoder using PLA. (06 Marks)  
c. Construct 8 : 1 mux using only 2 : 1 mux. (08 Marks)

Module-4

- 7 a. Given that A = "00101101" and B = "10011", Determine the value of F  
 $F \leftarrow \text{not } B \& "0111" \text{ or } A \& "1" \text{ and } "1" \& A$  (04 Marks)  
b. Write the complete VHDL code for 4 bit binary adder. (08 Marks)  
c. Explain how the VHDL code can be compiled simulated and synthesized with example. (08 Marks)

OR

- 8 a. Explain T Flip Flop with truth table. (07 Marks)  
b. Explain Master-Slave JK flip flop with neat diagram. (08 Marks)  
c. Write short notes on switch debouncing with an SR Latch. (05 Marks)

Module-5

- 9 a. Explain 8 bit serial in serial out shift register. (10 Marks)  
b. Explain n bit parallel adder with accumulator. (10 Marks)

OR

- 10 a. Design and explain mod 8 synchronous counter using JK flip flop. (10 Marks)  
b. Explain how moore transition and states can be constructed with examples. (10 Marks)

\*\*\*\*\*

Answers

Q1

Photodiode: A photodiode is a light detector semiconductor device that converts light energy into electric current or voltage which depends upon the mode of operation.

Construction:

 


Fig ①: Photodiode construction

- The typical construction of a photodiode is shown in fig ①.
- Here construction technique called ion implantation is used where the surface of a layer of N-type is bombarded with P-type silicon ions to produce a P-type layer about  $1\mu\text{m}$  thick.
- During formation of the diode, excess electrons move from n-type to p-type & excess holes move from p-type to n-type this process is called diffusion, resulting in creation of a depletion layer as shown in above fig ①

Astable multivibrator using 555:

→ Astable multivibrator does not have any stable state.  
it is also called as free running multivibrator.  
operation:


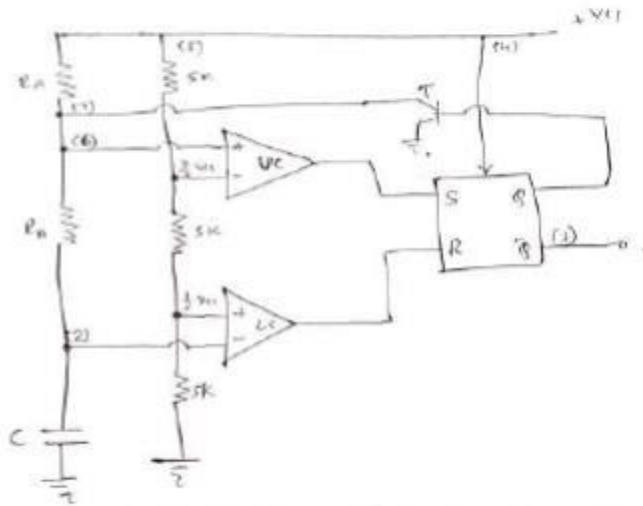


Fig ① Astable multivibrator using 555

 

→ At  $t=0$ , the voltage on the capacitor  $V_c=0$ , the  $V_{cc}$  voltage is applied to both trigger point of lower comparator and upper comparator.

→ As  $V_c=0$ , which is less than  $\frac{1}{3}V_{cc}$ , the output of lower comparator goes high ( $\bar{Q}=1$ ) and  $Q=0$ .

→ The capacitor starts charging through  $R_A$  & when  $V_c$  reaches  $\frac{2}{3}V_{cc}$ , the upper comparator output goes high & it will set the SR FF i.e.  $Q=1$ ,  $\bar{Q}=0$ .

→ The capacitor starts discharging through  $R_B$  transistor  $T$ , when  $V_c = \frac{1}{3}V_{cc}$ , the lower comparator output goes high.

→ This process of charging and discharging is continuous & hence circuit is called digital oscillator.

→ The on period  $T_{on}$  is given by

$$T_{on} = 0.693 (R_A + R_B) C$$

→ The discharging time  $T_{off}$  is

$$T_{off} = 0.693 R_B C$$

→ duty cycle is given by

$$D = \frac{\text{on time}}{\text{Total time}} = \frac{T_{on}}{T}$$

(15)

$$\therefore \% D = \frac{T_{on} \times 100}{T}$$

$$= \frac{0.693 C(R_A + R_B) \cancel{f}}{0.693 C(R_A + 2R_B) \cancel{f}} \times 100$$

$$\therefore \% D = \frac{R_A + R_B}{R_A + 2R_B} \times 100$$

Photodiode: A photodiode is a light detector semiconductor device that converts light energy into electric current or voltage which depends upon the mode of operation.

Construction:

 


Fig ①: Photodiode construction

- The typical construction of a photodiode is shown in fig ①.
- Here construction technique called ion implantation is used where the surface of a layer of N-type is bombarded with P-type silicon ions to produce a P-type layer about  $1\mu\text{m}$  thick.
- During formation of the diode, excess electrons move from n-type to p-type & excess holes move from p-type to n-type this process is called diffusion, resulting in creation of a depletion layer as shown in above fig ①

## Peak detectors:

- Peak detector detects the peak values of non-sinusoidal wave. Peak detector detects and holds the most positive value attained by the input signal.
- Fig ① shows peak detector circuit

 


Fig ① peak detector circuit.

- During positive half cycle of the input, diode is forward biased and capacitor C charges to peak value of input as shown in Fig ②.

### **Q3**

#### **4-bit parallel Adder**

```
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY FA IS  
PORT(A,B,CIN:IN STD_LOGIC;SUM,COUT:OUT STD_LOGIC);  
END FA;
```

```
ARCHITECTURE BEHV OF FA IS  
BEGIN  
SUM<=A XOR B XOR CIN;  
COUT<=(A AND B) OR (B AND CIN) OR (A AND CIN);  
END BEHV;
```

```
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY ADDER_4BIT IS  
PORT(A,B:IN STD_LOGIC_VECTOR(3 DOWNTO 0);S:OUT STD_LOGIC_VECTOR(3 DOWNTO 0);C:OUT STD_LOGIC);  
END ADDER_4BIT;
```

```
ARCHITECTURE BEHV OF ADDER_4BIT IS  
SIGNAL TEMP:STD_LOGIC:= '0';  
SIGNAL CAR:STD_LOGIC_VECTOR(2 DOWNTO 0);  
BEGIN  
FA1:ENTITY WORK.FA PORT MAP(A(0),B(0),TEMP,S(0),CAR(0));
```



```

FA2:ENTITY WORK.FA PORT MAP(A(1),B(1),CAR(0),S(1),CAR(1));
FA3:ENTITY WORK.FA PORT MAP(A(2),B(2),CAR(1),S(2),CAR(2));
FA4:ENTITY WORK.FA PORT MAP(A(3),B(3),CAR(2),S(3),C);


```

END BEHV;

**Q4**

**SR Latch – Switch Debouncing:**

FIGURE 11-9  
Switch Debouncing  
with an S-R Latch

 

When a mechanical switch is opened or closed, the switch contacts tend to vibrate or bounce open and closed several times before settling down to their final position. This produces a noisy transition, and this noise can interfere with the proper operation of a logic circuit. This can be avoided by contacting to SR latch.

The input to the switch in Figure above is connected to a logic 1 (+V). The pull-down resistors connected to contacts *a* and *b* assure that when the switch is between *a* and *b* the latch inputs *S* and *R* will always be at a logic 0, and the latch output will not change state.


The timing diagram shows what happens when the switch is flipped from *a* to *b*.

As the switch leaves *a*, bounces occur at the *R* input; when the switch reaches *b*, bounces occur at the *S* input.


After the switch reaches *b*, the first time *S* becomes 1, after a short delay the latch switches to the *Q* = 1 state and remains there.

Thus *Q* is free of all bounces even though the switch contacts bounce.

 This debouncing scheme requires a *double throw* switch that switches between two contacts; it will not work with a *single throw* switch that switches between one contact and open.



CLK	D	Q	Status
0	X	$Q_0$	No change
↑	0	0	Reset
↑	1	1	Set

 

Q5

Truth Table of T Flip-flop

Input T	Outputs	
	Present State $Q_n$	Next State $Q_{n+1}$
0	0	0
0	1	1
1	0	1
1	1	0

Excitation Table of D Flip-flop


T Input	Outputs		D Input
	Present State $Q_n$	Next State $Q_{n+1}$	
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

Outputs		Input D
Present State $Q_n$	Next State $Q_{n+1}$	
0	0	0
0	1	1
1	0	0
1	1	1

**D to T Conversion Table**

	$Q_n$	
	0	1
$T$	0	1
0	0 <sup>0</sup>	1 <sup>1</sup>
1	1 <sup>2</sup>	0 <sup>3</sup>

$$D = T\bar{Q}_n + \bar{T}Q_n$$

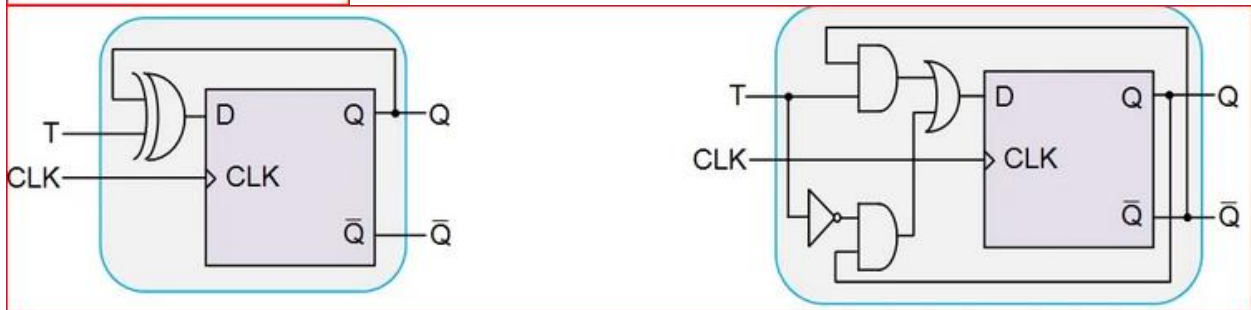
$$= T \oplus Q_n$$


#### Master Slave JK F/F:

In "JK Flip Flop", when both the inputs and CLK set to 1 for a long time, then Q output toggle until the CLK is 1. Thus, the uncertain or unreliable output produces. This problem is referred to as a race-round condition in JK flip-flop and avoided by ensuring that the CLK set to 1 only for a very short time.


The master-slave flip flop is constructed by combining two [JK flip flops](#). These flip flops are connected in a series configuration. In these two flip flops, the 1st flip flop work as "master", called the master flip flop, and the 2nd work as a "slave", called slave flip flop. The master-slave flip flop is designed in such a way that the output of the "master" flip flop is passed to both the inputs of the "slave" [flip flop](#). The output of the "slave" flip flop is passed to inputs of the master flip flop.

 In "master-slave flip flop", apart from these two flip flops, an inverter or [NOT gate](#) is also used. For passing the inverted clock pulse to the "slave" flip flop, the inverter is connected to the clock's pulse. In simple words, when CP set to false for "master", then CP is set to true for "slave", and when CP set to true for "master", then CP is set to false for "slave".



**Q6 D flip-flop**


FIGURE 11-13 D Flip-Flops

 

Next state  $Q^+$  output 1 when  $D=1$

**(b) T flip-flop**


FIGURE 11-22 T Flip-Flop

 

Next state  $Q^+$  output 1 when  $T=1$  and  $Q=0$  or  $T=0$  and  $Q=1$

**(c) S-R latch or flip-flop**


FIGURE 11-8 Derivation of  $Q^+$  for an S-R Latch

 

$Q^+ = S + R'Q$  ( $SR = 0$ )

$Q^+$  -next state     $Q$  -present state

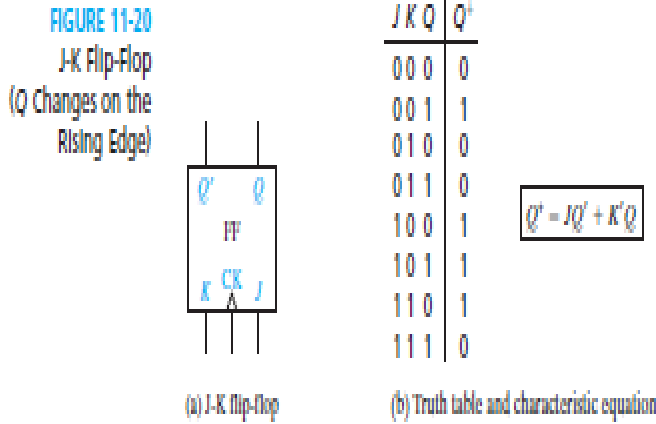
Next state  $Q^+$  output 1 when  $S=1$  or when  $R=0$  and  $Q=1$ .  
 (d) J-K flip-flop



Next state  $Q^+$  output 1 when  $J=1$  and  $Q=0$  or  $K=0$  and  $Q=1$   
 The J-K flip-flop (Figure above) is an extended version of the S-R flip-flop.
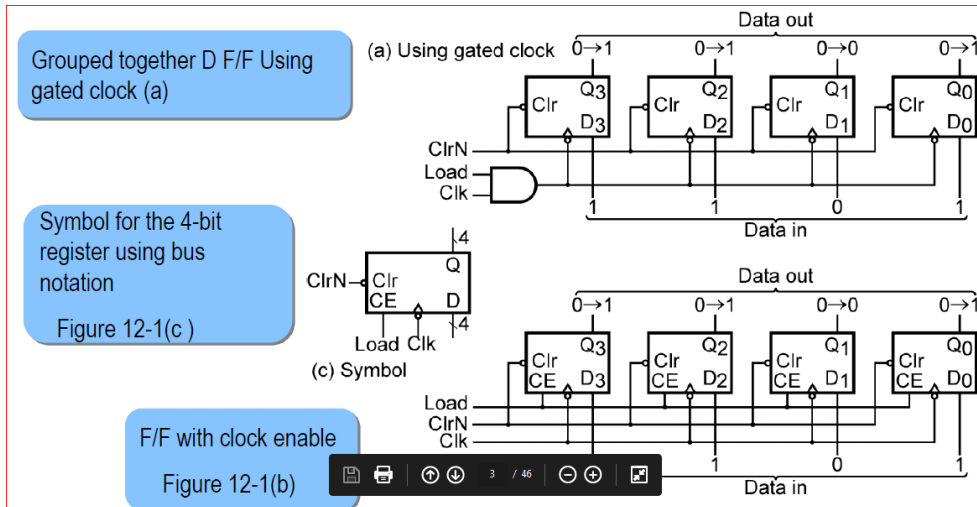
### Register

A Register is a device which is used to store such information. It is a group of flip flops connected in series used to store multiple bits of data.



When it is time to load data into register, Load is set to 1 for one clock period. When, Load = 1, the clock signal (Clk) is transmitted to the FF clock inputs and the data applied to the D FF inputs will be loaded into the FFs on the falling edge of the clock. E.g., if the outputs are 0000 ( $Q_3 = Q_2 = Q_1 = Q_0 = 0$ ) and the data inputs are 1101 ( $D_3 = 1, D_2 = 1, D_1 = 0, D_0 = 1$ ), after the falling edge of the clock Q will change from 0000 to 1101. ClrN is the clear signal. A logic 0 is required to clear the FF.


### T Flip Flop Excitation Table

PRESENT STATE		NEXT STATE	T
0	0	0	0
0	1	1	1
1	0	0	1
1	1	1	0


So, the above table is the excitation table for T Flip Flop.

### State Table with excitation table

PRESENT STATE			NEXT STATE			FLIP FLOP		
$Q_2$	$Q_1$	$Q_0$	$Q_2'$	$Q_1'$	$Q_0'$	$T_2$	$T_1$	$T_0$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

 

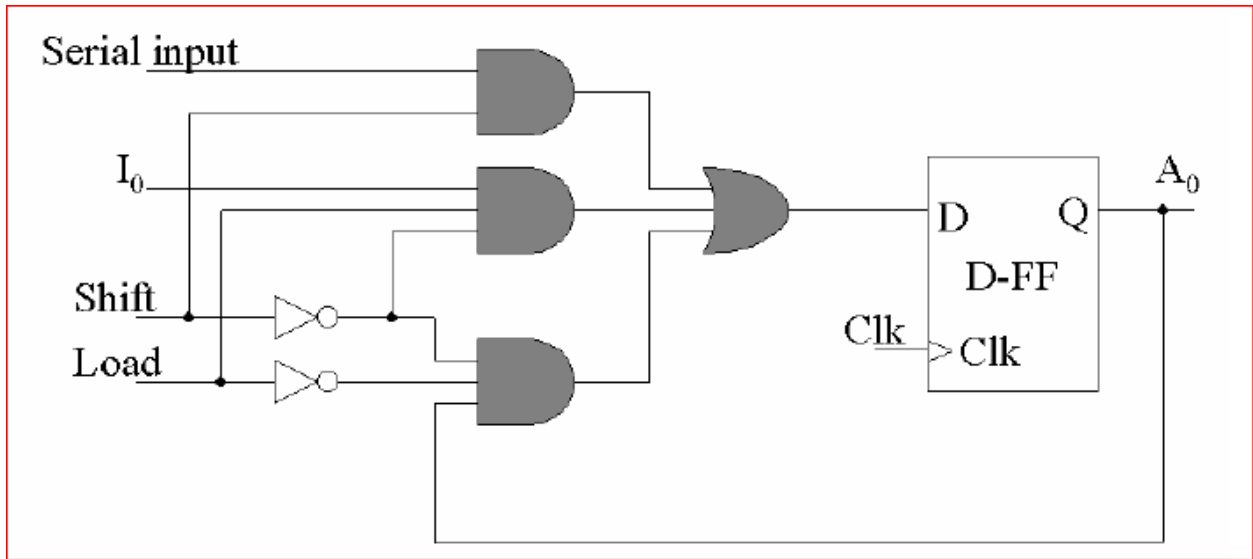**Q8** Design a 4-bit shift register with parallel load using *D flip-flops*. These are two control inputs: shift and load. When shift = 1, the content of the register is shifted by one position. New data is transferred into the register when load = 1 and shift = 0. If both control inputs are equal to 0, the content of the register does not change.





Q9Answer:


□ A parity checker for serial data

- $Z = 1 \Leftrightarrow$  the total number of 1 inputs received is odd (i.e., input parity is odd)
- $Z = 0$  initially

Block diagram

  




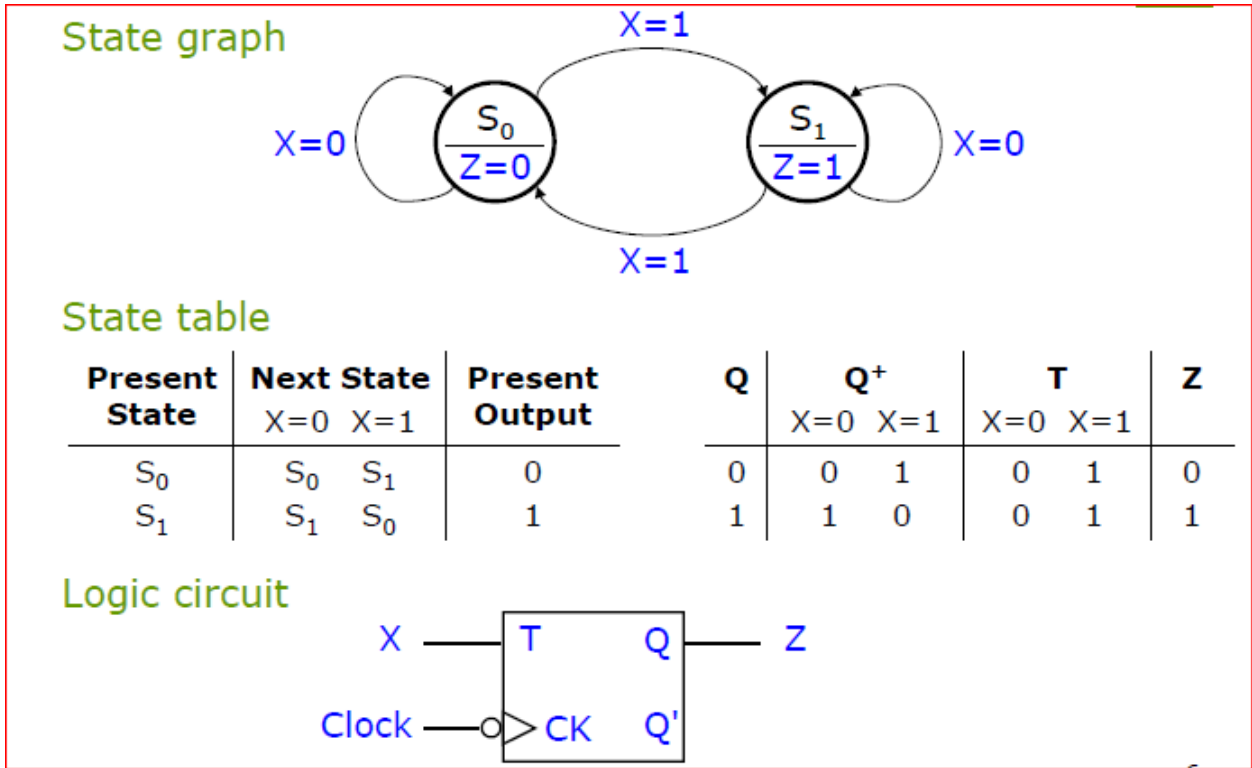

 Q10 ParallelAdder

A single full adder performs the addition of two one bit numbers and an input carry. But a Parallel Adder is a digital circuit capable of finding the arithmetic sum of two binary numbers that is greater than one bit in length by operating on corresponding pairs of bits in parallel. It consists of full adders connected in a chain where the output carry from each full adder is connected to the carry input of the next higher order full adder in the chain. A n bit parallel adder requires n full adders to perform the operation. So for the two-bit number, two adders are needed while for four bit number, four adders are needed and so on. Parallel adders normally incorporate carry lookahead logic to ensure that carry propagation between subsequent stages of addition does not limit addition speed.

Answer: An accumulator is a register for storing short-term & intermediate data generated from any arithmetic or logical data processing or operation.



The circuit shows 4-bit parallel binary adder using a register of flip-flops are known as accumulator. In this design a full adder circuit is used for parallel addition. Initially, carry ( $C_0$ ) is assumed to be zero, i.e.,  $C_0 = 0$  which is applied to the first Full adder i.e.,  $FA_0$ . The 'Ad' signal is used to load the adder o/p into the accumulator on the rising edge of clock. Initially, 4-bit number  $X_3 X_2 X_1 X_0$  is stored in the accumulator. The number (addend)  $Y_3 Y_2 Y_1 Y_0$  is applied to the adder after carry propagation to the adder.

hence, Accumulator =  $X_3 X_2 X_1 X_0$  (augend) at time to  
 addend =  $Y_3 Y_2 Y_1 Y_0$  at time to

$$\begin{array}{r} \text{sum} = S_3 S_2 S_1 S_0 \end{array}$$

If  $S_i = 1$ , after applying this signal into D/F/F at active edge of clock signal  $Q^+ = 1$ , else,  $S_i = 0$  then  $Q^+ = 0$ . This sum  $S_3 S_2 S_1 S_0$  is stored in respective F/Fs and in the next iteration the same value will be used as an augend.

at time to

$$\begin{array}{r} \text{augend} = X_3 X_2 X_1 X_0 \\ \text{addend} = Y_3 Y_2 Y_1 Y_0 \\ \hline \text{accumulator} = S_3 S_2 S_1 S_0 \end{array}$$

at time  $t_1$

$$\begin{array}{r} \text{augend} = S_3 S_2 S_1 S_0 \\ \text{addend} = Y_3' Y_2' Y_1' Y_0' \\ \hline \text{accum.} = S_3' S_2' S_1' S_0' \end{array}$$


at time  $t_2$

$$\begin{array}{r} \text{augend} = S_3' S_2' S_1' S_0' \\ \text{addend} = Y_3'' Y_2'' Y_1'' Y_0'' \\ \hline \text{acc.} = S_3'' S_2'' S_1'' S_0'' \end{array} \quad \text{and so on.}$$


- Moore machine ...

- Output of a sequential circuit is a function of the present state only

- Two examples ...

 

 - The state graph for a Moore machine has the output associated with the state



- Analyze the circuit below ... input sequence  $X = 01101 \dots$  Initial state is  $A = B = 0$
- Initially ...  $X = 0 \dots$  so  $D_A = 1 \dots$  and ...  $D_B = 0$
- The state will change to  $A = 1$  and  $B = 0$  after the first rising clock edge

