

## CBCS SCHEME

USN 

--	--	--	--	--	--	--	--	--	--

21EC34

**Third Semester B.E. Degree Examination, Jan./Feb. 2023**  
**Analog Electronic Circuits**

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

Module-1

- 1 a. Explain the classical discrete circuit bias (voltage divider bias) method of BJT. (08 Marks)  
 b. Explain the three biasing methods to bias MOS Amplifier circuits. (12 Marks)

OR

- 2 a. Explain the T equivalent circuit model of MOSFET. (08 Marks)  
 b. Derive an expression for voltage gain of MOSFET with necessary waveforms. (06 Marks)  
 c. Explain biasing a BJT using collector to base feedback resistor. (06 Marks)

Module-2

- 3 a. Explain the common source amplifier and derive the expression for voltage gain. (10 Marks)  
 b. A transistor amplifier is fed with a signal source having an open circuit voltage  $V_{sig}$  of 10mV and an internal resistance  $r_{sig}$  of 100K $\Omega$ . The voltage  $V_i$  at the amplifier input and the output voltage  $V_o$  are measured both without and with load resistance  $R_L = 10K\Omega$  connected to the amplifier output. The measured results are as follows :

	$V_i$ (mv)	$V_o$ (mv)
Without $R_L$	9	90
With $R_L$ connected	8	70

Find all the amplifier parameters. (10 Marks)

OR

- 4 a. With a neat diagram, explain the three frequency bands of MOSFET. (06 Marks)  
 b. Explain the high frequency model of MOSFET. (06 Marks)  
 c. Explain common source follower and derive the expression of voltage gain. (08 Marks)

Module-3

- 5 a. Explain the properties of negative feedback. (10 Marks)  
 b. Explain the transformer coupled class – A power amplifier and show that efficiency is 50%. (10 Marks)

OR

- 6 a. Explain the circuit operation of class – B power amplifier and also explain the transfer characteristics. (08 Marks)  
 b. Explain the Four basic feedback topologies of the amplifier. (12 Marks)

Module-4

- 7 a. Explain R and 2R resistor digital to analog (D/A) converter and also derive the expression of output voltage. (10 Marks)  
 b. Explain the first order lowpass Butterworth filter with necessary voltage gain. (10 Marks)

1 of 2

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42-8 = 50, will be treated as malpractice.

21EC34

OR

- 8 a. Explain the operation of monostable multivibrator.  
b. Explain the two types of Bandpass filters.

(10 Marks)  
(10 Marks)

Module-5

- 9 a. Explain the block diagram of power electronic system.  
b. List and explain the applications of power electronics.  
c. Explain the static anode – Cathode characteristics of SCR.

(06 Marks)  
(06 Marks)  
(08 Marks)

OR

- 10 a. Explain the turn on methods of a Thyristor.  
b. Explain the construction and working of UJT.


(10 Marks)  
(10 Marks)

\*\*\*\*\*

**Module-1**

- 1 a. Explain the classical discrete circuit bias (voltage divider bias) method of BJT. (08 Marks)  
 b. Explain the three biasing methods to bias MOS Amplifier circuits. (12 Marks)

To get Thevenin equivalent

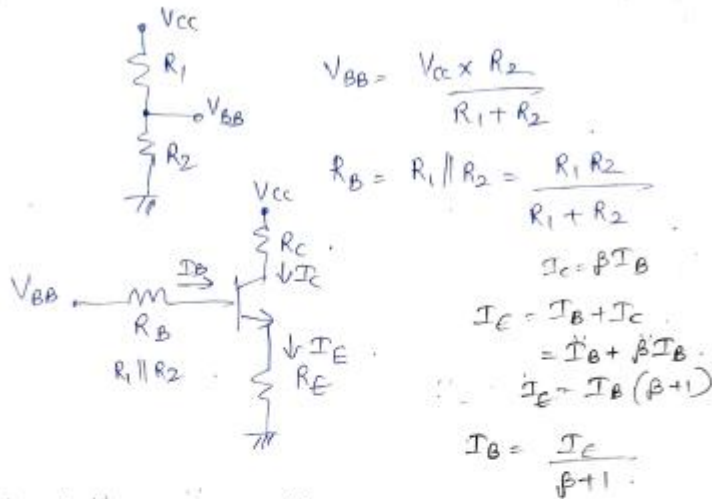

$$V_{BB} = I_B R_B + V_{BE} + I_E R_E$$

$$V_{BB} = \frac{I_E}{\beta + 1} R_B + V_{BE} + I_E R_E$$

$$V_{BB} = I_E \left[ R_E + \frac{R_B}{\beta + 1} \right] + V_{BE}$$

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{\beta + 1}}$$

To make  $I_E$  insensitive to temperature variations and  $\beta$  variation,

$$R_E \gg \frac{R_B}{\beta + 1}$$

$$V_{BB} \gg V_{BE}$$

As a rule of thumb, we design for,

$$V_{BB} = \frac{1}{3} V_{CC}$$

$$V_{CB} \text{ (or } V_{CE}) = \frac{1}{3} V_{CC} \text{ . and}$$

$$I_C R_C = \frac{1}{3} V_{CC} \text{ .}$$

This is required because we cannot make  $V_{BB}$  very very large. Next to get high voltage gain, the voltage  $V_{CB}$  (or  $V_{CE}$ ) should be large to provide a large signal swing.

And  $R_E \gg R_B$ . ~~make~~ <sup>To make</sup>  $I_E$  insensitive to variation in  $\beta$  could be satisfied by selecting  $R_B$  small.

To make  $R_B$  small,  $R_1$  and  $R_2$  values should be low.

Lower values of  $R_1$  and  $R_2$  mean a higher current drain from the power supply and will lower the input resistance of the amplifier [which is not desirable.]

The voltage divider is determining the base voltage. So the current in the voltage divider is made much larger than the base current. So we will select  $R_1$  and  $R_2$  in such a way that their currents is in the range of  $I_E$  to  $0.1 I_E$ .

#### 4.5 Biasing in MOS Amplifier Circuits



- Establishment of an appropriate dc operating point for the transistor (MOSFET)
- To get a stable and predictable dc drain current  $I_D$  and a dc drain-to-source voltage  $V_{DS}$  that ensures operation in the saturation region for all expected input-signal levels.


Biasing by fixing  $V_{GS}$  - If we fix  $V_{GS}$  voltage and try to provide desired  $I_D$ , it is not a good option because of the following points:-

→ We have  $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$  - in saturation region


→ Values  $C_{ox}$ ,  $V_t$  and  $\frac{W}{L}$  vary widely among devices

→ Both  $V_t$  and  $\mu_n$  depend on temperature.

 → So if we fix  $V_{GS}$ , the drain current  $I_D$  becomes very much temperature dependant as in fig below



 Biasing by fixing  $V_{G1}$  and connecting a Resistance in the source. (12)



Fix the gate voltage  $V_G$  and connect a resistor  $R_S$  in the source as shown

$$V_{G1} = V_{GS} + I_D R_S \quad \text{--- (1)}$$


$$I_D = \frac{V_{G1} - V_{GS}}{R_S} = \frac{V_{G1}}{R_S} - \frac{V_{GS}}{R_S}$$

If  $V_{G1}$  is much greater than  $V_{GS}$ , then  $I_D$  will be mostly determined by the values of  $V_{G1}$  and  $R_S$ .

$R_S \rightarrow$  provides negative feedback, which acts to stabilize the value of the bias current  $I_D$ .

If  $I_D \uparrow$ ,  $V_{G1}$  (constant),  $V_{GS}$  has to  $\downarrow$  causing a decrease in  $I_D$  (because  $V_{G1}$  constant)

 $R_S$  is also called degeneration resistance.



$$I_D = \left( \frac{V_{G1}}{R_S} \right) - \frac{V_{GS}}{R_S}$$



$$y = c + mx$$

$$m = -\frac{1}{R_S}$$

- 2 a. Explain the T equivalent circuit model of MOSFET. (08 Marks)
- b. Derive an expression for voltage gain of MOSFET with necessary waveforms. (06 Marks)
- c. Explain biasing a BJT using collector to base feedback resistor. (06 Marks)
  
### 4.6.5 Small signal equivalent circuit models

- \* FET behaves as a voltage controlled current source
  - \* It accepts  $v_{gs}$  and provides  $i_d = g_m v_{gs}$  at the drain terminal.
  - \* Input resistance of MOSFET is very high, ideally infinite.
  - \* The o/p resistance looking into the drain is also high
- putting it all together, the small signal equivalent circuit is as shown below:-



Under small signal condition,

$$v_D = V_{DD} - R_D [i_d + I_D]$$

$$v_D = \underbrace{V_{DD} - I_D R_D} - i_d R_D$$

$$v_D = V_D - i_d R_D$$

∴ The a.c. signal component of the drain voltage is


$$v_d = -i_d R_D$$

$$\boxed{v_d = -g_m v_{gs} R_D} \quad \text{--- (9)}$$

$$\text{Voltage gain } \boxed{A_V = \frac{v_d}{v_{gs}} = -g_m R_D} \quad \text{--- (10)}$$

Biasing using a collector to base feedback resistor:

(3.5.3)

 

$R_B$  provides -ve feedback which helps to stabilize the bias point of BJT.

$$V_{CC} = \underbrace{(I_C + I_B)}_{I_E} R_C + I_B R_B + V_{BE}$$

$$V_{CC} = I_E R_C + \frac{I_E}{\beta + 1} R_B + V_{BE}$$

$$V_{CC} = I_E \left( R_C + \frac{R_B}{\beta + 1} \right) + V_{BE}$$

Also  $V_{CE} = I_B R_B + V_{BE}$

$$\boxed{I_E = \frac{V_{CC} - V_{BE}}{R_C + \frac{R_B}{\beta + 1}}}$$



### Module-2

- 3 a. Explain the common source amplifier and derive the expression for voltage gain. (10 Marks)  
b. A transistor amplifier is fed with a signal source having an open circuit voltage  $V_{sig}$  of  $10\text{mV}$  and an internal resistance  $r_{sig}$  of  $100\text{K}\Omega$ . The voltage  $V_i$  at the amplifier input and the output voltage  $V_o$  are measured both without and with load resistance  $R_L = 10\text{K}\Omega$  connected to the amplifier output. The measured results are as follows :

	$V_i$ (mv)	$V_o$ (mv)
Without $R_L$	9	90
With $R_L$ connected	8	70

Find all the amplifier parameters.

(10 Marks)

Solution :-

$$A_{v_o} = \frac{V_o}{V_i} = \frac{90}{9} = 10$$

(when  $R_L = \infty$ )

$$G_{v_o} = \frac{R_i}{R_i + R_{sig}} A_{v_o} \quad \text{and} \quad G_{v_o} = \frac{V_o}{V_{sig}} \Big|_{R_L = \infty}$$

$$\therefore G_{v_o} = \frac{90\text{mV}}{10\text{mV}} = 9.$$

$$\boxed{G_{v_o} = 9}$$

$$\rightarrow 9 = \frac{R_i}{R_i + 100\text{K}} \times 10.$$

$$\Rightarrow \boxed{R_i = 900\text{K}\Omega}$$

When  $R_L = 10k$  is Connected

$$A_v = \frac{V_o}{V_i} = 8.75$$

$$G_v = \frac{V_o}{V_{sig}} = \frac{70}{10} = 7$$

To find  $R_o$  :-

$$A_v = A_{v0} \frac{R_L}{R_L + R_o}$$

$$8.75 = 10 \cdot \frac{10}{10 + R_o} \Rightarrow R_o = 1.43k$$

To get  $R_{out}$  :-

$$G_v = G_{v0} \cdot \frac{R_L}{R_L + R_{out}}$$

$$7 = 9 \cdot \frac{10}{10 + R_{out}} \Rightarrow R_{out} = 2.86k$$

To get  $R_{in}$  :-

$$\frac{V_i}{V_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}}$$

$$\frac{8}{10} = \frac{R_{in}}{R_{in} + 100} \Rightarrow R_{in} = 400k$$

To get  $G_m$  :-


$$G_m = \frac{A_{v0}}{R_o} = \frac{10}{1.43k} = 7mA/V$$

- 4
- With a neat diagram, explain the three frequency bands of MOSFET.
  - Explain the high frequency model of MOSFET.
  - Explain common source follower and derive the expression of voltage gain.

(06 Marks)


(06 Marks)

(08 Marks)

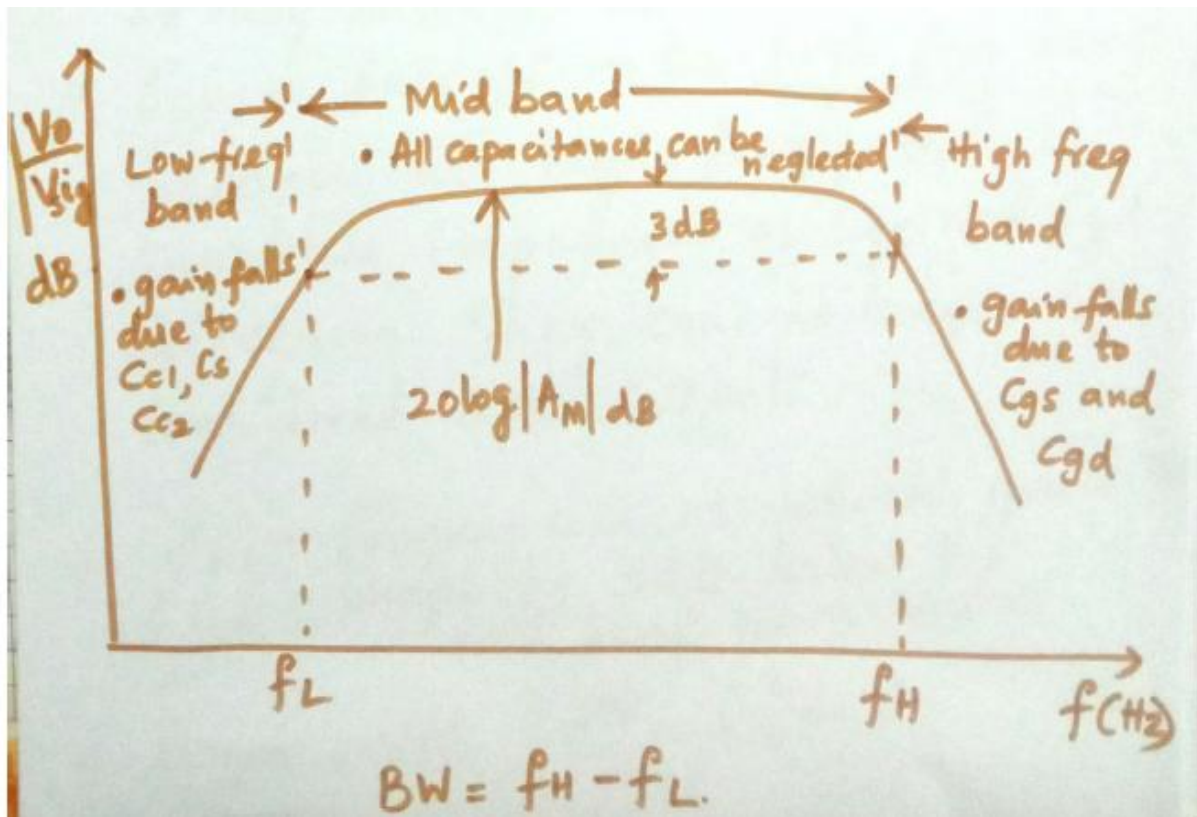
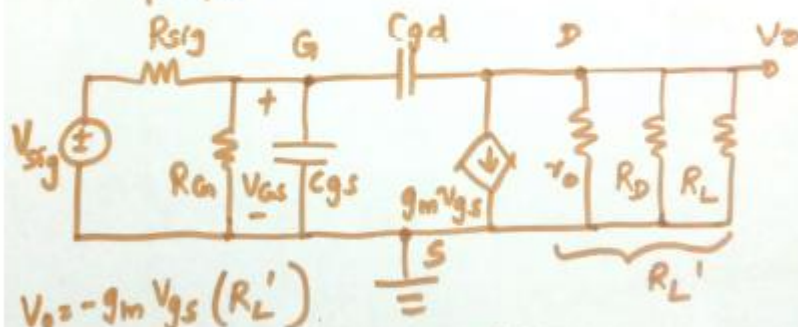
### HIGH FREQ RESPONSE (4.9.2)

- \* At high freq,  $C_{c1}, C_{c2}, C_s$  act as perfect short circuits
- \* high freq equivalent circuit of CS amplifier need to be drawn as :-



$$V_o = -g_m V_{gs} (R_L')$$

$$\text{where } R_L' = r_o \parallel R_D \parallel R_L$$

$$\text{Upper cutoff freq } f_H = \frac{1}{2\pi C_{in} R'_{sig}}$$

$$\text{where } C_{in} = C_{gs} + C_{gd} (1 + g_m R_L')$$

\* Considers both capacitors together

$$R'_{sig} = R_{sig} \parallel R_G$$

### Module-3

- 5 a. Explain the properties of negative feedback. (10 Marks)  
 b. Explain the transformer coupled class – A power amplifier and show that efficiency is 50%. (10 Marks)

## BW Extension

- Consider an amplifier with single pole
- $A_M$  mid band Gain and  $W_H$  upper 3db frequency

$$A(s) = \frac{A_M}{1 + \frac{s}{W_H}}$$

- Feedback network is frequency independent



$$A_{f(s)} = \frac{A(s)}{1 + \beta A(s)}$$

$$A_{f(s)} = \frac{\frac{A_M}{1 + A_M \beta}}{1 + \frac{s}{W_H(1 + A_M \beta)}}$$

$$A_{f(s)} = \frac{A_{Mf}}{1 + \frac{s}{W_{Hf}}}$$
  
## Noise Reduction

- S/N signal to Noise ratio
- Noisy stage is preceded by a noise free stage
- e.g.: Pre amplifier in case of Power amplifier stage of audio amplifier




Superposition:

$$V_o = V_s \frac{A_1 A_2}{1 + A_1 A_2 \beta} + V_n \frac{A_1}{1 + A_1 A_2 \beta}$$


$$\left( \frac{S}{N} \right) = \frac{V_s}{V_n} A_2$$

- 6 a. Explain the circuit operation of class – B power amplifier and also explain the transfer characteristics. (08 Marks)  
 b. Explain the Four basic feedback topologies of the amplifier. (12 Marks)

## Class B Operation

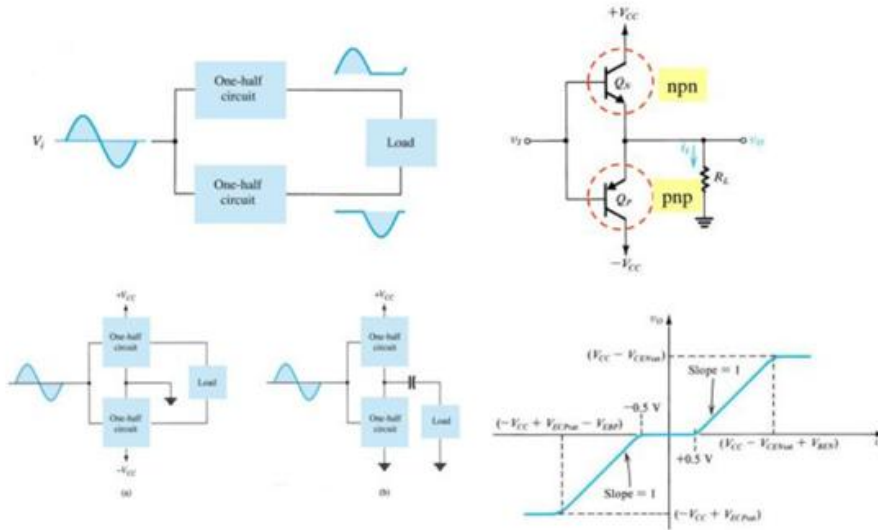

## Four basic Amplifier Configurations

 


Type of Amplifier	Input	Output	Transfer Gain	Ideal \$R_i\$	Ideal \$R_o\$
Voltage Amplifier	V	V	$A_v \left( = \frac{V_o}{V_i} \right)$	$\infty$	0
Current Amplifier	I	I	$A_i \left( = \frac{I_o}{I_i} \right)$	0	$\infty$
Transconductance Amplifier	V	I	$G_m \left( = \frac{I_o}{V_i} \right)$	$\infty$	$\infty$
Transresistance Amplifier	I	V	$R_{tm} \left( = \frac{V_o}{I_i} \right)$	0	0

**Module-4**



- 7 a. Explain R and 2R resistor digital to analog (D/A) converter and also derive the expression of output voltage. (10 Marks)
- b. Explain the first order lowpass Butterworth filter with necessary voltage gain. (10 Marks)

## DAC:R-2R


D/A Converter With R and 2R Resistors

 

D/A Converter With R and 2R Resistors

  
 
# First order Butterworth Low Pass Filter



$$v_1 = \frac{-jX_c}{R - jX_c} V_{in}$$

$$v_1 = \frac{V_{in}}{1 + j2\pi fRC}$$

$$v_{out} = \left(1 + \frac{R_f}{R_1}\right) \frac{V_{in}}{1 + j2\pi fRC}$$

$$\frac{v_{out}}{V_{in}} = \frac{A_F}{1 + j2\pi fRC}$$

$$\left| \frac{v_{out}}{V_{in}} \right| = \frac{A_F}{\sqrt{1 + (2\pi fRC)^2}}$$

$$A_F = \left(1 + \frac{R_f}{R_1}\right)$$

$$X_c = \frac{1}{2\pi fC}$$

At Cut off freq Magnitude of gain will be  $\frac{A_F}{\sqrt{2}}$



$$f_H = \frac{1}{2\pi RC}$$


- 8 a. Explain the operation of monostable multivibrator.  
b. Explain the two types of Bandpass filters.

(10 Marks)

(10 Marks)

# Monostable MULTIVIBRATOR

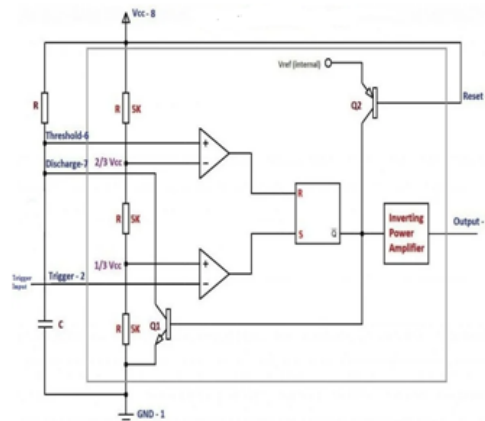 

 

### Pulse Duration : $t_p/T_{ON}$

$$V_C(t_p) = V_{CC} + (0 - V_{CC})e^{-\frac{t_p}{RC}}$$

$$\frac{2}{3}V_{CC} = V_{CC} - V_{CC}e^{-\frac{t_p}{RC}}$$

$$\frac{1}{3} = e^{-\frac{t_p}{RC}}$$

$$t_p = \ln 3 * RC$$

$$t_p = 1.1 * RC$$


### Capacitor Charging equation

$$V_C(t) = V_{final} + (V_{initial} - V_{final})e^{-\frac{t}{RC}}$$

$$t_p = T_{ON} = 1.1 * RC$$
 
### Module-5

- 9 a. Explain the block diagram of power electronic system. (06 Marks)  
 b. List and explain the applications of power electronics. (06 Marks)  
 c. Explain the static anode – Cathode characteristics of SCR. (08 Marks)




Relationship of PE to power, electronics and control


 
## SCR static Anode- Cathode Characteristics

- To understand the **SCR working principle** we have to look into the different ways it can operate. Depending on the polarity of the voltage applied and the gate pulse given to the SCR, it can operate in four different modes such as
- Forward Blocking mode
- Forward Conduction mode
- Reverse Blocking mode
- *Reverse Breakdown (avoided)*




- 10 a. Explain the turn on methods of a Thyristor. (10 Marks)  
b. Explain the construction and working of UJT. (10 Marks)

## SCR Turn –ON Methods

- With a voltage applied to the SCR, if the anode is made positive with respect to the cathode, the SCR becomes forward biased. Thus, the SCR comes into the forward blocking state. The SCR can be made to conduct or switching into conduction mode is performed by any one of the following methods.
- Forward voltage triggering
- Temperature triggering (Thermal Triggering)
- dv/dt triggering
- Light triggering (Radiation Triggering)
- Gate triggering

# Unijunction Transistor (UJT)

 

- For a Unijunction transistor, the resistive ratio of R<sub>B1</sub> to R<sub>B2</sub> is called the **intrinsic stand-off ratio (η)**.

$$\eta = \frac{R_{B1}}{R_{B1} + R_{B2}}$$

- Typical standard values of η range from 0.5 to 0.8 for most common UJT's.

