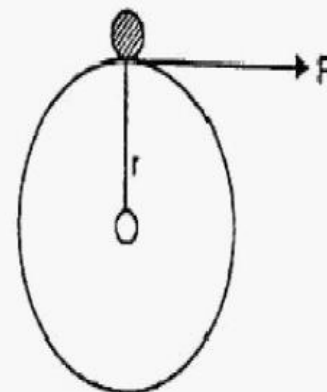


**Internal Assessment Test - I**

Sub:	<b>Electric Motors</b>						Code:	<b>21EE44</b>	
Date:	05.07.2023 (02.00 -3.30PM)	Duration:	90 mins	Max Marks:	50	Sem:	IV	Branch:	EEE
<b>Answer Any FIVE FULL Questions</b>									

		M ar ks	OBE	
			C O	R B T
1a	<p>What is meant by back EMF? (2marks)</p> <ul style="list-style-type: none"> <li>• When the armature of a d.c. motor rotates under the influence of the driving torque, the armature conductors move through the magnetic field and hence e.m.f. is induced in them as in a generator</li> <li>• The induced e.m.f. acts in opposite direction to the applied voltage V (Lenz's law) and is known as back or counter e.m.f. Eb.</li> <li>• The back e.m.f. (<math>E_b = \frac{Z N P}{60} A</math>) is always less than the applied voltage V, although this difference is small when the motor is running under normal conditions.</li> </ul> <p>Explain the significance of Back EMF. (2 marks)</p> <ul style="list-style-type: none"> <li>• Back emf in a DC motor regulates the flow of armature current i.e., it automatically changes the armature current to meet the load requirement.</li> <li>• Eb acts like a governor, it makes a motor self regulating so that it draws as much current as is just necessary.</li> </ul>	4	CO 1	L2
1b	<p>Derive the torque equation of a D.C. Motor</p> <h2 style="text-align: center; color: magenta;">Torque Equation</h2> <p>Torque <math>T = F \times r</math> (Nm)                      Let in a d.c. motor  <math>r</math> = average radius of armature in m  <math>l</math> = effective length of each conductor in m  <math>Z</math> = total number of armature conductors  <math>A</math> = number of parallel paths  <math>i</math> = current in each conductor = <math>I_a/A</math>  <math>B</math> = average flux density in Wb/m<sup>2</sup>  <math>\Phi</math> = flux per pole in Wb  <math>P</math> = number of poles</p> <p>Force on each conductor, <math>F = B i l</math> newtons</p> <p>Torque due to one conductor = <math>F \times r</math> newton-metre</p> <p>Total armature torque, <math>T_a = Z F r</math> newton-metre</p> $T_a = Z B i l r$	3+3	CO 1	L2



Now  $i = I_a/A$ ,  $B = \phi/a$  where  $a$  is the x-sectional area of flux path per pole at radius  $r$ . Clearly,  $a = 2\pi r \ell/P$ .

$$\begin{aligned} \therefore T_a &= Z \times \left(\frac{\phi}{2}\right) \times \left(\frac{I_a}{A}\right) \times \ell \times r \\ &= Z \times \frac{\phi}{2\pi r \ell/P} \times \frac{I_a}{A} \times \ell \times r = \frac{Z\phi I_a P}{2\pi A} \text{ N - m} \end{aligned}$$

or  $T_a = 0.159 Z\phi I_a \left(\frac{P}{A}\right) \text{ N - m}$  (i)

Since  $Z$ ,  $P$  and  $A$  are fixed for a given machine,

$$\therefore T_a \propto \phi I_a$$

Hence torque in a d.c. motor is directly proportional to flux per pole and armature current.

(i) For a shunt motor, flux  $\phi$  is practically constant.

$$\therefore T_a \propto I_a$$

(ii) For a series motor, flux  $\phi$  is directly proportional to armature current  $I_a$  provided magnetic saturation does not take place.

$$\therefore T_a \propto I_a^2$$

2 What is the necessity of a starter for a D.C. Motor? (2 marks)

## Necessity of D.C. Motor Starter

- ✓ **At starting, when the motor is stationary, there is no back e.m.f. in the armature.**
- ✓ **Consequently, if the motor is directly switched on to the mains, the armature will draw a heavy current ( $I_a = V/R_a$ ) because of small armature resistance.**
- ✓ **As an example, 5 H.P., 220 V shunt motor has a full-load current of 20 A and an armature resistance of about 0.5  $\Omega$ .**
- ✓ **If this motor is directly switched on to supply, it would take an armature current of  $220/0.5 = 440$  A which is 22 times the full-load current.**
- ✓ **This high starting current may result in:**
  - (i) **burning of armature due to excessive heating effect,**
  - (ii) **damaging the commutator and brushes due to heavy sparking,**
  - (iii) **excessive voltage drop in the line to which the motor is connected.**
- ✓ **In order to avoid excessive current at starting, a variable resistance (known as starting resistance) is inserted in series with the armature circuit.**
- ✓ **This resistance is gradually reduced as the motor gains speed (and hence  $E_b$  increases) and eventually it is cut out completely when the motor has attained full speed.**
- ✓ **The value of starting resistance is generally such that starting current is limited to 1.25 to 2 times the full-load current.**

Explain, with a neat sketch, the working of a 3- point D.C. Shunt motor starter, bringing out the protective features incorporated in it. List the drawbacks of three point starter.

Diagram – 3 marks

Explanation – 2 marks

Protecting devices – 2 marks

Drawback – 1 mark

10 CO L2  
1


# Three Point Starter

- ✓ Important Parts
- ✓ Resistance stud
- ✓ Handle
- ✓ Spring
- ✓ Soft Iron Piece

## ✓ Protective Devices

- ✓ No volt release coil
- ✓ Over load release coil

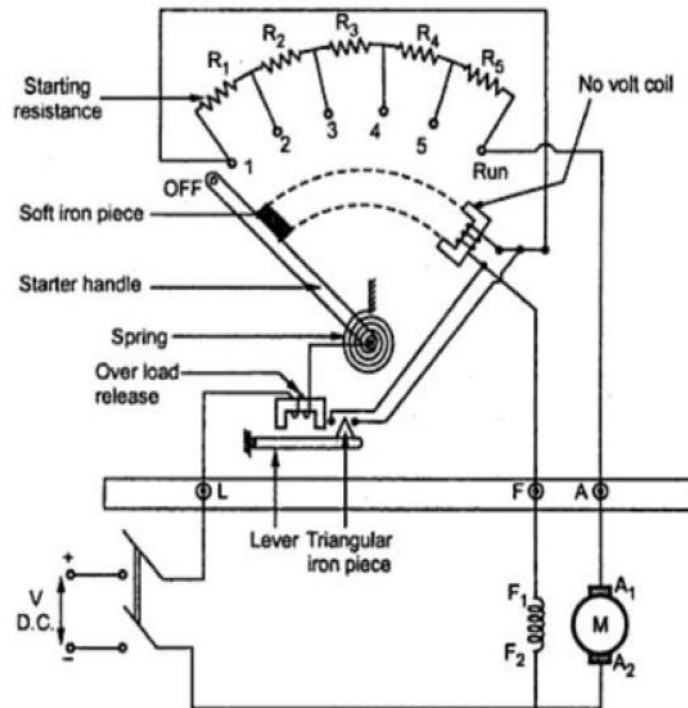1. 'L' Line terminal to be connected to positive of supply.
2. 'A' To be connected to the armature winding.
3. 'F' To be connected to the field winding.



## Function of No Volt Coil

1. The supply to the field winding is derived through NVC. So when field current flows, it magnetizes the NVC. When the handle is in the 'RUN' position, soft iron piece connected to the handle gets attracted by the magnetic force produced by NVC. Design of NVC is such that it holds the handle in 'RUN' position against the force of the spring as long as supply to the motor is proper. Thus NVC holds the handle in the 'RUN' position and hence also called hold on coil.
2. Whenever there is supply failure or if field circuit is broken, the current through NVC gets affected. It loses its magnetism and hence not in a position to keep the soft iron piece on the handle, attracted. Under the spring force, handle comes back to OFF position, switching off the motor. So due to the combination of NVC and the spring, the starter handle always comes back to OFF position whenever there is any supply problems. The entire starting resistance comes back in series with the armature when attempt is made to start the motor every time. This prevents the damage of the motor caused due to accidental starting.
3. NVC performs the similar action under low voltage conditions and protects the motor from such dangerous supply conditions as well.

# Action of Overload Release

- ✓ The current through the motor is taken through the OLR, an electromagnet.
- ✓ Under overload condition, high current is drawn by the motor from the supply which passes through OLR.
- ✓ Below this magnet, there is an arm which is fixed at its fulcrum and normally resting in horizontal position.
- ✓ Under overloading, high current through OLR produces enough force of attraction to attract the arm upwards.
- ✓ Normally magnet is so designed that up to a full load value of current, the force of attraction produced is just enough to balance the gravitational force of the arm and hence not lifting it up.
- ✓ At the end of this arm, there is a triangular iron piece fitted. When the arm is pulled upwards the triangular piece touches the two points which are connected to the two ends of NVC.
- ✓ This shorts the NVC and voltage across NVC becomes zero due to which NVC loses its magnetism.
- ✓ So under the spring force, handle comes back to the OFF position, disconnecting the motor from the supply.
- ✓ Thus motor gets saved from the overload conditions.

## Functions of Protective Devices

- (i) when the supply fails, thus preventing the armature being directly across the mains when this voltage is restored. For this purpose, we use **no-volt release coil**.
- (ii) when the motor becomes overloaded or develops a fault causing the motor to take an excessive current. For this purpose, we use **overload release coil**.

# Operations of Three Point Starter


- (i) The d.c. supply is switched on with handle in the OFF position.
- (ii) The handle is now moved clockwise to the first stud. As soon as it comes in contact with the first stud, the shunt field winding is directly connected across the supply, while the whole starting resistance is inserted in series with the armature circuit.
- (iii) As the handle is gradually moved over to the final stud, the starting resistance is cut out of the armature circuit in steps. The handle is now held magnetically by the no-volt release coil which is energized by shunt field current.
- (iv) If the supply voltage is suddenly interrupted or if the field excitation is accidentally cut, the no-volt release coil is demagnetized and the handle goes back to the OFF position under the pull of the spring. If **no-volt release coil** were not used, then in case of failure of supply, the handle would remain on the final stud. If then supply is restored, the motor will be directly connected across the supply, resulting in an excessive armature current.
- (v) If the motor is over-loaded (or a fault occurs), it will draw excessive current from the supply. This current will increase the ampere-turns of the **over-load release coil** and pull the armature C, thus short-circuiting the no volt release coil. The no-volt coil is demagnetized and the handle is pulled to the OFF position by the spring. Thus, the motor is automatically disconnected from the supply.

## Drawback of 3 Point Starter

- ✓ In a three-point starter, the no-volt release coil is connected in series with the shunt field circuit so that it carries the shunt field current.
- ✓ While exercising speed control through field regulator, the field current may be weakened to such an extent that the no-volt release coil may not be able to keep the starter arm in the ON position.
- ✓ This may disconnect the motor from the supply when it is not desired.
- ✓ This drawback is overcome in the four point starter.

3a	<p>Explain why dc series motor should never run unloaded (2 marks)</p> <p>At no-load, the armature current is very small and so is the flux. Hence, the speed rises to an excessive high value (<math>\because N \propto 1/\phi</math>). This is dangerous for the machine which may be destroyed due to centrifugal forces set up in the rotating parts. Therefore, a series motor should never be started on no-load. However, to start a series motor, mechanical load is first put and then the motor is started.</p> <p>The minimum load on a d.c. series motor should be great enough to keep the speed within limits. If the speed becomes dangerously high, then motor must be disconnected from the supply.</p>	2	CO 2	L2
3b	<p>Explain the different losses in DC machines with power flow diagram. Derive the condition for the maximum efficiency.</p> <p>Losses – 2 marks Derivation to get maximum efficiency – 6 marks</p>	8	CO 3	L2

# Losses in DC Motor

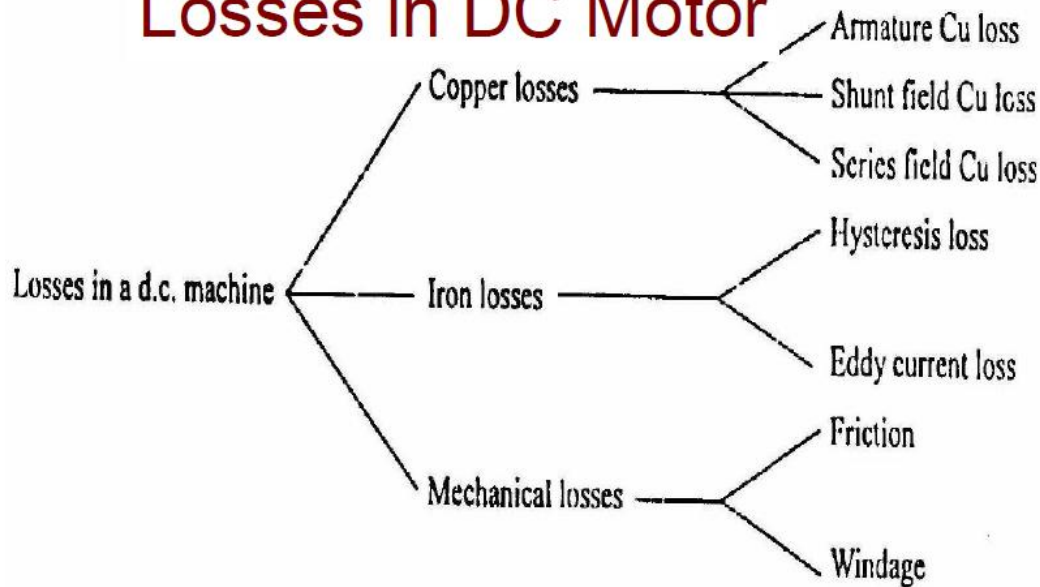

## Condition for Maximum Efficiency

### Condition of Maximum Efficiency of DC Motor

If we neglect the shunt field current, we can say supply current is the same as armature current in a dc motor. Hence now we can simplify the expression of the overall efficiency of dc motor as

$$\eta_c = \frac{VI_a - I_a^2 R_a - W_c}{VI_a} = 1 - \left( \frac{I_a R_a}{V} + \frac{W_c}{VI_a} \right)$$

Now the efficiency is maximum when the term under brackets in the above expression is minimum. Again, this condition is satisfied when

$$\begin{aligned} \frac{d}{dI_a} \left( \frac{I_a R_a}{V} + \frac{W_c}{VI_a} \right) &= 0 \\ \Rightarrow \frac{R_a}{V} - \frac{W_c}{VI_a^2} &= 0 \\ \Rightarrow W_c = I_a^2 R_a \Rightarrow I_a &= \sqrt{\frac{W_c}{R_a}} \end{aligned}$$

The just above expression shows that the efficiency of a dc motor is maximum when

$$\text{Copper Loss} = \text{Core Loss}$$

**Condition for Maximum Efficiency**

**Variable losses = Constant losses**

**CU losses = constant losses**

**CU loss = Iron loss**

A 200V shunt motor on no load runs at 1200 rpm and takes 3A current. The total armature and shunt field resistances are 0.3 and 150 respectively. Calculate the speed when loaded and take a line current of 40A. Due to Armature reaction the field weakened by 3%.

Formula : 1 mark

Eb1 : 3 marks

Eb2 : 3 marks

N2 : 3 marks

4)  $V = 200V$ , Shunt Motor.

$N_1 = 1200 \text{ rpm}$ ,  $I_{L1} = 3A$  (No load)

$R_a = 0.3\Omega$ ;  $R_{sh} = 150\Omega$

$N_2 = ?$ ,  $I_{L2} = 40A$  (Load).

$\phi_2 \Rightarrow$  weakened by 3%.

$\phi_2 \Rightarrow 97\% \phi_1 = 0.97 \phi_1$

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \times \frac{\phi_1}{\phi_2}$$

$$E_{b2} = V - I_{a2} R_a$$

$$I_{a1} = I_{L1} - I_{sh}$$

$$I_{sh} = \frac{V}{R_{sh}} = \frac{200}{150} = 1.33A$$

$$I_{a1} = I_{L1} - I_{sh} = 3 - 1.33 = 1.67A$$

$$E_{b1} = 200 - (1.67 \times 0.3) = \underline{199.5V}$$

$$I_{a2} = I_{L2} - I_{sh} = 40 - 1.33 = 38.67A$$

$$E_{b2} = V - I_{a2} R_a = 200 - (38.67 \times 0.3)$$

$$\boxed{E_{b2} = 188.4V}$$

$$N_2 = \frac{E_{b2}}{E_{b1}} \times \frac{\phi_1}{\phi_2} \times N_1 = \frac{188.4}{199.5} \times \frac{\phi_1}{0.97\phi_1} \times 1200$$

$$\boxed{N_2 = 1168.3 \text{ rpm.}}$$

5 Explain the different methods of speed control of DC shunt and series motor.

CO L  
4 2

Speed Control of shunt Motor – Diagram and explanation (5 marks)

Speed Control of series Motor – Diagram and explanation (5 marks)



✓ The speed of a dc motor is given by the relation,

$$N = K \frac{(V - I_a R_a)}{\phi} = \frac{K E_b}{\phi}$$

1. Flux / pole  $\Phi$  (Flux Control)
2. Resistance  $R_a$  of armature circuit (Rheostatic control)
3. Applied voltage  $V$  (Voltage Control)

## Speed Control of Shunt Motors

### i. Flux Control Method

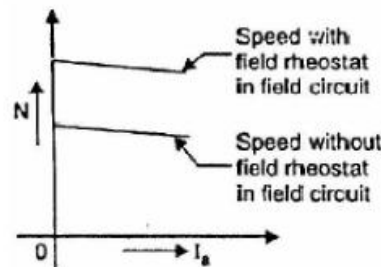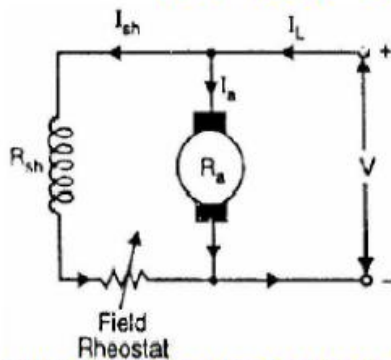

- ✓ It is based on the fact that by varying the flux  $\Phi$ , the motor speed ( $N \propto 1/\Phi$ ) can be changed and hence the name flux control method.
- ✓ In this method, a variable resistance (known as shunt field rheostat) is placed in series with shunt field winding as shown in Fig.
- ✓ The shunt field rheostat reduces the shunt field current  $I_{sh}$  and hence the flux  $\Phi$ .
- ✓ Therefore, we can only raise the speed of the motor above the normal speed.
- ✓ Wider speed ranges tend to produce instability and poor commutation.
- ✓ In non interpolar machine the speed ratio is 2 : 1.
- ✓ In machines with interpoles the speed ratio is 6 : 1



# Advantages & Disadvantages of Flux control method

## Advantages



- (i) This is an easy and convenient method.
- (ii) It is an inexpensive method since very little power is wasted in the shunt field rheostat due to relatively small value of  $I_{sh}$ .
- (iii) The speed control exercised by this method is independent of load on the machine.

## Disadvantages

- (i) Only speeds higher than the normal speed can be obtained since the total field circuit resistance cannot be reduced below  $R_{sh}$ —the shunt field winding resistance.
- (ii) There is a limit to the maximum speed obtainable by this method. It is because if the flux is too much weakened, commutation becomes poorer.

**Note.** The field of a shunt motor in operation should never be opened because its speed will increase to an extremely high value.
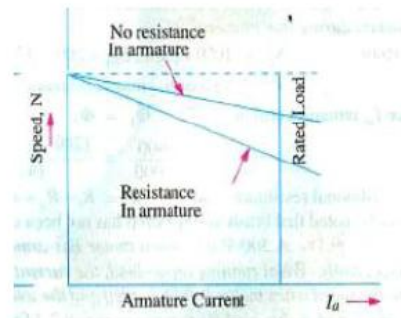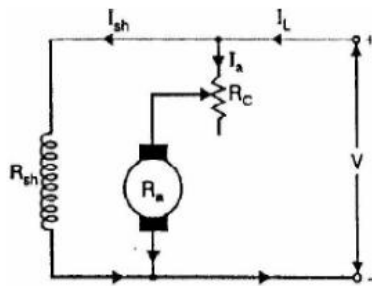
## ii. Armature or Rheostatic control method



- ✓ This method is based on the fact that by varying the voltage available across the armature, the back e.m.f and hence the speed of the motor can be changed.
- ✓ This is done by inserting a variable resistance  $R_C$  (known as controller resistance) in series with the armature as shown in Fig.

$$N \propto V - I_a(R_a + R_C)$$

- ✓ Due to voltage drop in the controller resistance, the back e.m.f. ( $E_b$ ) is decreased.
- ✓ Since  $N \propto E_b$ , the speed of the motor is reduced.
- ✓ The highest speed obtainable is that corresponding to  $R_C = 0$  i.e., normal speed.
- ✓ Hence, this method can only provide speeds below the normal speed

# Disadvantages of Armature control method

## Disadvantages

- (i) A large amount of power is wasted in the controller resistance since it carries full armature current  $I_a$ .
- (ii) The speed varies widely with load since the speed depends upon the voltage drop in the controller resistance and hence on the armature current demanded by the load.
- (iii) The output and efficiency of the motor are reduced.
- (iv) This method results in poor speed regulation.

Due to above disadvantages, this method is rarely used to control the speed of shunt motors.

## Note.

- ✓ The armature control method is a very common method for the speed control of d.c. series motors.
- ✓ The disadvantage of poor speed regulation is not important in a series motor which is used only where varying speed service is required.

## iii. Voltage Control Method

### (i) Multiple voltage control.


- ✓ In this method, the shunt field of the motor is connected permanently across a fixed voltage source.
- ✓ The armature can be connected across several different voltages through a suitable switchgear.
- ✓ In this way, voltage applied across the armature can be changed.
- ✓ The speed will be approximately proportional to the voltage applied across the armature.
- ✓ Intermediate speeds can be obtained by means of a shunt field regulator.

## Speed Control of DC Series Motor

### 1. Flux Control Method
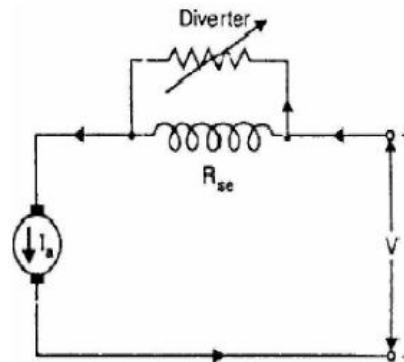
#### (i) Field diverters.


- ✓ In this method, a variable resistance (called field diverter) is connected in parallel with series field winding as shown in Fig.
- ✓ Its effect is to shunt some portion of the line current from the series field winding, thus weakening the field and increasing the speed ( $N \propto 1 / \Phi$ ).
- ✓ The lowest speed obtainable is that corresponding to zero current in the diverter (i.e., diverter is open).
- ✓ Obviously, the lowest speed obtainable is the normal speed of the motor.
- ✓ Consequently, this method can only provide speeds above the normal speed.
- ✓ The series field diverter method is often employed in traction work.



# Flux Control Method
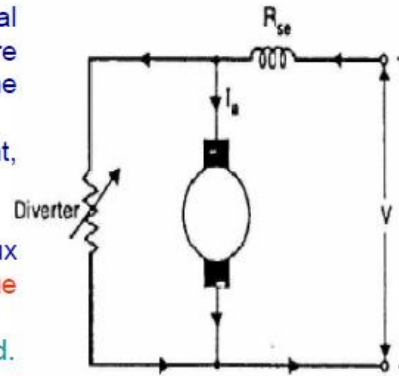
## ii) Armature Diverter


- ✓ In order to obtain speeds below the normal speed, a variable resistance (called armature diverter) is connected in parallel with the armature as shown in Fig.
- ✓ The diverter shunts some of the line current, thus reducing the armature current.
- ✓ Now for a given load, if  $I_a$  is decreased, the flux  $\Phi$  must increase ( $T_a \propto \Phi I_a$ ) because the torque is maintained as a constant.
- ✓ Since  $N \propto 1/\Phi$ , the motor speed is decreased.
- ✓ By adjusting the armature diverter, any speed lower than the normal speed can be obtained.



## Flux Control Method

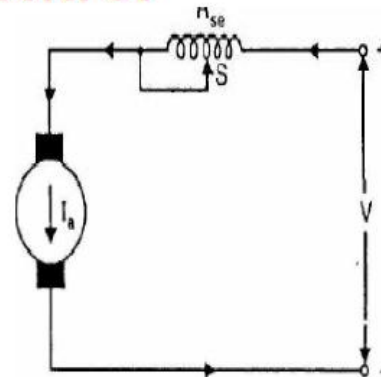
### iii) Tapped field control

- ✓ In this method, the flux is reduced (and hence speed is increased) by decreasing the number of turns of the series field winding as shown in Fig.
- ✓ The switch S can short circuit any part of the field winding, thus decreasing the flux and raising the speed.
- ✓ With full turns of the field winding, the motor runs at normal speed and as the field turns are cut out, speeds higher than normal speed are achieved.



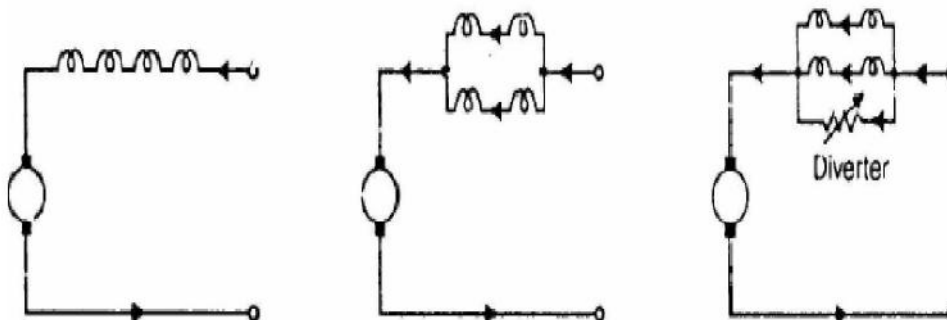
### iv) Paralleling field coils


- ✓ This method is usually employed in the case of fan motors.
- ✓ By regrouping the field coils as shown in Fig.
- ✓ several fixed speeds can be obtained.



## 2. Armature-resistance control

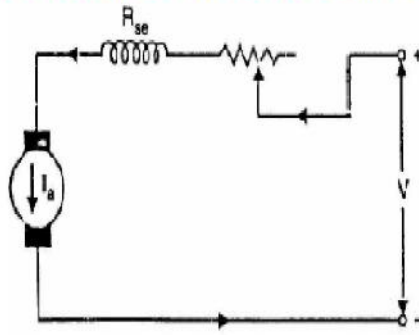

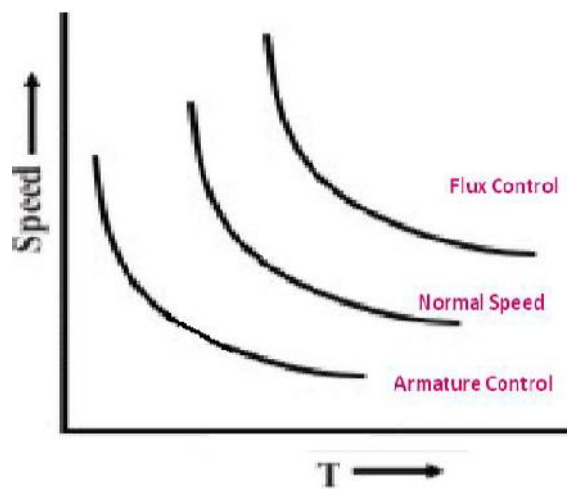- ✓ In this method, a variable resistance is directly connected in series with the supply as shown in Fig.
- ✓ This reduces the voltage available across the armature and hence the speed falls.
- ✓ By changing the value of variable resistance, any speed below the normal speed can be obtained.
- ✓ This is the most common method employed to control the speed of d.c. series motors.



6

A 200V dc series motor which has a total resistance of 0.2 runs at 1000 rpm and takes full load current of 200A. Calculate the speed of the motor at which it develops half of the full load torque.

Formula : 1 mark

Eb1 : 3 marks

Eb2 : 3 marks

N2 : 3 marks

10

CO

L

4

3

Q)  $V = 200V$  ; DC series motor.

$$R_a + R_{se} = 0.2 \Omega$$

$$N_1 = 1000 \text{ rpm} ; I_{L1} = I_a = I_{sh1} = 200A.$$

$$N_2 = ? \quad T_{a2} = \frac{T_{a1}}{2}.$$

$$\frac{T_{a2}}{T_{a1}} = \frac{I_{a2}^2}{I_{a1}^2}$$

$$\frac{T_{a1}}{2 \cdot T_{a1}} = \frac{I_{a2}^2}{(200)^2}.$$

$$I_{a2}^2 = \frac{200^2}{2} = 20000$$

$$I_{a2} = 141.42 A.$$

DC series Motor.

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \times \frac{I_{a1}}{I_{a2}}.$$

$$E_{b1} = V - I_{a1}(R_a + R_{se}) = 200 - (200 \times 0.2) = \underline{160V}$$

$$E_{b2} = V - I_{a2}(R_a + R_{se}) = 200 - (141.42 \times 0.2) = \underline{171.716V}.$$

$$N_2 = \frac{E_{b2}}{E_{b1}} \times \frac{I_{a1}}{I_{a2}} \times N_1 = \frac{171.716}{160} \times \frac{200}{141.42} \times 1000$$

$$N_2 = \underline{1517.78 \text{ rpm}}$$

A DC shunt motor runs at 1000 rpm on 200V supply its armature resistance is 0.8 and the armature current drawn is 40 amps. What resistance must be connected in series with the armature to reduce the speed to 600 rpm, the armature current remaining same? Neglect armature reaction

Formula : 1 mark

Eb1 : 3 marks

Eb2 : 3 marks

N2 : 3 marks

7) Shunt Motor,  $V = 200V$

$$N_1 = 1000 \text{ rpm} ; R_a = 0.8 \Omega$$

$$I_{a1} = 40A.$$

$$R_c = ? \quad N_2 = 600 \text{ rpm}, \quad I_{a2} = 40A.$$

Speed control by armature control method.

$$E_{b1} = V - I_{a1} R_a = 200 - (40 \times 0.8) = 168V.$$

$$E_{b2} = V - I_{a2} (R_a + R_c).$$

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

$$E_{b2} = \frac{N_2}{N_1} \times E_{b1} = \frac{600}{1000} \times 168 = 100.8V$$

$$E_{b2} = V - I_{a2} (R_a + R_c).$$

$$100.8 = 200 - 40(0.8 + R_c).$$

$$40(0.8 + R_c) = 200 - 100.8 = 99.2.$$

$$32 + 40R_c = 99.2$$

$$40R_c = 99.2 - 32 = 67.2.$$

$$R_c = 1.68 \Omega.$$

Extra Resistance to be connected in series with armature is 1.68  $\Omega$ .

A 220 V shunt motor with an armature resistance of 0.5 ohm is excited to give constant main field. At full load the motor runs at 500rpm and takes an armature current of 30A. If a resistance of 1.0 ohm is placed in the armature circuit, find the speed at (a) full-load torque (b) double full-load torque.

$$\textcircled{7} \quad V = 220V \quad \text{Shunt Motor.} \quad ($$

$$R_a = 0.5\Omega \quad \phi \rightarrow \text{constant.}$$

$$N_1 = 500 \text{ rpm.} \quad I_{a1} = 30A.$$

$$R_c = 1\Omega$$

(a)  $N_2$  @ full load torque.

(b)  $N_2$  @ double full load torque

$$T_a \propto \phi I_a$$

↳ constant.

$$T_a \propto I_a$$

(1 mark)

(a) Speed at Full load Torque.

$$E_{b1} = V - I_{a1} R_a \quad 934$$

$$E_{b1} = 220 - (30 \times 0.5) = 205V.$$

$$N_1 = 500 \text{ rpm.}$$

$$E_{b2} = V - I_{a2} (R_a + R_c)$$

$$= 220 - 30(0.5 + 1) = 175V.$$

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} = \frac{175}{205}$$

$$N_2 = \frac{175}{205} \times 500 = 426.83 \text{ rpm}$$

(4marks)

(b) Speed at double the full load Torque. (6)

$$R_c = 1 \Omega; R_a = 0.5 \Omega$$

$$T_{a2} = 2 T_{a1} \quad T_{a1} \rightarrow \text{Full load Torque.}$$

$$\frac{T_{a2}}{T_{a1}} = \frac{I_{a2}}{I_{a1}}$$

$$I_{a2} = \frac{T_{a2}}{T_{a1}} \times I_{a1} = \frac{2 T_{a1}}{T_{a1}} \times I_{a1}$$

$$I_{a2} = 2 I_{a1} = 2 \times 30 = \underline{\underline{60 \text{ A}}}$$

$$E_{b2} = V - I_{a2} (R_a + R_c)$$
$$= 220 - 60 (0.5 + 1)$$

$$E_{b2} = \underline{\underline{130 \text{ V}}}$$

(3 marks)

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} = \frac{130}{205}$$

$$N_2 = \frac{E_{b2}}{E_{b1}} \times N_1 = \frac{130}{205} \times 500$$

$$\boxed{N_2 = 317.07 \text{ rpm}}$$

(2 marks)

CI

CCI

HOD