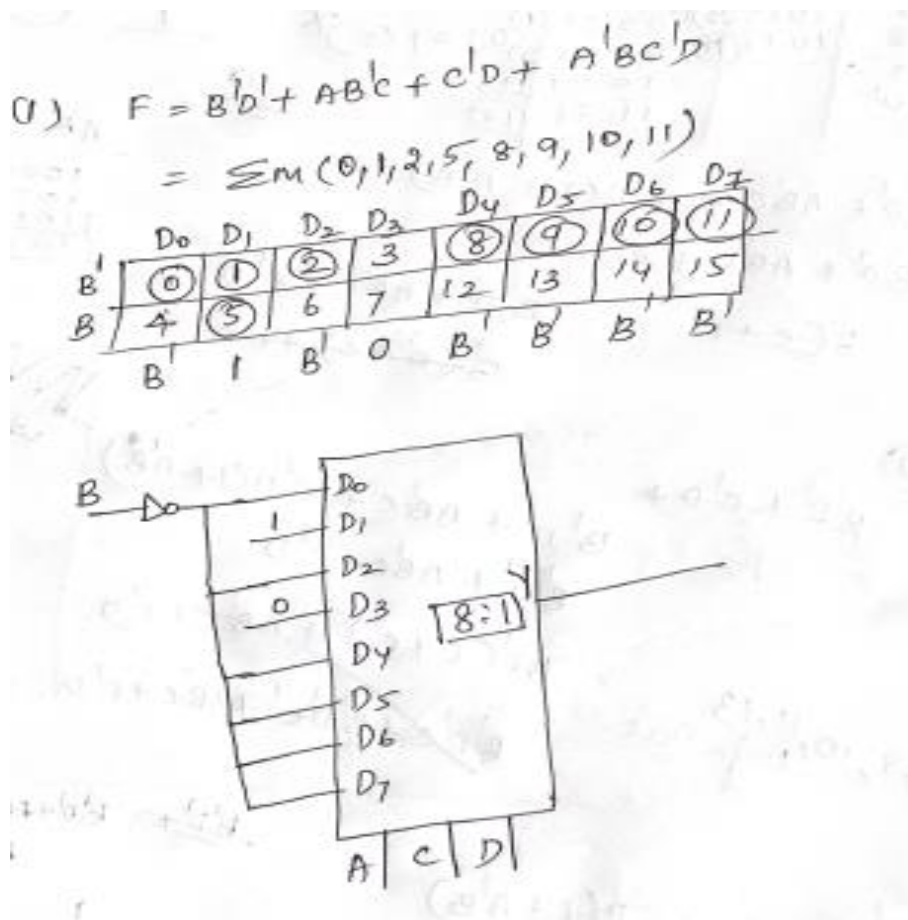


Internal Assessment Test - II





Sub:	DIGITAL SYSTEM DSEIGN						Code:	21EE42		
Date:	8/08/2023	Duration:	90 mins	Max Marks:	50	Sem:	4th	Branch:	EEE	
Answer Any FIVE FULL Questions										
								Marks	OBE	
									CO	RBT
1	Implement the following Boolean function $F=B'D'+AB'C+C'D+A'BC'D$ using a 8:1 MUX with A,C and D as select lines .						10	CO2	L3	
2	Design a combinational logic circuit that will convert BCD digit to Excess-3 BCD digit using gates. Construct truth table and simplify the expression using K-maps.						10	CO2	L3	
3	Design a 4:16 line decoder by cascading 2:4 line decoder which has active low output and active low enable input.						10	CO2	L2	
4	Implement the following Boolean function using a 8:1 MUX with w,y and z as select lines $f(w,x,y,z)=\sum m(0,1,2,5,7,8,9,12,13)$						10	CO2	L3	
5	Write the truth table of 2 bit magnitude comparator. Using K-map obtain the expression and represent the same using basic gates						10	CO2	L3	
6	What is a Flip-Flop? Discuss the working principal of SR Flip-Flop with the help of truth table.						10	CO3	L2	


1.




2.

Decimal Number	BCD Code				Excess-3 Code			
	A	B	C	D	W	x	y	z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10	1	0	1	0	X	X	X	X
11	1	0	1	1	X	X	X	X
12	1	1	0	0	X	X	X	X
13	1	1	0	1	X	X	X	X
14	1	1	1	0	X	X	X	X
15	1	1	1	1	X	X	X	X

   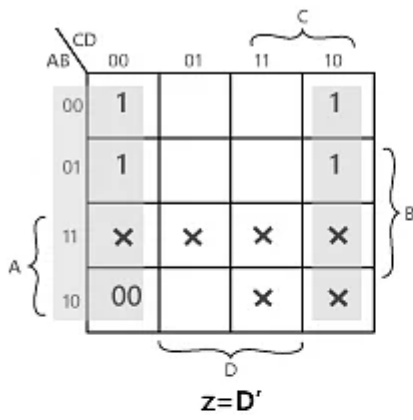


 

3.

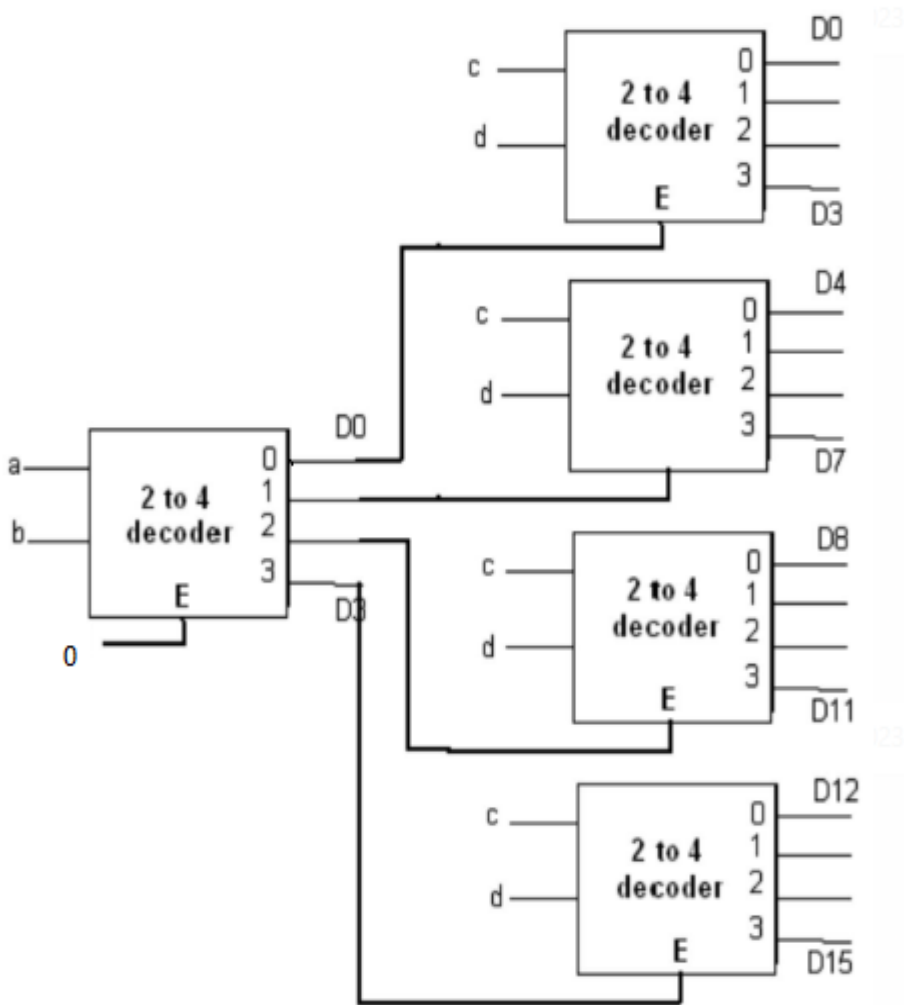

4.

 

5.

INPUT				OUTPUT		
A1	A0	B1	B0	A<B	A=B	A>B
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

		A > B			
		B1B0	00	01	11
A1A0	00	0	0	0	0
	01	1	0	0	0
	11	1	1	0	1
	10	1	1	0	0

		A = B			
		B1B0	00	01	11
A1A0	00	1	0	0	0
	01	0	1	0	0
	11	0	0	1	0
	10	0	0	0	1

Truth Table of Output A=B

Truth Table of Output A<B

		A < B			
		B1B0	00	01	11
A1A0	00	0	1	1	1
	01	0	0	1	1
	11	0	0	0	0
	10	0	0	1	0

$$A > B : A1B1' + A0B1'B0' + A1A0B0'$$


$$A = B : A1'A0'B1'B0' + A1'A0B1'B0 + A1A0B1B0 + A1A0'B1B0'$$

$$: A1'B1' (A0'B0' + A0B0) + A1B1 (A0B0 + A0'B0')$$

$$: (A0B0 + A0'B0') (A1B1 + A1'B1')$$

$$: (A0 \text{ Ex-Nor } B0) (A1 \text{ Ex-Nor } B1)$$

$$A < B : A1'B1 + A0'B1B0 + A1'A0'B0$$

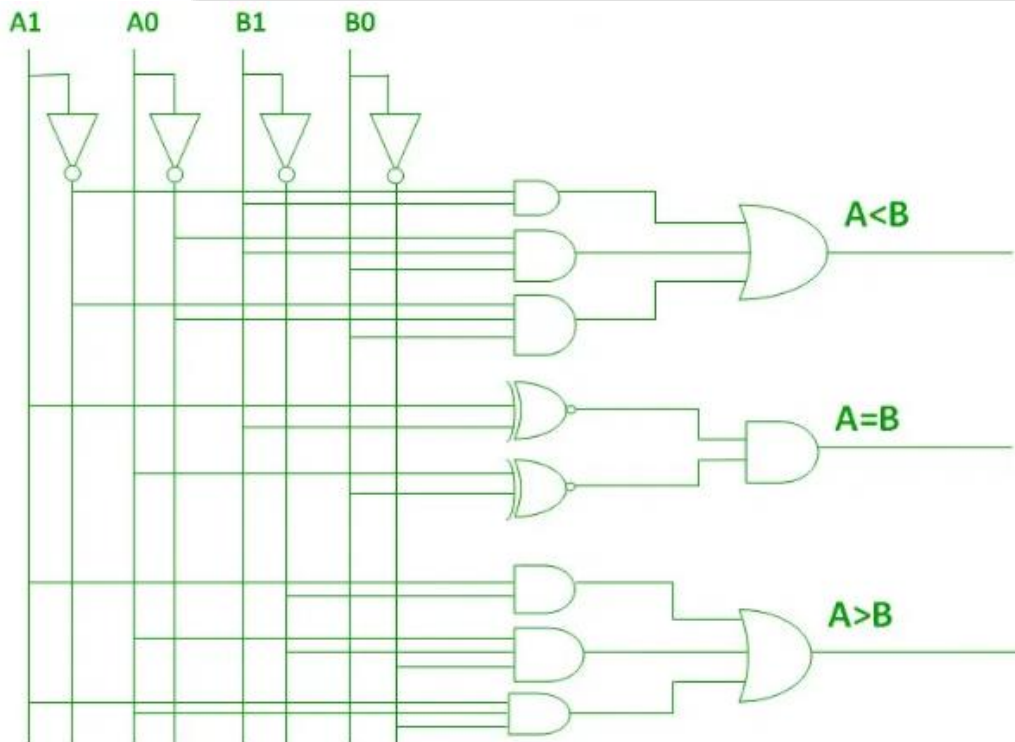

2-Bit Magnitude Comparator

6.

Flip-flop is a circuit that maintains a state until directed by input to change the state. A basic flip-flop can be constructed using four-NAND or four-NOR gates.

SR flip-flop is a gated set-reset flip-flop. The S and R inputs control the state of the flip-flop when the clock pulse goes from LOW to HIGH. The flip-flop will not change until the clock pulse is on a rising edge. When both S and R are simultaneously HIGH, it is uncertain whether the outputs will be HIGH or LOW.


 


Fig:- Logic Diagram of SR Flip flop.

 

Truth Table

CLK	S	R	Q_n	Q_{n+1}	State
0	X	X	0	0	No change/ Memory
0	X	X	1	1	
1	0	0	0	0	No change/ Memory
1	0	0	1	1	
1	1	0	0	1	Set
1	1	0	1	1	
1	0	1	0	0	Reset
1	0	1	1	0	
1	1	1	0	X	Forbidden
1	1	1	1	X	

