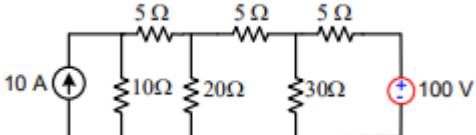
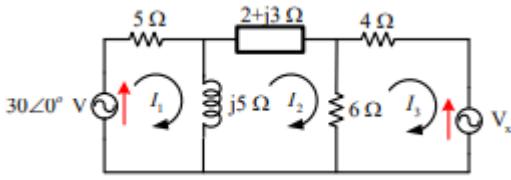
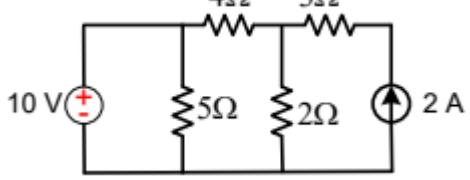
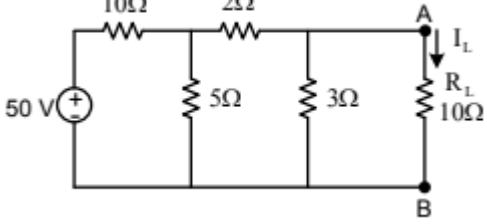
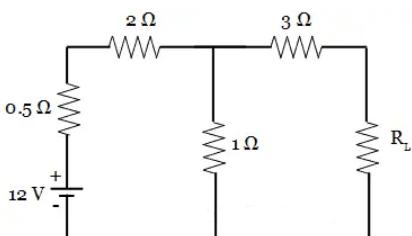


Internal Assessment Test 1 – July 2023

Sub:	Circuits & Controls	Sub Code:	21EC43	Branch:	ECE			
Date:	05-07-2023	Duration:	90 Minutes	Max Marks:	50	Sem / Sec:	4/A,B,C,D	OBE
<u>Answer any FIVE FULL Questions</u>						MARKS	CO	RBT
1	In the circuit shown in fig.1 determine all branch currents by mesh current analysis. Fig.1	[10]	CO1	L2				
								
2	Use loop analysis to find V_x in the circuit shown in fig.2. Such that the current through $2 + j3 \Omega$ is zero. Fig.2	[10]	CO1	L3				
								
3	Using superposition theorem find the voltage drop across 2Ω resistance of the circuit shown in fig.3. Fig.3	[10]	CO1	L2				
								
4	Find the Thevenin and Norton equivalent for the circuit shown in fig.4 with respect terminals A-B Fig.4	[10]	CO1	L3				
								
5	Find the value of R_L at which maximum power is transferred to the load in the following circuit shown in fig.5. Also, find the maximum power transferred. Fig.5	[10]	CO1	L2				
								

6	<p>Obtain the z parameters for the network in Fig. 6.</p> <p>Fig.6.</p>	[10]	CO2	L2
7	<p>Find the y parameters of the two-port network shown in fig.7. Then determine the current in a 4Ω load, that is connected to the output port when a 2A source is applied at the input port.</p> <p>Fig.7.</p>	[10]	CO2	L2

COURSE INSTRUCTOR

CCI


HOD

2IEC43 - Circuits & Controls


Internal Assessment Test 1

Answer key

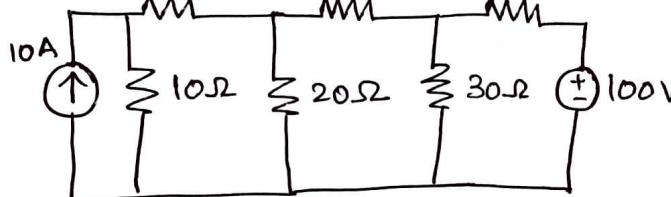1. Determine all branch currents by Mesh Analysis



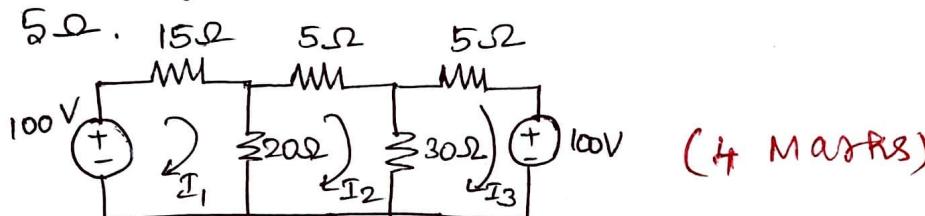Converting current source to voltage source and then 10Ω is in series with



Applying the KVL for the loop

$$35I_1 - 20I_2 = 100 \quad \text{--- (1)}$$

$$-20I_1 + 55I_2 - 30I_3 = 0 \quad \text{--- (2)}$$

$$-30I_2 + 35I_3 = -100 \quad \text{--- (3)}$$

$$\Delta = \begin{bmatrix} 35 & -20 & 0 \\ -20 & 55 & -30 \\ 0 & -30 & 35 \end{bmatrix}$$

$$= 25875 - 14000 = 21875$$

$$\Delta_1 = \begin{bmatrix} 100 & -20 & 0 \\ 0 & 55 & -30 \\ -100 & -30 & 35 \end{bmatrix} = 42500$$

$$\Delta_3 = \begin{bmatrix} 35 & -20 & 100 \\ -20 & 55 & 0 \\ 0 & -30 & -100 \end{bmatrix}$$

$$\frac{\Delta_1}{\Delta} = \frac{42500}{21875} \Rightarrow I_1 = 1.9428 \text{ A} \quad \text{(2 Marks)}$$

$$= 35(-5500) + 20(2000) + 100(600)$$

$$\Delta_2 = \begin{bmatrix} 35 & 100 & 0 \\ -20 & 0 & -30 \\ 0 & -100 & 35 \end{bmatrix} = -35000$$


$$= -192500 + 40000 + 60000$$

$$\frac{\Delta_2}{\Delta} = \frac{-35000}{21875} \Rightarrow I_2 = -1.6 \text{ A} \quad \text{(2 Marks)} = -92500$$

$$\frac{\Delta_3}{\Delta} = \frac{-92500}{21875} \Rightarrow I_3 = -4.2285 \text{ A} \quad \text{(2 Marks)}$$

$I_1 = 1.9428 \text{ A}, I_2 = -1.6 \text{ A}, I_3 = -4.2285 \text{ A}$

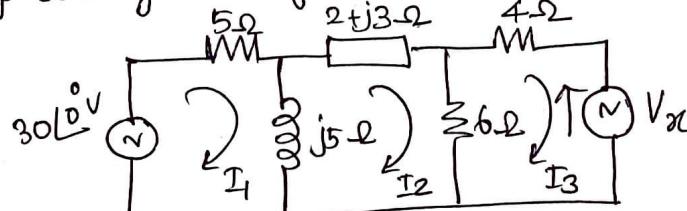2. Use loop analysis to find V_{zx} such that the current through $2+j3\Omega$ is zero.



Applying KVL to mesh I₁,

$$5I_1 + j5(I_1 - I_2) - 30 \angle 0^\circ = 0$$

$$(5+j5)I_1 - j5I_2 = 30 \angle 0^\circ \quad \text{--- (1)}$$

Applying KVL to mesh I₂

$$(2+j3)I_2 + 6(I_2 - I_3) + j5(I_2 - I_1) = 0$$

$$-j5I_1 + (8+j8)I_2 - 6I_3 = 0 \quad \text{--- (2)}$$

Finding V_x.


$$\Delta_2 = \begin{bmatrix} 5+j5 & 30 & 0 \\ -j5 & 0 & -6 \\ 0 & -V_x & 10 \end{bmatrix}$$

$$0 = (5+j5)(-6V_x) + j1500$$


$$6V_x = \frac{j1500}{5+j5} = \frac{1500 \angle 90^\circ}{7.07 \angle 45^\circ} \quad \text{(4 Marks)}$$

$$V_x = 35.36 \angle 45^\circ \text{ V}$$

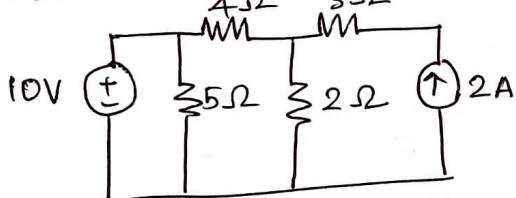3. Using superposition theorem, find the voltage drop across 2Ω resistance of the circuit



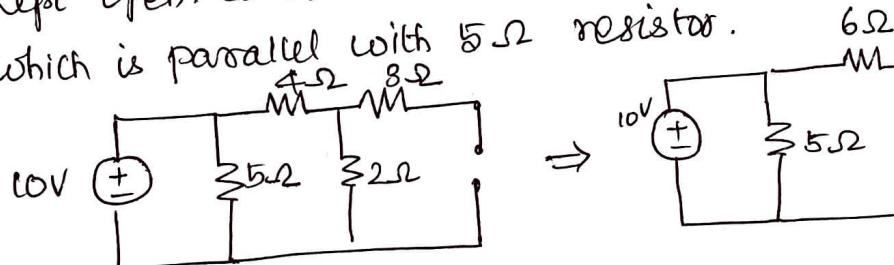Considering a single voltage source of 10V and the current source is kept open. So the 4Ω and 2Ω resistors are connected in series, which is parallel with 5Ω resistor.



(4 Marks)

$$R = \frac{5 \times 6}{5+6} = 2.727\Omega$$



$$I = \frac{V}{R} = \frac{10}{2.727} = 3.666\text{ A}$$

Using current division method, the current through 2Ω resistor is

$$I_1 = \frac{3.666 \times 5}{5+6} = 1.666\text{ A}$$

$$I_1 = 1.666\text{ A}$$

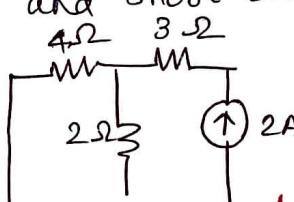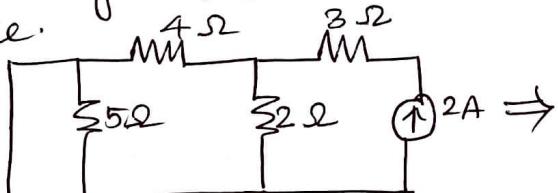Considering current source of 2A and short circuiting the voltage source.



$$R = \frac{4 \times 2}{4+2} = 1.333\Omega$$

(4 Marks)

Applying KVL to mesh I₃

$$4I_3 + 6(I_3 - I_2) + V_x = 0$$

$$-6I_2 + 10I_3 = -V_x \quad \text{--- (3)}$$

$$\Delta = \begin{bmatrix} 5+j5 & -j5 & 0 \\ -j5 & 8+j8 & -6 \\ 0 & -6 & 10 \end{bmatrix}$$

$$= (5+j5)(80+j80 - 36) + j5(-j50)$$

$$= 870 + j620 = 1068 \angle 35.47^\circ$$

Using current division method, the current through 2Ω resistor is

$$I_1 = \frac{2(1.333)}{2} = 1.333 \text{ A.}$$


Total current in the 2Ω resistor is

$$I_1 = 1.666 \text{ A} + 1.333 \text{ A} = 3 \text{ A} \quad (2 \text{ Marks})$$

Voltage across 2Ω resistor is

$$V = 2 \times 3 = 6 \text{ V.}$$

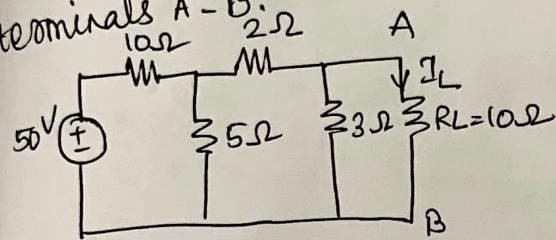4. Find Thevenin and Norton equivalent for the circuit with respect to terminals A - B.



Determine the Thevenin voltage V_{TH} . (2 Marks)

Apply KVL for the circuit given

$$15x - 5y = 50$$

$$-5x + 10y = 0$$

By solving $x = 4 \text{ A}, y = 2 \text{ A}$

$$V_{TA} = 2A \times 3 = 6 \text{ V}$$


(2 Marks)

Find R_{TH} .


$$R_{TH} = [(10||5) + 2]||3 \\ = [3.33 + 2]||3 \\ = 5.33||3$$

$$R_{TH} = 1.92 \Omega \quad (3 \text{ Marks})$$

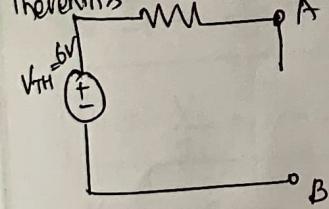Equivalent Ckt. · Thevenin's $R_{TH} = 1.92$




Equivalent Ckt. of Norton's

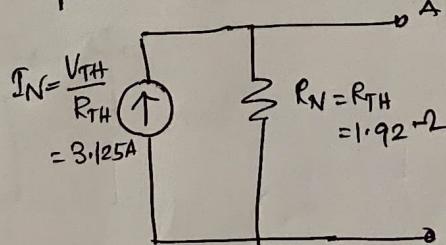

(3 Marks)

Current through R_L is $I_L = \frac{V_{TH}}{R_L + R_{TH}} = \frac{6}{1.92 + 10} = 0.503 \text{ A.}$

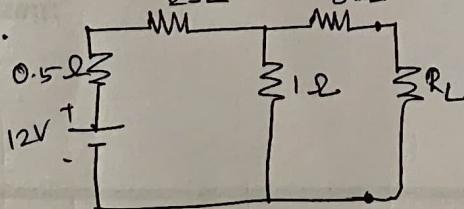
5. Find the value of R_L at which maximum power is transferred to load.



$$R_{TH} = \frac{2.5 \times 1}{2.5 + 1} = 1.714 \Omega$$

(2 Marks)

To find V_{TH} remove R_L .

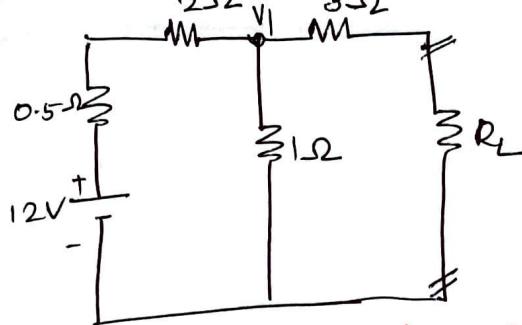

$$V_{TH} = V_1$$

Apply KCL to the circuit.

$$\frac{V_1 - 12}{2.5} + \frac{V_1}{1} + \frac{V_1}{3} = 0 \Rightarrow \frac{V_1 - 12 + 2.5V_1}{2.5} = 0$$

$$3.5V_1 - 36 + 7.5V_1 + 2.5V_1 = 0$$

$$13V_1 = 36$$


$$V_1 = 2.76 \text{ V}$$

$$R_L = R_{eq} = R_{TH}$$

$$= \frac{3.714 \Omega}{1.76 \Omega}$$

$$P_{Max} = \frac{V_{TH}^2}{4R_L} = \frac{(3.43)^2}{4 \times 1.76} = \frac{11.76}{7.04} = 1.67 \text{ W}$$

6. Obtain Z -parameters.

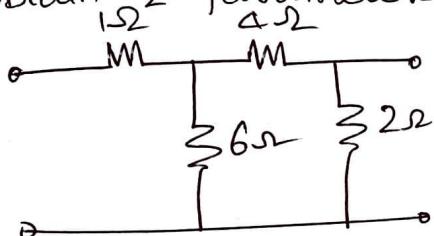

$$P = 0.7919 \text{ W}$$

Z parameter eq.

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$


$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

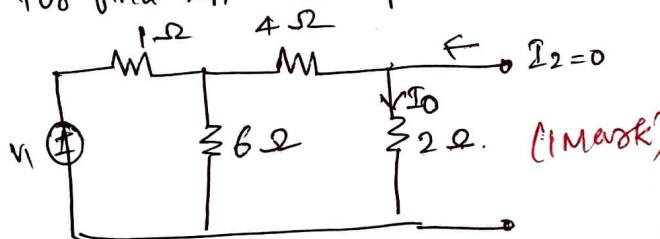For find Z_{11} & Z_{21} open circuit $\rightarrow I_2$.




$$Z_{11} = \frac{V_1}{I_1} \Rightarrow \text{Resistance } R = \frac{6 \times 4}{6+4} + 1 = 4 \Omega$$

$$I_0 = \frac{1}{2}I_1 \Rightarrow I_0 = 2I_0$$

$$Z_{11} = \frac{V_1}{I_1} = 4 \Omega \quad (2 \text{ Marks})$$

$$V_2 = 2I_0 = I_1$$
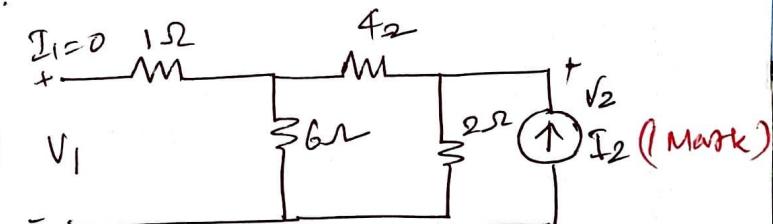
$$Z_{21} = \frac{V_2}{I_1} = 1 \Omega \quad (2 \text{ Marks})$$



$$Z_{22} = \frac{V_2}{I_2} = 2 \times (4+6) = 20 \Omega$$


$$I_0 = \frac{2}{2+10} I_2 = \frac{1}{6} I_2$$

$$V_1 = 6I_0 = V_2$$

$$Z_{12} = \frac{V_1}{I_2} = 1 \Omega \quad (2 \text{ Marks})$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 4 & 1 \\ 1 & 20 \end{bmatrix} \Omega$$

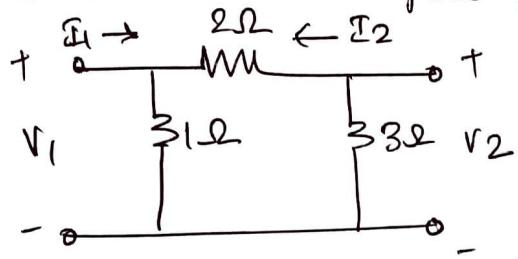Find Y parameter, then determine the current in a 4Ω load, that is connected to the output port when a 2A source is connected to the input port.



To find y_{11} & $y_{21} \rightarrow SC \rightarrow O/P$ terminal

$$I_1 = \frac{V_1}{1\Omega || 2\Omega} = \frac{V_1}{1+2} = \frac{V_1}{3} = \frac{3}{2} V_1$$

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{3}{2} S$$

(1 Mark)

Using CD rule

$$-I_2 = \frac{I_1 \times 1}{1+2} = +\frac{1}{3} I_1$$

$$-I_2 = \frac{1}{3} I_1 \Rightarrow -I_2 = \frac{1}{3} \left(\frac{3}{2}\right) V_1 = \frac{1}{2} V_1$$

$$y_{21} = \frac{I_2}{V_1} = -\frac{1}{2} S$$

(2 Marks)

To find y_{12} and y_{22} , $SC \rightarrow I/P$ terminals.

$$I_2 = \frac{V_2}{2\Omega || 3\Omega} = \frac{V_2}{2 \times 3 / 2+3} = \frac{5V_2}{6} \Rightarrow y_{22} = \frac{I_2}{V_2} = \frac{5}{6} S$$

(1 Mark)

$$\text{Using CD rule } -I_1 = \frac{I_2 \times 3}{2+3} = -I_1 = \frac{3}{5} I_2$$


$$y_{12} = \frac{-I_1}{V_2} = \frac{3/5 I_2}{6/5 I_2} = -\frac{1}{2} S$$

(2 Marks)

$$I_1 = \frac{3}{2} V_1 - \frac{1}{2} V_2 \quad (1)$$

$$I_2 = -\frac{1}{2} V_1 + \frac{5}{6} V_2 \quad (2) \text{ 2A}$$
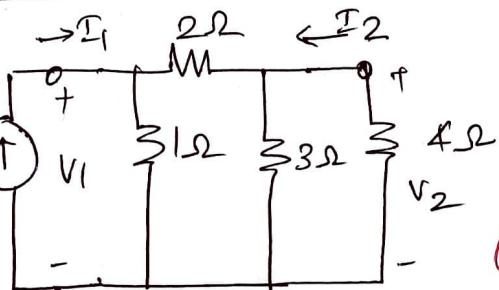
$$\begin{bmatrix} \frac{3}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{5}{6} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$



(4 Marks)

$I_1 = 2A$, $V_2 = -4I_2$. Substituting we get

$$2 = \frac{3}{4} V_1 - \frac{1}{2} V_2$$

$$\text{mul. eq(2) by } (-4) \text{ we get, } -4I_2 = 2V_1 - \frac{20}{6} V_2.$$

$$V_2 = 2V_1 - \frac{20}{6} V_2$$

$$0 = 2V_1 - \left(\frac{20}{6} + 1\right) V_2$$

$$0 = -\frac{1}{2} V_1 + \frac{13}{12} V_1$$

Solving we get $V_2 = \frac{3}{2} V$, $I_2 = \frac{-1}{4} V_2 = -\frac{3}{8} A$.