



CBCS SCHEME

17ELN15/25

USN

First/Second Semester B.E. Degree Examination, Dec.2023/Jan.2024 Basic Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Draw and explain the V-I characteristics for silicon and germanium diode. (08 Marks)
b. Define the following diode parameters :
i) Knee voltage
ii) Minimum forward current
iii) Reverse breakdown voltage
iv) Peak inverse voltage. (08 Marks)
c. Derive the relationship between α and β . A certain transistor has $\beta = 200$ and base current is $50\mu\text{A}$. Determine the collector current and α . (04 Marks)

OR

- 2 a. With a neat diagram, explain the input and output characteristics of a transistor in common emitter configurations. (08 Marks)
b. With neat circuit diagram and waveform, explain the working of full-wave bridge rectifier. (08 Marks)
c. Explain Zener diode voltage regulator circuit. (04 Marks)

Module-2

- 3 a. What is DC load line? Explain with neat circuit the operation of voltage divider bias circuit. (08 Marks)
b. Explain the characteristics of an ideal op-amp in detail. (08 Marks)
c. Explain the base bias circuit. (04 Marks)

OR

- 4 a. Explain inverting and non-inverting operational amplifiers. (08 Marks)
b. Explain the inverting summing amplifier with neat circuit diagram. Calculate the output voltage of three input inverting summing amplifier having :
 $R_1 = 200\text{K}\Omega$ $R_2 = 250\text{K}\Omega$ $R_3 = 500\text{K}\Omega$ $R_f = 1\text{M}\Omega$,
 $V_1 = -2\text{V}$ $V_2 = -1\text{V}$ and $V_3 = +3\text{V}$. (08 Marks)
c. Draw the base bias circuit using a silicon transistor with $\beta = 50$, $R_B = 100\text{K}\Omega$, $R_C = 1\text{k}\Omega$ and $V_{CC} = 10\text{V}$. Find the values of I_C and V_{CE} . (04 Marks)

Module-3

- 5 a. State and prove the De – Morgan's theorem. (06 Marks)
b. Explain the full adder circuit with truth table. (06 Marks)
c. Convert the following :
 $(49.5)_{10} = (?)_{16}$
 $(1062.403)_8 = (?)_{10}$
 $(642.71)_8 = (?)_2$
 $(734)_{10} = (?)_2$ (08 Marks)

OR

- 6 a. Realize AND, OR and NOT gates using universal gates. (06 Marks)
- b. Simplify the given Boolean equation : $y = (A + \bar{B}) \cdot (CD + E)$ and realize using NAND gates only. (06 Marks)
- c. Perform the subtraction with the following binary numbers using 1's and 2's compliment method.
- i) $(10010)_2 - (10011)_2$
- ii) $(11010)_2 - (10000)_2$ (08 Marks)

Module-4

- 7 a. Explain clocked R-S flip-flop and R-S flip-flop with its logic diagram, logic symbol and truth table. (10 Marks)
- b. Explain the architecture of 8051 microcontroller with block diagram in detail. (10 Marks)

OR

- 8 a. With the help of block diagram, explain the microcontroller based stepper motor control system. (08 Marks)
- b. Explain NAND gate and NOR gate latch with logic diagram and truth table. (08 Marks)
- c. Compare microcontroller and micro processor. (04 Marks)

Module-5

- 9 a. Explain the construction and working of LVDT and its applications. (10 Marks)
- b. Explain elements of communication system with block diagram. (04 Marks)
- c. List the differences between amplitude modulation and frequency modulation. (06 Marks)

CMRIT LIBRARY
BANGALORE - 560 037

OR

- 10 a. Define amplitude modulation. Derive mathematical expression and draw waveforms. (08 Marks)
- b. Explain the piezoelectric transducer and photoelectric transducer. (06 Marks)
- c. Explain the frequency modulation with neat waveforms. (06 Marks)
