USN

Seventh Semester B.E. Degree Examination, Dec.2023/Jan.2024
Industrial Drives and Applications

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. What are electrical drives? Draw a block diagram of an electrical drive and explain the parts of an electrical drive. (07 Marks)
 - b. A motor drive has a load which has rotational motion, coupled through a reduction gear with a = 0.1 and efficiency of 85%. The load has a moment of inertia of 10kg-m² and a torque of 10N-m. Motor has an inertia of 0.2kg-m² and runs at a constant speed of 1420rpm. Determine equivalent inertia referred to the motor shaft and power developed by the motor. (06 Marks)
 - c. Explain with a block diagram, the closed-loop converter fed dc motor drives.

OR

- 2 a. Explain the factors on which the choice of an electrical drive depends on. (07 Marks)
 - b. A motor equipped with a flywheel is to supply a load torque of 2000N-m for 8 sec followed by a light load period of 180N-m long enough for flywheel to regain its steady-state speed. It is desired to limit the motor torque to 800N-m. Motor has an inertia of 10kg-m². Its no load speed is 500rpm and slip at a torque of 500N-m is 5%. Assuming, speed-torque characteristics of motor to be a straight line, calculate the moment of inertia of the fly wheel.

 (07 Marks)
 - c. Explain modes of operation of an electrical drive.

(06 Marks)

(07 Marks)

Module-2

- 3 a. With circuit diagram and necessary waveforms, explain single phase fully controlled rectifier control of dc separately excited motor. Derive the expression of average voltage.
 - b. A separately excited dc motor is fed from a 230V, 50Hz supply through a single phase, half controlled bridge rectifier. Armatures resistance and inductance are respectively 0.3Ω and 0.06H. The motor voltage constant is $K_a = 0.9V/A$ rad/s and field resistance is $R_f = 104\Omega$. The field current is set to maximum possible value. The load torque is $T_L = 50N-m$ at 800rpm. Assuming armature and field current are continuous and ripple free, compute the field current and firing angle of the converter in armature circuit. (10 Marks)

OR

- 4 a. Explain first quadrant operation of a class A chopper connected to a dc separately excited motor. (07 Marks)
 - b. Explain chopper control of dc series motor.

(07 Marks)

c. A separately excited dc motor with an armature resistance of 0.01Ω works on a dc supply of 220V, it draws an armature current of 100A and rated speed is 1000rpm. It is fed from a chopper controller. Assuming continuous conduction, calculate duty ratio at rated torque with speed of 500rpm during motoring. (06 Marks)

Module-3

- Explain stator voltage control of Induction motors. Draw typical speed-torque curves for 5 variation in stator voltage.
 - b. For a 3-φ star connected 4 pole, 50Hz, 415V, 1460rpm squirell cage induction motor has $R_1 = 0.65\Omega, R_2 = 0.35\Omega, X_1 = 0.95\Omega, X_m = 28\Omega, X_2 = 1.43\Omega$. The motor is operated by varying stator voltage and frequency keeping V/F ratio constant at the rated condition. Determine the maximum torque and speed at which it occurs for stator frequencies of (09 Marks) i) 50Hz, ii) 35Hz.

c. Explain single phasing of induction motors

(05 Marks)

a. Explain Variable Voltage Frequency (V/F) control of induction motors. (06 Marks) 6

b. A 440V, 3¢, 50Hz, 6 pole, 945rpm delta connected induction motor has following parameters referred to stator side. $R_1 = 2\Omega$, $R_2 = 2\Omega$, $X_1 = 3\Omega$, $X_2 = 4\Omega$. Motor speed is controlled by stator voltage control to run motor at 800rpm. Calculate:

Torque developed by the motor

Voltage to be applied to motor ii)

The current drawn. iii)

(09 Marks)

Explain operation of three phase induction motor with unbalanced motor impedances.

(05 Marks)

- Explain with necessary diagrams the control of induction motors by current source inverter. 7
 - b. For a 3-phase, delta connected 6-pole 50Hz, 400V, 925rpm squirell cage induction motor, $R_s = 0.2\Omega$, $X_s = 0.5\Omega$, $X_r = 1.1\Omega$. The motor is operated from voltage source inverter with constant V/F ratio from 0 to 50Hz and having constant voltage of 400V above 50Hz frequency. Calculate:

Speed for a frequency of 35Hz with half full load torque.

(06 Marks)

Torque for a frequency of 35Hz for a speed of 650rpm. Explain with a diagram, the variable frequency control of synchronous motors (multiple (06 Marks) motors).

- Explain with diagrams, cycloconverter control of three phase induction motors. (08 Marks)
 - Explain speed-torque characteristics of a synchronous motor with a fixed frequency supply. (06 Marks)
 - Explain speed control of single phase induction motors.

(06 Marks)

CMRIT LIBRARY Module-5 BANGALORE - 560 037

- Explain self controlled synchronous motor drive employing load commutated thyristor 9 (10 Marks)
 - Explain industrial drives used in
 - Textile mills i)
 - ii) Steel rolling mills.

(10 Marks)

OR

- Explain torque versus stepping rate characteristics of a stepper motor. (06 Marks) 10
 - Write short notes on Brushless DC motor drives.

(08 Marks)

Explain industrial drives used for cranes and hoists.

(06 Marks)

* * * * *