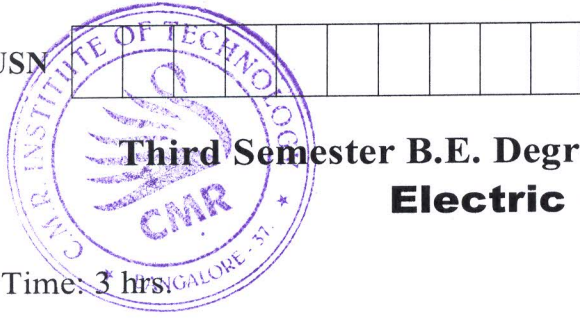


USN



Third Semester B.E. Degree Examination, Dec.2023/Jan.2024 Electric Circuit Analysis

Time: 3 hrs

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Determine ' V_x ' in the accompanying circuit in Fig. Q1 (a) using source transformation.

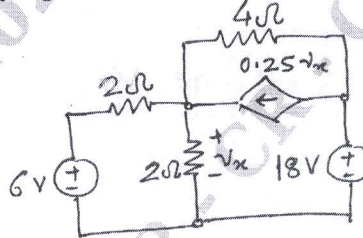


Fig. Q1 (a)

(07 Marks)

- b. Solve the accompanying circuit in Fig. Q1 (b) using mesh analysis and determine ' V_o '.

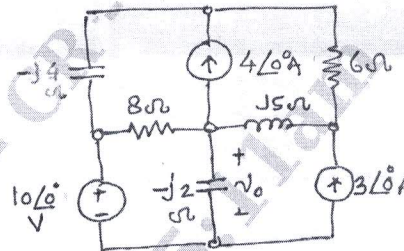


Fig. Q1 (b)

(08 Marks)

- c. Determine the node voltages for the accompanying circuit in Fig. Q1 (c), using nodal analysis.

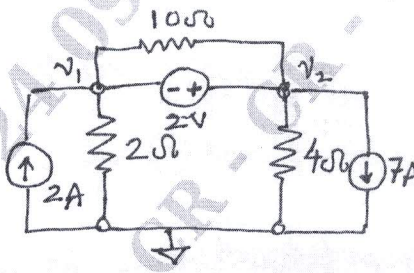


Fig. Q1 (c)

(05 Marks)

OR

- 2 a. Determine the voltage ' V_x ' in accompanying circuit in Fig. Q2 (a) using source transformation.

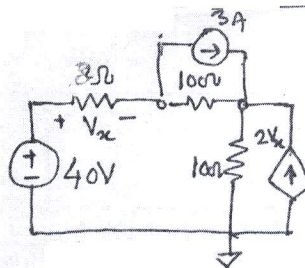


Fig. Q2 (a)

(07 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- b. Use mesh analysis to determine i_o in the accompanying circuit in Fig. Q2 (b).

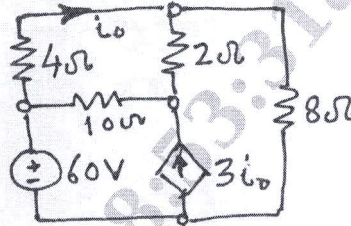


Fig. Q2 (b)

(06 Marks)

- c. Compute V_1 and V_2 using nodal analysis in the accompanying circuit in Fig. Q2 (c).

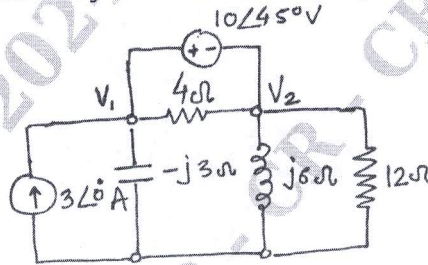


Fig. Q2 (c)

(07 Marks)

Module-2

- 3 a. Determine I_o in the accompanying circuit in Fig. Q3 (a), using principle of superposition.

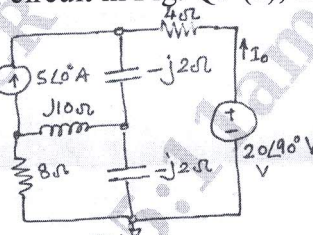


Fig. Q3 (a)

(08 Marks)

- b. Solve the accompanying circuit for 'I', using Thevenin's theorem for the Fig. Q3 (b).

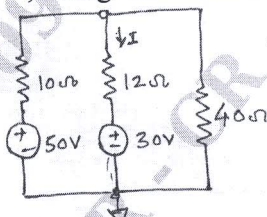


Fig. Q3 (b)

(07 Marks)

- c. State and explain reciprocity theorem, using an appropriate illustration.

(05 Marks)

OR

CMRIT LIBRARY
BANGALORE - 560 037

- 4 a. Compute ' i_o ' in the accompanying circuit in Fig. Q4 (a), using Thevenin's theorem.

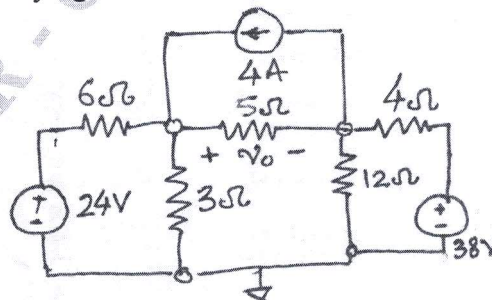


Fig. Q4 (a)

(07 Marks)

- b. Determine 'V_x' using principle of superposition in the accompanying circuit, in Fig. Q4 (b).

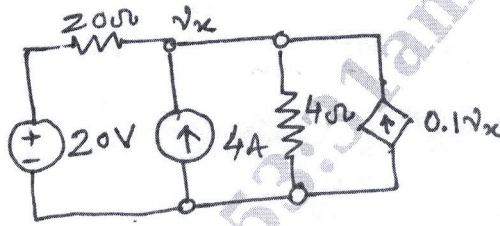


Fig. Q4 (b)

(07 Marks)

- c. Determine the value of 'R_L', that will draw maximum power transport of the circuit, in accompanying circuit Fig. Q4 (c). Also calculate the maximum power.

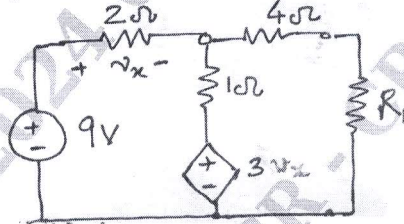


Fig. Q4 (c)

(06 Marks)

Module-3

- 5 a. For the accompanying circuit Fig. Q5 (a), determine :
- (i) Resonant frequency ' ω_0 '.
 - (ii) Half power frequencies ' ω_1 ', ' ω_2 '.
 - (iii) Quality factor and bandwidth.
 - (iv) Amplitude of current at ' ω_0 ', ' ω_1 ' and ' ω_2 '

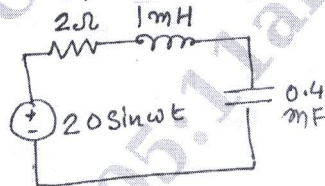


Fig. Q5 (a)

(08 Marks)

- b. The key 'K' in accompanying circuit Fig. Q5 (b) closed at $t = 0$. Assuming the capacitor in a discharged state for $t < 0$, obtain an expression for capacitor voltage $V_C(t)$.

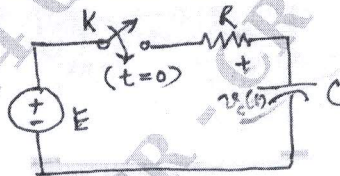


Fig. Q5 (b)

(06 Marks)

- c. Explain the concept of resonance in a series R-L-C circuit with help of appropriate mathematical expression. Draw indicative plots for current V/s frequency and phase V/s frequency for the same and explain.

(06 Marks)

OR

CMRIT LIBRARY
BANGALORE - 560 037

- 6 a. The accompanying circuit in 'Fig. Q6 (a)' is assumed unexcited for $t < 0$. The key 'K' is closed at $t = 0$. Obtain the expression for $V_0(t)$.

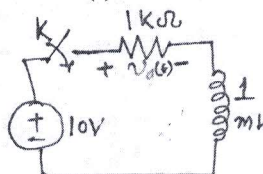


Fig. Q6 (a)

(07 Marks)

- b. For the parallel R-L-C circuit in Fig. Q6 (b) shown in accompanying diagram, Find :
- Resonance frequency ' ω_0 '.
 - Half power frequencies ' ω_1 ' and ' ω_2 '.
 - Power dissipated at ' ω_0 ', ' ω_1 ' and ' ω_2 '.

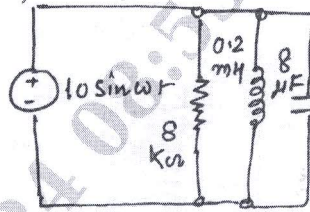


Fig. Q6 (b)

(07 Marks)

- c. Derive the expression for quality factor (Q-factor) for a parallel resonance circuit. Explain its utility in comparing resonant circuits selectivity. (06 Marks)

Module-4

- 7 a. Determine Laplace's transform of the saw-tooth wave shown in accompanying diagram in Fig. Q7 (a).

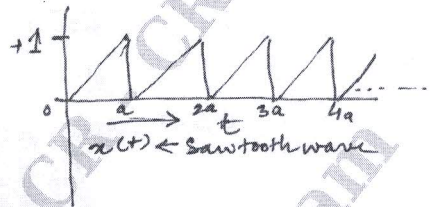


Fig. Q7 (a)

(07 Marks)

- b. The circuit shown in the accompanying diagram in Fig. Q7 (b) excited by $V(t) = 12 \sin 5t$ volts, the initial current $i(0^+)$ is 5A, capacitor voltage as $t = 0^+$, $V_c(0^+)$ is 1 V, with polarity indicated. Determine $i(t)$, using Laplace's transformation method.

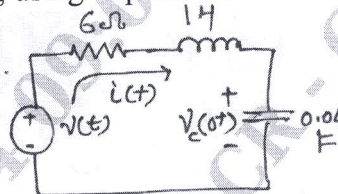


Fig. Q7 (b)

(08 Marks)

- c. Given Laplace's transform of $x(t)$, $u(t)$ is $X(s)$. Prove that, the Laplace's transform of $x(t-a)$, $u(t-a)$ is $\exp(-as)X(s)$. (05 Marks)

CMRIT LIBRARY
BANGALORE - 560 037

OR

- 8 a. Determine the Laplace's transform of square wave shown in accompanying diagram in Fig. Q8 (a).

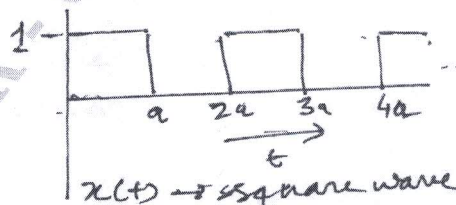


Fig. Q8 (a)

(07 Marks)

- b. The circuit in Fig. Q8 (b) accompanying diagram, is excited by a voltage pulse of height 2V and duration 5 sec. Determine the current flowing in the circuit $i(t)$. Use Laplace's transform method. (Assume zero initial condition).

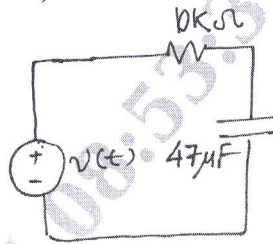


Fig. Q8 (b)

(08 Marks)

- c. State and prove the initial value theorem of Laplace's transform.

(05 Marks)

Module-5

- 9 a. A balanced, 3 phase, voltage 400 V, RYB sequence drives a delta connected load of $Z_{RY} = 10\angle 60^\circ \Omega$, $Z_{YB} = 20\angle 90^\circ \Omega$ and $Z_{BR} = 25\angle 30^\circ \Omega$. Determine the line currents and total power supplied to the load.

(07 Marks)

- b. Derive expressions for 'Z' parameters of a 2-port network in terms of its 'Y' parameters.

(06 Marks)

- c. Find Y-parameters of the network shown in Fig. Q9 (c) accompanying diagram.

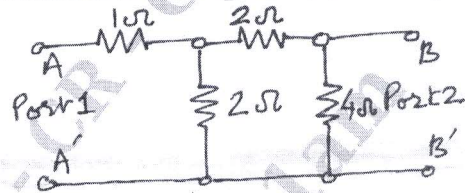


Fig. Q9 (c)

(07 Marks)

OR

CMRIT LIBRARY
BANGALORE - 560 037

- 10 a. In a 3 ph, 3 wire $400\angle 0^\circ$ V, R-Y-B system, a 3-phase unbalanced load, $Z_R = 6\angle 0^\circ \Omega$, $Z_Y = 6\angle 0^\circ \Omega$ and $8\angle -90^\circ \Omega$. Compute : line currents and power delivered to the load.

(07 Marks)

- b. What are the conditions for a 2-port network to be termed as reciprocal? Derive the conditions for a network to be reciprocal, in terms of its transmission parameters.

(06 Marks)

- c. Obtain the Y-parameters for the 2-port network shown in accompanying diagram, in Fig. Q10 (c).

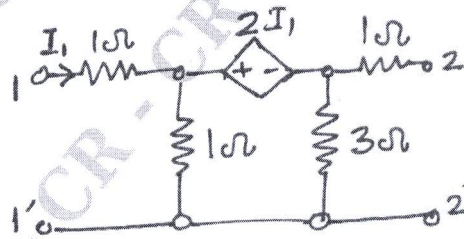


Fig. Q10 (c)

(07 Marks)
