 


CBCS SCHEME



17EE34

Module-1

- 1 a. Draw a double ended clipper circuit and explain the working principle with transfer characteristics. (10 Marks)
- b. What is the clamper? Explain the operation of positive clamper with reference :
 - i) Zero
 - ii) Positive (V_R)
 - iii) Negative ($-V_R$). (10 Marks)

OR

- 2 a. Design a voltage divider biasing circuit with a supply voltage of 10V and $V_{CE} = \frac{V_{CC}}{2}$. The load resistance is $2K\Omega$. Take $\beta = 100$. (08 Marks)
- b. Derive the expression for stability factor for fixed bias circuit with respect to I_{CO} , I_{BE} and β . (07 Marks)
- c. Explain how a transistor can be used as a switch. (05 Marks)

Module-2

- 3 a. Draw the circuit of common emitter amplifier with voltage divider biasing. Derive the expression for current gain, voltage gain, input and output impedance using the h model. (08 Marks)
- b. Derive equations for miller input capacitance and output capacitance. (08 Marks)
- c. The h-parameter for the transistor are $h_{ie} = 1.1K\Omega$, $h_{fe} = 99$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oc} = 25\mu A/v$. Find h-parameters for CC configuration. (04 Marks)

OR

- 4 a. A voltage source of negligible internal resistance drives a common collector transistor amplifier. The load resistance is 2500Ω . The transistor h parameters are $h_{ic} = 1000\Omega$, $h_{rc} = 1$, $h_{fc} = -50$, $h_{oc} = 25\mu A/v$. Compute A_i , A_v , Z_i and Z_o . (08 Marks)
- b. Starting from fundamentals, define h-parameters and obtain h-parameter equivalent circuit of CE configuration. (08 Marks)
- c. Compare the characteristics of CB, CE and CC configuration. (04 Marks)

Module-3

- 5 a. Drive expression for Z_i and A_i for a Darlington emitter follower circuit. (10 Marks)
- b. An amplifier consists of 3 identical stages in cascade. If the bandwidth of the overall amplifier extends from 20Hz to 20KHz, calculate the bandwidth of the individual stage. (06 Marks)
- c. List the advantages of negative feedback. (04 Marks)

OR

- 6 a. Draw the block diagram of voltage series feedback amplifier and find the effect of input and output impedance. (10 Marks)
- b. Explain the need of a cascading amplifier. Draw and explain the block diagram of two stage cascade amplifier. (06 Marks)
- c. An amplifier has a midband voltage gain of 1000 with $f_L = 50\text{Hz}$ and $f_H = 50\text{KHz}$. If 5% feedback is applied, then calculate f_L and f_H with feedback. (04 Marks)

Module-4

- 7 a. Explain the operation of class B push pull amplifier. Prove that the maximum efficiency of class B configuration is 78.5%. (08 Marks)
- b. Explain the classification of power amplifier with neat circuit diagram and waveforms of collector current and collector voltage for each type of power amplifier. (08 Marks)
- c. A crystal has the following parameters : $L = 3\text{H}$, $C_s = 0.05\text{pF}$, $R = 2\text{K}\Omega$, $C_m = 10\text{pF}$. What are the series and parallel resonant frequencies of the crystal? (04 Marks)

OR

- 8 a. Derive an expression for frequency of oscillation of RC phase shift oscillator. (10 Marks)
- b. Explain the principle of operation of oscillator and the effect of loop gain (A_β) on the output of oscillator. (06 Marks)
- c. The following distortion readings are available for a power amplifier :
 $D_2 = 0.1$, $D_3 = 0.02$, $D_4 = 0.03$ with $I_1 = 4\text{A}$, $R_C = 8\Omega$.
 Calculate :
 i) Total harmonic distortion
 ii) Fundamental power
 iii) Total power. (04 Marks)

Module-5

- 9 a. With a neat diagram, explain the construction and working and characteristics of n channel JFET. (10 Marks)
- b. For the following circuit, find voltage gain and output impedance :
 i) if $r_d = 20\text{K}\Omega$ ii) $r_d = \infty$. (Refer Fig.Q9(b))

 


Fig.Q9(b)

$V_{DD} = 10\text{V}$

$I_{DSS} = 10\text{mA}$

$V_P = -4\text{V}$

CMRIT LIBRARY
BANGALORE - 560 037

(10 Marks)

OR

- 10 a. Explain the construction, working and characteristics of n-channel enhancement type MOSFET. (10 Marks)
- b. Draw the circuit of common source amplifier using JFET. With the help of small signal model derive an expression for input impedance, voltage gain and output impedance. (10 Marks)
