 


USN



## Third Semester B.E. Degree Examination, Dec.2023/Jan.2024 Digital System Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Simplify using K map  
i)  $f(a, b, c, d) = \sum m(0, 1, 4, 8, 9, 10) + d(7, 11)$   
ii)  $f(a, b, c, d) = \pi m(0, 1, 4, 10, 11, 14, 15)$  (08 Marks)
- b. Convert the given function into corresponding canonical formula and decimal notation form  
i)  $f(a, b, c) = ab + a\bar{c} + bc$  (08 Marks)  
ii)  $f(a, b, c) = (a + b)(b + c)$  (08 Marks)
- c. Define Canonical minterm formula and Canonical maxterm formula. (04 Marks)

OR

- 2 a. Find the minimal sum and minimal product for the given Boolean function  
 $f(a, b, c, d) = \sum m(2, 3, 4, 5, 13, 15) + d(8, 9, 10, 11)$  (06 Marks)
- b. Simplify using K map  
 $f(a, b, c, d, e) = \sum m(0, 1, 4, 5, 7, 8, 9, 12, 13, 15, 21, 23, 29, 31)$  (06 Marks)
- c. Simplify using Quine - Mc Cluskey method.  
 $f(a, b, c, d) = \sum m(0, 2, 8, 10, 12)$  (08 Marks)

### Module-2

- 3 a. With a neat diagram, explain the operation of a look ahead carry generator. (08 Marks)
- b. Implement the given function using  
i) 8 : 1 MUX with a, b, c as select lines  
ii) 4 : 1 MUX with a, b as select lines  
 $f(a, b, c, d) = \sum m(4, 5, 7, 8, 10, 12, 15)$  (08 Marks)
- c. Design a 16:1 MUX using 4:1 MUX. (04 Marks)

OR

- 4 a. What is a magnitude comparator? Design a 2 bit magnitude comparator. (08 Marks)
- b. Implement the multiple output function using 3:8 decoder with active low output lines  
 $F_1(a, b, c) = \sum m(1, 4, 5, 7)$   
 $F_2(a, b, c) = \pi m(2, 3, 6, 7)$  (06 Marks)
- c. Design a logic circuit with inputs P, Q, R so that output is high wherever  $P = 0$  or  $Q = R = 1$ . (06 Marks)

### Module-3

- 5 a. With a neat diagram, explain the working of a master slave JK flipflop along with waveforms. (10 Marks)
- b. With a neat diagram, explain different modes of operation of universal shift register. (10 Marks)

OR

- 6 a. Give the logic diagram and counting sequence of ring counter and Johnson counter. (06 Marks)
- b. Derive the characteristics equation of SR, JK, D and T flipflop. (08 Marks)
- c. Design a mod 6 synchronous counter using T Flip Flop. (06 Marks)

**Module-4**

- 7 a. Compare Mealy and Moore synchronous sequential circuit with neat block diagram. (08 Marks)
- b. Design a counter with the sequence 7, 4, 3, 1, 6, 0, 7 with JK flipflop (12 Marks)

OR

- 8 a. Analyze the given synchronous sequential circuit given below and draw the state table and state diagram.

 


Fig Q8(a)

(10 Marks)

- b. Construct a sequential circuit with single input single output by obtaining the state and excitation table for the given diagram using JK Flipflop.

 


Fig Q8(b)

(10 Marks)

**Module-5**

- 9 a. Explain the structure of VHDL module and verilog module with an example of half adder. (10 Marks)
- b. Explain the shift operators of VHDL and verilog with an example. (10 Marks)

OR

CMRIT LIBRARY  
BANGALORE - 560 037

- 10 a. Explain the data types available in VHDL. (10 Marks)
- b. Explain the structure of behavioural description and data flow description with a suitable example. (10 Marks)

\*\*\*\*\*