

# CBCS SCHEME

18EE32

USN 

|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|

## Third Semester B.E. Degree Examination, Dec.2023/Jan.2024 Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Reduce the network shown in Fig.Q1(a) to a single voltage source in series with a resistance.

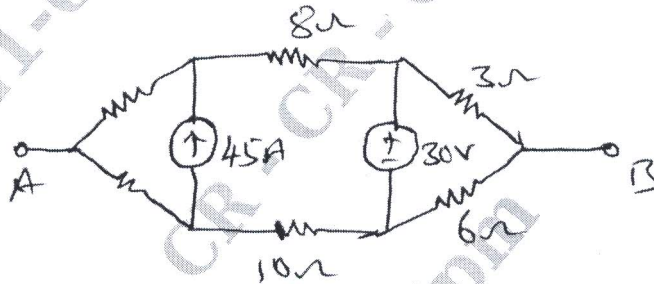


Fig.Q1(a)

(08 Marks)

- b. Determine the nodal voltages  $V_1$ ,  $V_2$ ,  $V_3$  and  $V_4$  in the circuit shown in Fig.Q1(b).

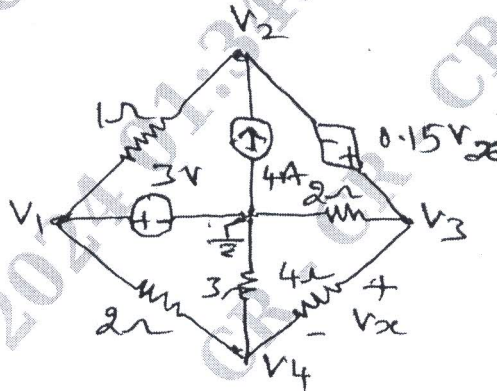


Fig.Q1(b)

(08 Marks)

- c. Compute the resistance between A and B in network shown in Fig.Q1(c) using star - Delta transformation.

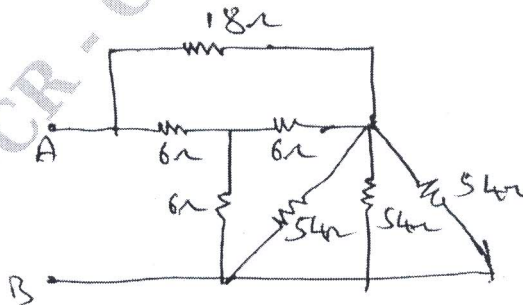


Fig.Q1(c)

(04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 2 a. For the circuit shown in Fig.Q2(a) determine  $I_x$  using Mesh analysis.

(08 Marks)

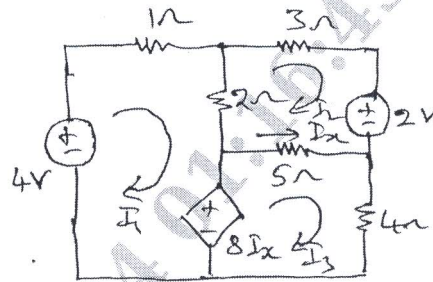


Fig.Q2(a)

- b. Determine node voltages in network shown in Fig.Q2(b).

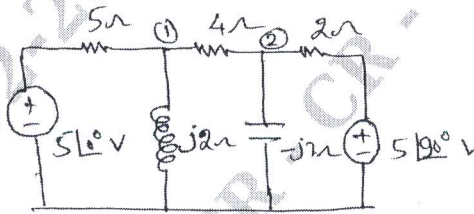


Fig.Q2(b)

(06 Marks)

- c. Find current  $I$  using Mesh analysis in the network shown in Fig.Q2(c).

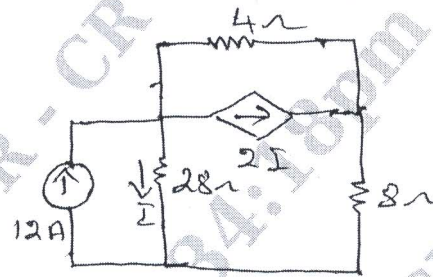


Fig.Q2(c)

(06 Marks)

**Module-2** CMRIT LIBRARY  
BANGALORE - 560 037

- 3 a. State and explain super Position theorem.

(06 Marks)

- b. Determine the current  $I$  in the network shown in Fig.Q3(b) and verify reciprocity theorem.

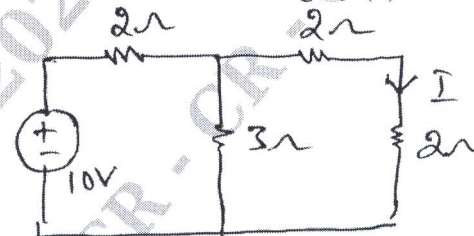


Fig.Q3(b)

(06 Marks)

- c. Obtain Thevenin's equivalent of the network shown in Fig.Q3(c) between terminals A and B and find the power dissipation in load resistance  $4\Omega$ .

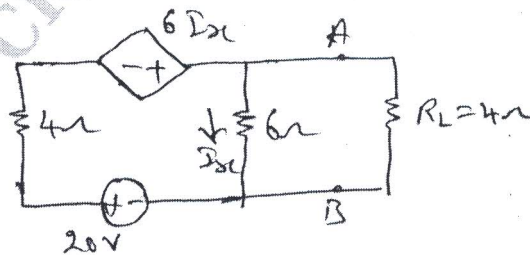


Fig.Q3(c)

(08 Marks)

OR

- 4 a. State and prove Norton's theorem. (06 Marks)  
 b. Using Millman's theorem find  $I_L$  through  $R_L$  for the network shown in Fig.Q4(b).

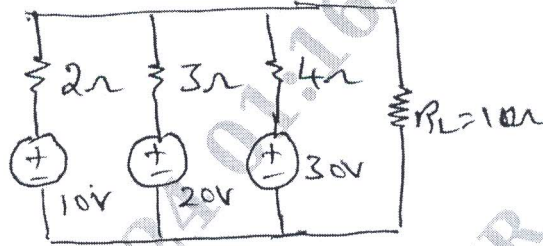


Fig.Q4(b)

(06 Marks)

- c. Find the value of load resistance when maximum power is transferred across it also find the value of maximum power transferred. (Refer Fig.Q4(c)).

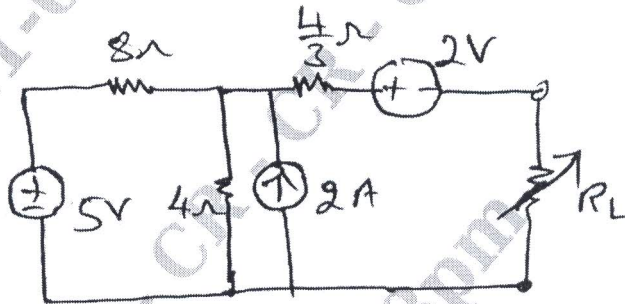


Fig.Q4(c)

(08 Marks)

Module-3

- 5 a. Define the following terms with respect to resonant circuit :  
 i) Resonant frequency  
 ii) Q Factor  
 iii) Bandwidth  
 iv) Selectivity. Write the expression of each. (08 Marks)
- b. A series RLC circuit has  $R = 1\Omega$ ,  $L = 0.01\text{H}$  and  $C = 0.01\mu\text{F}$  and it is connected across  $\theta$  variable frequency source. Determine :  
 i) Resonant frequency  
 ii) Quality factor  
 iii) Bandwidth  
 iv) Cut off frequencies  $f_1$  and  $f_2$ . (06 Marks)
- c. Find  $i(0^+)$ ,  $\frac{di}{dt}(0^+)$  and  $\frac{d^2i}{dt^2}(0^+)$  in the network shown in Fig.Q5(c).

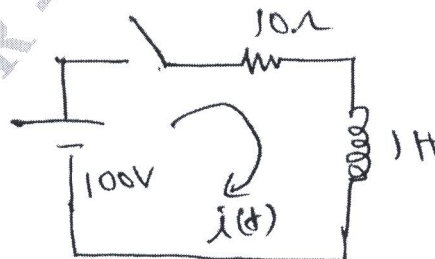


Fig.Q5(c)

(06 Marks)



OR

- 6 a. In the network shown in Fig.Q6(a) switch 'K' is changed from position 'Q' to 'b' at  $t = 0$ . Solve for  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ , if  $R = 1000\Omega$ ,  $L = 1H$ ,  $C = 0.1$  and  $v = 1000V$ . Assume capacitor is initially uncharged.

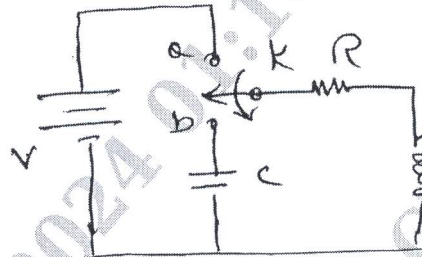


Fig.Q6(a)

(08 Marks)

- b. Show that the resonant frequency at a series RLC circuit is equal to geometric mean of two half power frequencies. (06 Marks)
- c. For the circuit shown in Fig.Q6(c) find two values of capacitor for the reasonable. Consider  $f = 50Hz$ .

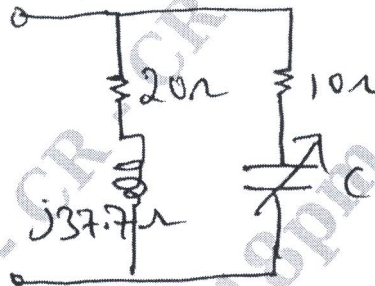


Fig.Q6(c)

(06 Marks)

**Module-4**

- 7 a. Find  $i(t)$  for  $t \geq 0$  for the network shown in Fig.Q7(a) using Laplace transformers.

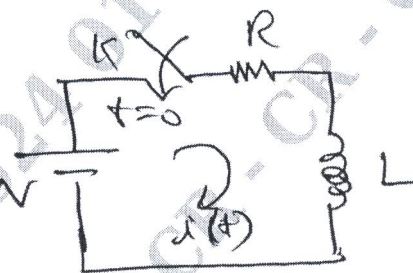


Fig.Q7(a)

(06 Marks)

- b. State and prove :
- Initial value theorem **CMRIT LIBRARY**
  - Final value theorem. **BANGALORE - 560 037**
- c. Obtain the Laplace transform of triangular waveform shown in Fig.Q7(c).

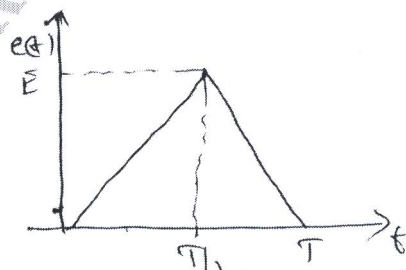


Fig.Q7(c)

(08 Marks)

OR

- 8 a. Find the Laplace transform of the waveform shown in Fig.Q8(a).

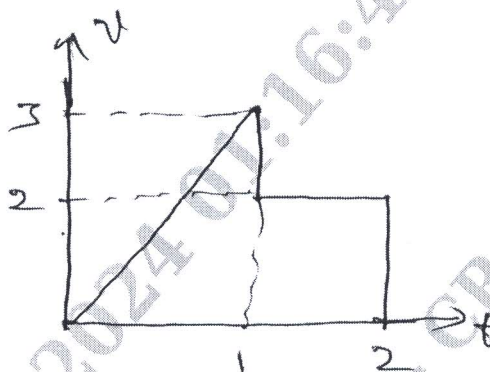


Fig.Q8(a)

(08 Marks)

- b. Find the Laplace transform of periodic waveform shown in Fig.Q8(b).

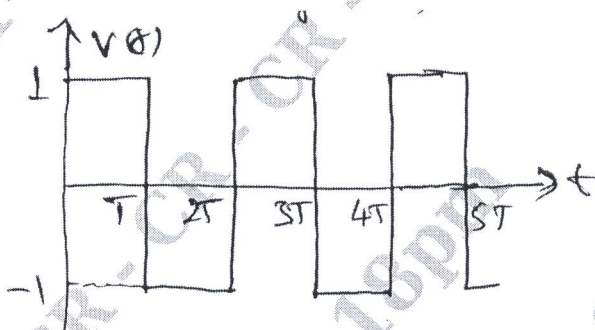


Fig.Q8(b)

(08 Marks)

- c. Find the Laplace transform of the following function : i)  $u(t)$  ii)  $\delta(t)$ .

(04 Marks)

**CMRIT LIBRARY**  
BANGALORE - 560 037

Module-5

- 9 a. Find the open circuit impedance parameters for the current shown in Fig.Q9(a).

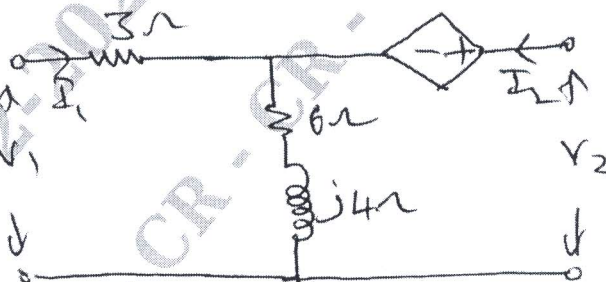


Fig.Q9(a)

(06 Marks)

- b. Derive expressions for 'Y' parameters in terms of Z - parameters.

(06 Marks)

- c. A 3 - phase 400V, 4 wire system has a star connected load with  $Z_R = 10\Omega$ ,  $Z_Y = (15 + j10)\Omega$  and  $Z_B = j5\Omega$ . Find the line current and current through neutral conductor. Draw the vector diagram.

(08 Marks)

OR

- 10 a. Find 'Y' parameters of the two port network shown in Fig.10(a). Also find 'Z' parameters.

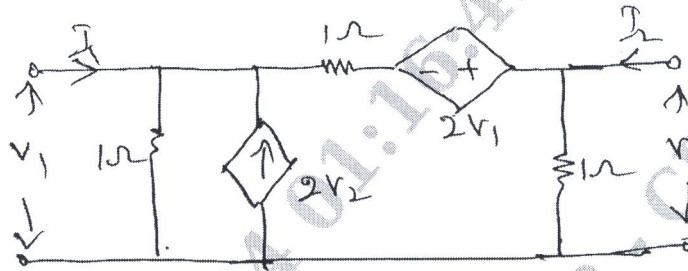


Fig.Q10(a)

(10 Marks)

- b. A balanced set of three phase voltages is connected to an unbalanced set of 'Y' connected impedances.  $V_{RY} = 212 \angle 90^\circ \text{V}$ ,  $V_{YB} = 212 \angle -150^\circ \text{V}$  and  $V_{BR} = 212 \angle -30^\circ \text{V}$ ,  $Z_R = (10 + j0)\Omega$ ,  $Z_Y = (10 + j0)\Omega$  and  $Z_C = (0 - j20)\Omega$ .

Find :

- The line current
- Phase voltages
- Power dissipated in each phase.

CMRIT LIBRARY  
BANGALORE - 560 037

(10 Marks)

\*\*\*\*\*