

CBCS SCHEME



USN

--	--	--	--	--	--	--	--	--	--

18EC42

Fourth Semester B.E. Degree Examination, Dec.2023/Jan.2024 Analog Circuits

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- a. Mention and explain the design issues of a classical biasing for BJT using collector-to-base feedback resistor and which uses single power supply. (10 Marks)
b. Design classical bias network of amplifier to establish a current $I_E = 1$ mA using a power supply $V_{CC} = +12$ V and transistor has $\beta = 100$. (10 Marks)

OR

- a. Explain the design of biasing technique for discrete MOSFET by fixing V_G and connecting a resistance in source and drain-to-Gate feedback resistor. (10 Marks)
b. Determine voltage gain of transistor amplifier for the circuit shown in Fig.Q2(b). Assume $\beta = 100$.

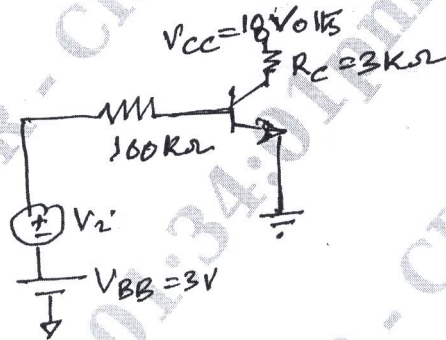


Fig.Q2(b)

(10 Marks)

Module-2

- a. Deduce and expression for upper cut off frequency of MOSFET – common source amplifier. (10 Marks)
b. Find the mid band gain A_M and the upper 3-dB frequency f_H of a CS amplifier fed with a signal source having an internal resistance $R_{sig} = 100$ K Ω . The amplifier has $R_G = 4.7$ M Ω , $R_D = R_L = 15$ K Ω , $g_m = 1$ mA/V, $r_o = 150$ K Ω , $C_{gs} = 1$ PF and $C_{gd} = 0.4$ pf. (10 Marks)

OR

- a. With a neat circuit diagram, explain the operation of FET based phase shift oscillator. (10 Marks)
b. With a neat circuit diagram, explain the operation of crystal oscillator along with relevant equation for frequency of oscillation. (10 Marks)

Module-3

- a. Discuss the properties of negative feedback. (10 Marks)
b. Using ideal structure and equivalent circuit. Deduce an expression for input and output resistance of:
(i) Series shunt feedback amplifiers
(ii) Shunt-shunt configuration (10 Marks)

OR

- 6 a. Derive an expression efficiency of class C power amplifier. (10 Marks)
- b. Deduce an expression for output resistance by discussing the circuit operation of class AB output stage. (10 Marks)

Module-4

- 7 a. For a practical inverting amplifier the values of R_1 and R_f are 470Ω and $4.7 K\Omega$. The various specifications for opamp used are:
 Open loop gain = 2×10^5
 Input resistance = $2 M\Omega$
 Output resistance = 75Ω
 Single break frequency = 5 Hz
 Supply voltages = $\pm 15\text{V}$
 Calculate closed loop voltage gain, i/p and o/p resistance and bandwidth with feedback. (10 Marks)
- b. Mention and explain the requirements of a good instrumentation amplifier and analyze three opamp instrumentation amplifier. (10 Marks)

OR

- 8 a. Design an opamp Schmitt trigger with following specifications $UTP = 2\text{V}$, $LTP = -4\text{V}$ and the output swings between $\pm 10\text{V}$. If the input is $5\sin\omega t$, plot the waveforms of input and output. (10 Marks)
- b. Discussing the circuit operation of (i) DC amplifiers (ii) AC amplifiers, using OPAMPS. (10 Marks)

CMRIT LIBRARY
RANGALORE - 560 037

Module-5

- 9 a. Explain the circuit operation of monoshot using IC555. Derive the expression of pulse width. (10 Marks)
- b. For the circuit shown in Fig.Q9(b), determine the lower cutoff frequency and then plot the frequency response of filter. (10 Marks)

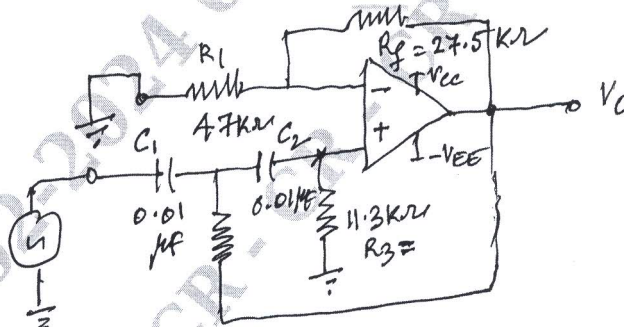


Fig.Q9(b)

(10 Marks)

OR

- 10 a. Discuss the circuit operation of Astable multivibrator using IC555. Derive an expression for frequency of oscillations. (10 Marks)
- b. Discuss the working of successive approximation ADC. (10 Marks)
