



USN

--	--	--	--	--	--	--	--	--	--

Fourth Semester B.E. Degree Examination, Dec.2023/Jan.2024
Linear Integrated Circuits

Max. Marks: 80

Time: 3 hrs.

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define the following terms as applied to Op-Amp and mention their typical values for IC 741. i) CMRR ii) Slew rate iii) PSRR. (06 Marks)
- b. With a neat circuit diagram explain the basic Op-Amp circuit. (06 Marks)
- c. An operational amplifier has a specified input voltage range of $\pm 8V$ and an output voltage range of $\pm 14V$ when the supply voltage is $\pm 15V$. Calculate the maximum output voltage that can be produced i) When the Op-Amp is used as a voltage follower ii) When it is used as an amplifier with a voltage gain of 2. (04 Marks)

OR

- 2 a. With a neat circuit diagram, explain direct coupled inverting amplifier with design steps, input impedance and output impedance. (08 Marks)
- b. Derive an output voltage equation of 3 input inverting summing circuit and show how it can be converted into averaging circuit. (08 Marks)

Module-2

- 3 a. Draw the circuit of a capacitor coupled non-inverting amplifier and explain with necessary design equations. Design a high input impedance capacitor coupled non-inverting amplifier with a gain of 100 and lower cut off frequency of 100 Hz. Assume the load resistance is $2.2 K\Omega$ and input parasitic capacitance as 15 pF. (10 Marks)
- b. Design a capacitor coupled inverting amplifier for a pass band gain of 100, lower cut off frequency of 120 Hz and upper cutoff frequency to be 5 kHz. Use LF353 BIFET opamp and assume load resistance as $2 K\Omega$. (06 Marks)

OR

- 4 a. Draw the circuit of an instrumentation amplifier and explain. Also show the method of nulling common mode outputs and how dc output voltage can be level shifted. (09 Marks)
- b. Design a non-saturating precision half wave rectifier to produce a 2 V peak output from a 1 MHz sine wave input with a 0.5 V peak value. Use a bipolar op-amp with a supply voltage of $\pm 15V$. (07 Marks)

Module-3

- 5 a. With neat circuit diagram and waveforms, explain sample and hold circuit. (08 Marks)
- b. Explain differentiating circuit operation with neat circuit diagram and design steps. (08 Marks)

OR

- 6 a. Using 741 Op-Amp with a supply of $\pm 12V$, design a phase shift oscillator to have an output frequency of 3.5KHz. (06 Marks)
- b. Explain log amplifier and derive its output voltage equation. (06 Marks)
- c. Using a 741 Op-Amp with supply voltage of $\pm 12V$, design an inverting Schmitt trigger circuit to have trigger points of $\pm 2V$. (04 Marks)

Module-4

- 7 a. Explain the operation of first order low pass filter with neat circuit diagram, frequency response and design steps. Using a 741 opamp, design a first order active low pass filter to have a cutoff frequency of 2 kHz. (08 Marks)
- b. Draw the circuit of a single stage band pass filter and explain the operation with necessary design equations. (08 Marks)

OR

- 8 a. Draw the standard representation of 78XX series 3-terminal IC regulator and enumerate the characteristics of this type of regulators. Also define the following performance parameters of a voltage regulator. (i) Line regulation (ii) Load regulation (iii) Ripple rejection (08 Marks)
- b. With a neat diagram, explain the operation of low voltage regulator using IC723. Design a voltage regulator circuit using LM723 to obtain $V_0 = 5\text{ V}$ and $I_0 = 2\text{ A}$. (08 Marks)

Module-5

- 9 a. Draw the block diagram of PLL and explain its operation, list the application of PLL. (05 Marks)
- b. Explain the operation of analog to digital conversion using successive approximation technique. (05 Marks)
- c. Design astable multivibration using 555 timer for the frequency of oscillation 2 kHz with 25% duty cycle. Sketch the circuit after design. (06 Marks)

OR

- 10 a. With necessary circuit, explain how PLL can be used as frequency multiplier and divider. (05 Marks)
- b. Explain how 4-bit digital information converted to analog using R-2R ladder network DAC. (05 Marks)
- c. List the specification parameters of ADC and briefly discuss on same (min 4 parameters). (06 Marks)
