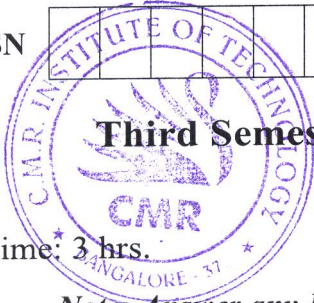


USN

--	--	--	--	--	--	--	--	--	--

15EC34



Third Semester B.E. Degree Examination, Dec.2023/Jan.2024 Network Analysis

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Reduce the network shown in Fig.Q1(a) to a single voltage source in series with a resistance using source shift and source transformations.

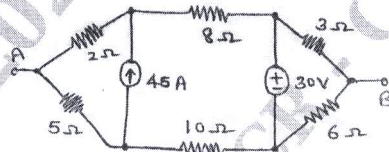


Fig.Q1(a)

(08 Marks)

- b. Using star/delta transformation, determine the resistance between M and N for the network shown in Fig.Q1(b).

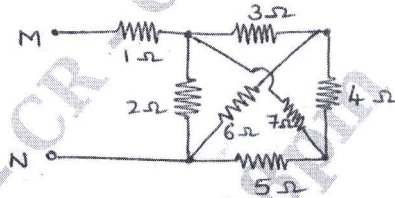


Fig.Q1(b)

(08 Marks)

OR

- 2 a. Find the power delivered by the dependent voltage source in the circuit shown in Fig.Q2(a) by Mesh current method.

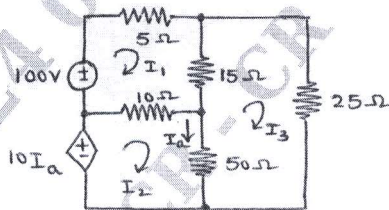


Fig.Q2(a)

(06 Marks)

- b. Define super Mesh and super node.
c. Use the node-voltage method to find the power developed by the 20V source in the circuit shown in Fig.Q2(c).

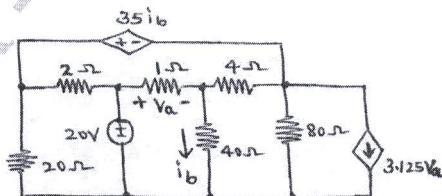


Fig.Q2(c)

(08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-2

- 3 a. Using Millman's theorem, find the current through load resistance R_L for the circuit shown in Fig.Q3(a). (08 Marks)

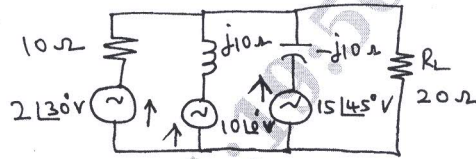


Fig.Q3(a)

- b. State the maximum power transfer theorem and also prove that $P_{max} = \frac{V_{th}^2}{4R_L}$, where V_{th} = thevenins voltage. (08 Marks)

OR

- 4 a. Obtain the Thevenin's equivalent of the circuit shown in Fig.Q4(a). (08 Marks)
 b. Using superposition theorem, find the current in 6Ω resistor in the network shown in Fig.Q4(b).

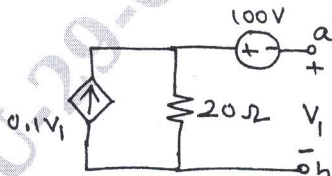


Fig.Q4(a)

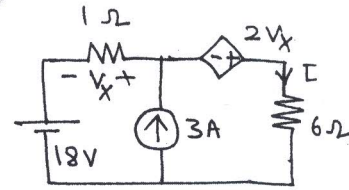


Fig.Q4(b)

(08 Marks)

Module-3

- 5 a. In the network shown in Fig.Q5(a), K is changed from position a to b at $t = 0$. Solve for i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$, if $R = 1000\Omega$, $L = 1H$, $C = 0.1\mu F$ and $V = 100V$. Assume that the capacitor is initially uncharged.

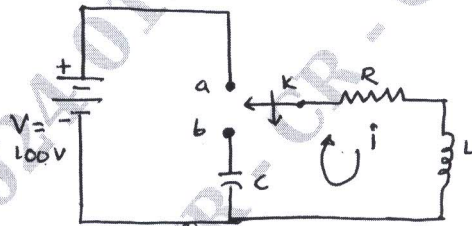


Fig.Q5(a)

CMRIT LIBRARY
BANGALORE - 560 037

(08 Marks)

- b. Determine the response current $i(t)$ in the circuit shown in Fig.Q5(b) using Laplace transform.

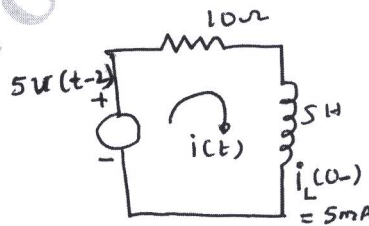


Fig.Q5(b)

(08 Marks)

OR

- 6 a. Synthesis the waveform shown in Fig.Q6(a) and find the Laplace transform of the periodic waveform. (08 Marks)

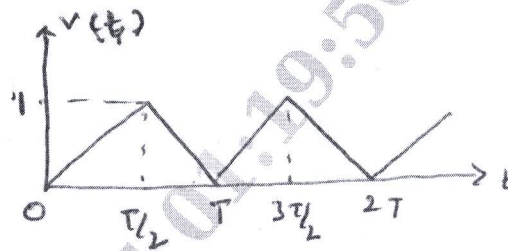


Fig.Q6(a)

- b. Determine v , $\frac{dv}{dt}$ and $\frac{d^2v}{dt^2}$ at $t = 0^+$ when the switch k is opened at $t=0$ in Fig.Q6(b).

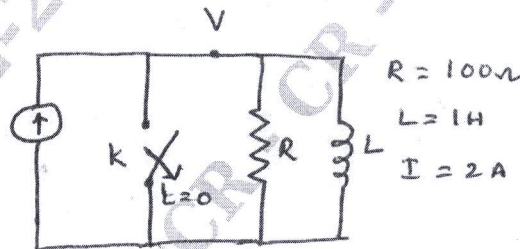


Fig.Q6(b)

(08 Marks)

Module-4

- 7 a. Derive the expressions of half power frequencies W_1 and W_2 and also bandwidth of a series resonance circuit. (09 Marks)
 b. Find the values of L at which the circuit shown in Fig.Q7(b) resonates at a frequency of 500 r/s.

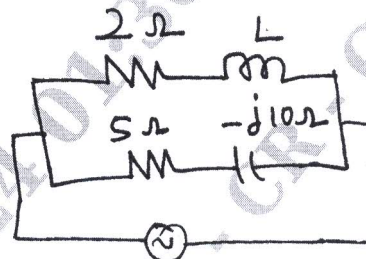


Fig.Q7(b)

(07 Marks)

CMRIT LIBRARY
 BANGALORE - 560 037

OR

- 8 a. Derive the expressions of a resonance frequency and dynamic impedance of a parallel resonance circuit. (09 Marks)
 b. A coil has a $R = 20\Omega$, $L = 80\text{mH}$ and $C = 100\text{pF}$ are connected in series. Determine :
 i) impedance at resonance ii) resonance frequency iii) quality factor iv) circuit current if supply voltage is 50V. (07 Marks)

Module-5

- 9 a. Derive Y parameters and transmission parameters of a circuit in terms of its z-parameters. (08 Marks)
- b. Find the z-parameters for the network shown in Fig.Q9(b).

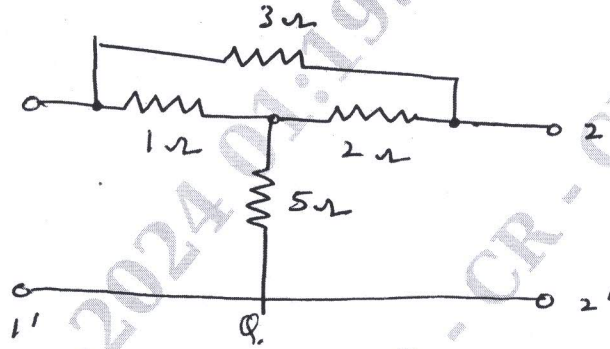


Fig.Q9(b)

(08 Marks)

OR

- 10 a. The z parameters of a two port network are $z_{11} = 20\Omega$, $z_{22} = 30\Omega$, $z_{12} = z_{21} = 10\Omega$. Find Y and ABCD parameters. (08 Marks)
- b. Determine Y parameters of the two port network shown in Fig.Q10(b).

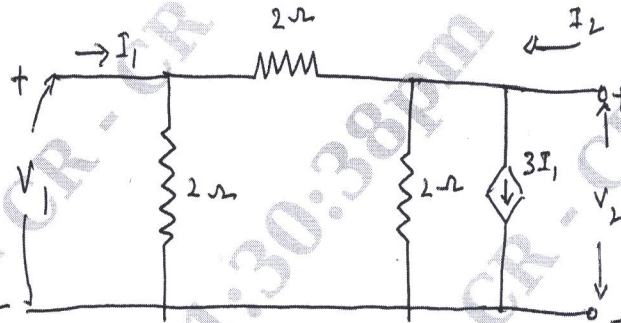


Fig.Q10(b)

CMRIT LIBRARY
BANGALORE - 560 037

(08 Marks)
