





**Third Semester B.E./B.Tech. Degree Examination, Dec.2023/Jan.2024**  
**Network Analysis**

Max. Marks: 100

*Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.  
 2. M : Marks , L: Bloom's level , C: Course outcomes.*


Module - I			M	L	C
Q.1	a.	Explain the classification of electrical networks.	8	L2	CO1
	b.	For the network shown in Fig. Q1(b), find the current through load resistor 'R' using loop analysis.	6	L3	CO1
		Fig. Q1(b)			
	c.	For the network shown in Fig. Q1(c), find the equivalent resistance between the terminals A - B using Star - Delta transformation.	6	L3	CO1
		Fig. Q1(c)			
<b>OR</b>					
Q.2	a.	Derive an expression for the equivalent impedances between the terminals for Delta - Star transformation.	6	L2	CO1
	b.	Use modal analysis to find the value of voltage 'V <sub>x</sub> ' in the circuit shown in Fig. Q2(b), such that the current through (2 + j3)Ω impedance is zero.	7	L3	CO1
		Fig. Q2(b)			
	c.	Determine the current through 12Ω resistor shown in Fig. Q2(c), using Source Shifting / Transformation method.	7	L3	CO1
		Fig. Q2(c)			

Module - 2

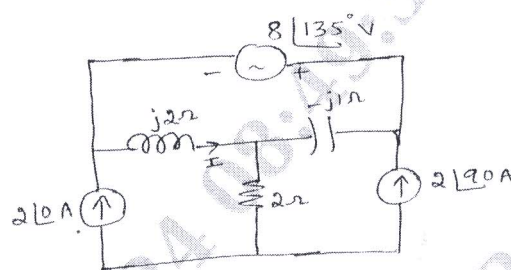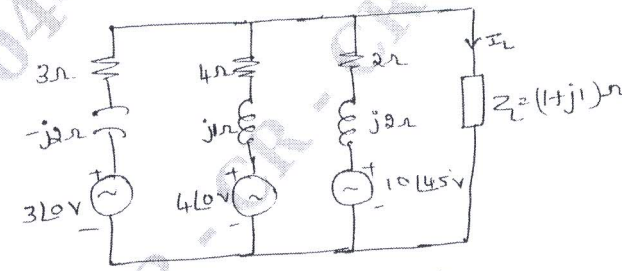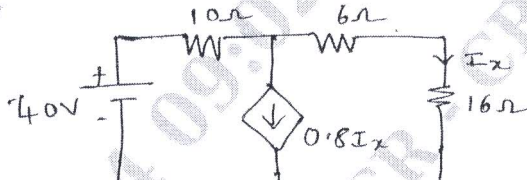
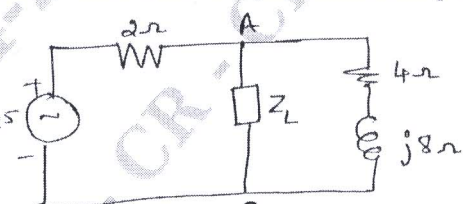
<p>Q.3</p>	<p>a. Using Superposition theorem, obtain the current 'I' for the network shown in Fig. Q3(a).</p>  <p>Fig. Q3(a)</p>	<p>10</p>	<p>L2</p>	<p>CO1</p>
	<p>b. Using Millman's theorem, calculate the current through the load in the circuit shown in Fig. Q3(b).</p>  <p>Fig. Q3(b)</p>	<p>10</p>	<p>L3</p>	<p>CO2</p>
<p>OR</p>				
<p>Q.4</p>	<p>a. State and explain Norton's theorem.</p>	<p>6</p>	<p>L2</p>	<p>CO2</p>
	<p>b. For the network shown in Fig. Q4(b), find the current through 16Ω resistor using Thevenin's theorem.</p>  <p>Fig. Q4(b)</p>	<p>7</p>	<p>L3</p>	<p>CO2</p>
	<p>c. For the network shown in Fig. Q4(c), find the value of <math>Z_L</math> for which maximum power transfer occurs. Also find the maximum power.</p>  <p>Fig. Q4(c)</p>	<p>7</p>	<p>L3</p>	<p>CO2</p>
<p>Module - 3</p>				
<p>Q.5</p>	<p>a. Explain the initial and final conditions in basic elements.</p>	<p>6</p>	<p>L2</p>	<p>CO3</p>

CMRIT LIBRARY  
BANGALORE - 560 037

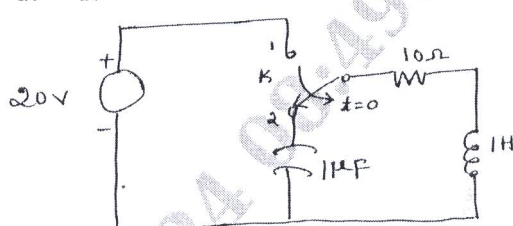


	<p>b. For the circuit shown in Fig. Q5(b), the switch 'K' is changing the position from 1 to 2 at <math>t = 0</math>. Steady state condition has been reached at position 1. Find the value of <math>i</math>, <math>\frac{di}{dt}</math>, <math>\frac{d^2i}{dt^2}</math> at <math>t = 0^+</math>.</p>  <p>Fig. Q5(b)</p>	8	L3	CO3
	<p>c. Obtain an expression for transient response <math>i(t)</math> of a series R – L circuit when excited by DC supply.</p>	6	L2	CO3

OR

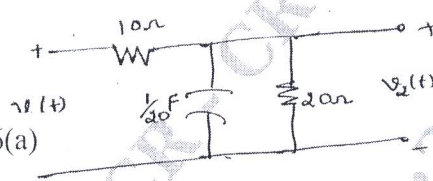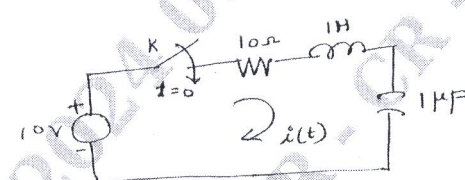
<p>Q.6</p>	<p>a. In the circuit shown in Fig. Q6(a), <math>v_1(t) = e^{-t}</math> for <math>t \geq 0</math> and zero for all <math>t &lt; 0</math>. If the capacitor is initially uncharged, determine the value of <math>v_2(t)</math>, <math>\frac{dv_2(t)}{dt}</math>, <math>\frac{d^2v_2(t)}{dt^2}</math> and <math>\frac{d^3v_2(t)}{dt^3}</math> at <math>t = 0^+</math>.</p>  <p>Fig. Q6(a)</p>	10	L3	CO3
	<p>b. For the circuit shown in Fig. Q6(b), the switch is closed at <math>t = 0</math>. Determine <math>i</math>, <math>\frac{di}{dt}</math>, <math>\frac{d^2i}{dt^2}</math> and <math>\frac{d^3i}{dt^3}</math> at <math>t = 0^+</math>.</p>  <p>Fig. Q6(b)</p>	10	L3	CO3

Module – 4
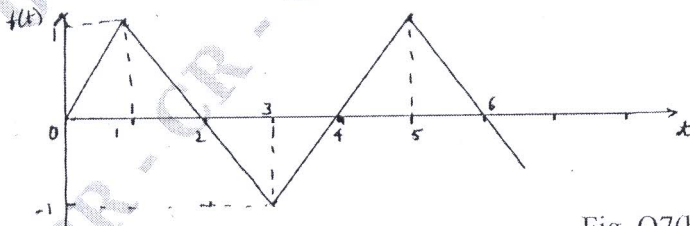
<p>Q.7</p>	<p>a. State and prove Initial Value Theorem.</p>	6	L2	CO3
	<p>b. Find the Laplace Transform of the periodic waveform shown in Fig. Q7(b).</p>  <p>Fig. Q7(b)</p>	8	L3	CO3

	c.	Using Laplace transform, determine the current $i(t)$ in the circuit shown in Fig. Q7(c), when the switch 'S' is closed at $t = 0$ . Assume zero initial conditions.	6	L3	CO3
--	----	--	---	----	-----

Fig. Q7(c)

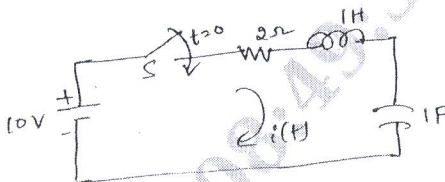


OR

Q.8	a.	State and prove differentiate by 'S' domain property.	6	L2	CO3
-----	----	---	---	----	-----


	b.	In the circuit shown in Fig. Q8(b), the switch is closed at $t = 0$ . Obtain the expression for the current.	6	L3	CO3
--	----	--	---	----	-----

Fig. Q8(b)

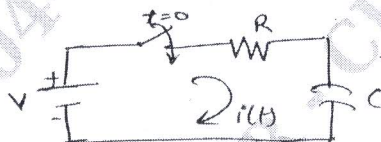

	c.	Obtain the Laplace Transform of the square wave shown in Fig. Q8(c).	8	L3	CO3
--	----	--	---	----	-----

Fig. Q8(c)

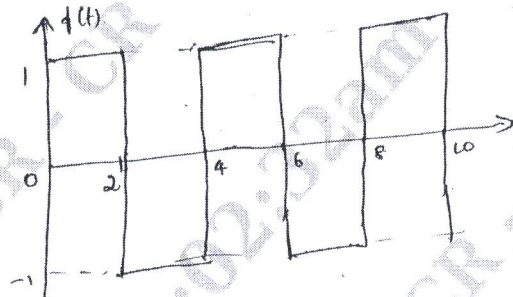


Module - 5

Q.9	a.	What are Impedance and Hybrid parameters? Derive the expression for the same.	8	L2	CO4
-----	----	---	---	----	-----

	b.	Derive an expression for Transmission parameters in terms of Z - parameters.	5	L2	CO4
--	----	--	---	----	-----

	c.	For the circuit shown in Fig. Q9(c), find Y - parameters.	7	L3	CO4
--	----	---	---	----	-----


Fig. Q9(c)

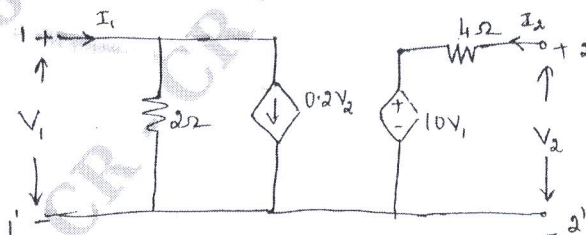

CMRIT LIBRARY  
BANGALORE - 560 037

OR

Q.10	a.	Derive an expression for bandwidth of a series Resonant circuit.	7	L2	CO5
------	----	--	---	----	-----

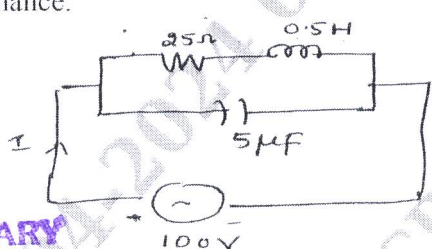b.	A series RLC circuit consists of a resistance of $1\text{ k}\Omega$ and an inductance of $100\text{mH}$ in series with capacitance of $10\text{PF}$ connected across $100\text{V}$ supply. Determine i) Resonant frequency ii) Quality factor iii) Maximum current in the circuit iv) Bandwidth v) Half power frequencies v) Selectivity factor.	7	L3	CO5
c.	<p>For the circuit shown in Fig. Q10(c), find i) Resonant frequency ii) Quality factor iii) Bandwidth iv) Impedance at resonance v) Current at resonance.</p>  <p>Fig. Q10(c)</p>	6	L3	CO5

CMRIT LIBRARY  
BANGALORE - 560 037

\*\*\*\*\*