

CBCS SCHEME

USN

| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

15EC35

Third Semester B.E. Degree Examination, Dec.2023/Jan.2024 Electronic Instrumentation

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- a. Describe different types of errors in measuring instruments. (08 Marks)
b. What is thermocouple? Explain different types of thermocouples. (08 Marks)

OR

- a. Find the voltage reading and % error of each reading obtained with a voltmeter on i) 5V range ii) 10V range iii) 30V range, if the instrument has a $20\text{K}\Omega/\text{V}$ sensitivity and it is connected across R_b of Fig.Q.2(a). (08 Marks)

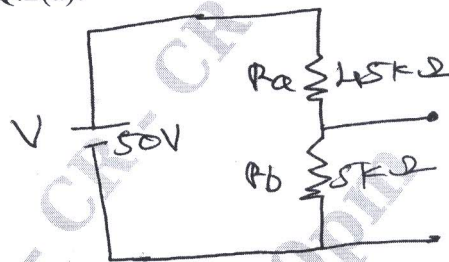


Fig.Q.2(a)

- b. Explain principle operation of true RMS voltmeter. (08 Marks)

Module-2

- a. Explain working of dual slope type DUM for voltage to time conversion. (08 Marks)
b. With diagram, explain the working of digital pH meter. (08 Marks)

OR

- a. Discuss the working of microprocessor based ramp type DVM. (08 Marks)
b. Explain working of digital tachometer with diagram. (08 Marks)

Module-3

- a. Describe basic principle of signal display (Function of Sweep generator). (08 Marks)
b. Explain the principle operation of AF sine and square wave generator. (08 Marks)

OR

- a. With block diagram of oscilloscope explain function of each block. (08 Marks)
b. Explain the working principle of function generator. (08 Marks)

Module-4

- a. Explain the working of phase-sensitive detector. (08 Marks)
b. Explain the operation of capacitance comparison bridge for measurement of unknown capacitance. (08 Marks)

OR

- 8 a. Explain the working of Maxwell's bridge for measurement of quality factor (Q). (08 Marks)
b. Discuss the principle operation of megger with diagram. (08 Marks)

Module-5

- 9 a. List the advantages of electrical transducer. (08 Marks)
b. Explain the working principle of resistance thermometer. (08 Marks)

OR

- 10 a. Explain the construction and working of LUDT with diagram. (08 Marks)
b. Discuss the operation of piezoelectrical transducer. (08 Marks)
