

Sub:	Introduction to Electrical Engineering						Code:	BESCK104B		
Date:	/ /2023	Duration:	90mins	Max Marks:	50	Sem:	1st sem	Branch:	Chemistry cycle	
Answer Any FIVE FULL Questions										
								Marks	OBE	
									CO	RBT
1.a	In a series RLC, circuit $R = 100 \Omega$, $L = 0.15 \text{ H}$, and $C = 25 \mu\text{F}$. If the source voltage and frequency are 220 V and 50 Hz, respectively. Calculate (i) impedance (ii) Power (iii) Power factor (iv) current						4	CO2	L3	
1. b	With the help of phasor diagram, show that the current drawn by the R-C series circuit, leads the applied voltage by an angle ϕ with respect to voltage.						6	CO2	L1	
2	With a neat diagram, explain the constructional details of DC generator.						10	CO3	L2	
3.a	A long shunt compound generator has an armature, series field and shunt field resistances of 0.04Ω , 0.03Ω and 200Ω respectively. It supplies a load current of 180 A at 400 V. Calculate the Generated e.m.f. Assume the contact drop per brush is 1 V.						6	CO3	L3	
3.b	Explain the function of following parts of DC machine. (i) Commutator (ii) Pole shoe						4	CO3	L2	
4.a	With usual notations derive an emf equation of D.C. generator.						4	CO3	L3	

P.T.O

4.b	A 4 pole short shunt compound generator has armature, shunt field and series field resistances of 0.4 ohms, 160 ohms and 0.2 ohms respectively. The armature is lap connected with 440 v conductors and is driven at 600rpm. Calculate the flux per pole when the machine is delivering 120 Amperes at 400v.						6	CO3	L3
5	Discuss the classification of different types of DC generators. What is the relation between induced emf and terminal voltage?						10	CO3	L2
6.a	Three coils having resistance of 10Ω and inductance of 0.02H are connected in star across 440V, 50Hz three phase supply. Calculate the line current, power factor and total power consumed.						6	CO3	L2
6.b	Differentiate between star and delta connection.						4	CO3	L1
7	What is phase sequence? Explain how 3-phase waveform is generated and also what are the limitations of 1-phase supply? Discuss about advantages of 3-phase supply.						10	CO2	L2

CCI

CI

HOD

BEE_IAT II_ Solution

1.a In a series RLC, circuit $R = 100 \Omega$, $L = 0.15 \text{ H}$, and $C = 25 \mu\text{F}$. If the source voltage and frequency are 220 V and 50 Hz , respectively. Calculate (i) impedance (ii) Power (iii) Power factor (iv) current

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Given $R = 100 \Omega$

$$C = 25 \mu\text{F} \quad X_C = \frac{1}{\omega C} = \frac{1}{25 \times 10^{-6} \times 2\pi \times 50} = 127.39 \Omega$$

$$L = 0.15 \text{ H} \quad X_L = \omega L = 0.15 \times 2\pi \times 50 = 47.1 \Omega$$

$$Z = \sqrt{100^2 + (X_L - X_C)^2} = 128.24 \angle -38.76^\circ \Omega$$



$$I = \frac{V}{Z} = \frac{220}{128.24 \angle -38.76^\circ} = 1.72 \angle 38.76^\circ \text{ A}$$

$$P = VI \cos \phi$$

$$\text{Pf} = \cos \phi = \frac{R}{Z} = \frac{100}{128.24 \angle -38.76^\circ} = 0.78 \angle 38.76^\circ$$

leading

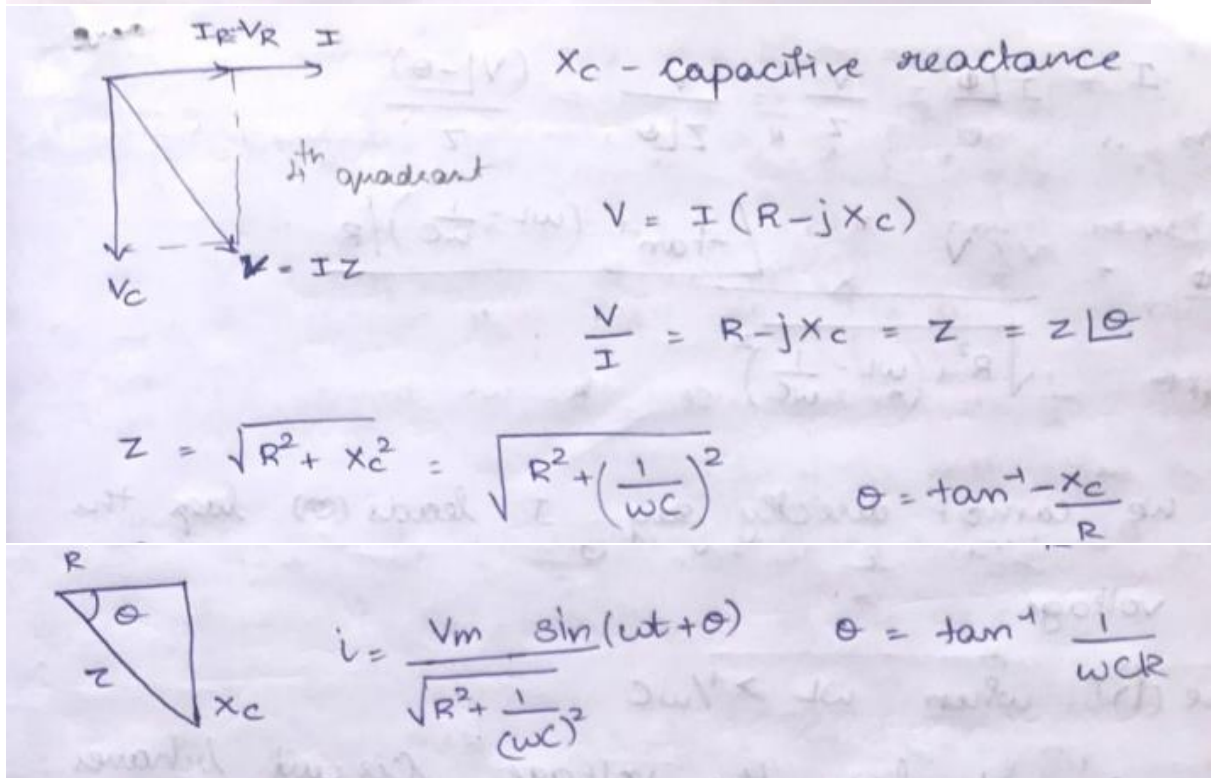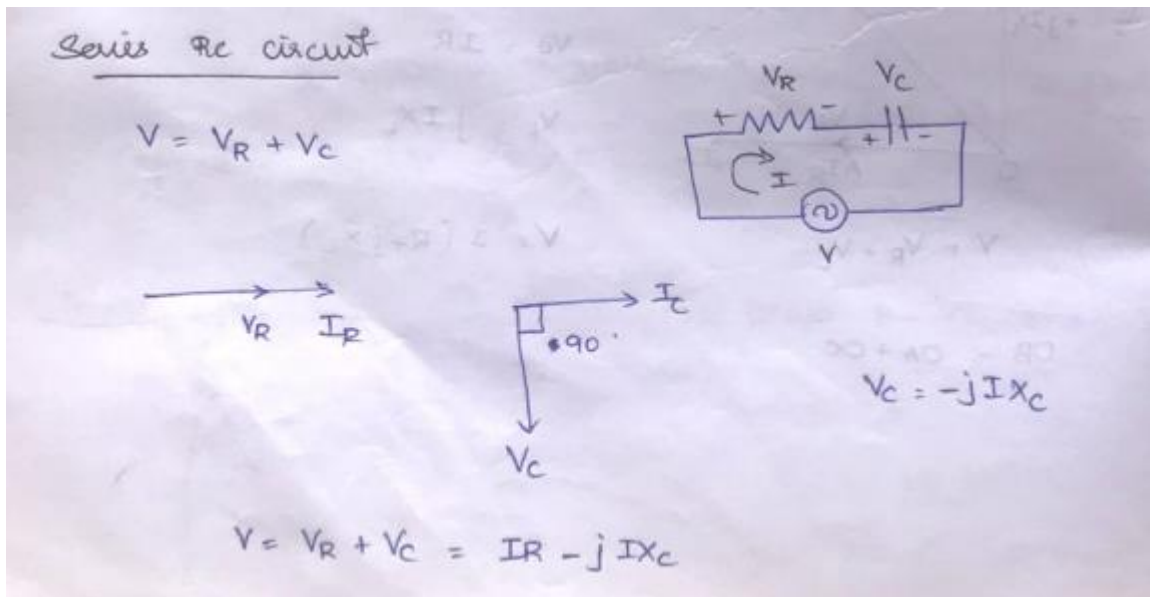1.b With the help of phasor diagram, show that the current drawn by the R-C series circuit, leads the applied voltage by an angle ϕ with respect to voltage.




Q.2 With a neat diagram, explain the constructional details of DC generator.
(Explanation of each part-2 marks)

Main components

1. Field system
2. Armature core
3. Armature winding
4. Commutator
5. Brushes

6. Shaft & Bearings

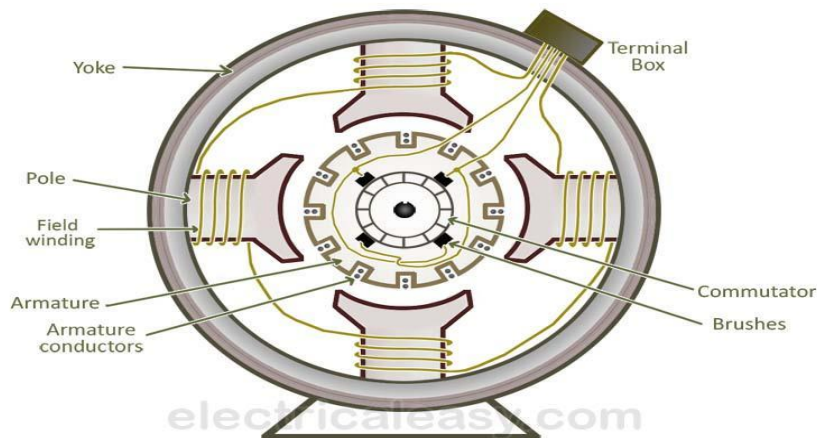

3.a A long shunt compound generator has an armature, series field and shunt field resistances of 0.04Ω , 0.03Ω and 200Ω respectively. It supplies a load current of 180 A at 400 V .

Calculate the Generated e.m.f. Assume the contact drop per brush is 1 V .

drop/brush = 1 V . $V_b = 2 \text{ V}$ $I_a = I_{sh} + I_L$ $I_a = 182 \text{ A}$

$$E_g = V_b + I_a R_a + I_a R_{se} + V_{brush}$$

$$E_g = 400 + I_a(0.04) + I_a(0.03) + 2$$

$$E_g = 400 + 182(0.07) + 2$$

$$E_g = 414.74$$

$I_{sh} = \frac{400}{200} = 2 \text{ A}$ $I_{sh} = \frac{400}{200} = 2 \text{ A}$

3.b Explain the function of following parts of DC machine.(i) Commutator (ii) Pole shoe

Commutator

- The function of the commutator is to convert alternating current induced in the armature to direct current
- The commutator is made up of copper segments insulated from each other by mica sheets

Pole shoes

- It supports the field winding
- It spreads out the flux uniformly in the air gap
- It reduces the reluctance of the magnetic path

4.a With usual notations derive an emf equation of D.C. generator.

Emf equation of generator

Notations for equations

ϕ = flux/pole in Wb

Z = total number of armature conductors

P = number of poles

A = number of parallel paths = 2 ... for wave winding

= P ... for lap winding

N = speed of armature in r.p.m

E_g = e.m.f of the generator = e.m.f /parallel path

Derivation of equation

Flux cut by one conductor in one revolution of the armature,

$$d\Phi = P\phi \text{ webers}$$

Time taken to complete one revolution,

$$dt = 60/N \text{ second}$$

e.m.f generated/conductor = $d\Phi/dt = p\phi N/60$ volts

Emf of generated,


$$E_g = \text{emf per parallel}$$

= (emf/conductor) * no. of conductor in series per parallel path

$$= P\phi NZ/60A$$

therefore $E_g = P\phi NZ/60A$

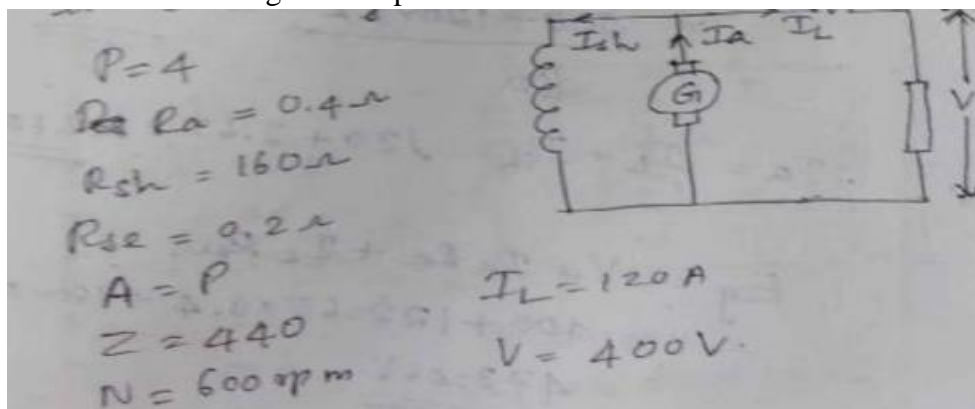4.b A 4 pole short shunt compound generator has armature, shunt field and series field resistances of 0.4 ohms, 160 ohms and 0.2 ohms respectively. The armature is lap connected with 440 conductors and is driven at 600rpm. Calculate the flux per pole when the machine is delivering 120 Amperes at 400v.



$$E_g = \frac{\phi Z N}{60} \left(\frac{P}{A} \right)$$

$$V = E_g - I_a R_a - I_L [R_{se}]$$

$$= E_g - I_a R_a - I_L R_{se}$$

$$= E$$

$$\therefore E_g = V + I_a R_a + I_L R_{se}$$

$$I_a = I_L + I_{sh}$$

$$I_{sh} = \frac{V + I_L R_{se}}{R_{sh}}$$

$$= \frac{400 + 120 \times 0.2}{160} = \underline{\underline{2.65 A}}$$

$$\therefore I_a = I_L + I_{sh} = 120 + 2.65 = \underline{\underline{122.65 A}}$$

$$\begin{aligned} \therefore E_g &= V + I_a R_a + I_L R_{se} \\ &= 400 + 122.65 \times 0.4 + 120 \times 0.2 \\ &= \underline{\underline{473.06 V}} \end{aligned}$$

5. Discuss the classification of different types of DC generators. What is the relation between induced emf and terminal voltage?

7(b) Generally **DC Generators** are classified according to the ways of excitation of their fields.

There are three methods of excitation. Field coils excited by permanent magnets – **Permanent magnet DC generators.**

- Field coils excited by some external source – **Separately excited DC generators.**
- Field coils excited by the generator itself – **Self excited DC generators.**

Separately Excited DC Generators

- These are the generators whose field magnets are energized by some external DC source such as battery.


A circuit diagram of separately excited DC generator is shown in figure.

I_a = Armature current

I_L = Load current

V = Terminal voltage

E_g = Generated emf

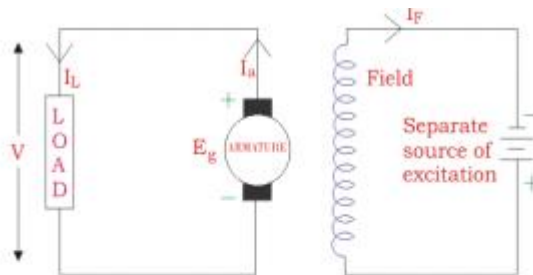

Separately Excited DC Generator

Voltage drop in the armature = $I_a R_a$

Let $I_a = I_L = I$

Voltage across the load, $V = I R_a$

Power generated, $P_g = E_g I$

Power delivered to the external load,

$$P_L = V I$$

According to the position of the field coils the self – excited DC Generators may be classified as :

- Series wound generators
- Shunt wound generators
- Compound wound generators

Series Wound Generator

Let R_{sc} = Series winding resistance

I_{sc} = Current flowing through the series field


R_a = Armature resistance

I_a = Armature current

I_L = Load current

V = Terminal voltage

E_g = Generated emf

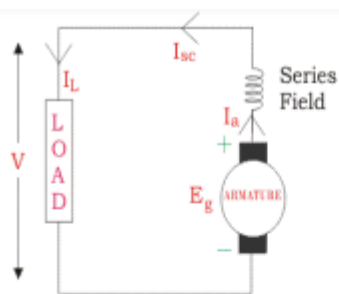

Series Wound Generator

- Here $I_a = I_{sc} = I_L = I$
- Voltage across the load, $V = E_g - I_a(R_a + R_{sc}) -$
Brush drop
- Power generated, $P_g = E_g I_a$
- Power delivered, $P_L = V I$

Shunt wound Generator

Let, R_{sh} = Shunt winding resistance

I_{sh} = Current flowing through the shunt field


R_a = Armature resistance

I_a = Armature current

I_L = Load current

V = Terminal voltage

E_g = Generated emf

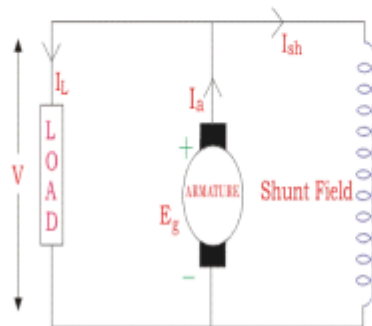

Shunt Wound Generator

Here $I_a = I_{sh} + I_L$

$I_{sh} = V / R_{sh}$

Voltage across the load,

$V = E_g - I_a R_a - \text{Brush drop}$


Power generated, $P_g = E_g I_a$

Power delivered to the load, $P_L = V I_L$

Compound Wound Generators

Short Shunt Compound Wound DC Generators

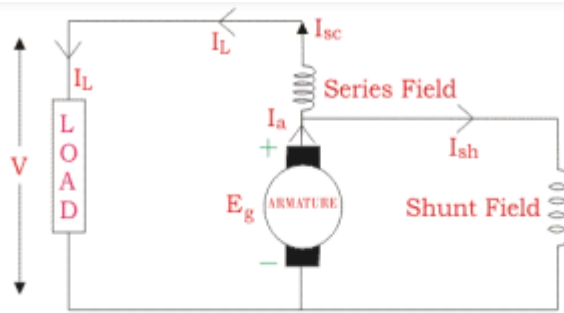These are the generators in which only shunt field winding is in parallel with the armature winding



Short Shunt Compound Wound Generator

$$I_{sc} = I_L$$

$$I_{sh} = (V + I_{sc} R_{sc}) / R_{sh}$$

$$I_a = I_{sh} + I_L$$


$$V = E_g - I_a R_a - I_{sc} R_{sc} - \text{Brush drop}$$

$$P_g = E_g I_a$$

$$P_L = V I_L$$

Long Shunt Compound Wound DC Generator

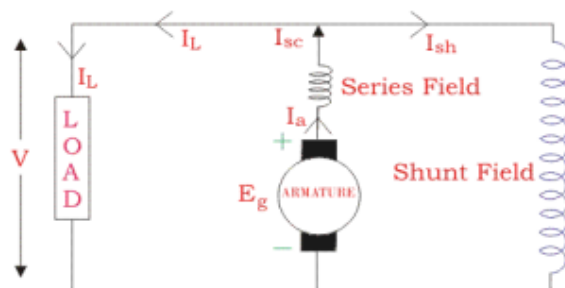The generators in which shunt field winding is in parallel with both series field and armature winding as shown in figure.



Long Shunt Compound Wound Generator

$$I_{sh} = V / R_{sh}$$

$$I_{sc} = I_L + I_{sh}$$

$$V = E_g - I_a R_a - I_{sc} R_{sc} - \text{Brush drop}$$

$$P_g = E_g I_a$$

$$P_L = V I_L$$

6.a Three coils having resistance of 10Ω and inductance of 0.02H are connected in star across 440V , 50Hz three phase supply. Calculate the line current, power factor and total power consumed.

Given

$$R = 10 \Omega, \quad L = 0.02 \text{ H}, \quad Y \text{ connected}$$

$$V_L = 440 \text{ V} \quad f = 50 \text{ Hz}, \quad 3\phi$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{440}{\sqrt{3}} = 254.03 \text{ V}$$

$$Z_{ph} = R + jX_L = 10 + j(0.02 \times 2\pi \times 50)$$

$$= 11.81 \angle 32.13^\circ \Omega$$

$$I_{ph} = V_{ph} / Z_{ph} = \frac{254.03}{11.81 \angle 32.13^\circ} = 21.51 \angle -32.13^\circ \text{ A}$$

$$= 21.51 \angle -32.13^\circ \text{ A}$$

In Y connected system $I_L = I_{ph}$

$$P = \sqrt{3} V_L I_L \cos\phi = \sqrt{3} \times 440 \times 21.51 \cos(32.13^\circ)$$

$$= 13.882 \text{ kW}$$

6.b Differentiate between star and delta connection.

Star (Y)

- $V_L = \sqrt{3} V_{ph}$ $I_L = I_{ph}$
- Neutral wire available
- 3 ϕ 4 wire s/m possible
- Both domestic & industrial loads can be handled
- Protection through Neutral wire

Δ - Connection

- $I_L = \sqrt{3} I_{ph}$ $V_L = V_{ph}$
- Neutral wire not available
- 3 ϕ 4 wire s/m - not possible.
- Only Industrial load
- Neutral wire absent, Protective devices cannot be used.

7. What is phase sequence? Explain how 3-phase waveform is generated and also what are the limitations of 1-phase supply? Discuss about advantages of 3-phase supply.

Phase rotation, or phase sequence, is the order in which the voltage waveforms of a polyphase AC source reach their respective peaks. For a three-phase system, there are only two possible phase sequences: 1-2-3 and 3-2-1, corresponding to the two possible directions of alternator rotation.

→ 1- ϕ AC voltage generated by using a single turn alternator.

→ No. of turns connected in series to form one winding armature

→ Poly phase systems - Armature winding is divided into No. of Phase required.

2 windings - 2 ϕ 3 windings - 3 ϕ

→ No. of independent voltage is the same as number of Phases of armature winding.

→ Various phases are arranged such a way that frequency & magnitude remain same but will have phase difference between them.


$$\text{Phase difference} = \frac{360}{\text{No. of phases.}}$$

for 2 ϕ s/m
 $\frac{360}{2} = 180^\circ$

for 3 ϕ
 $\frac{360}{3} = 120^\circ$

Generation

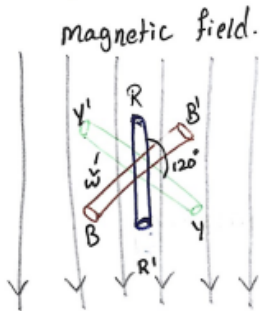In general, the 3 ϕ system is named as $\overset{\text{Yellow}}{R} \overset{\text{Red}}{Y} \overset{\text{Blue}}{B}$.
The fig. below illustrates principle of generation of 3 ϕ Voltage s/m.



The 3 coils wound on rotor has a displacement of 120° from one another.

The rotor is rotated ^{anti} clockwise in a uniform magnetic field with a uniform angular speed ω .

A sinusoidal emf is generated in each coil.

Because of the space displacement of the coils, after $\frac{1}{3}$ cycle of rotation coil YY' occupies the same position as RR' coil did.

\therefore The emf of coil YY' lags behind the emf of coil RR' by 120° . Similarly BB' lags YY' by 120° hence RR' by 240° .

\therefore If all three coils are \downarrow same amplitude and frequency but time displaced by 120° identical then we get emf. of

For generating emf in a coil we need relative motion between coil & magnetic field.

So we can either rotate coil keep field constant

or

rotate field and keep coil constant

In either way we can generate emf.

Generally coils are wound on stator with 120° phase displacement and field on rotor.

The emfs generated are


The emfs generated are

$$e_R = E_m \sin \omega t$$

$$e_Y = E_m \sin (\omega t - 120^\circ)$$

$$e_B = E_m \sin (\omega t - 240^\circ) \text{ or } E_m \sin (\omega t + 120^\circ)$$

$$e_R + e_Y + e_B = 0$$

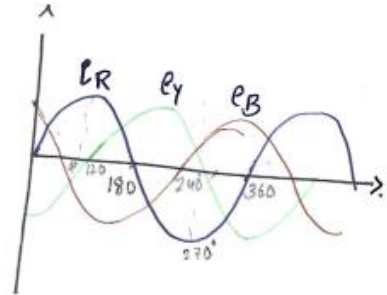

Depending on the interconnection of 3 phase winding:

3 ϕ system is divided in two category

1. Star
2. Delta.

Limitation :-

The biggest disadvantage of 3- ϕ system is that it cannot handle the overload; it might damage the equipment.

chances of repairing the equipment is higher. BCOZ cost of individual components are expensive.

Advantages of 3-phase system.

1. Three phase transmission lines require much less conductor material.
2. Phasor sum of currents in all phases is zero. So, saving of material as we need not provide neutral conductor or if we provide also it is single neutral with conductor of smaller size.
3. For a given frame size, a 3-phase machine gives a higher output than a single-phase machine.
4. Power in single phase system develops pulsating torque. While 3 ϕ is almost constant.
5. The 3 ϕ supply system can supply both domestic and commercial load.
6. Voltage regulation is better in 3 ϕ than 1 ϕ system.
7. Output of 3 ϕ machine is higher compared to 1 ϕ .
8. 3 ϕ supply produces rotating magnetic field this makes IM self starting.
9. 3 ϕ system is more efficient.

C. . .