

Department of ISE
Internal Assessment Test 1 – Dec. 2023
Evaluation scheme

Sub:	Digital Design and Computer Organization				Sub Code:	BCS302	Branch:	ISE	
Date:	18.12.2023	Duration:	90 min's	Max Marks:	50	Sem/Sec	03/ A,B,C		
<u>Answer any FIVE FULL QUESTIONS</u>							MARKS	CO	RB T
1(a)	Demonstrate the validity of the following identities by means of truth tables (i) $x + yz = (x + y)(x + z)$ Truth Table (2) (ii) $x(y + z) = xy + xz$ Truth Table (2)					4	CO1	L3	
1(b)	Solve the following Boolean expressions to a minimum number of literals. Also draw logic diagrams of the circuits that implement the original and simplified expressions (i) $(x + y)(x + y')$ Simplification (2) Logic Diagram (1) (ii) $xyz + x'y + xyz'$ Simplification (2) Logic Diagram (1)					6	CO1	L3	
2	Explain the Boolean theorems and postulates in detail 10 properties with truth table (each property carries 1 mark)					10	CO1	L2	
3(a)	Simplify the following Boolean expressions, using four-variable maps: $A'B'C'D + AB'D + A'BC' + ABCD + AB'C$ K-map (4) Simplified expression (1)					5	CO1	L3	
3(b)	Solve the following Boolean function F, together with the don't-care conditions d, and then express the simplified function in SOP and POS form. $F(A,B,C,D) = \Sigma(0, 6, 8, 13, 14)$ $d(A,B,C,D) = \Sigma(2, 4, 10)$ K-map (3) Simplified SOP (1) Simplified POS (1)					5	CO1	L3	
4(a)	Model the multiple-level NOR circuit for the following expression: $CD(B + C)A + (BC' + DE')$ Logic Diagram with basic gates (2) Logic Diagram with only NOR universal gate(3)					5	CO1	L3	
4(b)	Present the multiple-level NAND circuit for the following expression: $w(x + y + z) + xyz$ Logic Diagram with basic gates (2) Logic Diagram with only NAND universal gate(3)					5	CO1	L3	
5	Design a 3-bit subtractor combinational circuit using 2 bit subtractors Truth Table of Full subtractor (3)					10	CO2	L3	

	K-Map for Difference and Borrow (2) Simplified expression for Difference and Borrow (2) Logic Diagram using Half subtractor(3)			
6(a)	Discuss the combinational circuit that decodes 3 input variables? Truth Table of 3:8 decoder (2) K-Map for 3:8 decoder (2) Logic Diagram (1)	5	CO2	L2
6(b)	Discuss the combinational circuit that encodes 4 input variables? Truth Table of 4:2 encoder (2) K-Map for 4:2 encoder (2) Logic Diagram (1)	5	CO2	L2

CCI

CI

HOD

Department of ISE
Internal Assessment Test 1 – Dec. 2023
IAT-1 solution

1(a) Demonstrate the validity of the following identities by means of truth tables

(i) $x + yz = (x + y)(x + z)$

$x y z$	$x + yz$	$(x + y)$	$(x + z)$	$(x + y)(x + z)$
0 0 0	0	0	0	0
0 0 1	0	0	1	0
0 1 0	0	1	0	0
0 1 1	1	1	1	1
1 0 0	1	1	1	1
1 0 1	1	1	1	1
1 1 0	1	1	1	1
1 1 1	1	1	1	1


(ii) $x(y + z) = xy + xz$

$x y z$	$x(y + z)$	xy	xz	$xy + xz$
0 0 0	0	0	0	0
0 0 1	0	0	0	0
0 1 0	0	0	0	0
0 1 1	0	0	0	0
1 0 0	0	0	0	0
1 0 1	1	0	1	1
1 1 0	1	1	0	1
1 1 1	1	1	1	1

1(b) Solve the following Boolean expressions to a minimum number of literals. Also draw logic diagrams of the circuits that implement the original and simplified expressions

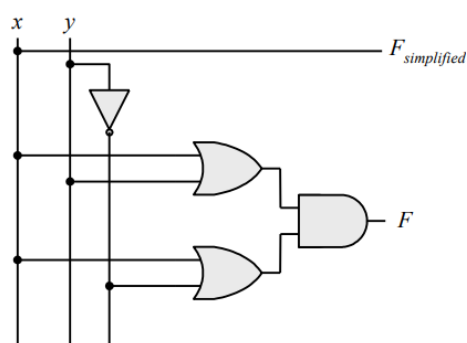
(i) $(x + y)(x + y')$

$$\begin{aligned}
 &= x + yy' \\
 &= x(x + y') + y(x + y') \\
 &= xx + xy' + xy + yy' \\
 &= x
 \end{aligned}$$



Dr.Ciyamala Kushbu S, AP/ISE
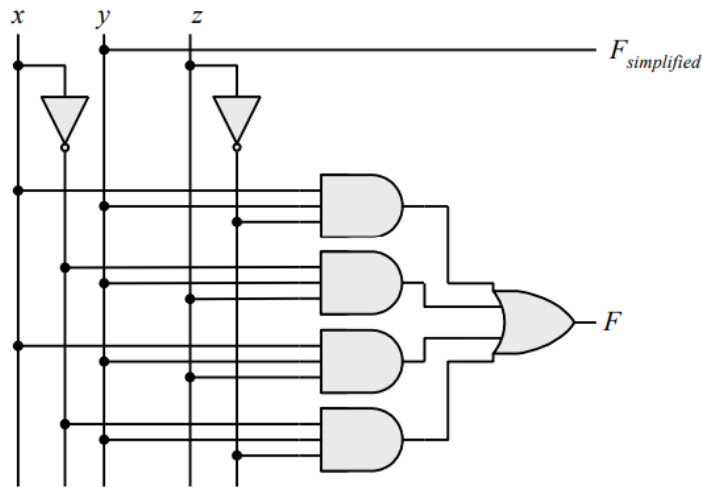
$$\begin{aligned}
 & \text{(ii)} \quad xyz + x'y + xyz' \\
 &= xy(z + z') + x'y \\
 &= xy + x'y \\
 &= y
 \end{aligned}$$




2 Explain the Boolean theorems and postulates in detail

S.No	Laws Names	AND property	OR Property																		
1	Identity Law	$A \cdot 1 = A$ <table border="1"> <tr><td>A</td><td>1</td><td>A · 1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> </table>	A	1	A · 1	1	1	1	0	1	0	$A + 0 = A$ <table border="1"> <tr><td>A</td><td>0</td><td>A + 0</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> </table>	A	0	A + 0	1	0	1	0	0	0
A	1	A · 1																			
1	1	1																			
0	1	0																			
A	0	A + 0																			
1	0	1																			
0	0	0																			
2	Zero And One Law	$A \cdot 0 = 0$ <table border="1"> <tr><td>A</td><td>0</td><td>A · 0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> </table>	A	0	A · 0	1	0	0	0	0	0	$A + 1 = 1$ <table border="1"> <tr><td>A</td><td>1</td><td>A + 1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> </table>	A	1	A + 1	1	1	1	0	1	1
A	0	A · 0																			
1	0	0																			
0	0	0																			
A	1	A + 1																			
1	1	1																			
0	1	1																			
3	Inverse Law	$A \cdot A' = 0$ <table border="1"> <tr><td>A</td><td>A'</td><td>A · A'</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> </table>	A	A'	A · A'	1	0	0	0	1	0	$A + A' = 1$ <table border="1"> <tr><td>A</td><td>A'</td><td>A + A'</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> </table>	A	A'	A + A'	1	0	1	0	1	1
A	A'	A · A'																			
1	0	0																			
0	1	0																			
A	A'	A + A'																			
1	0	1																			
0	1	1																			
4	Idempotent Law	$A \cdot A = A$ <table border="1"> <tr><td>A</td><td>A</td><td>A · A</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> </table>	A	A	A · A	1	1	1	0	0	0	$A + A = A$ <table border="1"> <tr><td>A</td><td>A</td><td>A + A</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> </table>	A	A	A + A	1	1	1	0	0	0
A	A	A · A																			
1	1	1																			
0	0	0																			
A	A	A + A																			
1	1	1																			
0	0	0																			

5	Commutative Law	$A \cdot B = B \cdot A$ <table border="1" data-bbox="496 143 767 304"> <thead> <tr> <th>A</th> <th>B</th> <th>A · B</th> <th>B · A</th> </tr> </thead> <tbody> <tr><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>0</td><td>0</td></tr> </tbody> </table>	A	B	A · B	B · A	1	1	1	1	1	0	0	0	0	1	0	0	0	0	0	0	$A + B = B + A$ <table border="1" data-bbox="992 143 1289 304"> <thead> <tr> <th>A</th> <th>B</th> <th>A + B</th> <th>B + A</th> </tr> </thead> <tbody> <tr><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>0</td><td>0</td></tr> </tbody> </table>	A	B	A + B	B + A	1	1	1	1	1	0	1	1	0	1	1	1	0	0	0	0																																																																				
A	B	A · B	B · A																																																																																																												
1	1	1	1																																																																																																												
1	0	0	0																																																																																																												
0	1	0	0																																																																																																												
0	0	0	0																																																																																																												
A	B	A + B	B + A																																																																																																												
1	1	1	1																																																																																																												
1	0	1	1																																																																																																												
0	1	1	1																																																																																																												
0	0	0	0																																																																																																												
6	Associative Law	$(A \cdot B) \cdot C = A \cdot (B \cdot C)$ <table border="1" data-bbox="448 387 839 640"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> <th>(A · B) · C</th> <th>A · (B · C)</th> </tr> </thead> <tbody> <tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> </tbody> </table>	A	B	C	(A · B) · C	A · (B · C)	1	1	1	1	1	1	1	0	0	0	1	0	1	0	0	1	0	0	0	0	0	1	1	0	0	0	1	0	0	0	0	0	1	0	0	0	0	0	0	0	$(A + B) + C = A + (B + C)$ <table border="1" data-bbox="927 387 1385 640"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> <th>(A + B) + C</th> <th>A + (B + C)</th> </tr> </thead> <tbody> <tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> </tbody> </table>	A	B	C	(A + B) + C	A + (B + C)	1	1	1	1	1	1	1	0	1	1	1	0	1	1	1	1	0	0	1	1	0	1	1	1	1	0	1	0	1	1	0	0	1	1	1	0	0	0	0	0																		
A	B	C	(A · B) · C	A · (B · C)																																																																																																											
1	1	1	1	1																																																																																																											
1	1	0	0	0																																																																																																											
1	0	1	0	0																																																																																																											
1	0	0	0	0																																																																																																											
0	1	1	0	0																																																																																																											
0	1	0	0	0																																																																																																											
0	0	1	0	0																																																																																																											
0	0	0	0	0																																																																																																											
A	B	C	(A + B) + C	A + (B + C)																																																																																																											
1	1	1	1	1																																																																																																											
1	1	0	1	1																																																																																																											
1	0	1	1	1																																																																																																											
1	0	0	1	1																																																																																																											
0	1	1	1	1																																																																																																											
0	1	0	1	1																																																																																																											
0	0	1	1	1																																																																																																											
0	0	0	0	0																																																																																																											
7	Absorption Law	$A(A + B) = A$ <table border="1" data-bbox="496 712 831 864"> <thead> <tr> <th>A</th> <th>B</th> <th>A + B</th> <th>A · (A + B)</th> </tr> </thead> <tbody> <tr><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>0</td><td>0</td></tr> </tbody> </table>	A	B	A + B	A · (A + B)	1	1	1	1	1	0	1	1	0	1	1	0	0	0	0	0	$A + A \cdot B = A$ <table border="1" data-bbox="943 712 1294 864"> <thead> <tr> <th>A</th> <th>B</th> <th>A · B</th> <th>A + (A · B)</th> </tr> </thead> <tbody> <tr><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>0</td><td>0</td></tr> </tbody> </table>	A	B	A · B	A + (A · B)	1	1	1	1	1	0	0	1	0	1	0	0	0	0	0	0																																																																				
A	B	A + B	A · (A + B)																																																																																																												
1	1	1	1																																																																																																												
1	0	1	1																																																																																																												
0	1	1	0																																																																																																												
0	0	0	0																																																																																																												
A	B	A · B	A + (A · B)																																																																																																												
1	1	1	1																																																																																																												
1	0	0	1																																																																																																												
0	1	0	0																																																																																																												
0	0	0	0																																																																																																												
8	Distribution Law	$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$ <table border="1" data-bbox="448 958 906 1167"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> <th>B + C</th> <th>A · (B + C)</th> <th>(A · B) + (A · C)</th> </tr> </thead> <tbody> <tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> </tbody> </table>	A	B	C	B + C	A · (B + C)	(A · B) + (A · C)	1	1	1	1	1	1	1	1	0	1	1	1	1	0	1	1	1	1	1	0	0	0	0	0	0	1	1	1	0	0	0	1	0	1	0	0	0	0	1	1	0	0	0	0	0	0	0	0	$A + (B \cdot C) = (A + B) \cdot (A + C)$ <table border="1" data-bbox="938 981 1353 1167"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> <th>B · C</th> <th>A + (B · C)</th> <th>(A + B) · (A + C)</th> </tr> </thead> <tbody> <tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> </tbody> </table>	A	B	C	B · C	A + (B · C)	(A + B) · (A + C)	1	1	1	1	1	1	1	1	0	0	1	1	1	0	1	0	1	1	1	0	0	0	1	1	0	1	1	1	1	1	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
A	B	C	B + C	A · (B + C)	(A · B) + (A · C)																																																																																																										
1	1	1	1	1	1																																																																																																										
1	1	0	1	1	1																																																																																																										
1	0	1	1	1	1																																																																																																										
1	0	0	0	0	0																																																																																																										
0	1	1	1	0	0																																																																																																										
0	1	0	1	0	0																																																																																																										
0	0	1	1	0	0																																																																																																										
0	0	0	0	0	0																																																																																																										
A	B	C	B · C	A + (B · C)	(A + B) · (A + C)																																																																																																										
1	1	1	1	1	1																																																																																																										
1	1	0	0	1	1																																																																																																										
1	0	1	0	1	1																																																																																																										
1	0	0	0	1	1																																																																																																										
0	1	1	1	1	1																																																																																																										
0	1	0	0	0	0																																																																																																										
0	0	1	0	0	0																																																																																																										
0	0	0	0	0	0																																																																																																										
9	De Morgan's Law	$(A \cdot B)' = A' + B'$ <table border="1" data-bbox="432 1350 895 1491"> <thead> <tr> <th>A</th> <th>B</th> <th>A · B</th> <th>(A · B)'</th> <th>A'</th> <th>B'</th> <th>A' + B'</th> </tr> </thead> <tbody> <tr><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	A · B	(A · B)'	A'	B'	A' + B'	1	1	1	0	0	0	0	1	0	0	1	0	1	1	0	1	0	1	1	0	1	0	0	0	1	1	1	1	$(A + B)' = A' \cdot B'$ <table border="1" data-bbox="938 1350 1441 1491"> <thead> <tr> <th>A</th> <th>B</th> <th>A + B</th> <th>(A + B)'</th> <th>A'</th> <th>B'</th> <th>A' · B'</th> </tr> </thead> <tbody> <tr><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	A + B	(A + B)'	A'	B'	A' · B'	1	1	1	0	0	0	0	1	0	1	0	0	1	0	0	1	1	0	1	0	0	0	0	0	1	1	1	1																																						
A	B	A · B	(A · B)'	A'	B'	A' + B'																																																																																																									
1	1	1	0	0	0	0																																																																																																									
1	0	0	1	0	1	1																																																																																																									
0	1	0	1	1	0	1																																																																																																									
0	0	0	1	1	1	1																																																																																																									
A	B	A + B	(A + B)'	A'	B'	A' · B'																																																																																																									
1	1	1	0	0	0	0																																																																																																									
1	0	1	0	0	1	0																																																																																																									
0	1	1	0	1	0	0																																																																																																									
0	0	0	1	1	1	1																																																																																																									
10	Double Complement Law	$(A')' = A$ <table border="1" data-bbox="759 1648 1026 1787"> <thead> <tr> <th>A</th> <th>A'</th> <th>(A')'</th> </tr> </thead> <tbody> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> </tbody> </table>		A	A'	(A')'	1	0	1	0	1	0																																																																																																			
A	A'	(A')'																																																																																																													
1	0	1																																																																																																													
0	1	0																																																																																																													

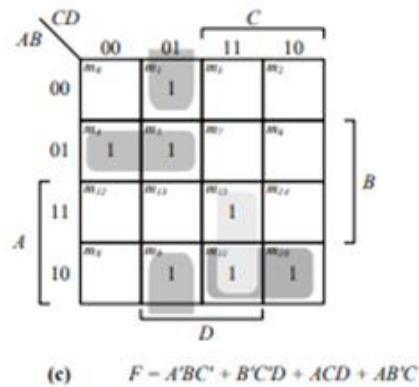
3(a) Simplify the following Boolean expressions, using four-variable maps:
 $A'B'C'D + AB'D + A'BC' + ABCD + AB'C$



3(b) Solve the following Boolean function F, together with the don't-care conditions d, and then express the simplified function in SOP and POS form.

$F(A,B,C,D) = \Sigma(0, 6,8,13,14)$

$d(A,B,C,D) = \Sigma(2, 4, 10)$

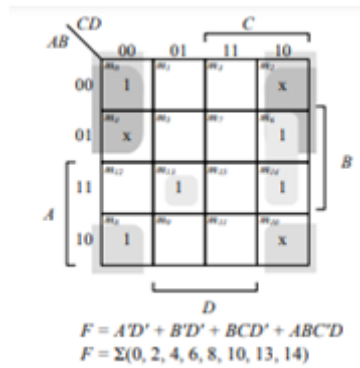

4(a) Model the multiple-level NOR circuit for the following expression: $CD(B + C)A + (BC' + DE)'$

Multi-level NOR:


$F = ACD(B + C) + (BC' + DE)'$

$F' = [ACD(B + C) + (BC' + DE)]'$

$F' = [(A' + C' + D')(B + C) + (B' + C)' + (D' + E)]'$

$F' = [((A' + C' + D') + (B + C)')' + (B' + C)' + (D' + E)]'$

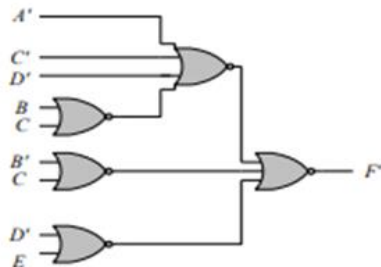
$F' = [(A' + C' + D' + (B + C)')' + (B' + C)' + (D' + E)]'$



4(b) Present the multiple-level NAND circuit for the following expression: $w(x + y + z) + xyz$

$$F = w(x + y + z) + xyz$$

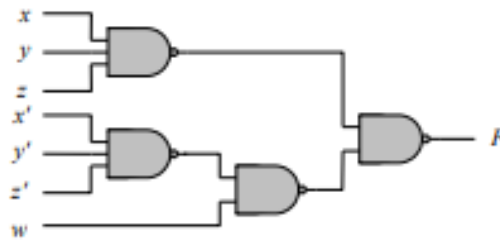
$$F' = [w(x + y + z)][xyz]' = [w(x'y'z')]'(xyz)'$$



5 Design a 3-bit subtractor combinational circuit using 2 bit subtractors

A 3-bit subtractor or full subtractor is a combinational circuit that performs subtraction involving three bits, namely A (minuend), B (subtrahend), and Bin (borrow-in). It accepts three inputs: A (minuend), B (subtrahend) and a Bin (borrow bit) and it produces two outputs: D (difference) and Bout (borrow out). The logic symbol and truth table are shown below.

Logic Symbol of Full subtractor

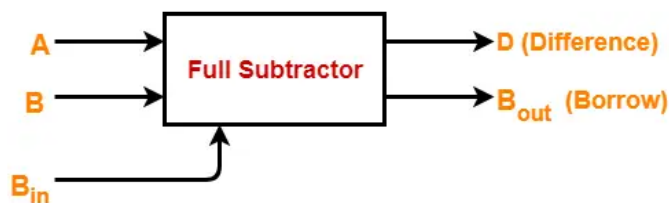


Truth Table of Full subtractor

A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


From the above truth table we can find the boolean expression using K-map

For D:

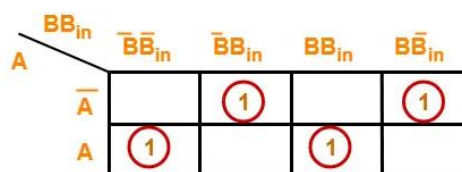


$$D = A \oplus B \oplus B_{in}$$

For B_{in} :

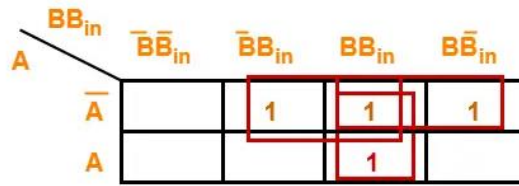


$$B_{out} = \bar{A} B + (\bar{A} + B) B_{in}$$

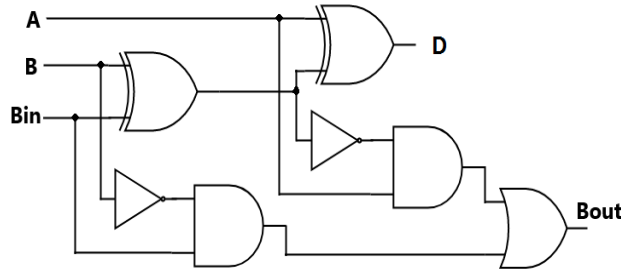From the equation we can draw the Full-subtractor circuit as shown



(Or)

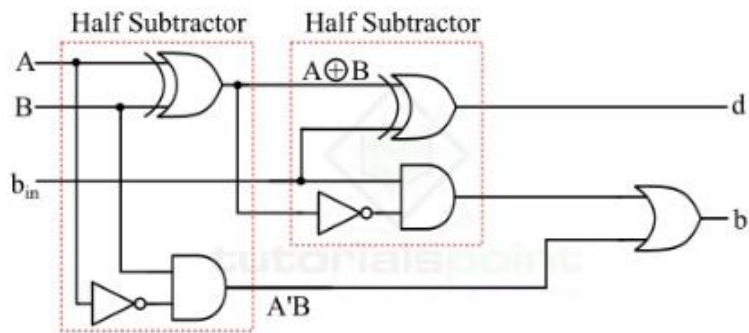

Circuit Diagram for Full subtractor using Half-subtractors

6(a) Discuss the combinational circuit that decodes 3 input variables?


Decoder:

The combinational circuit that change the binary information into 2^N output lines is known as Decoders. The binary information is passed in the form of N input lines. The output lines define the 2^N -bit code for the binary information. At a time, only one input line is activated for simplicity. The produced 2^N -bit output code is equivalent to the binary information.

3:8 Decoder:

The 3 to 8 line decoder is also known as Binary to Octal Decoder. In a 3 to 8 line decoder, there is a total of eight outputs, i.e., Y0, Y1, Y2, Y3, Y4, Y5, Y6, and Y7 and three outputs, i.e., A0, A1, and A2. This circuit has an enable input 'E'. Just like 2 to 4 line decoder, when enable 'E' is set to 1, one of these four outputs will be 1. The block diagram and the truth table of the 3 to 8 line encoder are given below.

Block Diagram:

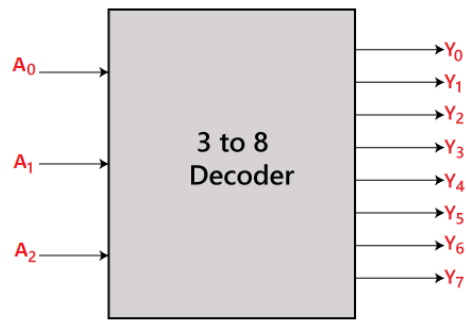


Truth Table:

Enable	INPUTS			Outputs							
E	A ₂	A ₁	A ₀	Y ₇	Y ₆	Y ₅	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

The logical expression of the term Y₀, Y₁, Y₂, Y₃, Y₄, Y₅, Y₆, and Y₇ is as follows: (solve using k-map)

$$\begin{aligned} Y_0 &= A_0' \cdot A_1' \cdot A_2' \\ Y_1 &= A_0 \cdot A_1' \cdot A_2' \\ Y_2 &= A_0' \cdot A_1 \cdot A_2' \\ Y_3 &= A_0 \cdot A_1 \cdot A_2' \\ Y_4 &= A_0' \cdot A_1' \cdot A_2 \\ Y_5 &= A_0 \cdot A_1' \cdot A_2 \\ Y_6 &= A_0' \cdot A_1 \cdot A_2 \\ Y_7 &= A_0 \cdot A_1 \cdot A_2 \end{aligned}$$

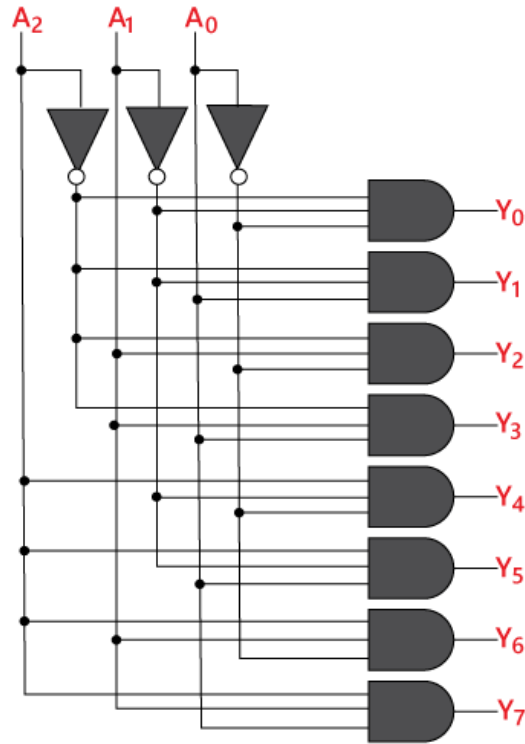Logical circuit of the above expressions is given below:



6(b) Discuss the combinational circuit that encodes 4 input variables?


Encoders:

The combinational circuits that change the binary information into N output lines are known as **Encoders**. The binary information is passed in the form of 2^N input lines. The output lines define the N-bit code for the binary information. In simple words, the **Encoder** performs the reverse operation of the **Decoder**. At a time, only one input line is activated for simplicity. The produced N-bit output code is equivalent to the binary information.

4 to 2 line Encoder:

In 4 to 2 line encoder, there are total of four inputs, i.e., Y_0 , Y_1 , Y_2 , and Y_3 , and two outputs, i.e., A_0 and A_1 . In 4-input lines, one input-line is set to true at a time to get the respective binary code in the output side. Below are the block diagram and the truth table of the 4 to 2 line encoder.

Block Diagram:

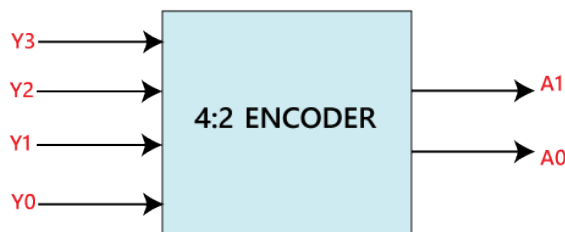

Truth Table:

INPUTS				OUTPUTS	
Y_3	Y_2	Y_1	Y_0	A_1	A_0
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

The logical expression of the term A_0 and A_1 is as follows: (solve using k-map)

$$A_1 = Y_3 + Y_2$$

$$A_0 = Y_3 + Y_1$$

Logical circuit of the above expressions is given below:

