

CBCS SCHEME

USN

BCS302

Third Semester B.E./B.Tech. Degree Examination, Dec.2023/Jan.2024

Digital Design and Computer Organization

Time: 3 hrs.

Max. Marks: 100

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.

2. M : Marks , L: Bloom's level , C: Course outcomes.

Module – 1			
		M	L
Q.1	a.		C
	a.	Obtain a minimum product of sums with a Karnaugh map. $F(w, x, y, z) = x' z' + w y z + w' y' z' + x' y.$	10 L3 CO1
	b.	Find the minimum sum of products for each function using a Karnaugh map i) $F_1(a, b, c) = M_0 + M_2 + M_5 + M_6$ ii) $F_2(d, e, f) = \sum m(0, 1, 2, 4)$ iii) $F_3(r, s, t) = r' + r's' + r's$	10 L3 CO1

OR

Q.2	a.	Identify the prime implicants and essential prime implicants of the following functions: i) $f(A, B, C, D) = \sum(1, 3, 4, 5, 10, 11, 12, 13, 14, 15)$ ii) $f(W, X, Y, Z) = \sum(0, 1, 2, 5, 7, 8, 10, 15).$	10	L3	CO1
	b.	Write the verilog code for the given expression using dataflow and behavioral model where $Y = (AB' + A'B)(CB + AD)(AB'C + AC).$	5	L2	CO1
	c.	Write the verilog code and time diagram for the given circuit with propagation delay where the AND, OR gate has a delay of 30ns and 10ns.	5	L2	CO1

 


Fig.Q.2(c)

Module – 2

Q.3	a.	What is Latch? With neat diagram, explain S-R latch using NOR gate. Derive characteristics equation	10	L3	CO2
	b.	What is priority encoder? Design 4:2 priority encoder with necessary diagrams.	10	L3	CO2

OR

Q.4	a.	Design and explain four bit adder with carry look ahead.	10	L3	CO2
	b.	What is multiplexer? Design 9:1 mux using 2:1 mux.	10	L3	CO2

Module - 3

Q.5	a.	Explain four types of operation performed by computer with an example.	10	L2	CO3
	b.	Show how below expression will be executed in one address, two address zero address and three address processor in an accumulator organization $X = (A * B) + (C * D)$.	10	L1	CO3

OR

Q.6	a.	What is addressing mode? Explain different types of addressing mode with an examples.	10	L2	CO3
	b.	With a neat diagram, explain basic operational concepts of a computer.	10	L2	CO3

Module - 4

Q.7	a.	Explain the following with respect to interrupts with diagram.	10	L2	CO3
	i)	Vector interrupt			
	ii)	Interrupt nesting			
	iii)	Simultaneous request.			

	b.	Explain Direct Memory Access with a neat diagram.	10	L2	CO3

OR

Q.8	a.	What is Bus arbitration? Explain different types of bus arbitration.	10	L2	CO3
	b.	Discuss different types of mapping functions of coaches.	10	L2	CO3

Module - 5

Q.9	a.	Draw and explain the single-bus organization of the data path inside a processor.	10	L2	CO4
	b.	List out the actions needed to execute the instruction ADD (R3), R1 write and explain the sequence of control steps for the execution of the same.	10	L2	CO4

OR

Q.10	a.	Analyze how does execution of a complete instruction carry out.	10	L4	CO4
	b.	What is pipeline? Explain the performance of pipeline with an example.	10	L4	CO4

1. a. $(y+z)(w+x+y)(\bar{w}+y+z) = 2m$

1	0	
0	0	0
0	0	1
0	0	
0	0	

kmap = 6m

$m_8 + m_2 + m_3 + m_4 + m_8 + m_{10} + m_{11} + m_{15} = 2m$

- b. (i) $b\bar{c} + \bar{a}\bar{c} + abc = 3m$
 (ii) $\bar{d}\bar{e} + \bar{e}\bar{f} + \bar{d}\bar{f} = 3m$
 (iii) $\bar{r} + \bar{t} = 4m$.

2. a. (i) Prime Implicant: $AB + \bar{A}\bar{B}D + B\bar{C} + AC + A\bar{C}D$ } 5m
 Essential P.I : $AB + A\bar{B}D + B\bar{C} + AC$

(ii) Prime Implicant: $\bar{x}\bar{z} + \bar{w}\bar{y}z + xyz + \bar{w}\bar{x}\bar{y} + \bar{w}xz$ } 5m
 E.P.I : $\bar{x}\bar{z} + \bar{w}\bar{y}z + xyz$

2.b. (i) Data modeling : $A^{\wedge}B \& (C \& B) | (A \& D) = 2m$.

(ii) Behavioural : always @ (A (or) B (or) C (or) D)
 begin

$$\Psi = ((A^{\wedge}B) \& (C \& B) | (A \& D)) \& ((A \& (\neg B) \& C) | (A \& C)) \rightarrow 3m.$$

2.c. AND (w_1, A_1, B)

AND (w_2, \bar{A}_1, B)

OR (w_3, C, \bar{D}) → 3m

OR (w_4, w_1, w_2)

AND (F, w_4, w_3).

waveform → 2m.

3.a. Latch definition → 1m

SR latch diagram → 2m

Truth Table → 6m

Characteristic Eq → 1m

3.b. Definition of Encoder → 1m
 Diagram → 3m

Explanation with Truth Table → 6m.

4. a. 4 bit adder + Explanation - 5+5

4. b. Multiplexer definition - 2m.

8:1 Using 2:1 Mux - 8M
(8 Mux for connecting it)

5. a. Data transfer - 2m

Program sequencing - 2m

I/O - 2m

ALU Operation - 2m

Example - 2m.

b. zero and One addressing - 3 each.
Two and Three addressing - 2 each.

6. a. Addressing mode - 2m

Types of addressing mode - 2m

Explanation with Example - 6M.

6. b. Diagram - 4m

Explanation - 6m.

7. a. (i) Vector Interrupt - 2m

(ii) Interrupt Diagram + Explanation - 4m

(iii) Simultaneous Request Diagram + Explanation - 4m.

7. b. DMA Diagram + Explanation - 4+6

8. a. Bus arbitration definition - 2m

Types  centralized - 4m
distributed - 4m.

8. b. 3-mapping - 1m.

Explanation with Diagram - 3 each.

9. a. Diagram - 4m

Explanation - 6m

9. b. Action needed - 2

sequence steps - 4m each.

10. (a) All steps - 10m

(b) Definition - 2m

Explanation with example - 8m.