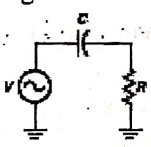


Internal Assessment Test - I

Sub:	Electronic Principles and Circuits	Code:	BEC303
Date:	19/12/2023	Duration:	90 mins
		Max Marks:	50
		Sem:	3rd
		Branch:	ECE
Answer Any FIVE FULL Questions			
			Marks
			OBE
			CO RBT
1	Explain the different criteria's involved in VDB Analysis.	10	CO1 L2
2	Design the resistor values in a voltage divider bias to meet these specifications: VCC = 10 V , VCE @ midpoint , IC = 10 mA and $\beta_{dc} = 100$ to 300.	10	CO1 L3
3	Discuss Emitter feedback bias and collector feedback bias.	10	CO1 L2
4	Derive voltage gain of common emitter amplifier from π model	10	CO1 L2

P.T.O

5	Explain the importance of coupling capacitor in base biased amplifier. if $R = 2k\Omega$ and the frequency range is from 20 Hz to 20 kHz, find the value of C needed to act as a good coupling capacitor in the below given Fig.5	10	CO1	L2
 <p>Fig 5</p>				
6	Explain in detail working of binary weighted resistor DAC with the neat circuit diagram	10	CO4	L2


Alas
CI

Manjiv S
CCI


R.B.L.L.
HOD

IAT - 1

 1. VDB or voltage divider bias is a circuit which has a stiff voltage divider at the input resistance of the transistor.



thevenin resistance

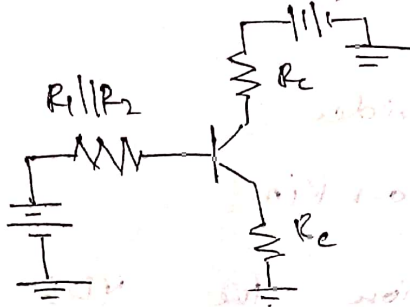

equivalent circuit

→ Thevenin Resistance

$$R_{TH} = R_1 || R_2$$

Because of this thevenin resistance the voltage of the VDB will not be ideal.

The current through the R_{TH} will reduce the voltage to base voltage from ideal voltage.

→ Accurate voltage divider

$$R_1 || R_2 < 0.01 R_{in}$$

A good VDB will follow this condition.

→ Stiff voltage divider

$$R_1 || R_2 < 0.01 R_{in}$$

$$R_{in} = \beta_{dc} R_e$$

$$\therefore R_1 \parallel R_2 < 0.01 \beta_{dc} R_E$$

Whenever possible, a designer will choose circuit values which follows these conditions. Hence the VDB will produce ultrastable Q-point.

→ From voltage divider

$$R_1 \parallel R_2 < 0.1 R_{in}$$

Under this condition the VDB will produce reasonable Q-point

→ close approximation

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + R_1 \parallel R_2 / \beta_{dc}}$$

$$R_1 \parallel R_2 = 10k\Omega \parallel 2.2k\Omega = 1.8k\Omega$$

$$\beta_{dc} R_E = 200 \times 1k\Omega = 200k\Omega$$

one-hundredth of ~~200kΩ~~

$$\frac{1}{100} \times 200 \times 10^3 = 2k$$

$\therefore 1.8k\Omega < 2k$ Hence VDB will act as a stiff VDB.

$$I_E = \frac{1.8V - 0.7}{1k + 1.8/200k} = \underline{\underline{1.094mA}}$$

2. $V_{CC} = 10V$

V_{CE} @ midpoint

$$I_E = 10mA$$

$$\beta_{dc} = 100 \text{ to } 300$$

$$V_E = 10\% V_{CC} = 0.01 \times 10 = 1V$$

$$I_E \approx I_C = 10mA$$

$$\therefore R_E = \frac{V_E}{I_E} = \frac{1}{10mA} = \underline{\underline{100\Omega}}$$

$$R_C = 4R_E = 4 \times 100 = \underline{\underline{400\Omega}}$$

$$R_2 < R_1$$

$$R_2 = 0.01 \beta_{dc} R_E$$

$$R_2 = 0.01 (100) (100)$$

$$R_2 = \underline{\underline{100\Omega}}$$

$$R_1 = \frac{V_1}{V_2} R_2 = \frac{8.3}{1.7} \times 100 = 488.23\Omega = \underline{\underline{490\Omega}}$$

$$V_2 = V_E + 0.7 = 1.7V$$

$$V_1 = V_{CC} - V_2 = 10 - 1.7 = 8.3V$$

∴ while designing a circuit which follows the given conditions,


$$R_1 = 490\Omega$$

$$R_2 = 100\Omega$$

$$R_E = 100\Omega$$


$$R_C = \underline{\underline{400\Omega}}$$

4. Common emitter amplifier

 

- $C_c \rightarrow$ coupling capacitor
- $C_B \rightarrow$ blocking capacitor
- $C_e \rightarrow$ bypass capacitor
- $R_L \rightarrow$ load resistance
- $V_{in} \rightarrow$ input voltage
- $V_{cc} \rightarrow$ DC input

T-model

 

$$V_{in} = i_b \beta r_e'$$

$$V_{out} = i_c (R_C \parallel R_L)$$

$$\therefore \text{voltage gain i.e. } A_v = \frac{V_{out}}{V_{in}}$$


$$A_v = \frac{i_c (R_C \parallel R_L)}{i_b \beta r_e'}$$

$$A_v = \frac{i_b \beta r_e' (R_C \parallel R_L)}{i_b \beta r_e'}$$

$R_C \parallel R_L \rightarrow r_c$ (equivalent resistance)

$$A_v = \frac{r_c}{r_e'}$$

T-model

 

$$V_{in} = i_b r_e'$$

$$V_{out} = i_c r_c$$


$$i_c \approx i_e$$

$$\therefore \text{voltage gain } A_v = \frac{V_{out}}{V_{in}} = \frac{i_e r_c}{i_b r_e'} = \frac{r_c}{r_e'}$$


$$A_v = \frac{r_c}{r_e'}$$

The above expression is same as the π -model because it is applicable to all transistors. Where the collector acts as an ac current source and emitter acts as an emitter resistance.

 5. A base biased amplifier is not much used in the industry but gives a basic idea about designing complicated circuits.



coupling capacitor

 

capacitor

for dc quantities open circuit

for ac quantities closed switch

- As the frequency increases the capacitive reactance decreases and becomes much smaller than the load resistance.

$$X_c = \frac{1}{2\pi f C}$$

$$f \uparrow = X_c \downarrow$$

- As a result input voltage appears across the load resistance.
- A capacitor that couples the input voltage with the output voltage is a coupling capacitor.
- A capacitor is an open circuit for dc ~~current~~ bias and not allow the current to leave the circuit.

$$R = 2k\Omega$$

$$f \text{ range} = 20\text{Hz to } 20\text{kHz}$$

$$C = ?$$

from the expression: $X_c < 0.01R$ @ lowest frequency

$$X_c < 0.01R @ 20\text{Hz}$$

$$X_c < 0.01(2k) @ 20\text{Hz}$$

$$X_c < 200\Omega$$

$$C = \frac{1}{2\pi f X_c}$$


$$C = \frac{1}{2\pi f X_c}$$

$$C = \frac{1}{2\pi (20)(200)}$$

$$C = \underline{\underline{39.8 \mu\text{F}}}$$

Hence capacitance value of $39.8 \mu\text{F}$ will be needed to act as a good coupling capacitor given in the diagram.

 6. Binary weighted resistor digital to analog converter.



Voltage gain $A_{V_0} = -\frac{R_f}{8R} = -\frac{1}{8} = -0.125$

Voltage gain $A_{V_1} = -\frac{R_f}{4R} = -\frac{1}{4} = -0.25$

Voltage gain $A_{V_2} = -\frac{R_f}{2R} = -\frac{1}{2} = -0.5$

Voltage gain $A_{V_3} = -\frac{R_f}{R} = -1$

total voltage gain

$$V_0 = V_{in} A_V$$

$$V_0 = A_{V_0} V_0 + A_{V_1} V_1 + A_{V_2} V_2 + A_{V_3} V_3$$

$$V_0 = -0.125 V_0 + -0.25 V_1 - 0.5 V_2 + V_3$$


$$\therefore V_0 = -(V_3 + 0.5 V_2 + 0.25 V_1 + 0.125 V_0)$$

8	4	2	1	
V_3	V_2	V_1	V_0	
0	0	0	0	→ 0
0	0	0	1	→ -0.125V
0	0	1	0	→ -0.25V
0	0	1	1	→ -0.375V
0	1	0	0	→ -0.5V
0	1	0	1	→ -0.625V
0	1	1	0	→ -0.75V
0	1	1	1	→ -0.875V
1	0	0	0	→ -1V
1	0	0	1	→ -1.125V
1	0	1	0	→ -1.25V
1	0	1	1	→ -1.375V
1	1	0	0	→ -1.5V
1	1	0	1	→ -1.625V
1	1	1	0	→ -1.75V
1	1	1	1	→ -1.875V

In binary weighted DAC, the output is not true analog, hence connected with a low pass filter to get a smooth curve at the output.

- This type of converter requires large number of different resistors as the number of inputs increases.
- Due to increase in number of resistors, loading effect will appear.
- This type of converter is used for limited inputs and where precision is not required.


3. Emitter feedback bias

 


- Emitter feedback bias is a technique used in transistor amplifiers.
- A negative feedback is connected to the base where an attempt is made to neutralise the change in collector current.
- In this method the Q-point moves all over the load line due to transistor replacement and temperature changes.
- When the feedback is connected the Q-points are stabilised by maintaining the temperature sensation and sensitivity of variation of other

transistor parameters.
 
$$I_E = \frac{V_{CC} - V_{BE}}{R_E + R_B/\beta_{DC}}$$



Collector feedback bias

 

- Also similar to emitter feedback bias to stabilize the Q-points.
- The main idea is to neutralise any change in collector current.
- In collector feedback bias, the negative feedback gives the voltage to the base where it reduces the change in original collector current.

$$I_E = \frac{V_{CC} - V_{BE}}{R_C + R_B/\beta_{DC}}$$

