

Internal Assessment Test 2 – January 2024

Sub:	Network Analysis				Sub Code:	BEC304	Branch:	ECE
Date:	19/01/2024	Duration:	90 Minutes	Max Marks:	50	Sem/Sec:	3/A, B, C, D	OBE

Answer Any Five Questions

MARKS CO RBT

1a State and explain Superposition Theorem.

[3] CO2 L2

Superposition Theorem :- The principle of superposition applicable only for linear systems.
 It states that,
 In any linear circuit containing multiple independent sources, the current or voltage at any point in the network may be calculated as algebraic sum of the individual combinations of each source acting alone.


stepwise approach :-

step 1: In a circuit comprising of many independent sources, only one source is allowed to be active, the rest are deactivated.

step 2: To deactivate voltage source, replace it with a short circuit and to deactivate current source, replace it with an open circuit.

step 3: The response obtained by applying each source, one at a time are then added algebraically to obtain a solution.

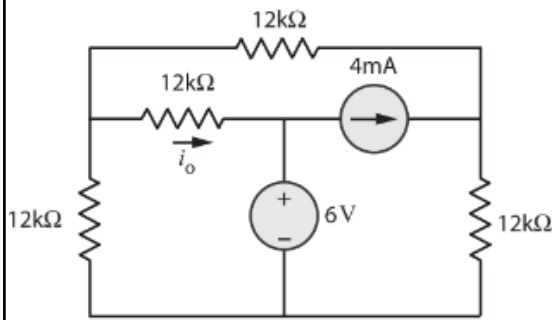Find i_0 in the network shown in Fig. using superposition.



As a first step, set the current source to zero. That is, the current source appears as an open circuit as shown in Fig. 3.5.


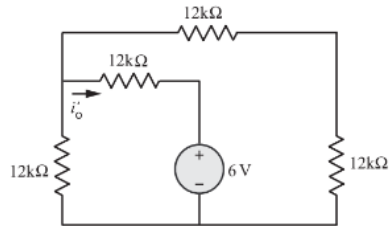


Figure 3.5

162 | Network Theory

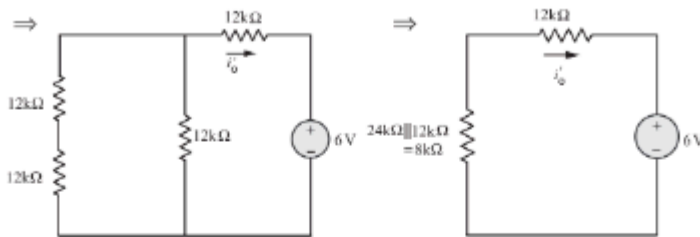

$$i_0' = \frac{-6}{(8 + 12) \times 10^3} = -0.3 \text{ mA}$$

As a second step, set the voltage source to zero. This means the voltage source in Fig. 3.4 is replaced by a short circuit as shown in Figs. 3.6 and 3.6(a). Using current division principle,

$$i_A = \frac{i R_2}{R_1 + R_2}$$

where $R_1 = (12 \text{ k}\Omega \parallel 12 \text{ k}\Omega) + 12 \text{ k}\Omega$
 $= 6 \text{ k}\Omega + 12 \text{ k}\Omega$
 $= 18 \text{ k}\Omega$

and $R_2 = 12 \text{ k}\Omega$
 $\Rightarrow i_A = \frac{4 \times 10^{-3} \times 12 \times 10^3}{(12 + 18) \times 10^3}$
 $= 1.6 \text{ mA}$

Again applying the current division principle,

$$i_0'' = \frac{i_A \times 12}{12 + 12} = 0.8 \text{ mA}$$

Thus, $i_0 = i_0' + i_0'' = -0.3 + 0.8 = 0.5 \text{ mA}$

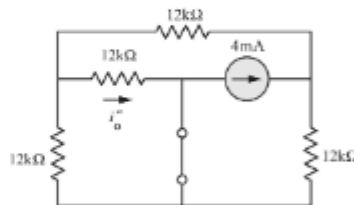


Figure 3.6

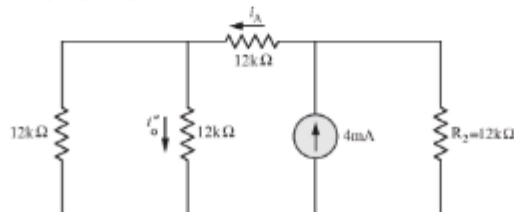


Figure 3.6(a)


2a

State and prove Maximum Power Transfer Theorem when both R_L and X_L are varying.

[5]

CO2

L2

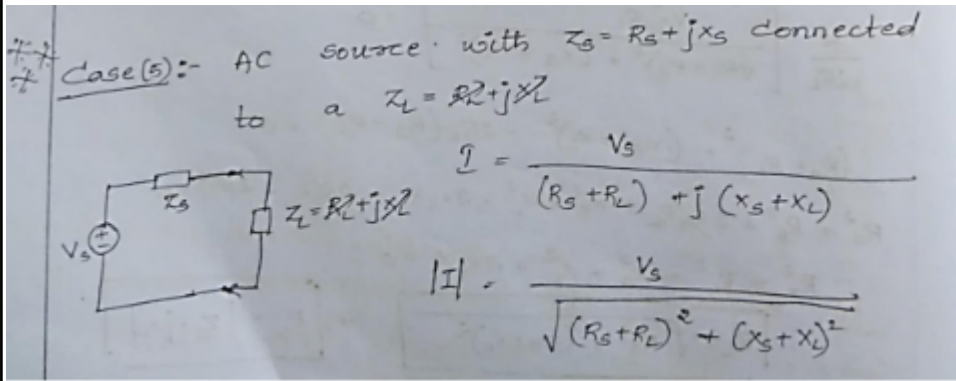

$$P = |I|^2 R_L = \frac{V_S^2 R_L}{(R_S + R_L)^2 + (X_S + X_L)^2}$$
 for max. power transfer, $\frac{dP}{dX_L} = 0$

$$\frac{d}{dX_L} \left[\frac{V_S^2 R_L}{(R_S + R_L)^2 + (X_S + X_L)^2} \right] = 0$$

$$0 - R_L [0 + 2(X_S + X_L)] = 0$$

$$X_S + X_L = 0$$

$$X_L = -X_S$$

The condition for max. power transfer is the load reactance should be conjugate of source reactance. Under this condition,

$$P_{max} = \frac{V_S^2 R_L}{(R_S + R_L)^2}$$

$$\therefore \frac{dP}{dR_L} = 0$$

$$\frac{d}{dR_L} \left[\frac{V_S^2 R_L}{(R_S + R_L)^2} \right] = 0$$

$$(R_S + R_L)^{-2} (0) - R_L [2(R_S + R_L)] = 0$$

$$R_S^2 + R_L^2 + 2R_S R_L - 2R_S R_L - 2R_L^2 = 0$$

$$R_S^2 - R_L^2 = 0$$

$$R_S^2 = R_L^2$$


NKT,

$$Z_L = R_L + jX_L$$

put, $R_L = R_S$ & $X_L = -X_S$

$$\therefore Z_L = R_S - jX_S$$

The condition for max. power transfer $Z_L = Z_S^*$ is the load impedance should be complex conjugate of source impedance.

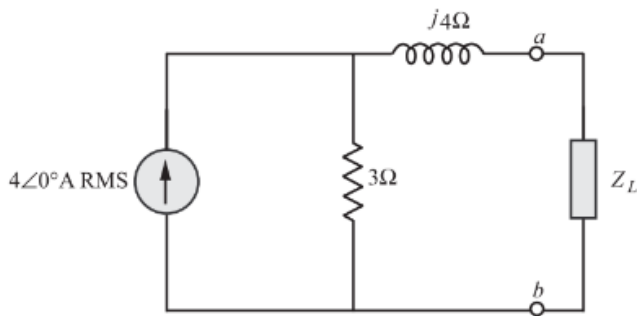**SOLUTION**

The first step in the analysis is to find the Thevenin equivalent circuit by disconnecting the load Z_L . This leads to a circuit diagram as shown in Fig. 3.114.

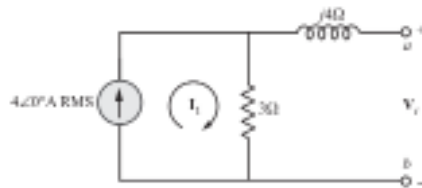


Figure 3.114

Hence

$$\begin{aligned} V_1 = V_{oc} &= 4 \angle 0^\circ \times 3 \\ &= 12 \angle 0^\circ \text{ Volts (RMS)} \end{aligned}$$

To find Z_L , let us deactivate all the independent sources of Fig. 3.114. This leads to a circuit diagram as shown in Fig. 3.114 (a):

$$Z_0 = 3 + j4 \Omega$$

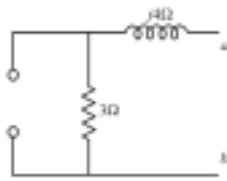


Figure 3.114 (a)

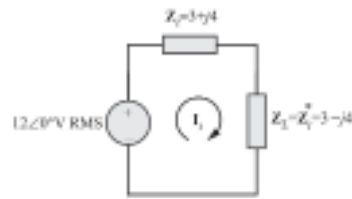


Figure 3.115

The Thevenin equivalent circuit with Z_L is as shown in Fig. 3.115.

For maximum average power transfer to the load, $Z_L = Z_0^* = 3 - j4$.

$$I_1 = \frac{12 \angle 0^\circ}{3 + j4 + 3 - j4} = 2 \angle 0^\circ \text{ A (RMS)}$$

Hence, maximum average power delivered to the load is

$$P = |I_1|^2 R_L = 4(3) = 12 \text{ W}$$

It may be noted that the scaling factor $\frac{1}{2}$ is not taken since the phase current is already expressed by its *RMS* value.

Millman's theorem states that if n number of generators having generated emfs E_1, E_2, \dots, E_n and internal impedances Z_1, Z_2, \dots, Z_n are connected in parallel, then the emfs and impedances can be combined to give a single equivalent emf of E with an internal impedance of equivalent value Z .

where
$$E = \frac{E_1 Y_1 + E_2 Y_2 + \dots + E_n Y_n}{Y_1 + Y_2 + \dots + Y_n}$$

and
$$Z = \frac{1}{Y_1 + Y_2 + \dots + Y_n}$$

where Y_1, Y_2, \dots, Y_n are the admittances corresponding to the internal impedances Z_1, Z_2, \dots, Z_n and are given by

$$Y_1 = \frac{1}{Z_1}$$

$$Y_2 = \frac{1}{Z_2}$$

\vdots

$$Y_n = \frac{1}{Z_n}$$

Fig. 3.134 shows a number of generators having emfs E_1, E_2, \dots, E_n connected in parallel across the terminals x and y . Also, Z_1, Z_2, \dots, Z_n are the respective internal impedances of the generators.

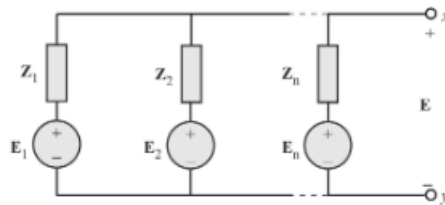


Figure 3.134

The Thevenin equivalent circuit of Fig. 3.134 using Millman's theorem is shown in Fig. 3.135. The nodal equation at x gives

$$\begin{aligned} & \frac{E_1 - E}{Z_1} + \frac{E_2 - E}{Z_2} + \dots + \frac{E_n - E}{Z_n} = 0 \\ \Rightarrow & \left[\frac{E_1}{Z_1} + \frac{E_2}{Z_2} + \dots + \frac{E_n}{Z_n} \right] = E \left[\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n} \right] \\ \Rightarrow & E_1 Y_1 + E_2 Y_2 + \dots + E_n Y_n = E \left[\frac{1}{Z} \right] \end{aligned}$$

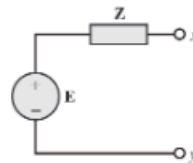


Figure 3.135

where Z = Equivalent internal impedance.

or
$$[E_1 Y_1 + E_2 Y_2 + \dots + E_n Y_n] = E Y$$

$$\Rightarrow E = \frac{E_1 Y_1 + E_2 Y_2 + \dots + E_n Y_n}{Y}$$

where
$$Y = Y_1 + Y_2 + \dots + Y_n$$


and
$$Z = \frac{1}{Y} = \frac{1}{Y_1 + Y_2 + \dots + Y_n}$$

3b Find the current through $(10 - j3) \Omega$ using Millman's theorem. Refer Fig.

[6]

CO2

L2

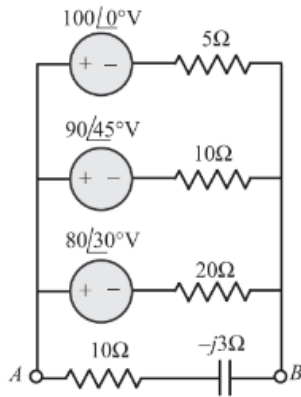

SOLUTION

The circuit shown in Fig. 3.138 is replaced by its Thevenin equivalent circuit as seen from the terminals, A and B using Millman's theorem. Fig. 3.139 shows the Thevenin equivalent circuit along with $Z_L = 10 - j3 \Omega$.

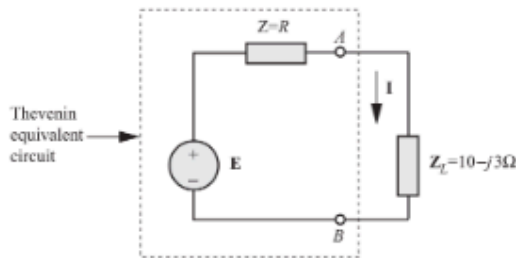


Figure 3.139

$$E = \frac{E_1 Y_1 + E_2 Y_2 - E_3 Y_3}{Y_1 + Y_2 + Y_3}$$

$$= \frac{100 \angle 0^\circ \left(\frac{1}{5}\right) + 90 \angle 45^\circ \left(\frac{1}{10}\right) + 80 \angle 30^\circ \left(\frac{1}{20}\right)}{\frac{1}{5} + \frac{1}{10} + \frac{1}{20}}$$

$$= 88.49 \angle 15.66^\circ \text{ V}$$

$$Z = R = \frac{1}{Y_1 + Y_2 + Y_3} = \frac{1}{\frac{1}{5} + \frac{1}{10} + \frac{1}{20}} = 2.86 \Omega$$

$$I = \frac{E}{Z + Z_L} = \frac{88.49 \angle 15.66^\circ}{2.86 + 10 - j3} = 6.7 \angle 28.79^\circ \text{ A}$$

Alternately,

$$E = \frac{E_1 Y_1 + E_2 Y_2 + E_3 Y_3 + E_4 Y_4}{Y_1 + Y_2 + Y_3 + Y_4}$$

$$= \frac{100 \times 5^{-1} + 90 \angle 45^\circ \times 10^{-1} + 80 \angle 30^\circ \times 20^{-1}}{5^{-1} + 10^{-1} + 20^{-1} + (10 - j3)^{-1}}$$

$$= 70 \angle 12^\circ \text{ V}$$

Therefore,

$$I = \frac{70 \angle 12^\circ}{10 - j3}$$


$$= 6.7 \angle 28.8^\circ \text{ A}$$

Find the Thevenin and Norton equivalent circuits for the network shown in Fig.

[10]

CO2

L3

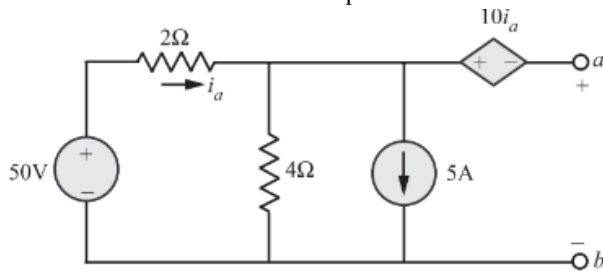**SOLUTION**

To find V_{oc} :

Performing source transformation on 5A current source, we get the circuit shown in Fig. 3.80 (b).

Applying KVL around Left mesh:

$$\begin{aligned} -50 + 2i_a - 20 + 4i_a &= 0 \\ \Rightarrow i_a &= \frac{70}{6} \text{ A} \end{aligned}$$

Applying KVL around right mesh:

$$\begin{aligned} 20 + 10i_a + V_{oc} - 4i_a &= 0 \\ \Rightarrow V_{oc} &= -90 \text{ V} \end{aligned}$$

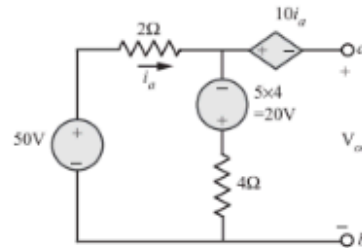


Figure 3.80(b)

To find i_{sc} (referring Fig 3.80 (c)):

KVL around Left mesh:

$$\begin{aligned} -50 + 2i_a - 20 + 4(i_a - i_{sc}) &= 0 \\ \Rightarrow 6i_a - 4i_{sc} &= 70 \end{aligned}$$

KVL around right mesh:

$$\begin{aligned} 4(i_{sc} - i_a) + 20 + 10i_a &= 0 \\ \Rightarrow 6i_a + 4i_{sc} &= -20 \end{aligned}$$


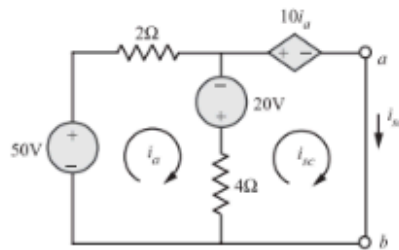


Figure 3.80(c)


Solving the two mesh equations simultaneously, we get $i_{sc} = -11.25 \text{ A}$

$$\text{Hence, } R_t = R_N = \frac{v_{oc}}{i_{sc}} = \frac{-90}{-11.25} = 8 \Omega$$

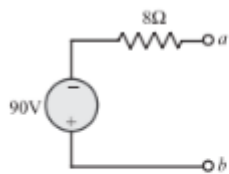Performing source transformation on Thevenin equivalent circuit, we get the norton equivalent circuit (both are shown below).




Thevenin equivalent circuit

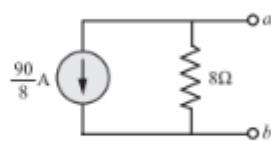

Norton equivalent circuit

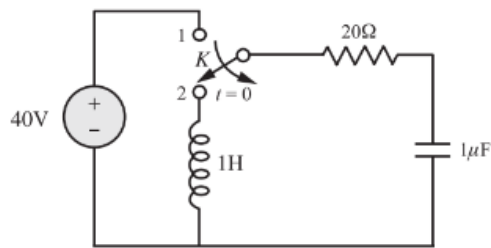Calculate i , $\frac{di}{dt}$, and $\frac{d^2i}{dt^2}$ at $t = 0^+$.



SOLUTION

The symbol for switch K implies that it is in position 1 at $t = 0^-$ and in position 2 at $t = 0^+$. Under steady-state condition, a capacitor acts as an open circuit. Hence at $t = 0^-$, the circuit diagram is as shown in Fig. 4.18(a).

We know that the voltage across a capacitor cannot change instantaneously. This means that $v_C(0^+) = v_C(0^-) = 40\text{ V}$.

At $t = 0^-$, inductor is not energized. This means that $i(0^-) = 0$. Since current in an inductor cannot change instantaneously, $i(0^+) = i(0^-) = 0$. Hence, the circuit diagram at $t = 0^+$ is as shown in Fig. 4.18(b).

The circuit diagram for $t \geq 0^+$ is as shown in Fig.4.18(c).

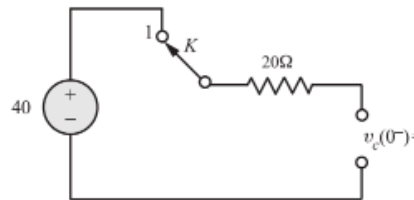


Figure 4.18(a)

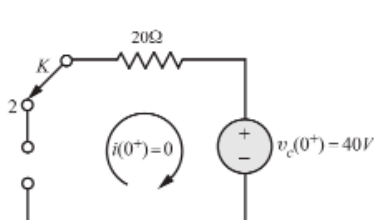


Figure 4.18(b)

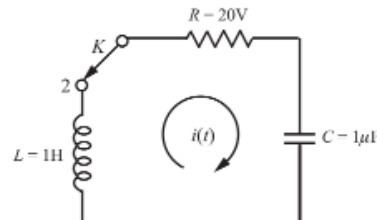


Figure 4.18(c)

Applying KVL clockwise, we get

$$Ri + L\frac{di}{dt} + \frac{1}{C} \int_{0^+}^t i(\tau) d\tau = 0 \quad (4.4)$$

$$\Rightarrow Ri + L\frac{di}{dt} + v_C(t) = 0$$

At $t = 0^+$, we get

$$Ri(0^+) + L\frac{di(0^+)}{dt} + v_C(0^+) = 0$$

$$\Rightarrow 20 \times 0 + 1\frac{di(0^+)}{dt} + 40 = 0$$

$$\Rightarrow \frac{di(0^+)}{dt} = -40\text{ A/sec}$$

Differentiating equation (4.4) with respect to t , we get

$$R\frac{di}{dt} + L\frac{d^2i}{dt^2} + \frac{i}{C} = 0$$

Putting $t = 0^+$ in the above equation, we get

$$R \frac{di(0^+)}{dt} + L \frac{d^2i(0^+)}{dt^2} + \frac{i(0^+)}{C} = 0$$

$$\Rightarrow R \times (-40) + L \frac{d^2i(0^+)}{dt^2} + \frac{0}{C} = 0$$

Hence $\frac{d^2i(0^+)}{dt^2} = 800 \text{A/sec}^2$

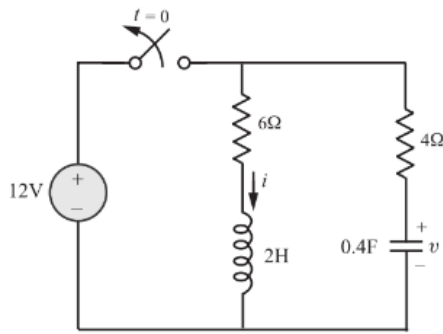
(a) $i(0^+)$ and $v(0^+)$ (b) $\frac{di(0^+)}{dt}$ and $\frac{dv(0^+)}{dt}$ (c) $i(\infty)$ and $v(\infty)$ **SOLUTION**

Figure 4.28

(a) From the symbol of switch, we find that at $t = 0^-$, the switch is closed and $t = 0^+$, it is open. At $t = 0^-$, the circuit has reached steady state so that the equivalent circuit is as shown in Fig.4.29(a).

$$i(0^-) = \frac{12}{6} = 2\text{A}$$

$$v(0^-) = 12\text{V}$$

Therefore, we have

$$i(0^+) = i(0^-) = 2\text{A}$$

$$v(0^+) = v(0^-) = 12\text{V}$$

(b) For $t \geq 0^+$, we have the equivalent circuit as shown in Fig.4.29(b).

(b) For $t \geq 0^+$, we have the equivalent circuit as shown in Fig.4.29(b).

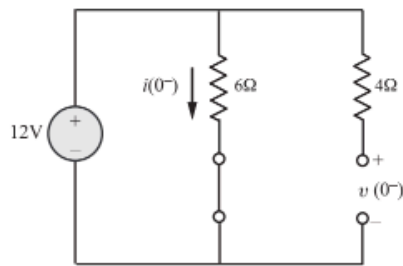


Figure 4.29(a)

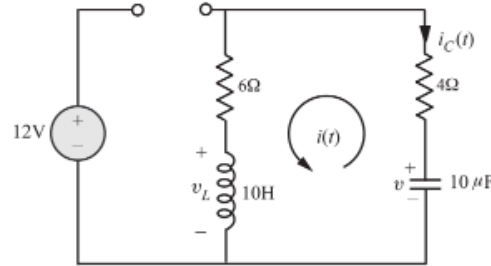


Figure 4.29(b)

Applying KVL anticlockwise to the mesh on the right, we get

$$v_L(t) - v(t) + 10i(t) = 0$$

Putting $t = 0^+$, we get

$$v_L(0^+) - v(0^+) + 10i(0^+) = 0$$

$$\Rightarrow v_L(0^+) - 12 + 10 \times 2 = 0$$

$$\Rightarrow v_L(0^+) = -8\text{V}$$

The voltage across the inductor is given by

$$\begin{aligned}v_L &= L \frac{di}{dt} \\ \Rightarrow v_L(0^+) &= L \frac{di(0^+)}{dt} \\ \Rightarrow \frac{di(0^+)}{dt} &= \frac{1}{L} v_L(0^+) \\ &= \frac{1}{10}(-8) = -0.8 \text{ A/sec}\end{aligned}$$

Similarly, the current through the capacitor is

or

$$\begin{aligned}i_C &= C \frac{dv}{dt} \\ \frac{dv(0^+)}{dt} &= \frac{i_C(0^+)}{C} = \frac{-i(0^+)}{C} \\ &= \frac{-2}{10 \times 10^{-6}} = -0.2 \times 10^6 \text{ V/sec}\end{aligned}$$

(c) As t approaches infinity, the switch is open and the circuit has attained steady state. The equivalent circuit at $t = \infty$ is shown in Fig.4.29(c).

$$i(\infty) = 0$$

$$v(\infty) = 0$$


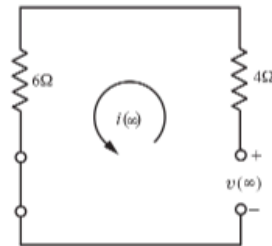


Figure 4.29(c)

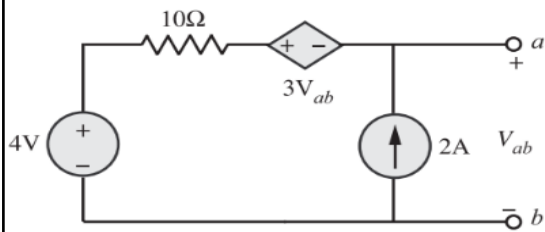

As a first step in the analysis, deactivate the independent current source. This results in a circuit diagram as shown in Fig. 3.15.

Applying KVL clockwise gives

$$-4 + 10 \times 0 + 3V_{ab_1} + V_{ab_1} = 0$$

$$\Rightarrow 4V_{ab_1} = 4$$

$$\Rightarrow V_{ab_1} = 1\text{V}$$

Next step in the analysis is to deactivate the independent voltage source, resulting in a circuit diagram as shown in Fig. 3.16.

Applying KVL gives

$$-10 \times 2 + 3V_{ab_2} + V_{ab_2} = 0$$

$$\Rightarrow 4V_{ab_2} = 20$$

$$\Rightarrow V_{ab_2} = 5\text{V}$$

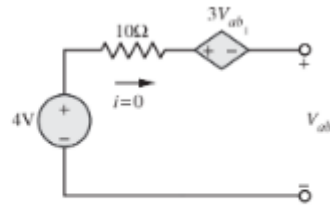


Figure 3.15

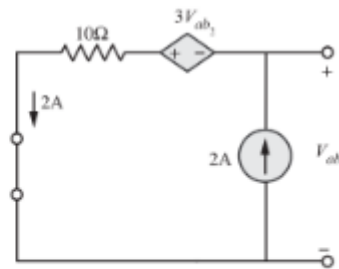
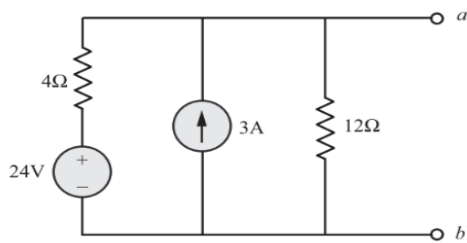


Figure 3.16

According to superposition principle,

$$\begin{aligned} V_{ab} &= V_{ab_1} + V_{ab_2} \\ &= 1 + 5 = \mathbf{6\text{V}} \end{aligned}$$

**SOLUTION**

As a first step, short the terminals $a - b$. This results in a circuit diagram as shown in Fig. 3.67.

Applying KCL at node a , we get

$$\frac{0 - 24}{4} - 3 + i_{sc} = 0$$

$$\Rightarrow i_{sc} = 9\text{A}$$

To find R_N , deactivate all the independent sources, resulting in a circuit diagram as shown in Fig. 3.68 (a). We find R_N in the same way as R_t in the Thevenin equivalent circuit.

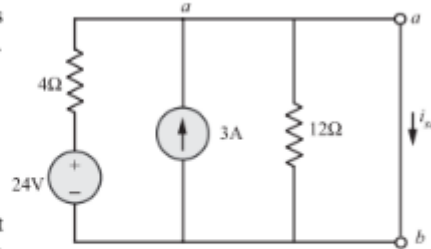


Figure 3.67

$$R_N = \frac{4 \times 12}{4 + 12} = 3\ \Omega$$

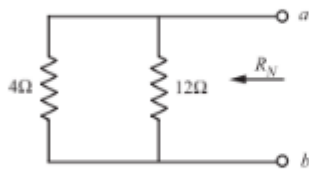


Figure 3.68(a)

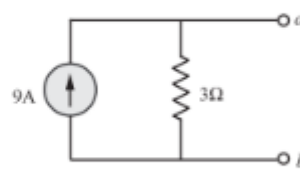


Figure 3.68(b)

Thus, we obtain Norton equivalent circuit as shown in Fig. 3.68(b).