

Internal Assessment Test - II

Sub:	Electronic Principles and Circuits						Code:	BEC303	
Date:	18/1/2024	Duration:	90 mins	Max Marks:	50	Sem:	3rd	Branch:	ECE
Answer Any FIVE FULL Questions									
							Marks	OBE	
								CO	RBT
1	Explain the circuit diagram and working of RC phase shift oscillator						10	CO3	L2
2	Explain the working of Astable multivibrator using 555 timer with internal diagram						10	CO3	L2
3	Explain the circuit diagram and working of crystal oscillator.						10	CO3	L2
4	Explain the operation of the first order stages for both LPF and HPF active filters						10	CO4	L2

P.T.O

5	Explain VCIS and ICVS negative feedback amplifiers	10	CO4	L2
6	Explain different Ideal responses of active filter.	10	CO4	L1



Handwritten signature
CI

Handwritten signature
CCI

Handwritten signature
R. E. Lal
HOD

IAT-2

R-C phase shift oscillator.

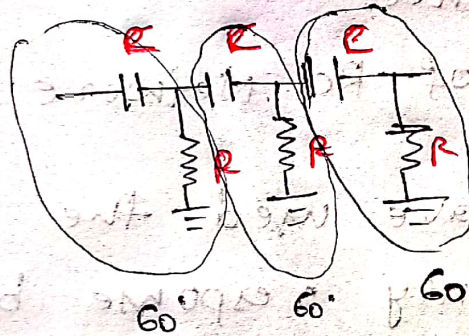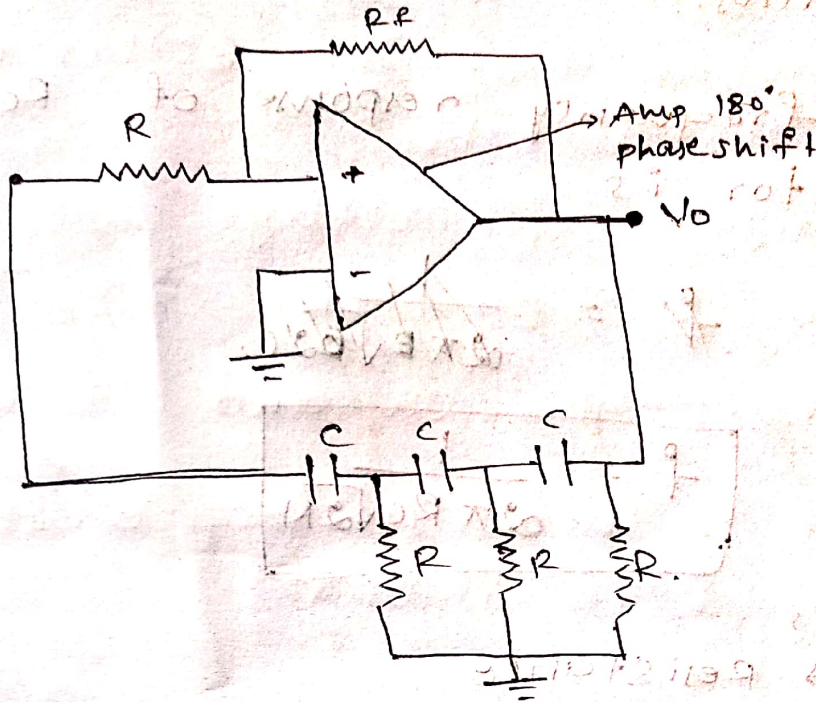

- the phase shift oscillator uses the 3 Lag Circuits (R-C)
- the Amplifier produces the 180° phase shift and 3 Lag Circuits produces the 180° phase shift. at some high frequency to get a open loop phase shift 0°
- if the AFB is greater than 1, then the Oscillator starts working.

→ it cannot be adjusted over the high order frequencies.

→ the frequency response of RC phase shift oscillator is

$$f = \frac{1}{2\pi RC\sqrt{6}}$$

$$f = \frac{1}{2\pi RC\sqrt{6N}}$$

Where,

R → Resistance

C → Capacitance

N → Number of RC Network.

In the fig.1 we have used the 3 R-C networks then the frequency response becomes,


$$f = \frac{1}{2\pi RC\sqrt{6}}$$

2) Multivibrator


→ multivibrator is a device which produces the square triangular pulse wave form called as non-linear operation employ building

block circuit is known as multivibrator.

Astable multivibrator.

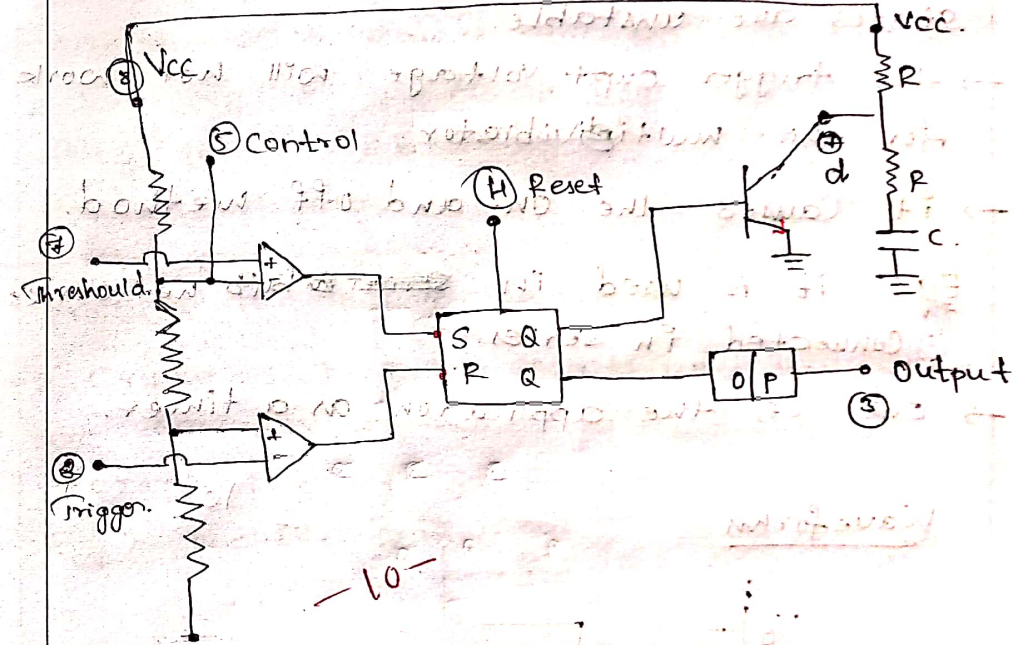


555 - internal diagram

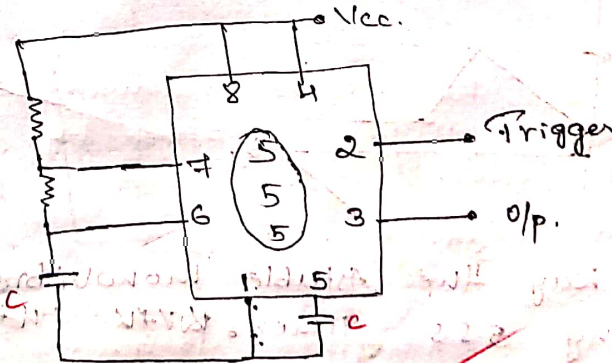

- the Astable monovibrator has both the unstable states. ~~which~~
- which means that the either of the states are unstable.
- the trigger output voltage will not work for this multivibrator.
- it causes the on and off method.
- Eg: it is used in ~~sub~~ networks connected in series.
- one of the application as a timer.

Waveforms

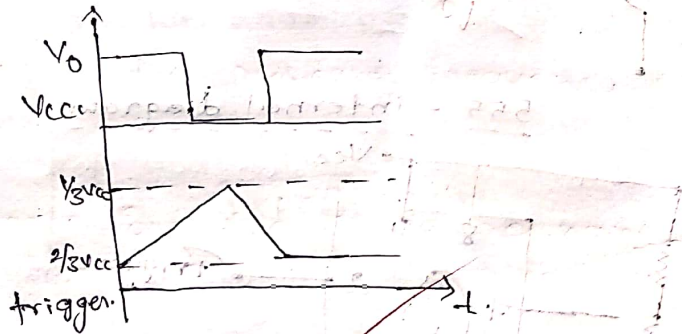



by this way the Astable monovibrator works using 555 timer.

3) Crystall Oscillator

→ piezoelectric effect


- ⇒ there are some natural elements on the earth which ^{obeys} ~~causes~~ the piezoelectric effect.
- when we apply a voltage around them they starts vibrating at frequency of applied voltage.
- when we mechanically force them they produces the AC voltage.
- Crystals, Rochelle salts and normaline are the devices which ^{allows} ~~obeys~~ the piezoelectric effect.

Eg: Rochelle Salts.

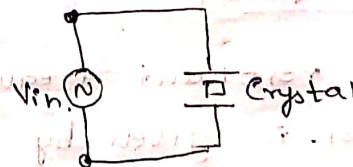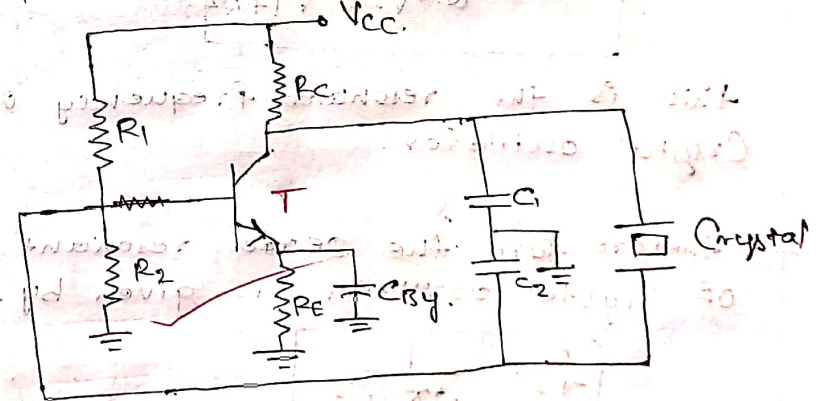

6

series parallel resonant frequency. CMR

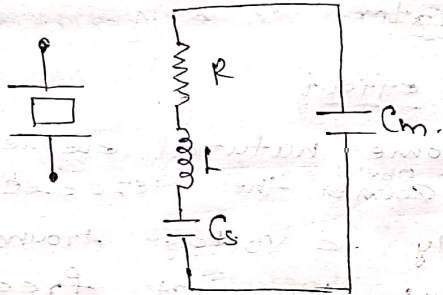

R → Resistance of Crystal

L → electrical equivalent inductance

Cs → Crystal Capacitance.

Cm → mounting conductance of Capacitor.

$$f_r = \frac{1}{2\pi\sqrt{LC}} \cdot \sqrt{\frac{Q^2}{1+Q^2}}$$

this is the resonant frequency of the Crystal oscillator.

→ therefore the series resonant frequency of Crystal oscillator is given by.

$$f_s = \frac{1}{2\pi\sqrt{LC_s}}$$

→ the parallel resonant frequency of Crystal oscillator is given by.

7

$$A_v = 1 + \frac{R_1}{R_2}$$

$$f = \frac{1}{2\pi R_1 C_1}$$

$$f_p = \frac{1}{2\pi\sqrt{LC_p}}$$


where $C_p = \frac{C_m C_s}{C_s + C_m}$

By this way the Crystal oscillator works.

4) First order stages

1) Low pass filter.

1) Non-inverting unity gain Amplifier.

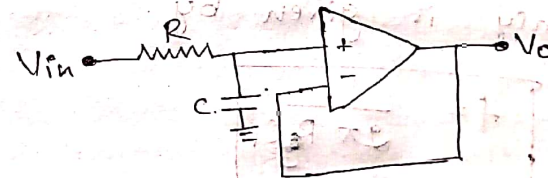

→ for this type of Amplifier the gain is


$$A_v = 1$$

→ frequency of this type of unity gain amplifier is given by

$$f_c = \frac{1}{2\pi R_1 C_1}$$

$$X_c = \frac{1}{2\pi f_c}$$

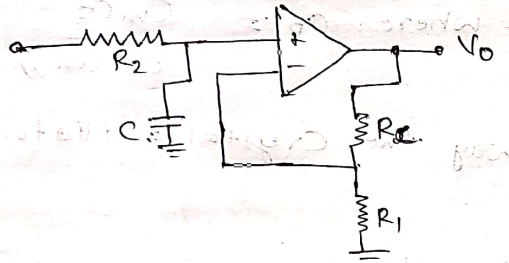ii) Non-inverting voltage gain Amplifier.




→ for this voltage gain Amplifier the gain is

$$A = 1 + \frac{R_f}{R_1}$$

→ frequency is given by.

$$f = \frac{1}{2\pi R_1 C_1}$$

iii) Inverting voltage gain Amplifier

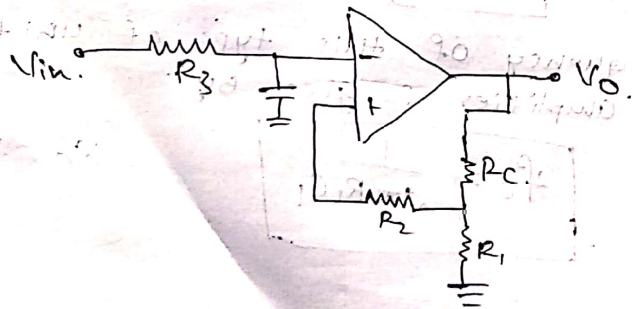

→ the ^{voltage} gain is given by:


$$A = -\frac{R_2}{R_1}$$

→ frequency is given by

$$f = \frac{1}{2\pi R_2 C_1}$$

High pass filter


i) Non-inverting unity gain Amplifier

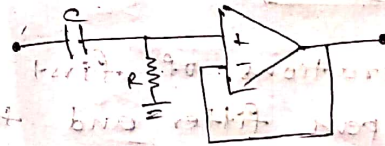

$$A_v = 1$$

$$f = \frac{1}{2\pi R_1 C_1}$$

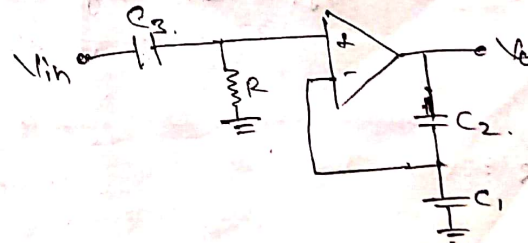ii) non-inverting voltage gain Amplifier.




$$A_v = 1 + \frac{R_2}{R_1}$$

$$f = \frac{1}{2\pi R_2 C_2}$$



ii) Inverting Voltage gain Amplifier

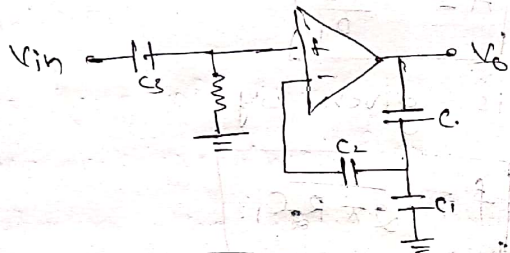

$$A_v = -\frac{C_2}{C_1}$$

$$f = \frac{1}{2\pi R_2 C_1}$$

⇒ these the operations of first order stages for both low pass filter and the high pass filter.

5) there are four types of negative feedback amplifier.

1) $V_c V_s$

2) $I_c V_s$

3) $V_c I_s$


4) $I_c I_s$

$V_c V_s$
 $I_c V_s$
 $V_c I_s$
 $I_c I_s$



① $V_c I_s$ (Voltage Controlled Current Source Amplifier)

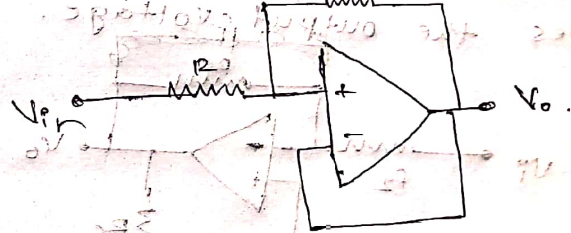→ this type of Amplifier is also called as trans Conductance Amplifier
 → it controls the o/p current of an amplifier



the gain of this amplifier is

$$A_v = \frac{A_{OL} (R_1 + R_2)}{R_1 (A_{OL} R_{in})}$$

$$A_v = \frac{R_1 + R_2}{R_1}$$

→ the impedance of closed loop amplifier

$$Z_{in}^{CL} = R_1 (1 + \beta A_{OL}) R_{in}$$

→ o/p imp of closed loop

$$Z_{out}^{CL} = R_1 (1 + A_{OL}) R_{out}$$


12



⑨ IC VS (Current Controlled Voltage Source Amplifier)

→ this type of Amplifier is also known as transresistive Amplifier.

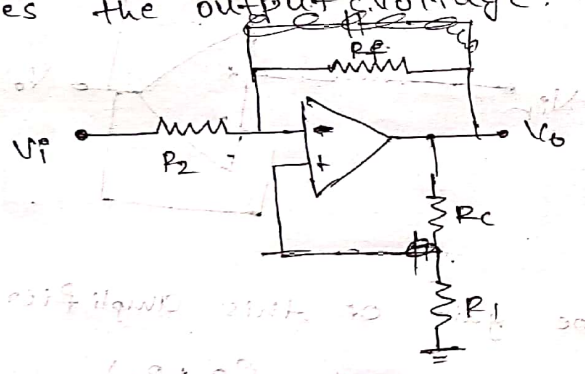→ it takes the input Current and gives the output voltage.



the gain of this amplifier is given as.

$$A_v = -V_o (-I_{in} V_{ref})$$

→ the input impedance of closed loop is given by

$$Z_{in} = \frac{R_{in}}{R_1 + R_2}$$

$$Z_{out} = \frac{R_{out}}{R_1 + R_2}$$

IAT-II

13




Q6 Ideal Responses for Active filter are:-

There are four type of Active filters


- (1) Low pass filter
- (2) High pass filter
- (3) Band pass filter
- (4) Band ~~stop~~ ^{stop} filter
- (5) All pass filter.

① for low pass filter

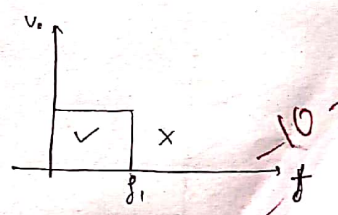


In low pass filter we get output only when frequency is low. at high frequency we ~~can~~ don't get any output.
 $f \downarrow \rightarrow$ output
 $f \uparrow \rightarrow$ No output.

② High pass filter

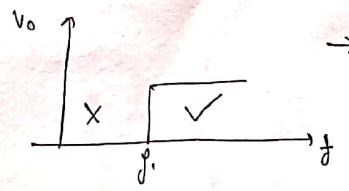


→ In High pass filter we get output after frequency crosses certain threshold then it will gives output.
 $f \downarrow \rightarrow$ No output
 $f \uparrow \rightarrow$ output.
 * $f > f_i$ output condition.

(3) Band - Pass filter.

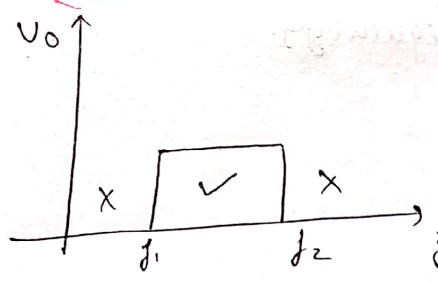

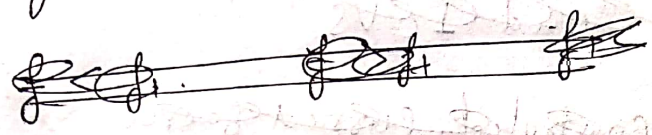
In this type of filter we get output only at selected frequency band we get output when frequency lies in the range of Band pass filter we get output.



$f < f_1$, No output
 $f > f_2$, No output
 $f_2 - f_1 = \text{Band width.}$

$\rightarrow f_1 < f < f_2$ we get output

(4) Band ^{stop} gap filter

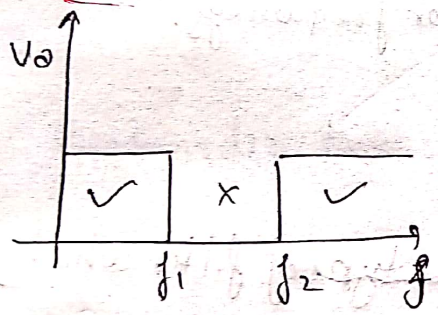


In this type of filters we don't get any output in selected frequency and we get output in other frequency.

* on certain frequency we don't get any output.

$f < f_1$ output we get
 $f > f_2$ output we get

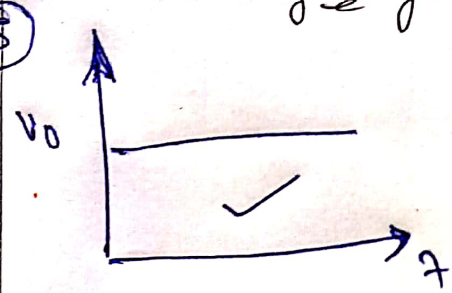~~$f_1 < f < f_2$~~ $f_1 < f < f_2 \rightarrow$ We don't get any output.



This filter gives o/p for all the frequency.