

USN										
-----	--	--	--	--	--	--	--	--	--	--



Internal Assessment Test 3 – March 2024

Sub:	Network Analysis					Sub Code:	BEC304	Branch:	ECE	
Date:	06/03/2024	Duration:	90 Minutes	Max Marks:	50	Sem/Sec:	3/A, B, C, D		OBE	
<u>Answer Any Five questions</u>								MARKS	CO	RBT


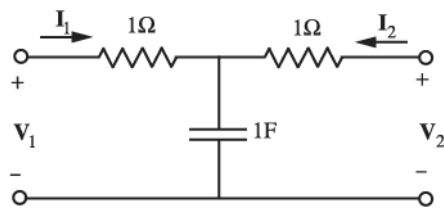


Fig 1

SOLUTION

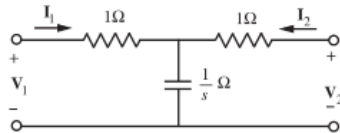The s domain equivalent circuit with the assumption that all the initial conditions are zero is shown in Fig. 7.47(a).



To find the parameters A and C , open-circuit the output port and connect a voltage source V_1 at the input port. The same is shown in Fig. 7.47(b).

$$I_1 = \frac{V_1}{1 + \frac{1}{s}} = \frac{sV_1}{s+1}$$

Then $V_2 = \frac{1}{s} I_1$

$$\Rightarrow V_2 = \frac{1}{s} \frac{sV_1}{s+1} = \frac{V_1}{s+1}$$

$$\Rightarrow A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = s+1$$

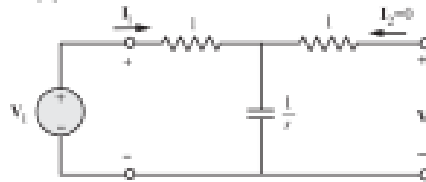


Figure 7.47(b)

Also, $V_2 = \frac{1}{s} I_1$

$$\Rightarrow C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = s$$

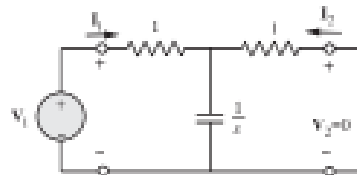


Figure 7.47(c)

To find the parameters B and D , short-circuit the output port and connect a voltage source V_1 to the input port as shown in Fig. 7.47(c).

The total impedance as seen by the source V_1 is

$$Z = 1 + \frac{\frac{1}{s} \times 1}{\frac{1}{s} + 1}$$

$$= 1 + \frac{1}{s+1} = \frac{s+2}{s+1}$$

$$I_1 = \frac{V_1}{Z} = \frac{V_1(s+1)}{(s+2)} \quad (7.44)$$

Using the principle of current division, we have

$$-I_2 = \frac{I_1 \left(\frac{1}{s} \right)}{\frac{1}{s} + 1} = \frac{I_1}{s+1} \quad (7.45)$$

Hence, $D = \left. \frac{I_1}{-I_2} \right|_{V_1=0} = s+1$

From equation (7.44) and (7.45), we can write

$$-I_2(s+1) = \frac{V_1(s+1)}{(s+2)}$$

Hence, $B = \left. \frac{-V_1}{I_2} \right|_{V_1=0} = s+2$

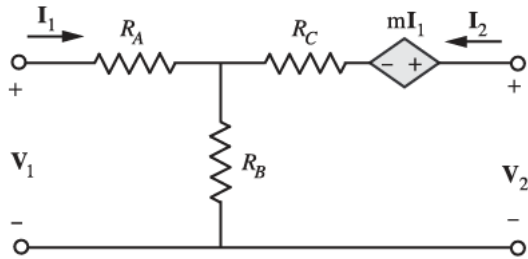


Fig 2

SOLUTION

To find the parameters **A** and **C**, open-circuit the output port as shown in Fig. 7.49(a) and connect a voltage source V_1 to the input port.

Applying KVL to the output mesh, we get

$$-V_2 + mI_1 + 0 \times R_C + I_1 R_A = 0$$

$$\Rightarrow V_2 = I_1 (m + R_A)$$

$$\text{Hence, } C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{m + R_A}$$

Applying KVL to the input mesh, we get

$$V_1 = I_1 (R_A + R_B)$$

$$\text{Hence, } A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{R_A + R_B}{m + R_A}$$

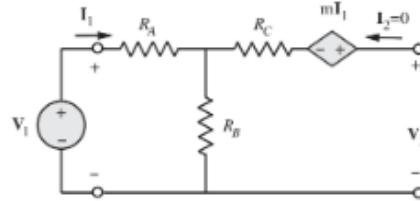


Figure 7.49(a)

To find the parameters **B** and **D**, short-circuit the output port and connect a voltage source V_1 to the input port as shown in Fig. 7.49(b).

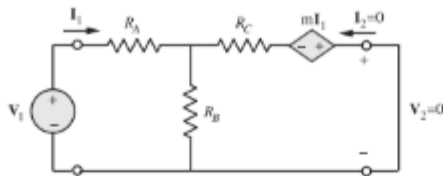


Figure 7.49(b)

Applying KVL to the right-mesh, we get

$$mI_1 + R_C I_2 + R_B (I_1 + I_2) = 0$$

$$\Rightarrow (m + R_B) I_1 = -(R_C + R_B) I_2$$

$$\Rightarrow I_1 = \frac{-(R_C + R_B)}{(m + R_B)} I_2$$

$$\text{Hence, } D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} = \frac{(R_C + R_B)}{(m + R_B)}$$

Applying KVL to the left-mesh, we get

$$-V_1 + R_A I_1 + R_B (I_1 + I_2) = 0$$

$$\begin{aligned} \Rightarrow V_1 &= (R_A + R_B) I_1 + R_B I_2 \\ &= (R_A + R_B) \left[\frac{-(R_C + R_B)}{(m + R_B)} I_2 \right] + R_B I_2 \\ &= - \left[\frac{R_C R_A + R_C R_B + R_B R_A - m R_B}{m + R_B} \right] I_2 \end{aligned}$$

$$\text{Hence, } B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} = \frac{R_C R_A + R_C R_B + R_B R_A - m R_B}{m + R_B}$$

Define Q factor, selectivity and band width. Prove that for a resonant circuit $f_0 = \sqrt{f_1 f_2}$, where f_1 and f_2 are two half power frequencies.

Q-factor (Quality Factor)

- Q factor is also known as figure of merit.
- In resonance circuit there are two storage elements i.e inductor (L) and capacitor (C). The efficiency at which these two energy storing elements store the energy is called quality factor.

Q factor is defined as

$$Q = 2\pi \frac{\text{Maximum energy stored per cycle}}{\text{Energy dissipated per cycle}}$$

Selectivity

It is defined by the equation:

$$\text{selectivity} = \frac{f_0}{\text{Bandwidth}} = \frac{f_0}{f_2 - f_1}$$

At resonance

$$\text{selectivity} = \frac{f_0}{R/2\pi L} = \frac{2\pi f_0 L}{R} = \frac{\omega_0 L}{R} \quad [\text{as } \omega_0 = 2\pi f_0]$$


$$\therefore \text{selectivity} = \frac{\omega_0 L}{R} = Q$$

$$\therefore \text{Selectivity} = \frac{f_0}{\text{BW}} = \frac{f_0}{f_2 - f_1} = \frac{\omega_0 L}{R} = Q$$

Low selectivity
Low Q
High selectivity
High Q.

Selectivity is defined as the ability of the resonating resonant circuit to distinguish or discriminate between desired and undesired frequencies.

Bandwidth and Selectivity:

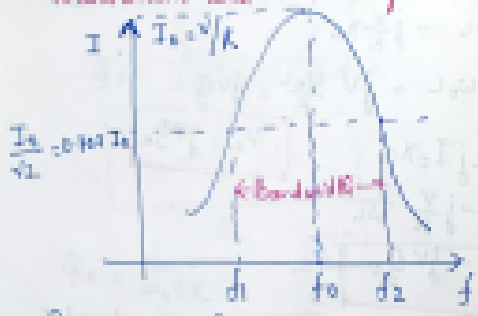

Power $P = I^2 R$

at resonance, $P = (I_0)^2 R = \left(\frac{V}{R}\right)^2 R = \frac{V^2}{R}$

At series resonance condition, power is maximum

Half power $\frac{P}{2} = \frac{I_0^2 R}{2} = \left(\frac{I_0}{\sqrt{2}}\right)^2 R$

Bandwidth is defined as range or band of frequencies at which power in the circuit is half of its maximum value of current is $\frac{1}{\sqrt{2}} = 0.707$ times of maximum current in the circuit.

i.e. $BW = (f_2 - f_1) Hz = \frac{R}{2\pi L}$

where f_2 is upper cut off frequency (or upper half power frequency) and f_1 is lower cut off frequency (or lower half power frequency)

Current in the series RLC circuit is given by

$$I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} \quad \text{--- (1)}$$

Also at resonance cut off frequency,

$I = \frac{I_0}{\sqrt{2}}$, where I_0 is maximum current

$$I = \frac{V}{R\sqrt{2}} \quad \text{--- (2)}$$

Equating (1) and (2)

$$\frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{V}{R\sqrt{2}}$$

$$\Rightarrow 2R^2 = R^2 + (X_L - X_C)^2$$

$$\Rightarrow R^2 = \left(\omega L - \frac{1}{\omega C}\right)^2$$

$$\text{On } \omega L - \frac{1}{\omega C} = \pm R. \quad \text{--- (3)}$$

At upper cut off frequency, f_2

$$R = \omega_2 L - \frac{1}{\omega_2 C} \quad \text{--- (4)}$$

At lower cut off frequency

$$-R = \omega_1 L - \frac{1}{\omega_1 C} \quad \text{--- (5)}$$

Adding (4) and (5)

$$\omega_2 L - \frac{1}{\omega_2 C} + \omega_1 L - \frac{1}{\omega_1 C} = R - R$$

$$\Rightarrow L(\omega_2 + \omega_1) - \frac{1}{C} \left(\frac{1}{\omega_2} + \frac{1}{\omega_1}\right) = 0$$

$$\Rightarrow L(\omega_2 + \omega_1) = \frac{1}{C} \left(\frac{\omega_1 + \omega_2}{\omega_1 \omega_2}\right)$$

$$L = \frac{1}{C} \times \frac{1}{\omega_1 \omega_2}$$

$$\Rightarrow \omega_1 \omega_2 = \frac{1}{LC}$$

$$\Rightarrow \omega_1 \omega_2 = \omega_0^2 \quad \left[\text{as } \omega_0^2 = \frac{1}{LC} \right]$$

$$\Rightarrow \boxed{f_1 f_2 = f_0^2}$$

\Rightarrow In series resonance circuit resonant frequency f_0 is geometrical mean of f_1 & f_2 .

9

a) Relation between Z and Y parameters

The two defining functions of Z parameters are

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)}$$

The two defining function of Y parameters

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (3)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (4)}$$

from eqn (3) $Y_{11} V_1 = I_1 - Y_{12} V_2$

$$V_1 = \frac{I_1}{Y_{11}} - \frac{Y_{12}}{Y_{11}} V_2 \quad \text{--- (5)}$$

from eqn (4) $Y_{22} V_2 = I_2 - Y_{21} V_1$

$$V_2 = \frac{I_2}{Y_{22}} - \frac{Y_{21}}{Y_{22}} V_1 \quad \text{--- (6)}$$

Substituting eqn (6) in eqn (5)

$$V_1 = \frac{I_1}{Y_{11}} - \frac{Y_{12}}{Y_{11}} \left(\frac{I_2}{Y_{22}} - \frac{Y_{21}}{Y_{22}} V_1 \right)$$

$$\text{or } V_1 = \frac{1}{Y_{11}} I_1 - \frac{Y_{12}}{Y_{11} Y_{22}} I_2 + \frac{Y_{12} Y_{21}}{Y_{11} Y_{22}} V_1$$

$$\Rightarrow V_1 - \frac{y_{12} y_{21}}{y_{11} y_{22}} V_1 = \frac{1}{y_{11}} I_1 - \frac{y_{12}}{y_{11} y_{22}} I_2 \quad (43)$$

$$\left(\frac{y_{11} y_{22} - y_{12} y_{21}}{y_{11} y_{22}} \right) V_1 = \frac{1}{y_{11}} \left[I_1 - \frac{y_{12}}{y_{22}} I_2 \right]$$

But $y_{11} y_{22} - y_{12} y_{21} = \Delta y$.

$$V_1 = I_1 \frac{y_{22}}{\Delta y} - \frac{y_{12}}{\Delta y} I_2 \quad (7)$$

By substituting eqn (5) in eqn (6).

$$\Rightarrow V_2 = \frac{1}{y_{22}} I_2 - \frac{y_{21}}{y_{22}} \left[\frac{I_1}{y_{11}} - \frac{y_{12}}{y_{11}} V_2 \right]$$

$$\text{or } V_2 - \frac{y_{21} y_{12}}{y_{22} y_{11}} V_2 = \frac{1}{y_{22}} I_2 - \frac{y_{21}}{y_{22} y_{11}} I_1$$

$$\text{or } V_2 \left(\frac{y_{22} y_{11} - y_{21} y_{12}}{y_{22} y_{11}} \right) = \frac{1}{y_{22}} \left[I_2 - \frac{y_{21}}{y_{11}} I_1 \right]$$

$$\text{or } V_2 = \frac{y_{11} I_2}{\Delta y} - \frac{y_{21}}{\Delta y} I_1$$

$$V_2 = -\frac{y_{21}}{\Delta y} I_1 + \frac{y_{11}}{\Delta y} I_2 \quad (8)$$

Comparing eqn (1) with eqn (7) and eqn (2) with eqn (8), we get

Z parameters in term of y parameters

$$Z = \begin{bmatrix} \frac{y_{22}}{\Delta y} & -\frac{y_{12}}{\Delta y} \\ -\frac{y_{21}}{\Delta y} & \frac{y_{11}}{\Delta y} \end{bmatrix} \Omega.$$

Relation between Z parameters and h parameters

The Z parameter equations are $V_1 = Z_{11} I_1 + Z_{12} I_2$ — (1)

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \text{ — (2)}$$

h-parameter equations are

$$V_1 = h_{11} I_1 + h_{12} V_2 \text{ — (3)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \text{ — (4)}$$

from eqn (4) $h_{22} V_2 = I_2 - h_{21} I_1$.

$$V_2 = \frac{1}{h_{22}} I_2 - \frac{h_{21}}{h_{22}} I_1 \text{ — (5)}$$

Substituting (5) in eqn (3)

$$V_1 = h_{11} I_1 + h_{12} \left[\frac{1}{h_{22}} I_2 - \frac{h_{21}}{h_{22}} I_1 \right]$$

$$\Rightarrow V_1 = I_1 \left[\frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} \right] + \frac{h_{12}}{h_{22}} I_2$$

$$\Rightarrow \boxed{V_1 = I_1 \left[\frac{\Delta h}{h_{22}} \right] + \frac{h_{12}}{h_{22}} I_2} \rightarrow \text{(6)}$$

from eqn (5) $V_2 = \frac{1}{h_{22}} I_2 - \frac{h_{21}}{h_{22}} I_1$

$$\text{Or } V_2 = -\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \text{ — (7)}$$

Comparing (1) with (6) and (2) with (7)

$$Z = \begin{bmatrix} \frac{\Delta h}{h_{22}} & \frac{h_{12}}{h_{22}} \\ -\frac{h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{bmatrix}$$

Find the y parameters of the two-port network shown in Fig 3. Then determine the current in a 4Ω load, that is connected to the output port when a $2A$ source is applied at the input port.

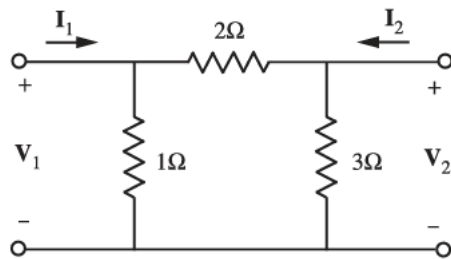


Fig 3

SOLUTION

To find y_{11} and y_{21} , short-circuit the output terminals and connect a current source I_1 to the input terminals. The resulting circuit diagram is shown in Fig. 7.8(a).

$$I_1 = \frac{V_1}{1\Omega \parallel 2\Omega} = \frac{V_1}{\frac{1 \times 2}{1+2}}$$

$$\Rightarrow I_1 = \frac{3}{2}V_1$$

Hence, $y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{3}{2}S$

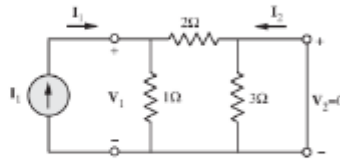


Figure 7.8(a)

Using the principle of current division,

$$-I_2 = \frac{I_1 \times 1}{1+2}$$

$$\Rightarrow -I_2 = \frac{1}{3}I_1$$

$$\Rightarrow -I_2 = \frac{1}{3} \left[\frac{3}{2}V_1 \right]$$

Hence, $y_{21} = \frac{I_2}{V_1} = \frac{-1}{2}S$

To find y_{12} and y_{22} , short the input terminals and connect a current source I_2 to the output terminals. The resulting circuit diagram is shown in Fig. 7.8(b).

$$I_2 = \frac{V_2}{2\Omega \parallel 3\Omega}$$

$$= \frac{V_2}{\frac{2 \times 3}{2+3}} = \frac{5V_2}{6}$$

Hence, $y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{5}{6}S$

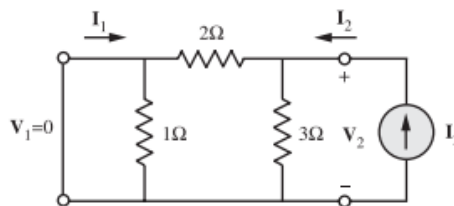


Figure 7.8(b)

Employing the current division principle,

$$-I_1 = \frac{I_2 \times 3}{2+3}$$

$$\Rightarrow -I_1 = \frac{3}{5}I_2$$

$$\Rightarrow -I_1 = \frac{3}{5} \left[\frac{5V_2}{6} \right]$$

$$\Rightarrow I_1 = \frac{-1}{2} V_2$$

Hence,
$$y_{12} = \frac{-I_1}{V_2} \Big|_{V_1=0} = \frac{-1}{2} S$$

Therefore, the equations that describe the two-port network are

$$I_1 = \frac{3}{2} V_1 - \frac{1}{2} V_2 \quad (7.3)$$

$$I_2 = -\frac{1}{2} V_1 + \frac{5}{6} V_2 \quad (7.4)$$

Putting the above equations (7.3) and (7.4) in matrix form, we get

$$\begin{bmatrix} \frac{3}{2} & \frac{-1}{2} \\ \frac{-1}{2} & \frac{5}{6} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Referring to Fig. 7.8(c), we find that $I_1 = 2A$ and $V_2 = -4I_2$

Substituting $I_1 = 2A$ in equation (7.3), we get

$$2 = \frac{3}{2} V_1 - \frac{1}{2} V_2 \quad (7.5)$$

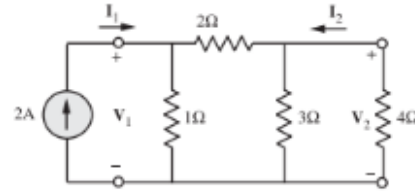


Figure 7.8(c)

Multiplying equation (7.4) by -4 , we get

$$\begin{aligned} & -4I_2 = 2V_1 - \frac{20}{6} V_2 \\ \Rightarrow & V_2 = 2V_1 - \frac{20}{6} V_2 \\ \Rightarrow & 0 = 2V_1 - \left(\frac{20}{6} + 1 \right) V_2 \\ \Rightarrow & 0 = \frac{-1}{2} V_1 + \frac{13}{12} V_2 \end{aligned} \quad (7.6)$$

Putting equations (7.5) and (7.6) in matrix form, we get

$$\begin{bmatrix} \frac{3}{2} & \frac{-1}{2} \\ \frac{-1}{2} & \frac{13}{12} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix}$$

It may be noted that the above equations are simply the nodal equations for the circuit shown in Fig. 7.8(c). Solving these equations, we get

$$V_2 = \frac{3}{2} V$$

$$I_2 = \frac{-1}{4} V_2 = \frac{-3}{8} A$$

and hence,

6

- A. Find the Laplace transform of the staircase waveform shown in Fig 4.
B. If this voltage were applied to an RL series circuit with $R=1\Omega$ and $L=1H$, find the current $i(t)$.

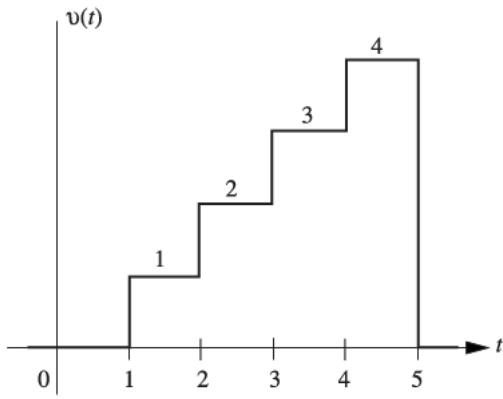


Fig 4

[10]

CO4

L3

SOLUTION

(a) We can express mathematically, the voltage waveform shown in Fig. 5.54 as,

$$v(t) = \begin{cases} 1, & 1 < t < 2 \\ 2, & 2 < t < 3 \\ 3, & 3 < t < 4 \\ 4, & 4 < t < 5 \\ 0, & \text{elsewhere} \end{cases}$$

or

$$\begin{aligned} v(t) &= [u(t-1) - u(t-2)] + 2[u(t-2) - u(t-3)] \\ &\quad + 3[u(t-3) - u(t-4)] + 4[u(t-4) - u(t-5)] \\ &= u(t-1) + u(t-2) + u(t-3) + u(t-4) - 4u(t-5) \end{aligned}$$

Taking the Laplace transform, we get

$$V(s) = \frac{1}{s} [e^{-s} + e^{-2s} + e^{-3s} + e^{-4s} - 4e^{-5s}]$$

(b) Assuming all initial conditions to be zero, the time domain circuit shown in Fig. 5.55 gets transformed to a circuit as shown in Fig. 5.56.

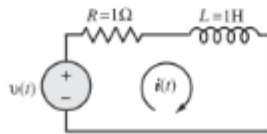


Figure 5.55 Time Domain Circuit

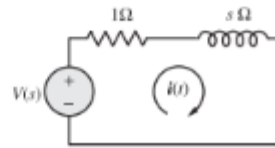


Figure 5.56 Frequency Domain Circuit

From Fig. 5.56, we can write

$$I(s) = \frac{V(s)}{s+1}$$

$$\begin{aligned} \Rightarrow I(s) &= \frac{1}{s(s+1)}e^{-s} + \frac{1}{s(s+1)}e^{-2s} + \frac{1}{s(s+1)}e^{-3s} + \frac{1}{s(s+1)}e^{-4s} - \frac{4}{s(s+1)}e^{-5s} \\ \Rightarrow I(s) &= \left[\left(\frac{1}{s} - \frac{1}{s+1} \right) e^{-s} + \left(\frac{1}{s} - \frac{1}{s+1} \right) e^{-2s} + \left(\frac{1}{s} - \frac{1}{s+1} \right) e^{-3s} \right. \\ &\quad \left. + \left(\frac{1}{s} - \frac{1}{s+1} \right) e^{-4s} - 4 \left(\frac{1}{s} - \frac{1}{s+1} \right) e^{-5s} \right] \end{aligned}$$

Taking the inverse Laplace transform, we get

$$\begin{aligned} i(t) &= [u(t) - e^{-t}u(t)]_{t-t-1} + [u(t) - e^{-t}u(t)]_{t-t-2} + [u(t) - e^{-t}u(t)]_{t-t-3} \\ &\quad + [u(t) - e^{-t}u(t)]_{t-t-4} - 4[u(t) - e^{-t}u(t)]_{t-t-5} \\ \Rightarrow i(t) &= [1 - e^{-(t-1)}] u(t-1) + [1 - e^{-(t-2)}] u(t-2) + [1 - e^{-(t-3)}] u(t-3) \\ &\quad + [1 - e^{-(t-4)}] u(t-4) - 4[1 - e^{-(t-5)}] u(t-5) \end{aligned}$$

Also find $\mathcal{L}\left\{\frac{dv(t)}{dt}\right\}$.

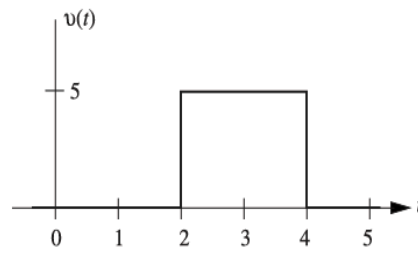


Fig 5

SOLUTION

The pulse shown in Fig. 5.37 is the gate function. This function may be regarded as a step function that switches on at $t = 2$ secs and switches off at $t = 4$ secs.

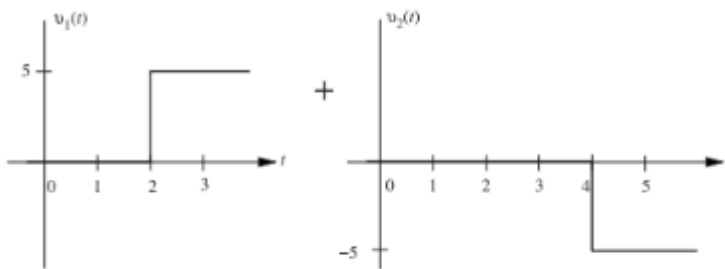


Figure 5.37(a)

Referring to Figs. 5.37 and 5.37 (a), we can write

$$\begin{aligned} v(t) &= v_1(t) + v_2(t) \\ \Rightarrow v(t) &= 5u(t-2) - 5u(t-4) \\ \text{Hence, } V(s) &= \frac{5}{s}e^{-2s} - \frac{5}{s}e^{-4s} \\ &= \frac{5}{s} [e^{-2s} - e^{-4s}] \end{aligned}$$

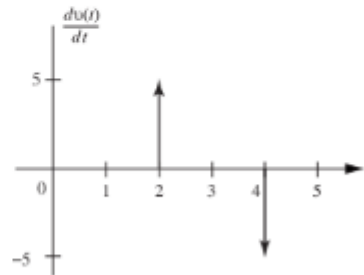


Figure 5.37(b)

Taking the derivative of $v(t)$, we get

$$\frac{dv(t)}{dt} = 5 [\delta(t-2) - \delta(t-4)]$$

Fig. 5.37(b) shows the graph of $\frac{dv(t)}{dt}$.

We can obtain Fig. 5.37(b) directly from Fig. 5.36 by observing that at $t = 2$ seconds, there is a sudden rise of 5V leading to $5\delta(t-2)$. Similarly, at $t = 4$ seconds, a sudden fall of 5V leading to $-5\delta(t-4)$.

We know the Laplace transform pair

$$\begin{aligned} \mathcal{L}\{\delta(t-a)\} &= e^{-as} \mathcal{L}\{\delta(t)\} \\ &= e^{-as} \end{aligned}$$

$$\text{Hence, } \mathcal{L}\left\{\frac{dv(t)}{dt}\right\} = 5 [e^{-2s} - e^{-4s}]$$

8 For the network shown in Fig 6., find $V_o(t)$, $t > 0$, using mesh analysis.

[10]

CO4

L3

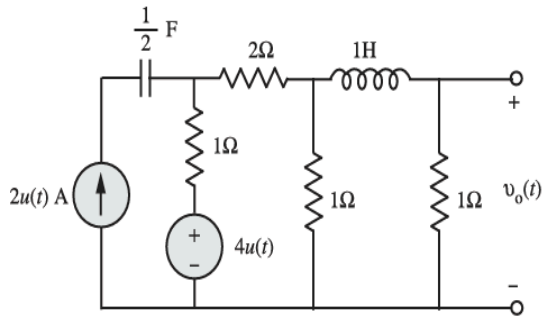


Fig 6

The step function $u(t)$ is defined as follows.

$$u(t) = \begin{cases} 1, & t \geq 0^+ \\ 0, & t \leq 0^- \end{cases}$$

Since the circuit is not energized for $t \leq 0^-$, there are no initial conditions in the circuit. For $t \geq 0^+$, the frequency domain equivalent circuit is shown in Fig. 5.29(b).

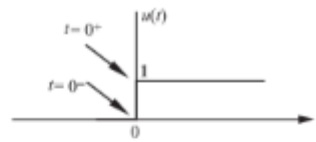


Figure 5.29(a)

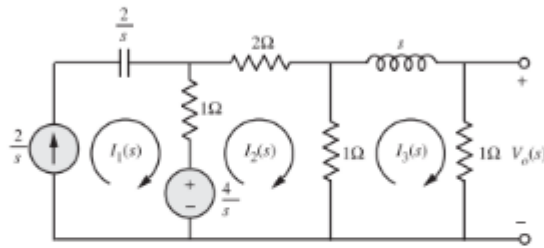


Figure 5.29(b)

By inspection, we find that $I_1(s) = \frac{2}{s}$

KVL clockwise for mesh 2:

$$\begin{aligned} \frac{-4}{s} + 1[I_2(s) - I_1(s)] + 2I_2(s) + 1[I_2(s) - I_3(s)] &= 0 \\ \Rightarrow \frac{-4}{s} - I_1(s) + I_2(s)[1 + 2 + 1] - I_3(s) &= 0 \end{aligned}$$

Substituting the value of $I_1(s)$, we get

$$\begin{aligned} \frac{-4}{s} + 4I_2(s) - I_3(s) &= \frac{2}{s} \\ \Rightarrow 4I_2(s) - I_3(s) &= \frac{6}{s} \end{aligned}$$

KVL clockwise for mesh 3:

$$\begin{aligned} 1[I_3(s) - I_2(s)] + sI_3(s) + 1I_3(s) &= 0 \\ \Rightarrow -I_2(s) + I_3(s)[s + 2] &= 0 \end{aligned}$$

Putting the KVL equations for mesh 2 and mesh 3 in matrix form, we get

$$\begin{bmatrix} 4 & -1 \\ -1 & s + 2 \end{bmatrix} \begin{bmatrix} I_2(s) \\ I_3(s) \end{bmatrix} = \begin{bmatrix} \frac{6}{s} \\ 0 \end{bmatrix}$$

Solving for $I_3(s)$, using Cramer's rule, we get

$$\begin{aligned} I_3(s) &= \frac{1.5}{s \left(s + \frac{7}{4} \right)} \\ \Rightarrow V_o(s) = I_3(s) \times 1 &= \frac{1.5}{s \left(s + \frac{7}{4} \right)} \end{aligned}$$

Using partial fractions, we can write

$$V_o(s) = \frac{K_1}{s} + \frac{K_2}{s + \frac{7}{4}}$$

We find that,

$$K_1 = \frac{6}{7}, \text{ and } K_2 = \frac{-6}{7}$$

Hence,

$$V_o(s) = \frac{6}{7} \left[\frac{1}{s} - \frac{1}{s + \frac{7}{4}} \right]$$

$$\Rightarrow v_o(t) = \frac{6}{7} [1 - e^{-\frac{7}{4}t}] u(t)$$

9	A series RLC circuit has a resistance of 10Ω , an inductance of 0.3H and a capacitance of $100\mu\text{F}$. The applied voltage is 230V . Find i) Resonant Frequency, ii) Quality Factor, iii) Lower and upper cut off frequencies, iv) Band width, v) current at resonance, vi) currents at f_1 and f_2 , vii) voltage across inductance at resonance.	[10]	CO5	L3
---	---	------	-----	----