



Third Semester B.E. Degree Examination, June/July 2024 Analog and Digital Electronics

Time: 3 hrs

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain the construction working and characteristics of Light Emitting Diode. (06 Marks)
- b. With a neat circuit diagram and Mathematical analysis explain fixed bias circuit. (07 Marks)
- c. Show how IC-555 timer can be used as Astable Multivibrator with Waveforms. (07 Marks)

OR

- 2 a. Discuss successive approximation register method of A to D converter with detailed conversion process. (08 Marks)
- b. With neat diagram and waveform, explain working of inverting Schmitt trigger circuit. (06 Marks)
- c. Explain Adjustable Voltage Regulator with diagram and suitable equations. (06 Marks)

Module-2

- 3 a. Simplify the following function using K-map and obtain simplified Boolean expressions:
 $f_1(a, b, c, d) = \sum m(0, 1, 2, 4, 5, 6, 8, 9, 10, 12, 13)$
 $f_2(a, b, c, d) = \sum m(1, 3, 5, 7, 9) + \sum d(6, 12, 13)$. (10 Marks)
- b. Simplify the following Boolean function by using Quine-Mcclusky (QM) method
 $F(A, B, C, D) = \sum m(0, 2, 3, 6, 7, 8, 10, 12, 13)$. Find all the prime implicants. (10 Marks)

OR

- 4 a. Minimize the following function using MEV technique, use 'd' a MEV variable
 $f(A, B, C, D) = \sum m(0, 1, 2, 7, 8, 9, 14, 15)$. (08 Marks)
- b. With an example, explain Petrik's method. (06 Marks)
- c. Solve the following clearly mention prime implicants and essential prime implicants
 $f(a, b, c, d) = \sum m(1, 5, 6, 7, 11, 12, 13, 15)$. (06 Marks)

Module-3

- 5 a. What are Hazards in digital systems? Explain static 1 and static - 0 hazards. (08 Marks)
- b. What is Multiplexer? Discuss 8 to 1 MUX with the help of logic diagram and equation. (06 Marks)
- c. Discuss the importance of three state buffer with example. (06 Marks)

OR

- 6 a. Show how using a 3 to 8 decoder and multiinput or gates following Boolean expressions can be realized simultaneously
 $F_1(A, B, C) = \sum m(0, 4, 6)$
 $F_2(A, B, C) = \sum m(0, 5)$
 $F_3(A, B, C) = \sum m(1, 2, 3, 7)$ (06 Marks)
- b. Realize $f(a, b, c, d) = \sum m(1, 5, 6, 10, 13, 14)$ using AND-OR logic with number of levels, Gates and Gate inputs. (06 Marks)
- c. Write a short note on PLA and PAL. (08 Marks)

Module-4

- 7 a. Discuss the operation of SR-Latch using NOR gates. Show how SR Latch can be used for switch debouncing. (08 Marks)
- b. Explain Gated SR-latch using NAND gate. (06 Marks)
- c. Differentiate between Latch and flip flop and explain the structure of VHDL program. (06 Marks)

OR

- 8 a. Explain the working operation of SR-flipflop and JK flip flop with truth table and waveforms. (08 Marks)
- b. Draw the logic diagram of master slave JK flip flop using NAND gates and explain the working with suitable timing diagram. (07 Marks)
- c. Discuss Toggle Flip Flop with truth table and characteristic equation. (05 Marks)

Module-5

- 9 a. Explain Parallel Adder with Accumulator with neat diagram and operation. (08 Marks)
- b. What is Register? Explain how 4 bit register with data load clear and clock constructed using D flip flops. (07 Marks)
- c. Discuss the operation of data transfer between Register. (05 Marks)

CMRIT LIBRARY
BANGALORE - 560 037

OR

- 10 a. Design the counter using D flip flop for the given sequence 0 - 3 - 2 - 6 - 4 - 7 - 0. (08 Marks)
- b. Explain synchronous Binary Counter with logical diagram and transition table. (06 Marks)
- c. Explain the working of 8 bit serial - in - serial - out shift register using SR flip flop. (06 Marks)
