 


CBCS SCHEME

21CS33

USN

--	--	--	--	--	--	--	--	--	--



Third Semester B.E. Degree Examination, June/July 2024 Analog and Digital Electronics

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- a. With a neat circuit diagram and mathematical analyses explain voltage divider bias circuit. (10 Marks)
b. With a neat circuit diagram explain the working of relaxation oscillator. (10 Marks)

OR

- a. List the advantages of active filters over passive filters. (05 Marks)
b. Explain any two performance parameters of power supply. (05 Marks)
c. Explain R-2R ladder type D to A converter. (10 Marks)

Module-2

- a. Simplify the following expression using K-Map and draw the logic circuit using basic gates. $F(A, B, C, D) = \sum m(7) + \sum d(10, 11, 12, 13, 14, 15)$. (10 Marks)
b. Simplify the expression using Quine-McClusky method $F(A, B, C, D) = \sum m(0, 2, 3, 6, 7, 8, 10, 12, 13)$. (10 Marks)

OR

- a. Using K-Map obtain SOP and POS expressions for $f(A, B, C, D) = \sum m(6, 8, 9, 10, 11, 12, 13, 14, 15)$. (10 Marks)
b. With example explain,
i) Map-Entered variable method
ii) Petricks method. (10 Marks)

Module-3

- a. What is Hazard? With example explain static-0 and static-1 Hazards. (10 Marks)
b. Implement following function using 8:1 multiplexer:
 $f(a, b, c, d) = \sum m(0, 1, 5, 6, 8, 10, 12, 15)$. (10 Marks)

OR

- a. Implement full adder using 3:8 decoder and NAND gates. (10 Marks)
b. Design 7-segment decoder using PLA. (10 Marks)

Module-4

- a. What are the 3 modeling styles in VHDL? Write VHDL code for full adder using structural model. (10 Marks)
b. Derive the characteristics equations for D, T, SR and JK flip flops. (10 Marks)

OR

- 8 a. Draw the logic diagram of master slave JK flipflop using NAND gates and explain its working. (10 Marks)
- b. Explain the working of SR flipflop and show how it can be used in debounce circuit. (10 Marks)

Module-5

- 9 a. What is shift register? What are the different types of shift registers? Explain 8 bit serial-in serial-out shift register. (10 Marks)
- b. Explain the following:
- i) Sequential Parity Checker
 - ii) Ring Counter.

CMRIT LIBRARY
BANGALORE - 560 037

(10 Marks)

OR

- 10 a. Design Mod-5 synchronous counter using JK flip flop. (10 Marks)
- b. With diagram explain parallel adder with accumulator. (10 Marks)
