

CBCS SCHEME



18EC72

Seventh Semester B.E. Degree Examination, June/July 2024 VLSI Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define Moore's law. (02 Marks)
- b. Consider the design of a CMOS compound OR-OR-AND invert gate computing $F = \overline{(A + B) \cdot (C + D)}$.
 - (i) Sketch a transistor level schematic
 - (ii) Sketch a stick diagram
 - (iii) Estimate area from a stick diagram. (10 Marks)
- c. Derive the transfer characteristics of CMOS Inverter (graphical). (08 Marks)

OR

- 2 a. Explain all the non-ideal effects in MOS transistor. (10 Marks)
- b. With neat sketches explain the operation of MOSFET and derive the equation for drain current in all the regions. (10 Marks)

Module-2

- 3 a. Explain VLSI design flow. (10 Marks)
- b. What is scaling? What are types of scaling and write scaling factors for device parameters? (10 Marks)

OR

- 4 a. Draw the schematic and layout of two input NAND gate. (06 Marks)
- b. Explain layout design rules for well, transistor rule and metal rules. (08 Marks)
- c. Define terms: (i) Metallization (ii) Passivation (iii) Metrology (06 Marks)

Module-3

- 5 a. Explain Elmore delay model. (03 Marks)
- b. Define logical effort. Write the logical efforts of common gates. (10 Marks)
- c. Estimate the delay of the Fanout - of - 4 (FO4) inverter shown in Fig.Q5(c). Assume the inverter is constructed in a 180 nm process with $\tau = 15$ ps.

 


Fig.Q5(c)

(07 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 6 a. What is Ratioed logic? Explain following ratioed logic circuits:
 (i) Pseudo nMOS
 (ii) Ganged CMOS
 (iii) Source follower pull-up logic (12 Marks)
- b. Explain Cascade Voltage Switch Logic (CVSL). Realize the input AND/NAND using CVSL. (08 Marks)

Module-4

- 7 a. Explain the general structure of ratioed synchronous dynamic circuits. (05 Marks)
- b. With necessary circuit diagram, explain dynamic shift register (ratioless) with enhancement load. (08 Marks)
- c. What are the advantages of dynamic CMOS logic and explain the working of dynamic CMOS inverter. (07 Marks)

OR

- 8 a. Write the basic building block of a CMOS transmission gate dynamic shift register. (04 Marks)
- b. With generalized circuit diagram, explain domino CMOS logic and using the same realize the following Boolean function: $Z = AB + (C + D)(E + F) + GH$ (11 Marks)
- c. With necessary diagram, explain a D flipflop with two phase non-overlapping clocks. (05 Marks)

Module-5

- 9 a. With neat circuit diagram, explain full CMOS SRAM cell. (08 Marks)
- b. Draw the circuit of 3-bit BIST register and explain. (06 Marks)
- c. Explain the terms: (i) Observability (ii) Fault coverage (iii) Controllability (06 Marks)

OR

- 10 a. With necessary circuit diagram, explain the operation of three transistor DRAM cell. (08 Marks)
- b. What is a fault model? Explain stuck-at model with examples. (07 Marks)
- c. Explain the logic verification principles. (05 Marks)

* * * * *