



**Fourth Semester B.E. Degree Examination, June/July 2024**  
**Analog Circuits**

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

**Module-1**

- 1 a. Explain the design concept of common emitter collector to Base feedback resistor biasing circuit and explain how collector to base feedback resistor provides a negative feedback in the circuit. (07 Marks)
- b. Considering the conceptual circuit of common source MOSFET amplifier, derive the expression for transconductance  $g_m$  and voltage gain  $A_v$ . (08 Marks)
- c. For common emitter voltage divider circuit having  $\beta = 100$ ,  $R_1 = 10 \text{ K}\Omega$ ,  $R_2 = 5 \text{ K}\Omega$ ,  $R_C = 1 \text{ K}\Omega$  and  $R_E = 500 \Omega$  is provided with DC biasing voltage  $V_{CC} = 10 \text{ V}$ , Calculate  $V_{CE}$  and  $I_C$ . (05 Marks)

**OR**

- 2 a. Derive an expression for small signal collector current, transconductance  $g_m$  and voltage gain  $A_v$  in BJT, when small signal  $V_{bc}$  is applied between base and emitter. (10 Marks)
- b. Design voltage divider bias circuit using MOSFET to establish  $I_D = 0.5 \text{ mA}$  and MOSFET parameter are  $V_t = 1 \text{ V}$  and  $K'_n \left(\frac{W}{L}\right) = 0.5 \text{ mA/V}^2$ . Assume  $V_{DD} = 15 \text{ V}$ . (10 Marks)

**Module-2**

- 3 a. Explain Three basic configurations of MOSFET amplifier and derive expression for characteristic parameter of amplifiers. (08 Marks)
- b. Briefly explain the Barkhausen criteria for oscillation. (04 Marks)
- c. For an n-channel MOSFET with  $t_{ox} = 10 \text{ nm}$ ,  $L = 1 \mu\text{m}$ ,  $W = 10 \mu\text{m}$ ,  $L_{ov} = 0.05 \mu\text{m}$ ,  $C_{sbo} = C_{dbo} = 10 \text{ fF}$ ,  $V_O = 0.6 \text{ V}$ ,  $V_{SB} = 1 \text{ V}$ ,  $V_{DS} = 2 \text{ V}$ . Calculate the following capacitance when the transistor is operating in saturation,  
 (i)  $C_{OX}$       (ii)  $C_{OV}$       (iii)  $C_{gs}$       (iv)  $C_{gd}$       (v)  $C_{sb}$  and  $C_{db}$ .  
 Consider  $\epsilon_{ox} = 3.45 \times 10^{-11}$  (08 Marks)

**OR**

- 4 a. Explain the working of RC phase shift oscillator and show how RC network provides  $180^\circ$  of phase shift. (08 Marks)
- b. In a transistor Colpitts oscillator  $C_1 = 1 \text{ nF}$  and  $C_2 = 1000 \text{ nF}$ . Find the value of L for a frequency of  $100 \text{ kHz}$ . (04 Marks)
- c. Explain the High frequency response of common source MOSFET amplifier with its equivalent circuit. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.

Module-3

- 5 a. Explain the effect of negative feedback on input and output resistance of voltage series feedback amplifier. (10 Marks)
- b. Explain transformer coupled Class A power amplifier and show that the maximum efficiency of transformer coupled Class A power amplifier is 50%. (10 Marks)

OR

- 6 a. Draw the block diagram of four types of feedback topologies and compare them with respect to input and output resistance. (10 Marks)
- b. Compare Class B pushpull and complementary symmetry power amplifiers. (04 Marks)
- c. In a Class B push pull amplifier operating with  $V_{CC} = 25V$  provides a 22 V peak signal to an  $8 \Omega$  load. Find  
 (i) Peak load current (ii) dc current drawn from the supply (iii) input power  
 (iv) Output current efficiency (v) power dissipation (06 Marks)

Module-4

- 7 a. State the ideal op-amp characteristics. (06 Marks)
- b. Design a linear combination circuit using op-amp to obtain output  $V_0 = -2V_1 - 8V_2 - V_3$  with  $R_m \geq 20k\Omega$  at all the inputs and all the resistances  $\leq 200 k\Omega$  (04 Marks)
- c. Draw the circuit of 3 op-amp instrumentation amplifier and derive the expression for its output voltage. (10 Marks)

OR

- 8 a. Explain the working of voltage follower using op-amp and show that its gain is unity. State its advantages. (06 Marks)
- b. Explain the working of zero crossing detectors. (06 Marks)
- c. Design an inverting Schmitt trigger to have trigger voltages of  $\pm 4V$  using op-amp 741 with supply of  $\pm 15V$ . Consider  $I_{B(max)} = 500 \mu A$ . (08 Marks)

Module-5

- 9 a. With neat circuit diagram, explain the operation of R-2R D/A converter. (10 Marks)
- b. Explain the working of pulse width modulation circuit using 555 IC. (06 Marks)
- c. Design a low pass filter using op-amp at a cut off frequency of 1 kHz with pass gain of 2 and choose  $C = 0.01 \mu F$  (04 Marks)

OR

**CMRIT LIBRARY**  
BANGALORE - 560 037

- 10 a. Explain with neat circuit diagram the working of positive precision Half Wave Rectifier. (06 Marks)
- b. Design a monostable 555 timer circuit to produce an output pulse of 10 sec wide and draw the circuit diagram. Choose  $C = 100 \mu F$ . (04 Marks)
- c. Draw the circuit of second order low pass filter and explain its operation. (10 Marks)

\* \* \* \* \*