



USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, June/July 2024

## Digital System Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- Design a combinational logic circuit so that an output is generated indicating when a majority of four inputs is true. (06 Marks)
  - Place the following equations into the proper canonical form
    - $f(w, x, y, z) = \bar{w}x + y\bar{z}$
    - $f(A, B, C, D) = A + \bar{B} + C)(\bar{A} + D)$(06 Marks)
  - Using K-map determine minimal sum of product expressions and implement the simplified equation using only NAND gates  $f(w, x, y, z) = \sum m(1, 2, 3, 4, 9) + \sum d(10, 11, 12, 13, 14, 15)$  (08 Marks)

OR

- Define the following terms literal, canonical sum of products, Karnaugh Map, Prime implicants. (04 Marks)
  - Find the minimal sum of the following Boolean function using Quine McClusky method  $f(w, x, y, z) = \sum(1, 3, 13, 15) + \sum d(8, 9, 10, 11)$  (08 Marks)
  - Using K-map determine minimal product of sum expression and implement the simplified equation using only NOR gates  $f(a, b, c, d) = \pi M(0, 4, 5, 7, 8, 9, 11, 12, 13, 15)$ . (08 Marks)

### Module-2

- Implement following multiple output function using 74LS138 decoder
$$F_1(A, B, C) = \sum m(1, 4, 5, 7)$$
$$F_2(A, B, C) = \pi m(2, 3, 6, 7)$$
(06 Marks)
  - Explain 4-bit carry look ahead adder with necessary diagram and relevant expression. (10 Marks)
  - Implement  $f(a, b, c, d) = \sum m(0, 1, 5, 6, 7, 9, 10, 15)$  using 8 : 1 MUX with a, b, c as select lines (04 Marks)

OR

- Implement full adder using 74138 decoder. (06 Marks)
  - Design a 2-bit Magnitude comparator. (08 Marks)
  - Design 4-line to 2 line priority uncoder which gives MSB the highest priority and LSB least priority. (06 Marks)

### Module-3

- What is race around condition? Explain JK master slave flip-flop with diagram function table and timing diagram. (08 Marks)
  - Explain the working of 4-bit Johnson counter using necessary diagram and waveform. (06 Marks)
  - Explain with a neat diagram and truth table, a 4-bit SIPO shift register to store binary number 1010. (06 Marks)

OR

- 6 a. Explain the operation of switch debouncer using SR latch with the help of circuit and waveform. (06 Marks)
- b. Explain the working of 3-bit Asynchronous up-down counter with necessary waveform and truth table. (10 Marks)
- c. Write the difference between combinational circuits and sequential circuits. (04 Marks)

Module-4

- 7 a. Design a synchronous Mod -6 counter using clocked D- Flip-Flop. (10 Marks)
- b. Design a Moore type sequence detector to detect a serial input sequence of 101. (10 Marks)

OR

- 8 a. Construct the excitation table, transition table and state diagram for the sequential circuit shown in Fig Q8(a).

 


Fig Q8(a)

- b. Design a synchronous decade counter using T-flip flop and draw the logic diagram. (10 Marks)

Module-5

- 9 a. List the guidelines for construction of state graphs. (10 Marks)
- b. Design a sequential circuit to convert BCD to excess - 3 code with state table state graph and transition table. (10 Marks)

OR

- 10 a. Explain with block diagram design of serial Adder with accumulator. (10 Marks)
- b. Explain with block diagram design of Binary multiplier. (10 Marks)

\*\*\*\*\*