

Internal Assessment Test - I

Sub:	Microwaves and Antennas	Code:	21EC62
Date:	3/6/2024	Duration:	90 mins
		Max Marks:	50
		Sem:	6th
		Branch:	ECE
Answer Any FIVE FULL Questions			


		Marks	OBE	
			CO	RBT
1.	With the help of a suitable diagram, derive the expression for the instantaneous voltage and current on a two wire transmission line.	[10]	CO1	L2
2.	A transmission line has the following primary constants per km of the line: $R=8\Omega/m$, $G=0.1\mu S/m$, $L=3.5mH/m$, $C=9nF/m$. Calculate Z_0 , α , β , v_p and γ at $\omega=5000$ rad/sec.	[10]	CO1	L2
3.	Define and derive an expression for reflection coefficient and standing wave ratio when the transmission line is terminated by load impedance (Z_L).	[10]	CO1	L3
4.	A load impedance of $Z_L=60-j80 \Omega$ is required to be matched to a 50Ω coaxial line, by using short circuited stub of length 'l' located at a distance 'd' from the load. The wavelength of operation is 1m. Design the single stub impedance matching system using Smith Chart.	[10]	CO1	L3
5.	Give detailed construction of the Smith chart with suitable diagrams.	[10]	CO1	L2,L3
6.	The characteristic impedance of a uniform transmission line is 2040Ω at a frequency of 800Hz. At this frequency the propagation constant was found to be $0.054 \angle 87.9^\circ$. Determine the values of the line constants R, L, G and C.	[10]	CO1	L3

Internal Assessment Test - I

Sub:	Microwaves and Antennas	Code:	21EC62
Date:	3/6/2024	Duration:	90 mins
		Max Marks:	50
		Sem:	6th
		Branch:	ECE
Answer Any FIVE FULL Questions			

		Marks	OBE	
			CO	RBT
1.	With the help of a suitable diagram, derive the expression for the instantaneous voltage and current on a two wire transmission line.	[10]	CO1	L2
2.	A transmission line has the following primary constants per km of the line: $R=8\Omega/m$, $G=0.1\mu S/m$, $L=3.5mH/m$, $C=9nF/m$. Calculate Z_0 , α , β , v_p and γ at $\omega=5000$ rad/sec.	[10]	CO1	L2
3.	Define and derive an expression for reflection coefficient and standing wave ratio when the transmission line is terminated by load impedance (Z_L).	[10]	CO1	L3
4.	A load impedance of $Z_L=60-j80 \Omega$ is required to be matched to a 50Ω coaxial line, by using short circuited stub of length 'l' located at a distance 'd' from the load. The wavelength of operation is 1m. Design the single stub impedance matching system using Smith Chart.	[10]	CO1	L3
5.	Give detailed construction of the Smith chart with suitable diagrams.	[10]	CO1	L2,L3
6.	The characteristic impedance of a uniform transmission line is 2040Ω at a frequency of 800Hz. At this frequency the propagation constant was found to be $0.054 \angle 87.9^\circ$. Determine the values of the line constants R, L, G and C.	[10]	CO1	L3

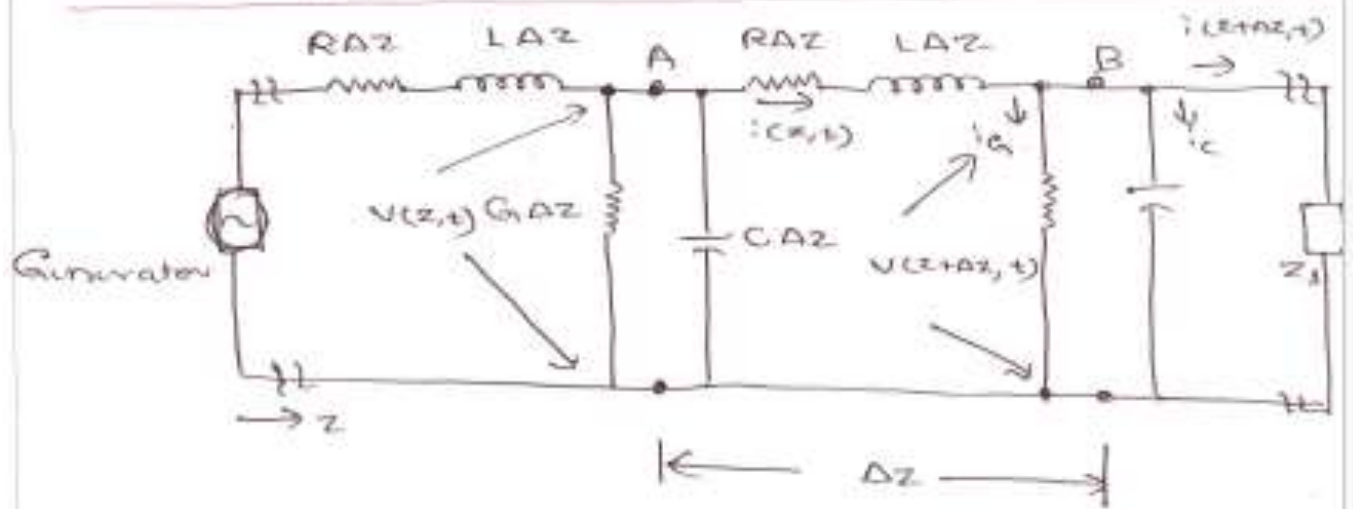Transmission Lines Equations and Solution



Elementary section of a transmission line.

By Kirchhoff's Voltage law, the summation of the voltage drops around the central loop is given by

$$\begin{aligned}
 V(z,t) &= R\Delta z i(z,t) + L\Delta z \frac{\partial i(z,t)}{\partial t} \\
 &\quad + V(z+\Delta z,t) \\
 &= R\Delta z i(z,t) + L\Delta z \frac{\partial i(z,t)}{\partial t} \\
 &\quad + V(z,t) + \frac{\partial V(z,t)}{\partial z} \Delta z \quad (1)
 \end{aligned}$$

Rearranging this equation, dividing it by Δz , and then omitting the argument (z,t) which is understood, we get

$$\left[-\frac{\partial V}{\partial z} - R i + i \frac{\partial z}{\partial t} \right] \quad (5)$$

Using Kirchoff's Current law, the summation of the currents at point B can be expressed as

$$i(z,t) = G \Delta z V(z+\Delta z, t) + C \frac{\partial V(z+\Delta z, t)}{\partial t} + i(z+\Delta z, t)$$

$$= G \Delta z \left[V(z, t) + \frac{\partial V(z, t)}{\partial z} \Delta z \right]$$

$$+ C \Delta z \frac{\partial}{\partial t} \left[V(z, t) + \frac{\partial V(z, t)}{\partial z} \Delta z \right]$$

$$+ i(z,t) + \frac{\partial i(z,t)}{\partial z} \Delta z \quad (3)$$

$$- G \Delta z V(z, t) + G$$

$$0 = G V(z, t) + G \frac{\partial V(z, t)}{\partial z} \Delta z + C \frac{\partial V(z, t)}{\partial t}$$

$$+ C \frac{\partial}{\partial t} \left[\frac{\partial V(z, t)}{\partial z} \Delta z \right]$$

$$+ \frac{\partial i(z, t)}{\partial z} \Delta z$$

$$\Rightarrow \left[-\frac{\partial i}{\partial z} = G V + C \frac{\partial V}{\partial t} \right] \quad (4)$$

Differentiating Eq. (2) w.r.t. z we get

$$-\frac{\partial^2 V}{\partial z^2} = R \frac{\partial i}{\partial z} + L \frac{\partial}{\partial t} \left(\frac{\partial i}{\partial z} \right) \quad (5)$$

Differentiating Eq. (4) w.r.t. t we get

$$-\frac{\partial}{\partial t} \left(\frac{\partial i}{\partial z} \right) = G \frac{\partial V}{\partial t} + C \frac{\partial^2 V}{\partial t^2} \quad (6)$$

Substituting equations (4) & (6) in Eq. (5)

we get

$$\begin{aligned} -\frac{\partial^2 V}{\partial z^2} &= R \left(-GV - C \frac{\partial V}{\partial t} \right) \\ &+ L \left(-G \frac{\partial V}{\partial t} - C \frac{\partial^2 V}{\partial t^2} \right) \\ &= -RGV - RC \frac{\partial V}{\partial t} - LG \frac{\partial V}{\partial t} \\ &\quad - LC \frac{\partial^2 V}{\partial t^2} \end{aligned}$$

$$\boxed{\frac{\partial^2 V}{\partial z^2} = RGV + (RC + LG) \frac{\partial V}{\partial t} + LC \frac{\partial^2 V}{\partial t^2}} \quad (6)$$

~~Also~~ Differentiating Eq. (2) w.r.t. t

we get

$$-\frac{\partial}{\partial t} \left(\frac{\partial V}{\partial z} \right) = R \frac{\partial i}{\partial t} + L \frac{\partial^2 i}{\partial t^2} \quad (7)$$

EMR

Differentiating Eq. (4) w.r.t z we get

$$-\frac{\partial^2 i}{\partial z^2} = G \frac{\partial v}{\partial z} + C \frac{\partial}{\partial z} \left(\frac{\partial v}{\partial t} \right) \quad (8)$$

Substituting Eqs (2), (4) in Eq. (8) we get

$$\begin{aligned} -\frac{\partial^2 i}{\partial z^2} &= G \left(-Ri - L \frac{\partial i}{\partial t} \right) \\ &+ C \left[-R \frac{\partial i}{\partial t} - L \frac{\partial^2 i}{\partial t^2} \right] \\ &= -RGi - LG \frac{\partial i}{\partial t} - RC \frac{\partial i}{\partial t} - LC \frac{\partial^2 i}{\partial t^2} \end{aligned}$$

$$\therefore \frac{\partial^2 i}{\partial z^2} = RGi + (LG + RC) \frac{\partial i}{\partial t} + LC \frac{\partial^2 i}{\partial t^2} \quad (9)$$

The voltage and current on the line are the functions of both position z and time t .

The instantaneous line voltage and current can be expressed as

$$v(z, t) = \operatorname{Re} V(z) e^{j\omega t} \quad (10)$$

$$i(z, t) = \operatorname{Re} I(z) e^{j\omega t} \quad (11)$$

where Re stands for "real part of".

The factors $V(z)$ and $I(z)$ are complex quantities of the sinusoidal functions of position z on the line and are known as phase

If we substitute $j\omega$ for $\frac{\partial}{\partial t}$ in equations (2), (4), (6) and (8) and divide each equation by $e^{j\omega t}$, the transmission-line equations in phasor form of the frequency domain become

$$\begin{aligned} \frac{dV}{dz} &= -(R + j\omega L) I \\ &= -Z I \end{aligned} \quad (12)$$

$$\begin{aligned} \frac{dI}{dz} &= -(G + j\omega C) V \\ &= -Y V \end{aligned} \quad (13)$$

$$\frac{d^2 V}{dz^2} e^{j\omega t} = RG V e^{j\omega t} + (RC + LG) j\omega V e^{j\omega t}$$

$$+ LC (j\omega)^2 V e^{j\omega t}$$

$$\begin{aligned} \frac{d^2 V}{dz^2} &= RG V + (RC + LG) j\omega V \\ &\quad + LC (j\omega)^2 V \end{aligned}$$

$$= \left[RG + RCj\omega + LGj\omega + LC(j\omega)^2 \right] V$$

$$= \left[R(G + j\omega C) + j\omega L(G + j\omega C) \right] V$$

$$= (R + j\omega L)(G + j\omega C) V$$

$$= ZY V$$

$$\frac{d^2 V}{dz^2} = r^2 V \quad (14)$$

$$\frac{d^2 I}{dz^2} = r^2 I \quad (15)$$

In which the following substitutions have been made:

$$Z = R + j\omega L \quad (\text{ohms per unit length}) \quad (16)$$

$$Y = G + j\omega C \quad (\text{ohms per unit length})$$

$$\gamma = \sqrt{ZY} = \alpha + j\beta \quad (\text{propagation constant})$$

α is the attenuation constant in nepers per unit length

β is the phase constant in radians per unit length

Solutions to Transmission Line Equations

The one possible solution for Eq. (14) is

$$\begin{aligned} V &= V_+ e^{-\gamma z} + V_- e^{\gamma z} \\ &= V_+ e^{-\alpha z} e^{-j\beta z} + V_- e^{\alpha z} e^{j\beta z} \end{aligned} \quad (17)$$

The factors V_+ and V_- represent complex quantities.

Problems

USN I C R

INTERNAL TEST

Instructor



1) A transmission line has the following parameters

$$\begin{array}{lll}
 R = 2 \Omega/\text{m} & G = 0.5 \text{ mS}/\text{m} & f = 1 \text{ GHz} \\
 0.2 \Omega/\text{m} & 0.5 \text{ mS}/\text{m} & 1.0 \text{ GHz} \\
 L = 8 \text{ nH}/\text{m} & C = 0.23 \text{ pF}/\text{m} & \\
 8.01 \text{ nH}/\text{m} & 0.23 \text{ pF}/\text{m} &
 \end{array}$$

Calculate: (a) the characteristic impedance;
(b) the propagation constant.

(a)

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$= \sqrt{\frac{2 + j 2\pi \times 1 \times 10^9 \times 8 \times 10^{-9}}{0.5 \times 10^{-3} + j 2\pi \times 1 \times 10^9 \times 0.23 \times 10^{-12}}}$$

$$= \sqrt{\frac{50.3 \angle 87.72^\circ}{1.529 \times 10^3 \angle 70.91^\circ}}$$

$$= 181.37 \angle 8.40^\circ$$

$$= 179.42 + j 26.49$$

$$154.01 \angle 10.45^\circ$$

(b)

$$\Gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= \sqrt{(50.3 \angle 87.72^\circ)(1.529 \times 10^3 \angle 70.91^\circ)}$$

$$= 0.2774 \angle 79.31^\circ$$

$$= 0.051 + j 0.272$$

$$= 0.0694 \angle 10.45^\circ$$

Reflection Coefficient and Transmission Coefficient

Reflection Coefficient

- We know that, in the equations of the solutions of transmission-line equations, the traveling wave along the line contains two components: one travelling in the positive z direction and the other travelling in the negative z direction.
- If the load impedance is equal to the line characteristic impedance, the reflected wave does not exist.

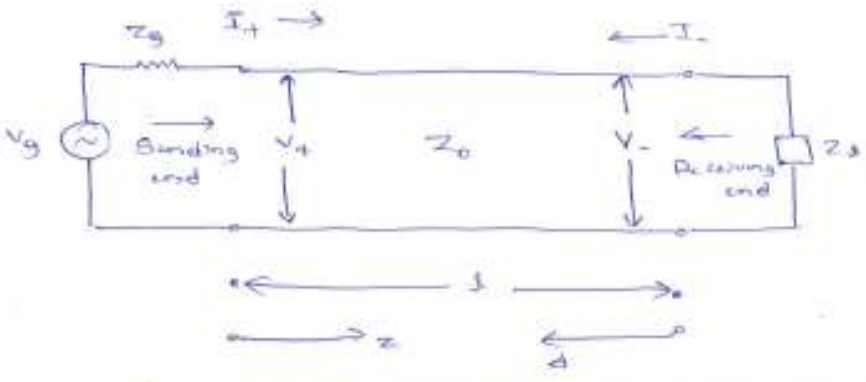


Fig: Transmission line terminated in a load impedance

The incident voltage and current waves travelling along the transmission line are given by

$$V = V_+ e^{-\gamma z} + V_- e^{+\gamma z} \quad (1)$$

$$I = \frac{V_+}{Z_0} e^{-\gamma z} - \frac{V_-}{Z_0} e^{+\gamma z} \quad (2)$$

The voltage and current at the load end are

$$V_d = V_+ e^{-\gamma d} + V_- e^{+\gamma d} \quad (3)$$

$$I_d = \frac{1}{Z_0} (V_+ e^{-\gamma d} - V_- e^{+\gamma d}) \quad (4)$$

$$Z_d = \frac{V_d}{I_d} = Z_0 \left[\frac{V_+ e^{-\gamma d} + V_- e^{+\gamma d}}{V_+ e^{-\gamma d} - V_- e^{+\gamma d}} \right] \quad (5)$$

Reflection coefficient = $\frac{\text{reflected voltage or current}}{\text{incident voltage or current}}$

$$\Gamma \equiv \frac{V_{refl}}{V_{inc}} = \frac{-I_{refl}}{I_{inc}} \quad (6)$$

$$\Gamma = \frac{V_- e^{+\gamma d}}{V_+ e^{-\gamma d}}$$

Solving eq (5) for $\frac{V_- e^{\gamma d}}{V_+ e^{-\gamma d}}$ we get

$$\frac{Z_L}{Z_0} = \frac{V_+ e^{-\gamma d} + V_- e^{\gamma d}}{V_+ e^{-\gamma d} - V_- e^{\gamma d}}$$

$$= \frac{1 + \frac{V_- e^{\gamma d}}{V_+ e^{-\gamma d}}}{1 - \frac{V_- e^{\gamma d}}{V_+ e^{-\gamma d}}}$$

$$= \frac{1 + \Gamma_L}{1 - \Gamma_L}$$

$$\Rightarrow Z_L (1 - \Gamma_L) = Z_0 (1 + \Gamma_L)$$

$$Z_L - Z_L \Gamma_L = Z_0 + Z_0 \Gamma_L$$

$$Z_L - Z_0 = Z_L \Gamma_L + Z_0 \Gamma_L = (Z_L + Z_0) \Gamma_L$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma_L = |\Gamma_L| e^{j\theta_L}$$

$|\Gamma_L|$ is the magnitude, $|\Gamma_L| \leq 1$

θ_L is the phase angle between incident and reflected voltages at the receiving end. Usually called the phase angle of the reflection coefficient.

Standing-Wave Ratio

The ratio of the maximum of the standing-wave pattern to the minimum is defined as the standing-wave ratio, designated by ρ .

i.e.,

Standing-wave ratio

$$= \frac{\text{maximum Voltage or Current}}{\text{minimum Voltage or Current}}$$

$$\rho = \frac{|V_{\max}|}{|V_{\min}|} = \frac{|I_{\max}|}{|I_{\min}|}$$

The Standing-wave ratio results from the fact that the two travelling-wave components of the equation for a voltage standing wave add in phase at some points and subtract at other points.

The distance between two successive maxima or minima is $\lambda/2$.

The Standing-wave ratio cannot be defined on a lossy line because the Standing-wave pattern changes markedly from one position to another (i.e. V_{\max} and V_{\min} change as V_{\max}/V_{\min}).

SWR is defined only for lossless line.

$$\rho = \frac{v_{\max}}{v_{\min}} = \frac{v_+ e^{-az} (1 + |\Gamma|)}{v_+ e^{-az} (1 - |\Gamma|)}$$

$$= \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$|\Gamma| = \frac{\rho - 1}{\rho + 1}$$

$$|\Gamma| \leq 1$$

$$\rho \geq 1$$

Problem: Standing wave Ratio

$$4) \quad Z_L = 60 - j80 \Omega$$

$$Z_0 = 50 \Omega$$

$$\text{Normalized load impedance } (\bar{Z}_L) = \frac{Z_L}{Z_0}$$

$$= \frac{60 - j80}{50} = 1.2 - j1.6$$

$$\bar{Y}_L = \frac{1}{\bar{Z}_L} = \frac{1}{1.2 - j1.6} = \underline{\underline{0.3 + j0.4}}$$

$$\underline{\underline{\lambda = 1\text{m}}}$$


$$\text{distance length of the stub} = 0.175\lambda - 0.066\lambda$$

$$= 0.109\lambda = \underline{\underline{0.109\text{m}}}$$

$$\text{length of the stub} = 0.25\lambda + 0.348\lambda$$

$$= 0.098\lambda$$

$$\boxed{l = 0.098\text{m}}$$

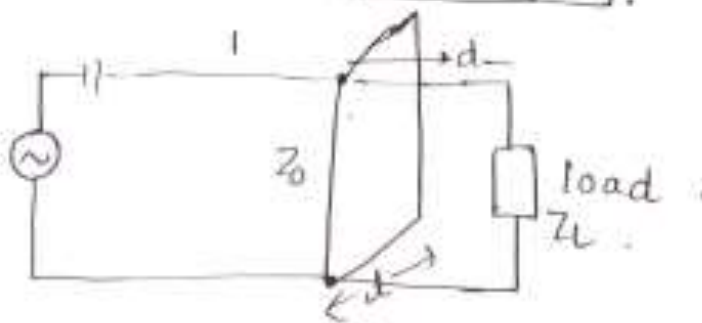

Smith Chart

The Smith Chart is a plot of the normalized impedance or admittance with angle and magnitude of a generalized complex reflection coefficient.

Normalized impedance,

$$\bar{Z} = \frac{Z}{Z_0} \quad (1)$$

At load end,

$$\begin{aligned} \bar{Z}_L &= \frac{Z_L}{Z_0} = \frac{1 + \Gamma_L}{1 - \Gamma_L} = \frac{R_L + jX_L}{Z_0} \quad (2) \\ &= r + jx \end{aligned}$$

$$\Gamma_L = \frac{\bar{Z}_L - 1}{\bar{Z}_L + 1} = \Gamma_r + j\Gamma_i \quad (3)$$

Substituting Eq. (3) into Eq. (2) we get

$$\begin{aligned} r + jx &= \frac{1 + \Gamma_r + j\Gamma_i}{1 - \Gamma_r - j\Gamma_i} = \frac{(1 + \Gamma_r) + j\Gamma_i}{(1 - \Gamma_r) - j\Gamma_i} \\ &\Rightarrow \frac{\Gamma_r + j\Gamma_i}{1 - \Gamma_r - j\Gamma_i} \\ &= \frac{(1 + \Gamma_r) + j\Gamma_i}{(1 - \Gamma_r) - j\Gamma_i} \times \frac{(1 - \Gamma_r) + j\Gamma_i}{(1 - \Gamma_r) + j\Gamma_i} \\ &= \frac{1 - \Gamma_r^2 - \Gamma_i^2 + 2j\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2} \\ &= \frac{1 - \Gamma_r^2 + 2j\Gamma_i - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2} \quad (4) \end{aligned}$$

$$x = \frac{1 - \Gamma_1^2 - \Gamma_2^2}{(1 - \Gamma_2)^2 + \Gamma_1^2} \quad (5)$$

$$\alpha = \frac{2\Gamma_1}{(1 - \Gamma_2)^2 + \Gamma_1^2} \quad (6)$$

From (5)

$$(1 + \Gamma_2^2 - 2\Gamma_2 + \Gamma_1^2)x = 1 - \Gamma_1^2 - \Gamma_2^2$$

$$x + \Gamma_2^2 x - 2\Gamma_2 x + \Gamma_1^2 x = 1 - \Gamma_1^2 - \Gamma_2^2$$

$$\Gamma_2^2 x - 2\Gamma_2 x + \Gamma_1^2 x + \Gamma_1^2 + \Gamma_2^2 = 1 - \Gamma_1^2 - \Gamma_2^2$$

$$(1 + \Gamma_2^2)x + \Gamma_1^2 x - 2\Gamma_2 x = 1 - \Gamma_1^2 - \Gamma_2^2$$

$$\div \text{ by } (1 + \Gamma_2^2) \quad \Gamma_1^2 x + \Gamma_2^2 x - \frac{2\Gamma_2 x}{1 + \Gamma_2^2} = \frac{1 - \Gamma_1^2 - \Gamma_2^2}{1 + \Gamma_2^2}$$

Adding $\left(\frac{\Gamma_2}{1 + \Gamma_2^2}\right)^2$ to both sides

$$\Gamma_1^2 x - \frac{2\Gamma_2 x}{1 + \Gamma_2^2} + \left(\frac{\Gamma_2}{1 + \Gamma_2^2}\right)^2 = \frac{1 - \Gamma_1^2 - \Gamma_2^2}{1 + \Gamma_2^2} + \left(\frac{\Gamma_2}{1 + \Gamma_2^2}\right)^2$$

$$+ \Gamma_2^2 x = \frac{1 - \Gamma_1^2 + \Gamma_2^2}{(1 + \Gamma_2^2)^2}$$

$$\left(\Gamma_1 x - \frac{\Gamma_2}{1 + \Gamma_2^2}\right)^2 + \Gamma_2^2 x = \left(\frac{\Gamma_2}{1 + \Gamma_2^2}\right)^2 \quad (7)$$

From Eq. (6), $(1 + \Gamma_2^2 - 2\Gamma_2)\alpha + \Gamma_1^2 \alpha = 2\Gamma_1$

$$\alpha + \Gamma_2^2 \alpha - 2\Gamma_2 \alpha + \Gamma_1^2 \alpha - 2\Gamma_1 = 0$$

$$\Gamma_2^2 \alpha - 2\Gamma_2 \alpha + \Gamma_1^2 \alpha = -\alpha$$

$$\left(\frac{\Gamma_r}{\Gamma_r - 1}\right)^2 + \Gamma_i^2 = \frac{2\Gamma_i}{\alpha}$$

$$\left(\frac{\Gamma_r}{\Gamma_r - 1}\right)^2 + \Gamma_i^2 - \frac{2\Gamma_i}{\alpha} = 0$$

Adding $\left(\frac{1}{\alpha}\right)^2$ to both sides

$$\left(\frac{\Gamma_r}{\Gamma_r - 1}\right)^2 + \Gamma_i^2 - \frac{2\Gamma_i}{\alpha} + \left(\frac{1}{\alpha}\right)^2 = \left(\frac{1}{\alpha}\right)^2$$

$$\left(\frac{\Gamma_r}{\Gamma_r - 1}\right)^2 + \left(\Gamma_i - \frac{1}{\alpha}\right)^2 = \left(\frac{1}{\alpha}\right)^2 \quad (7)$$

Equation (7) is an equation of family of circles in which each circle has a constant resistance r .


$$\text{Radius of any circle} = \frac{1}{1+r}$$

$$\text{center of any circle} = \left(\frac{r}{1+r}, 0\right)$$

along the real axis

where r varies from 0 to ∞ .

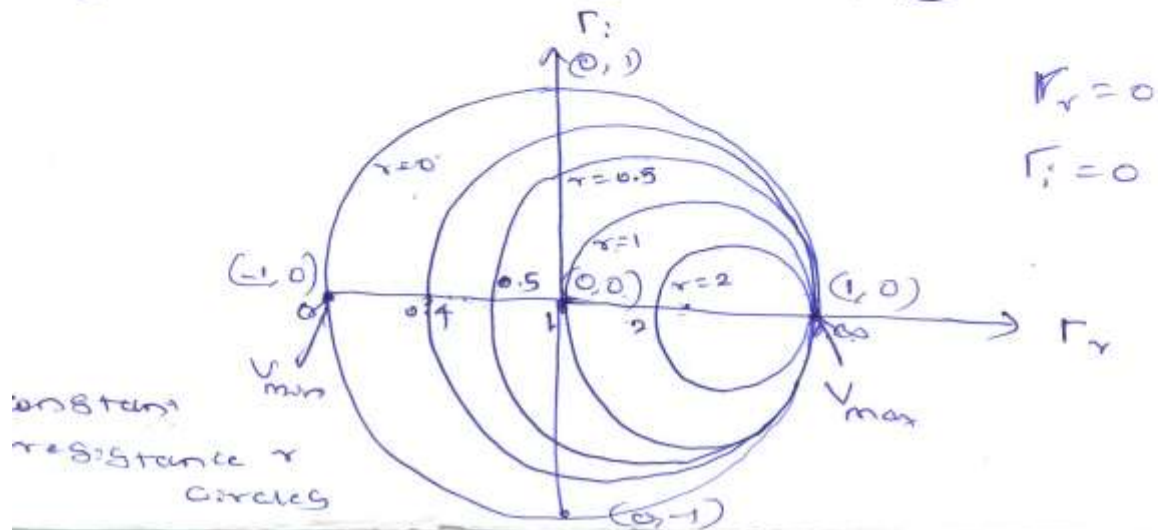All constant resistance circles are plotted in fig below according to Eq. (7)




→ Equation (8) also describes a family of circles, but each of these circles specifies a constant reactance α .

→ The radius of any circle is $(\frac{1}{\alpha})$ and the center of any circle is at

$$\Gamma_r = 1 \quad \Gamma_i = \frac{1}{\alpha} \quad (\text{where } -\infty \leq \alpha \leq \infty)$$

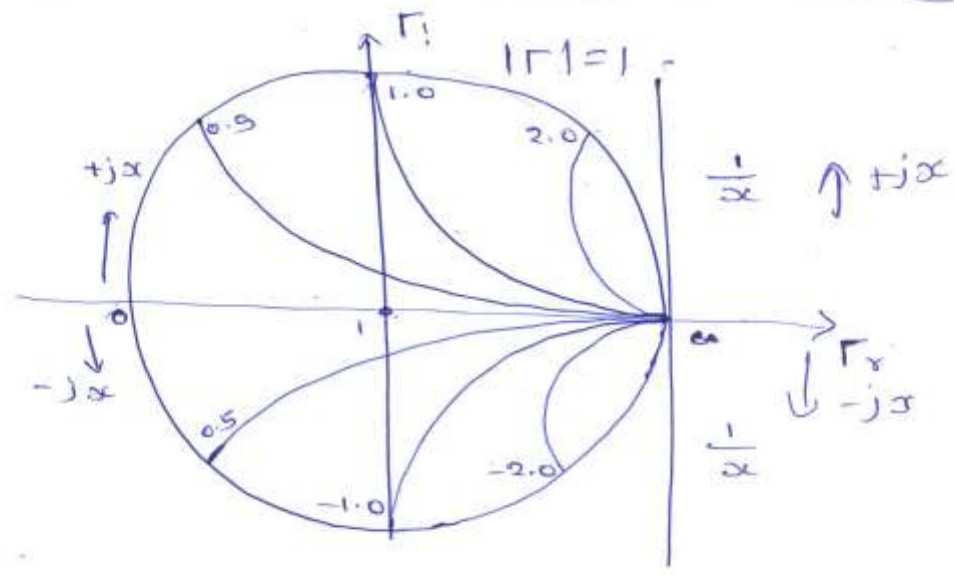→ All constant reactance circles are plotted in Fig. below according to Eq. (8)



constant reactance α circles

6.

In a certain microwave transmission line, the characteristic impedance was measured to be $210 \angle 10^\circ \Omega$ and the propagation constant is $0.2 \angle 18^\circ$. Determine the primary constants of the line, if the frequency of operation is 1 GHz.

$$\text{Given } Z_0 = 210 \angle 10^\circ \Omega$$

$$\gamma = 0.2 \angle 18^\circ$$

$$f = 1 \text{ GHz}$$

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\gamma = \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$Z_0 \gamma = R + j\omega L$$

$$\frac{\gamma}{Z_0} = G + j\omega C$$

$$\begin{aligned} \therefore R + j\omega L &= 210 \angle 10^\circ \times 0.2 \angle 18^\circ \\ &= 42 \angle 28^\circ \\ &= 1.465 + j 41.97 \end{aligned}$$

$$R = 1.465 \Omega/\text{m}$$

$$\omega L = 41.97$$

$$\begin{aligned} L &= \frac{41.97}{\omega} = \frac{41.97}{2\pi f} = \frac{41.97}{2\pi \times 1 \times 10^9} \\ &= 6.67 \times 10^{-9} \\ &= 6.67 \text{ nH/m} \end{aligned}$$

$$G + j\omega C = \frac{0.2 \angle 18^\circ}{210 \angle 10^\circ}$$

$$= 9.52 \times 10^{-4} \angle 8^\circ$$

$$= 3.56 \times 10^{-4} + j 8.82 \times 10^{-4}$$

$$G = 3.56 \times 10^{-4} \text{ mho/m}$$

$$\omega C = 8.82 \times 10^{-4}$$

$$C = \frac{8.82 \times 10^{-4}}{\omega} = \frac{8.82 \times 10^{-4}}{2\pi f}$$

$$= \frac{8.82 \times 10^{-4}}{2\pi \times 1 \times 10^9} = 1.4 \times 10^{-13} \text{ F/m}$$

Scheme of Evaluation

IATI MWA 21EGG2

1. Diagram of the wire transmission line - 2M

Applying KVL, KCL and getting

$$\frac{\partial V}{\partial z} + \frac{\partial I}{\partial z} = 0$$

Introducing phasors - 2M

$$V(z) = V_1 e^{jz} + V_2 e^{-jz}$$

$$I(z) = \frac{1}{Z_0} (V_1 e^{jz} - V_2 e^{-jz})$$

2. $Z_0 = \sqrt{\frac{R' + j\omega L}{G' + j\omega C}}$ 4M

$$\alpha = \sqrt{(R' + j\omega L)(G' + j\omega C)}$$
 2M

$$\alpha = \alpha + j\beta$$
 2M

$$\beta$$
 2M

3. Definition of reflection coefficient and standing wave ratio - 2M

Deriving $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$ - 4M

Deriving $VSWR(\Gamma) = \frac{1 + |\Gamma|}{1 - |\Gamma|}$ - 4M

4. Standing wave ratio 2M
 Definition of reflection coefficient 2M
 Standing wave ratio of the line 2M
 Finding length of the line 2M

5. Applying to

$$\alpha = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{\sqrt{(1 - \Gamma_r^2 + \Gamma_i^2)^2}}$$

$$\alpha = \frac{2\Gamma_r}{(1 - \Gamma_r^2 + \Gamma_i^2)}$$

Condition $\alpha = 0$ when $\Gamma_r = 0$ 2M

$$\left(\Gamma_r - \frac{1}{\Gamma_r}\right)^2 + \Gamma_i^2 = \left(\frac{1}{\Gamma_r}\right)^2$$

Positive real part $\Gamma_r = 1$ 2M

$$\left(\Gamma_r - 1\right)^2 + \left(\Gamma_r - \frac{1}{\Gamma_r}\right)^2 = \left(\frac{1}{\Gamma_r}\right)^2$$

6. $Z_0 = \sqrt{\frac{L}{C}}$; $\Gamma = \sqrt{Z_L/Z_0}$

$$\frac{1}{Z_0} = G' + j\omega C$$
 ; $Z_0 = R' + j\omega L$ 2M

$$\left. \begin{matrix} R' \\ G' \\ C \end{matrix} \right\} 6M$$