

| | | | | | | | | | | |
|-----|--|--|--|--|--|--|--|--|--|--|
| USN | | | | | | | | | | |
|-----|--|--|--|--|--|--|--|--|--|--|



CMR INSTITUTE OF TECHNOLOGY

Internal Assessment Test – II

| | | | | | | | | | | | |
|----------------------------------|---|------------------|----------------|-------------------|-----------|------------|--------------|---------------|--------------------|-----|--|
| Sub: | VLSI DESIGN & TESTING | | | | | | Code: | 21EC63 | | | |
| Date: | 09.07.2024 | Duration: | 90 mins | Max Marks: | 50 | Sem | VI | Branch | ECE-A,B,C,D | | |
| Answer Any Five Questions | | | | | | | | | | | |
| Questions | | | | | | | | Marks | OBE | | |
| | | | | | | | | | CO | RBT | |
| 1. | With neat diagrams explain n-well CMOS fabrication process. | | | | | | [10] | CO2 | L1 | | |
| 2. | Draw the stick and layout diagram for the function $Y = \overline{ABC} + D$. | | | | | | [10] | CO2 | L2 | | |
| 3. | Construct necessary equivalent circuits using RC delay model to compute the propagation delay of 3-input NAND Gate. | | | | | | [10] | CO2 | L2 | | |

| | | | | | | | | | | |
|-----|--|--|--|--|--|--|--|--|--|--|
| USN | | | | | | | | | | |
|-----|--|--|--|--|--|--|--|--|--|--|



CMR INSTITUTE OF TECHNOLOGY

Internal Assessment Test – II

| | | | | | | | | | | | |
|----------------------------------|---|------------------|----------------|-------------------|-----------|------------|--------------|---------------|--------------------|-----|--|
| Sub: | VLSI DESIGN & TESTING | | | | | | Code: | 21EC63 | | | |
| Date: | 09.07.2024 | Duration: | 90 mins | Max Marks: | 50 | Sem | VI | Branch | ECE-A,B,C,D | | |
| Answer Any Five Questions | | | | | | | | | | | |
| Questions | | | | | | | | Marks | OBE | | |
| | | | | | | | | | CO | RBT | |
| 1. | With neat diagrams explain n-well CMOS fabrication process. | | | | | | [10] | CO2 | L1 | | |
| 2. | Draw the stick and layout diagram for the function $Y = \overline{ABC} + D$. | | | | | | [10] | CO2 | L2 | | |
| 3. | Construct necessary equivalent circuits using RC delay model to compute the propagation delay of 3-input NAND Gate. | | | | | | [10] | CO2 | L2 | | |

| | | | | | | | | | |
|-----|--|--|--|--|--|--|--|--|--|
| USN | | | | | | | | | |
|-----|--|--|--|--|--|--|--|--|--|

| | | | | |
|----|---|------|-----|----|
| 4. | Make use of necessary circuit diagrams to compute logical effort of the following gates. (i) 2-input NOR gate and (ii) 3-input NAND Gate. | [10] | CO2 | L2 |
| 5. | With necessary circuit diagram, explain the operation of three transistor DRAM cell. | [10] | CO3 | L2 |
| 6. | Explain full CMOS SRAM cell with necessary circuit topology. | [10] | CO3 | L2 |

CI

CCI

HOD

| | | | | | | | | | |
|-----|--|--|--|--|--|--|--|--|--|
| USN | | | | | | | | | |
|-----|--|--|--|--|--|--|--|--|--|

| | | | | |
|----|---|------|-----|----|
| 4. | Make use of necessary circuit diagrams to compute logical effort of the following gates. (i) 2-input NOR gate and (ii) 3-input NAND Gate. | [10] | CO2 | L2 |
| 5. | With necessary circuit diagram, explain the operation of three transistor DRAM cell. | [10] | CO3 | L2 |
| 6. | Explain full CMOS SRAM cell with necessary circuit topology. | [10] | CO3 | L2 |


CI

CCI


HOD

7. Explain neat diagram explain n-well CMOS fabrication process.

 
(a) Blank wafer covered with a layer of SiO_2 using oxidation.



 
(b) Spin on the photoresist. Exposed to UV light using the n-well mask. (photo lithography)



 ③ Strip off the exposed photoresist using organic solvents.



 
④ Etch the uncovered oxide using HF (Hydrofluoric acid)




⑤ Etch the remaining photoresist using a mixture of acetone



 
⑥ n-well is formed using either diffusion or ion implantation



 ⑦ Strip off the remaining oxide using HF. Subsequent steps use the same photolithography process.




 ① Deposit thin layer of oxide. Use CVD to form poly and dope heavily to increase conductivity




polysilicon
Thin gate oxide

 ② Pattern poly using the previously discussed photolithography process




Polysilicon
Thin gate oxide

 
③ Cover with oxide to define n diffusion regions.



 
(1) Pattern oxide using n+ active mask to define n diffusion regions



 
(2) Diffusion (or) Ion Implantation used to create n diffusion region




 
(3) Strip off the oxide to complete patterning step



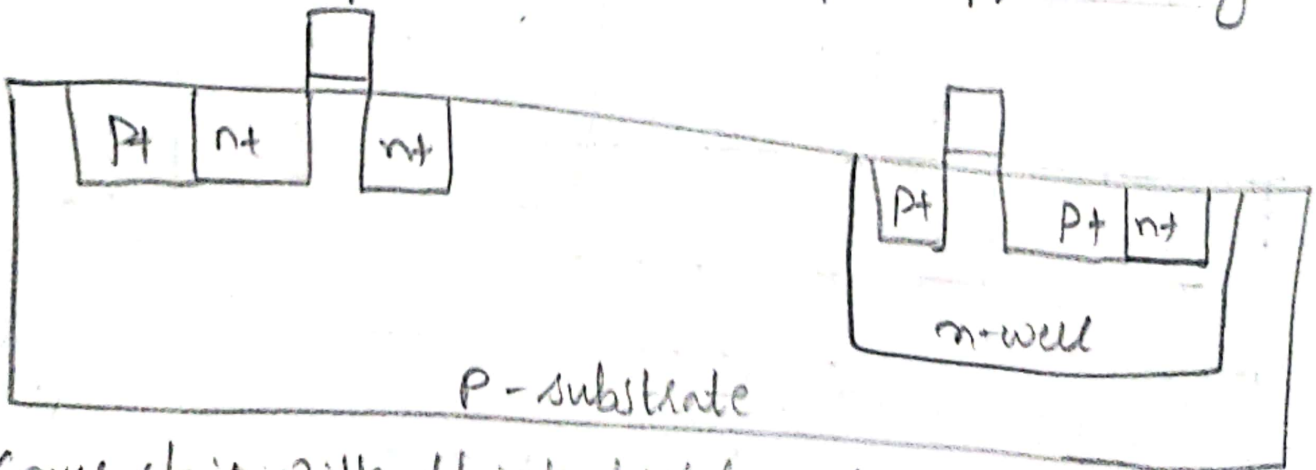
(4) Similar steps used to create p-diffusion regions



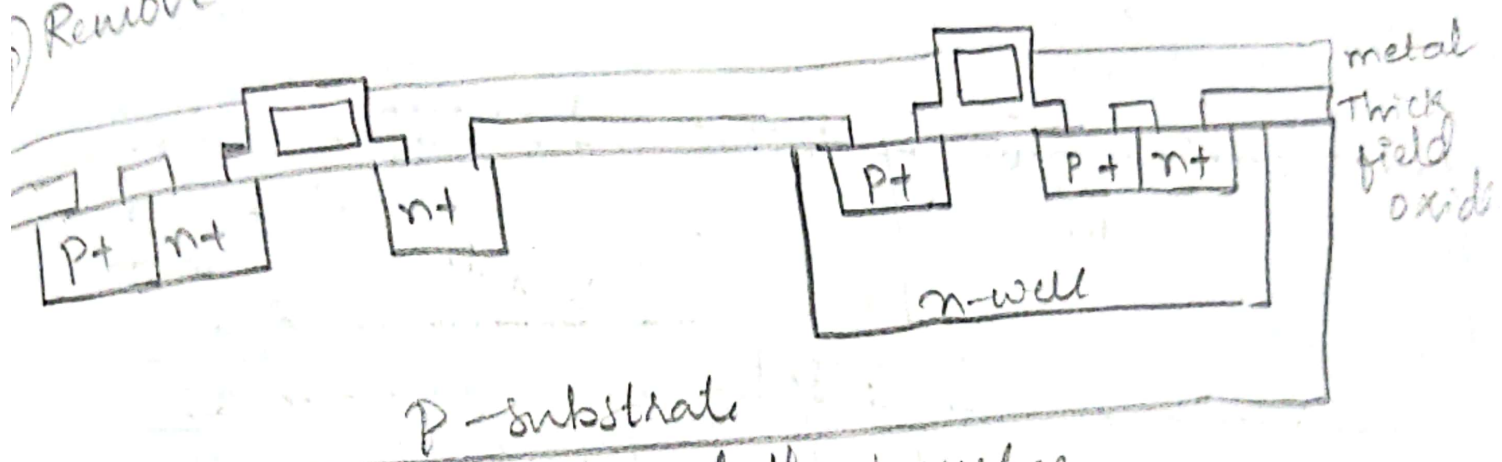 (5) Cover chip with thick field oxide and etch oxide where contact cuts are needed.



Layout (mask) view of the inverter.


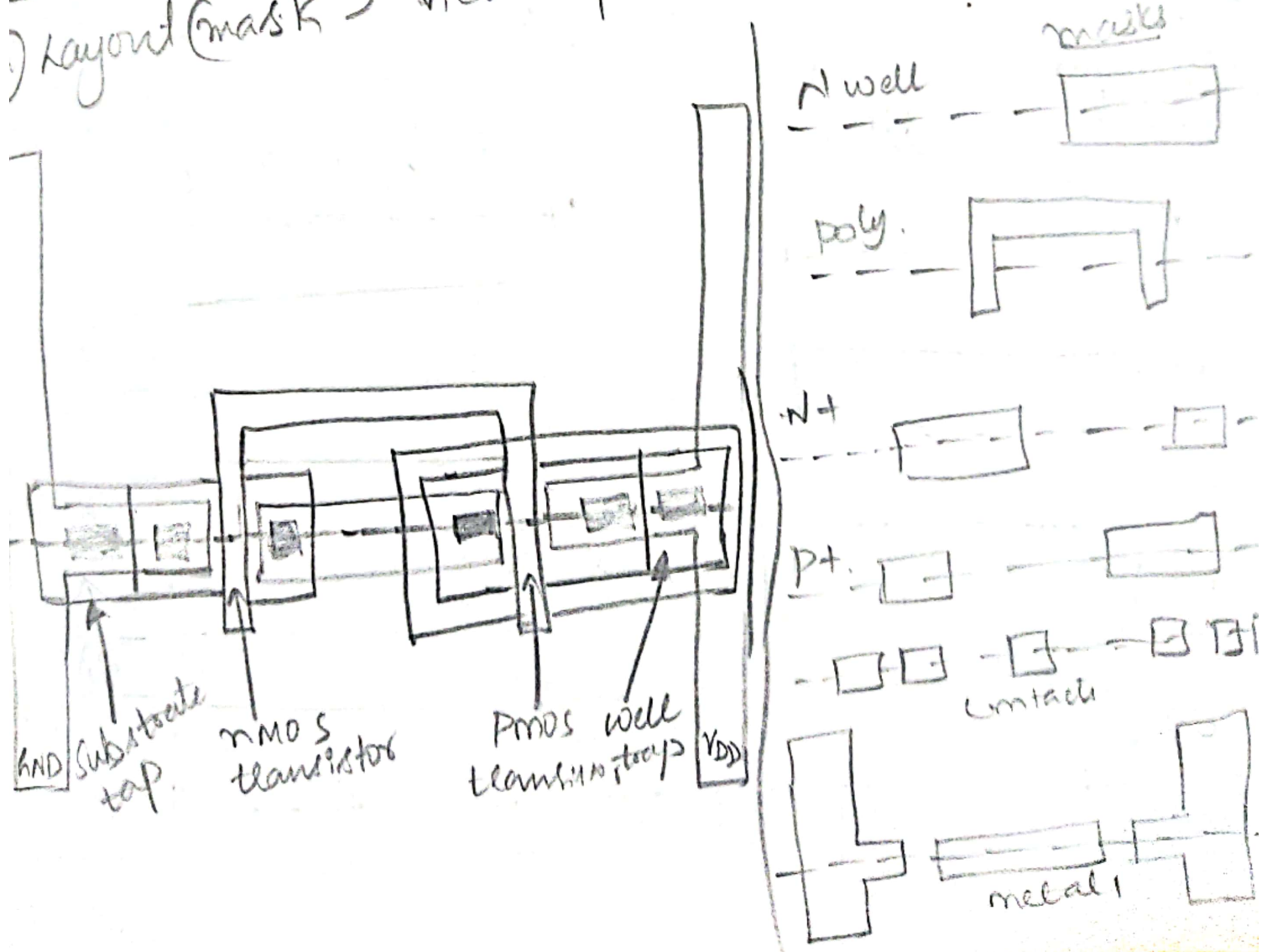


$$C_{in}(A) = W_p(A) + W_n(A) = 2 + 3 = 5$$

$$g_{mnd3} = \frac{C_{in}(A)}{C_{in}(inv)} = \frac{5}{3} \quad \text{u.}$$

$$\left(\frac{(n+2)}{3} \right)$$

Stick Diagram for $\overline{ABC+D}$

  


22

$z = z + b = (A)_{n \times n} + (A)_{q \times q} =$ N-active

$(A)_{n \times n}$ $(A)_{q \times q}$

ANP.

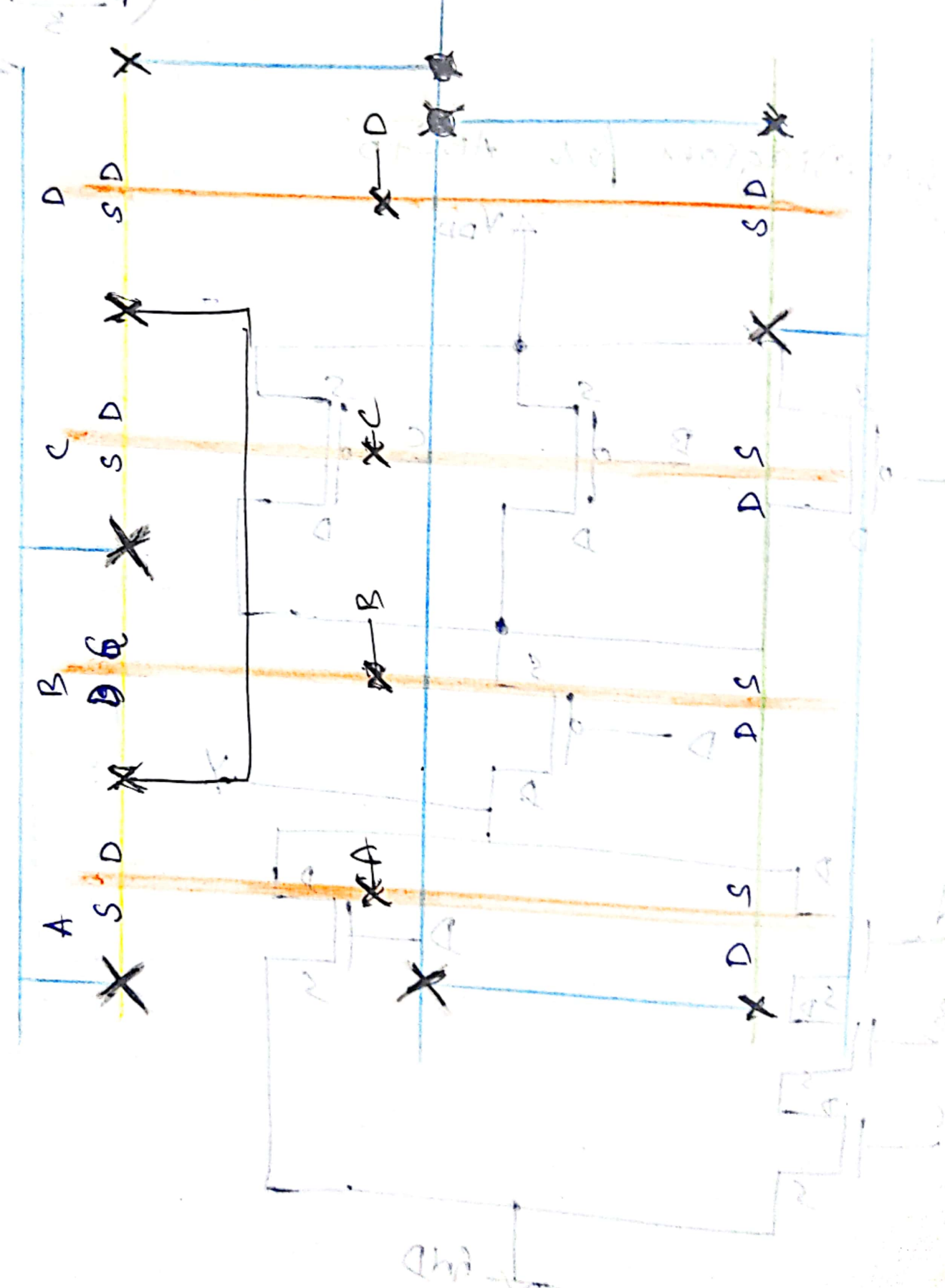

2. Construct necessary equivalent circuits using RC delay model to compute the propagation delay of 3-input NAND gate.

RC circuit models for NMOS and PMOS transistors with k with contacted diffusion on both source and drain.


The PMOS transistor has approximately twice the resistance of the NMOS transistor because holes have lower mobility than electrons.


The PMOS capacitors are shown with V_{DD} as their terminal because the n-well is usually tied high.

The equivalent circuits for logic gates are assembled from the individual transistors.



The unit inverters are composed from an NMOS transistor of unit size and a PMOS transistor of twice unit width to achieve equal rise and fall resistance.

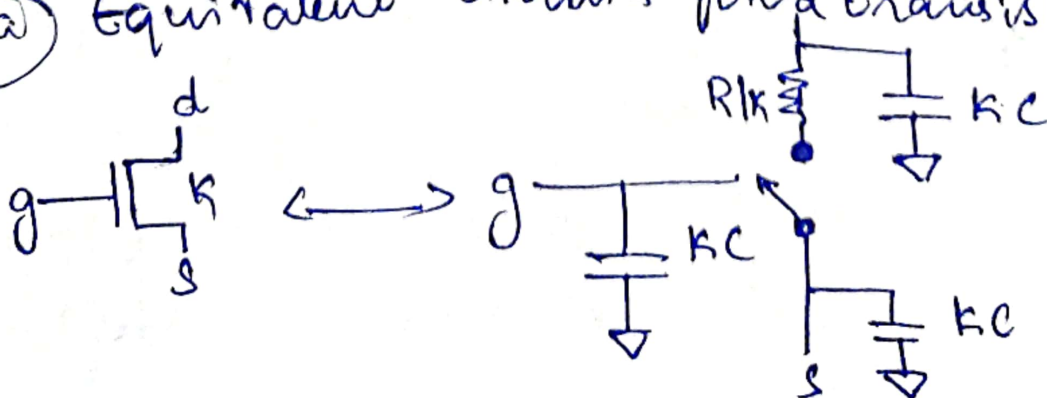(a) Equivalent circuits for a transistor.



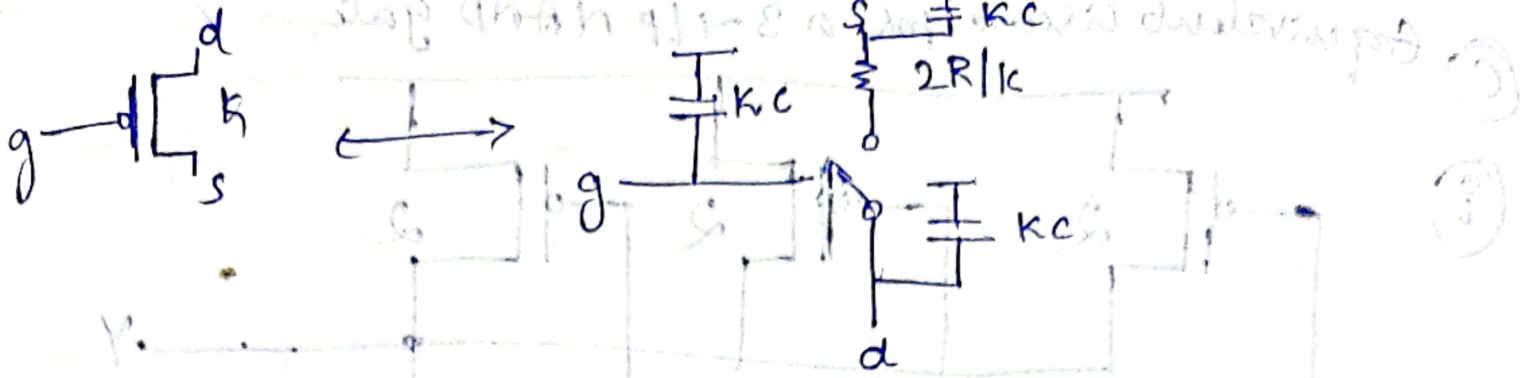


b) Equivalent circuit for an inverter.

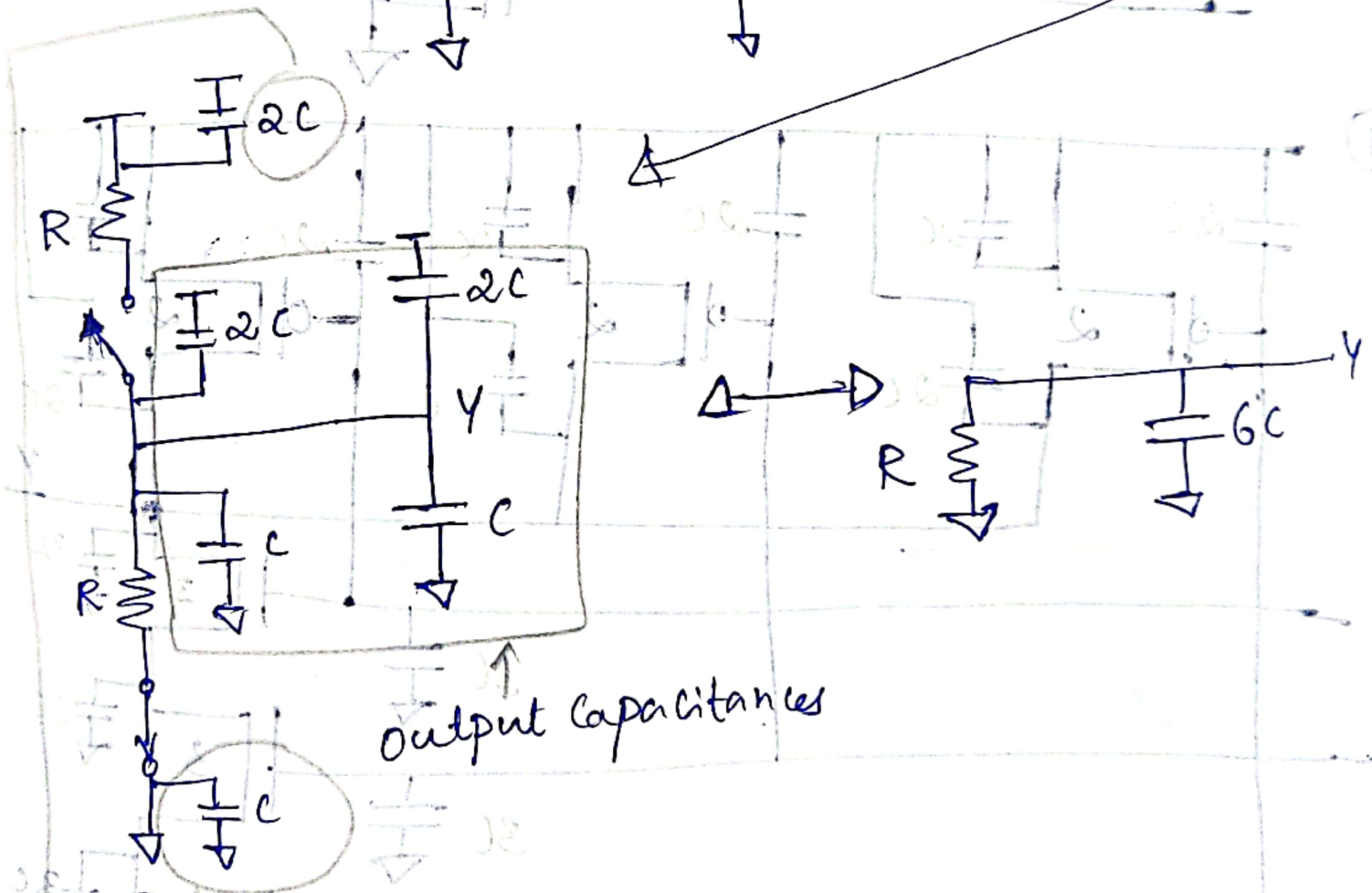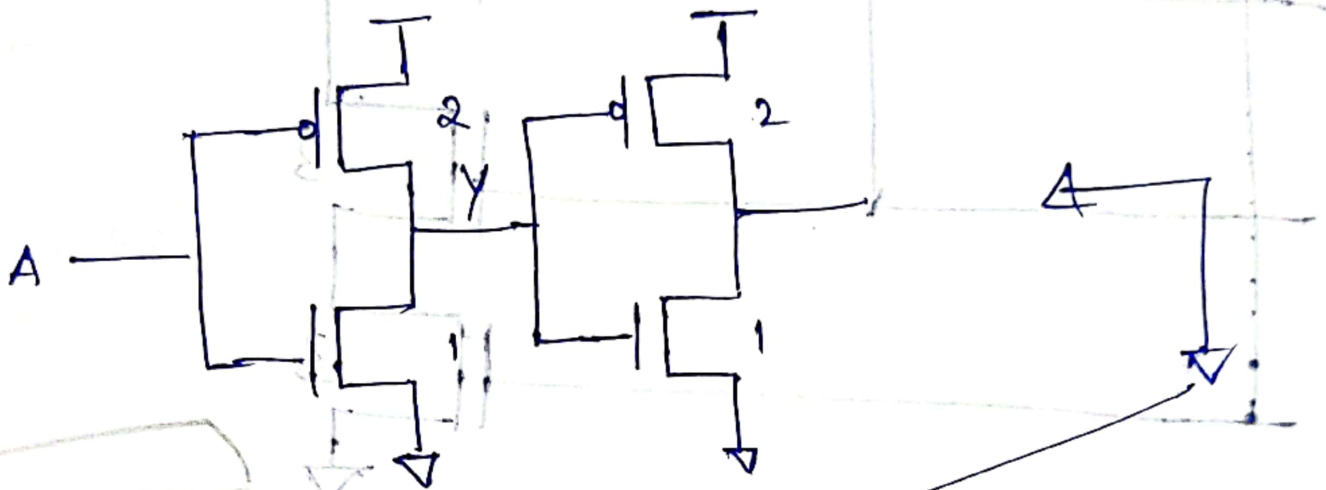


Non-switching capacitance is irrelevant


(c) Equivalent circuit for a 3-ILP NPNV gate

(i)

 


(ii)

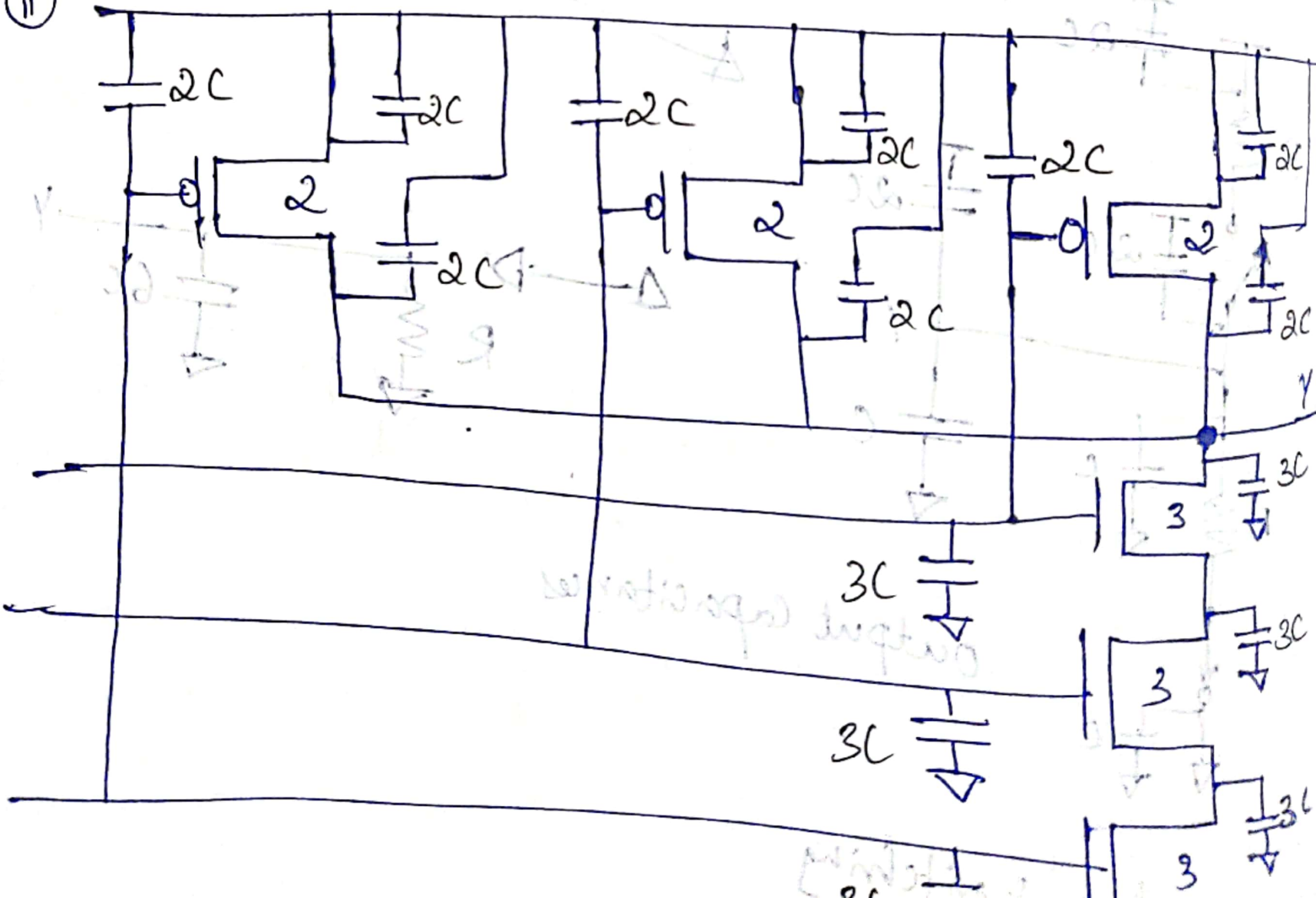


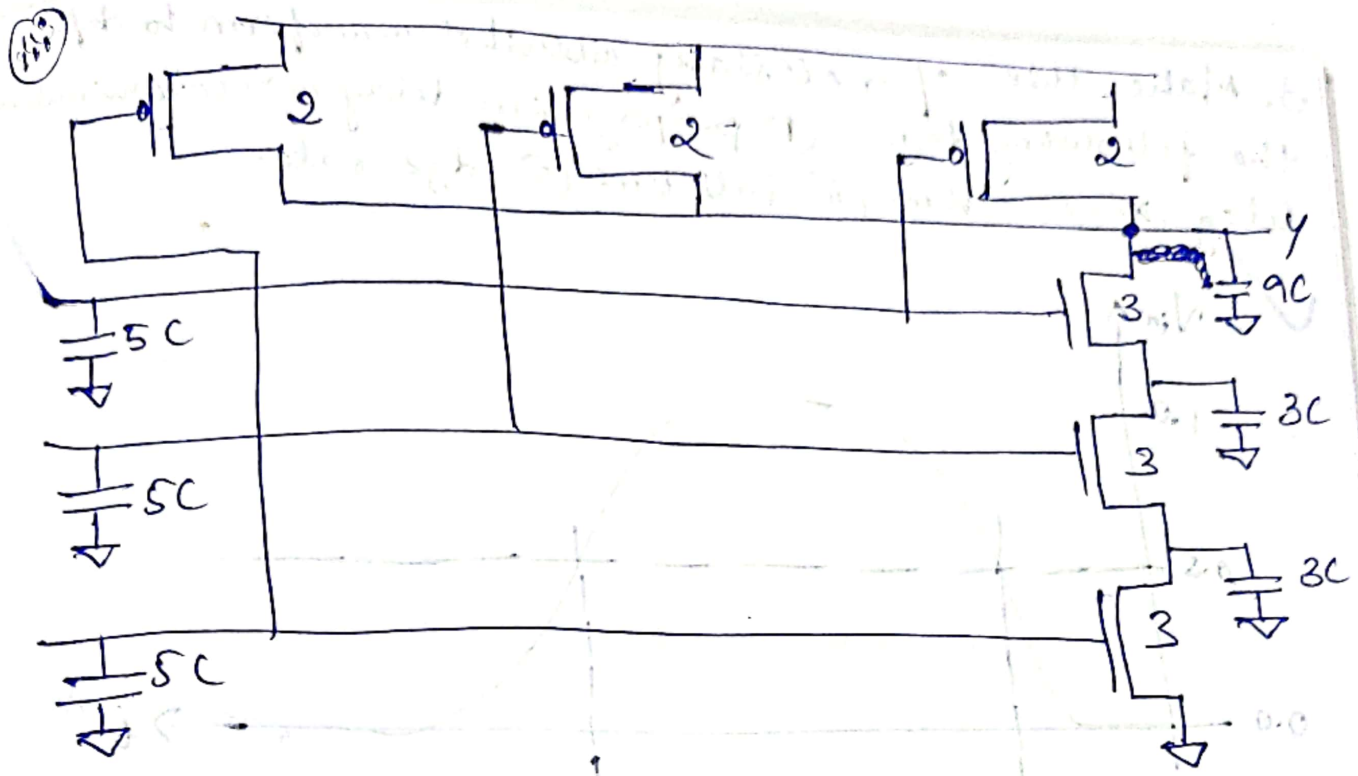


④ Falling

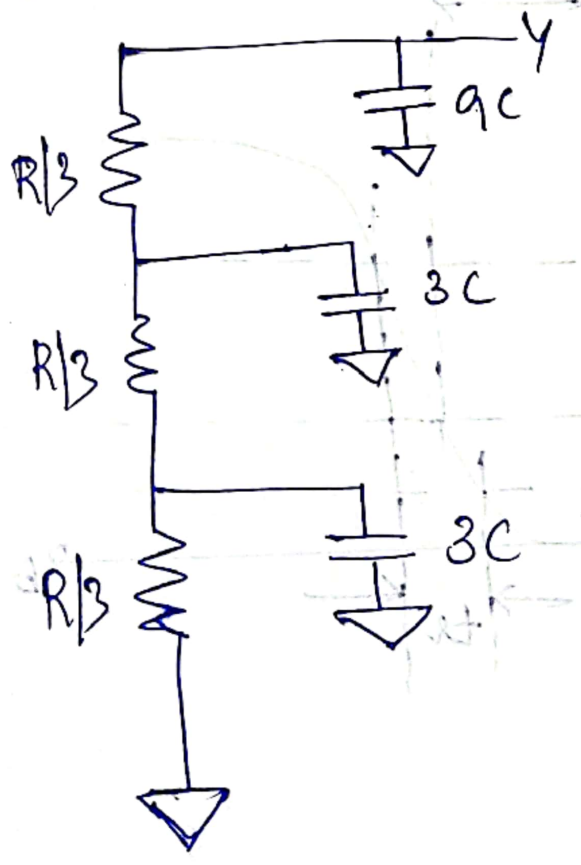

⑤ Raising

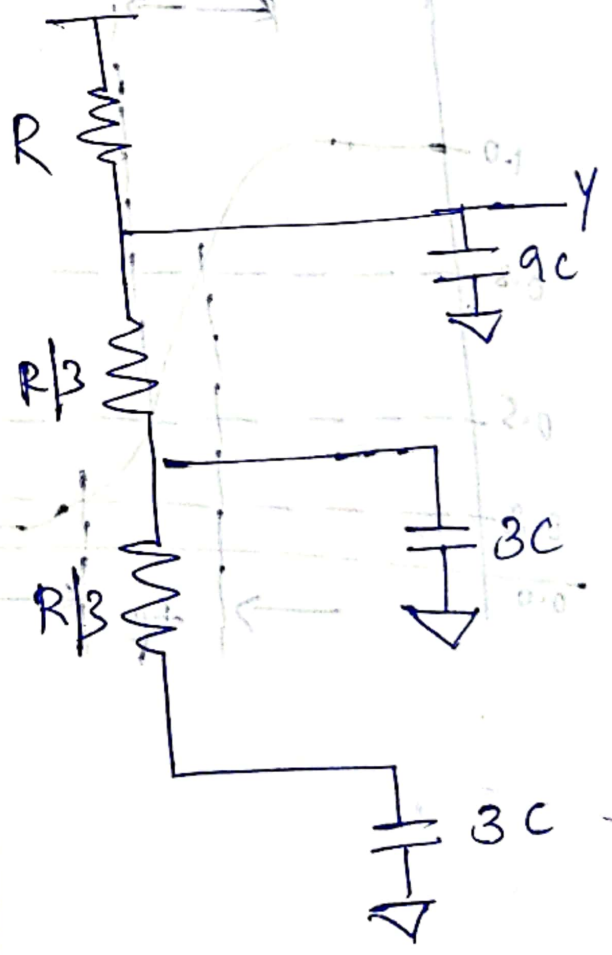

6T SRAM cell

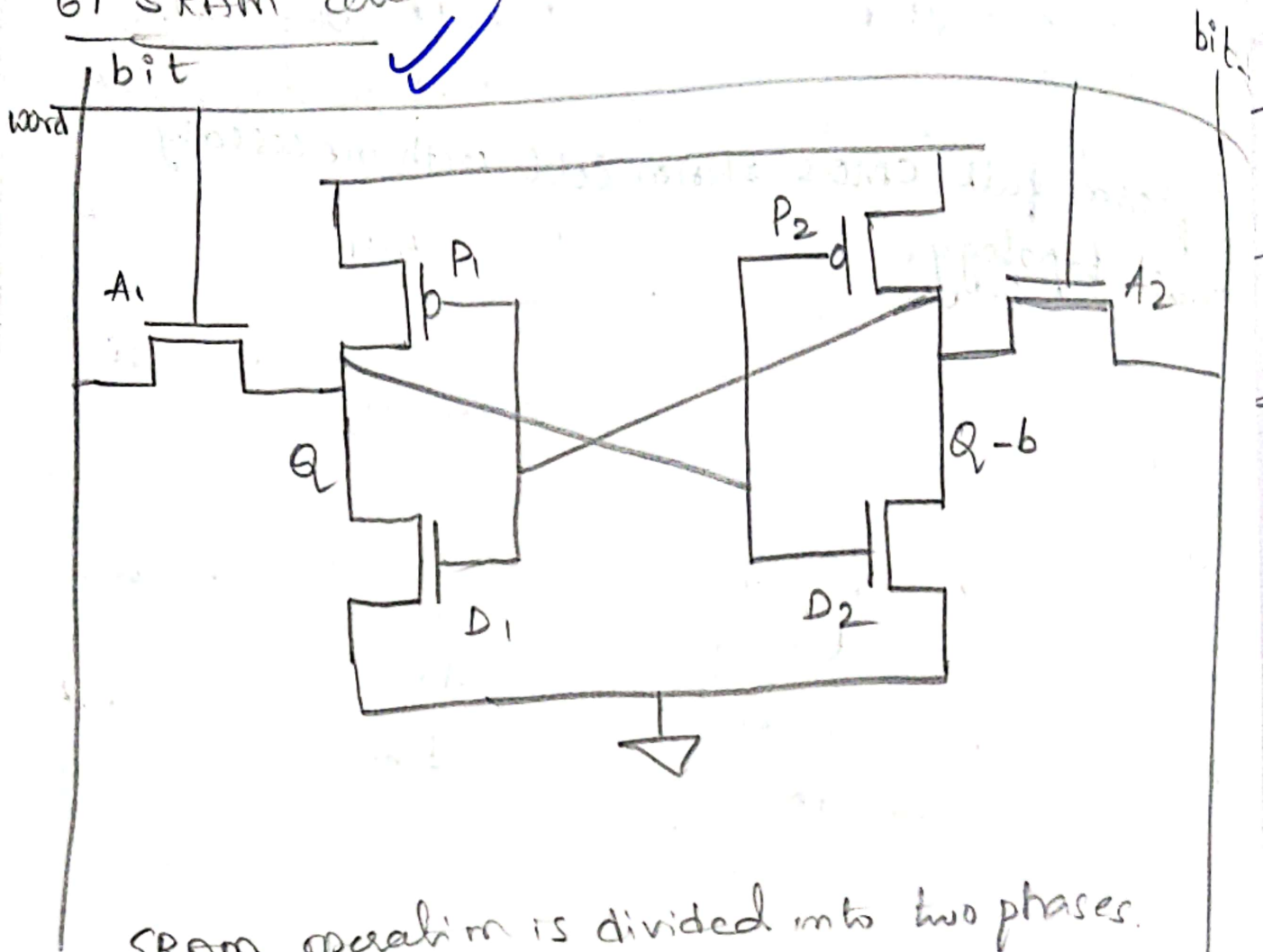

SRAM operation is divided into two phases.

The phases will be called ϕ_1 and ϕ_2 , but may actually be generated from clk and its complement clk_b .

Assume that in phase 2, the SRAM is precharged. In phase 1, the SRAM is read or written.

Read operation


→ SRAM cell being read.

→ The bitlines are both initially floating high.

→ Without loss of generality, assume Q is initially 0 and thus $Q-b$ is initially 1.

→ $Q-b$ and bit-b both should remain 1

- When the word line is raised, bit should be pulled down through driver and access transistors $D1$ and $A1$.
- At the same time bit is being pulled down, node Q tends to rise.
- Q is held low by $D1$, but raised by current flowing in from $A1$.
- Hence, the driver $D1$ must be stronger than the access transistor $A1$.
- The transistors must be ratioed such that node Q remains below the switching threshold of the $P2/N2$ inverter.
- This constraint is called read stability.
- observe that Q momentarily rises, but does not glitch badly enough to flip the cell.

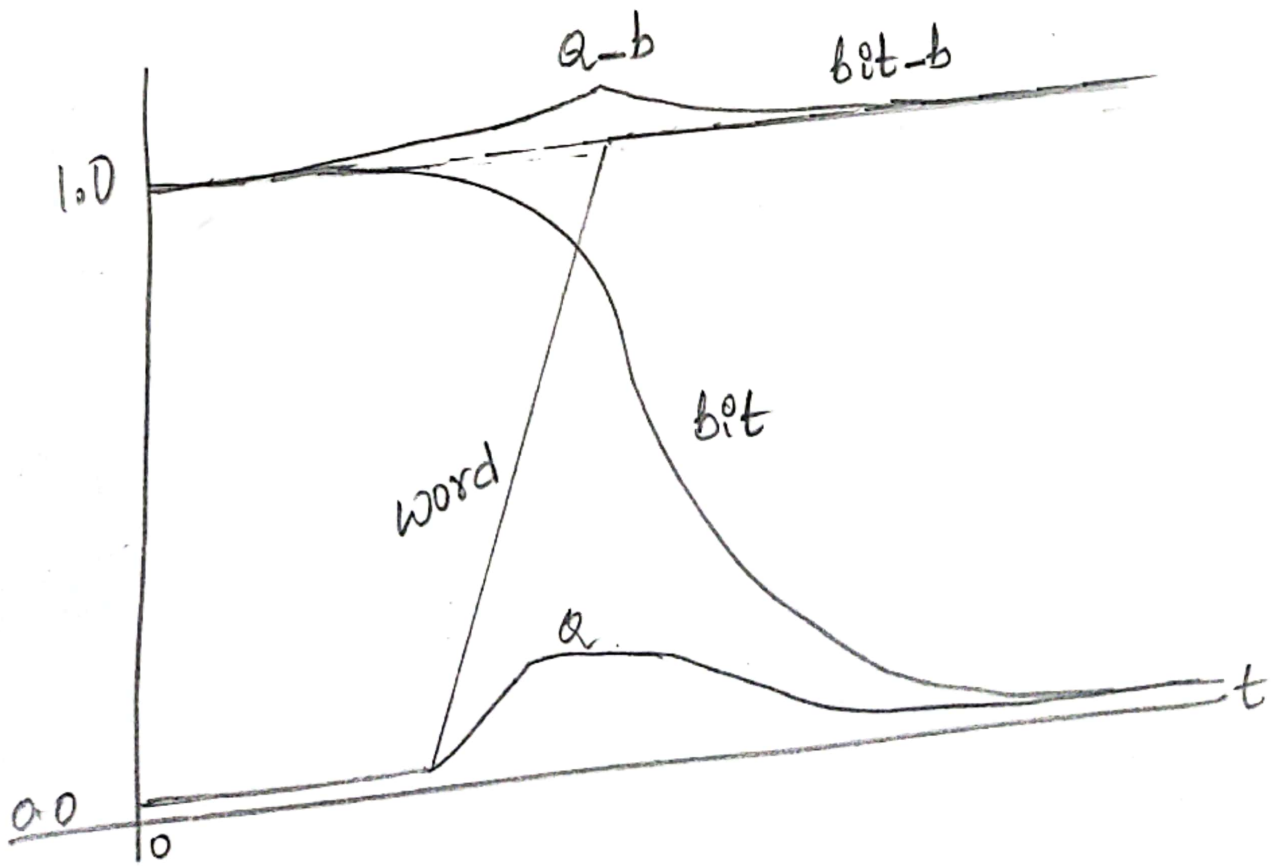

Write operation

- SRAM cell being written.
- Again, ^{assume} Q is initially 0 and that to write 1 into ^{the} cell.
- Bit is precharged high and left floating.
- bit-b is pulled low by a write driver.
- The read stability constraint that bit will be unable to force Q high through $A1$.
- Hence, the cell must be written by forcing $Q-b$ low through $A2$.
- $P2$ opposes this operation; thus, $P2$ must be weaker than $A2$ so that $Q-b$ can be pulled low enough.
- This constraint is called writability.
- Once $Q-b$ falls low, $D1$ turns OFF and $A1$ turns ON, pulling Q high as desired.