

USN									
-----	--	--	--	--	--	--	--	--	--



CMR INSTITUTE OF TECHNOLOGY

Internal Assessment Test – I

Sub:	ADVANCED VLSI						Code:	21EC71	
Date:	26.10.2024	Duration:	90 mins	Max Marks:	50	Sem	VII	Branch	ECE-A,B,C,D

Answer Any Five Questions


	Questions	Marks	OBE	
			CO	RBT
1.	Explain Application Specific Integrated Circuits (ASIC) in detail and outline their various classifications.	[10]	CO1	L1
2.	(a) Describe the 4-bit Carry Look-Ahead Adder, including its advantages and disadvantages. (b) Difference between PLA and PAL.	[10]	CO1	L1
3.	Explain the steps involved in the ASIC design process with neat labeled diagram.	[10]	CO1	L2

USN									
-----	--	--	--	--	--	--	--	--	--

4.	(a) Write short note on carry skip / carry by-pass adder. (b) Write short note on ASIC cell libraries.	[10]	CO1	L2
5.	Explain Booth's Algorithm in detail and illustrate it with an example.	[10]	CO1	L2
6.	Discuss the following types of Programmable Logic Devices with suitable diagrams: (a) Simple Programmable Logic Devices (SPLDs) (b) Field Programmable Gate Arrays (FPGAs)	[10]	CO1	L2

INTERNAL ASSESSMENT TEST - I

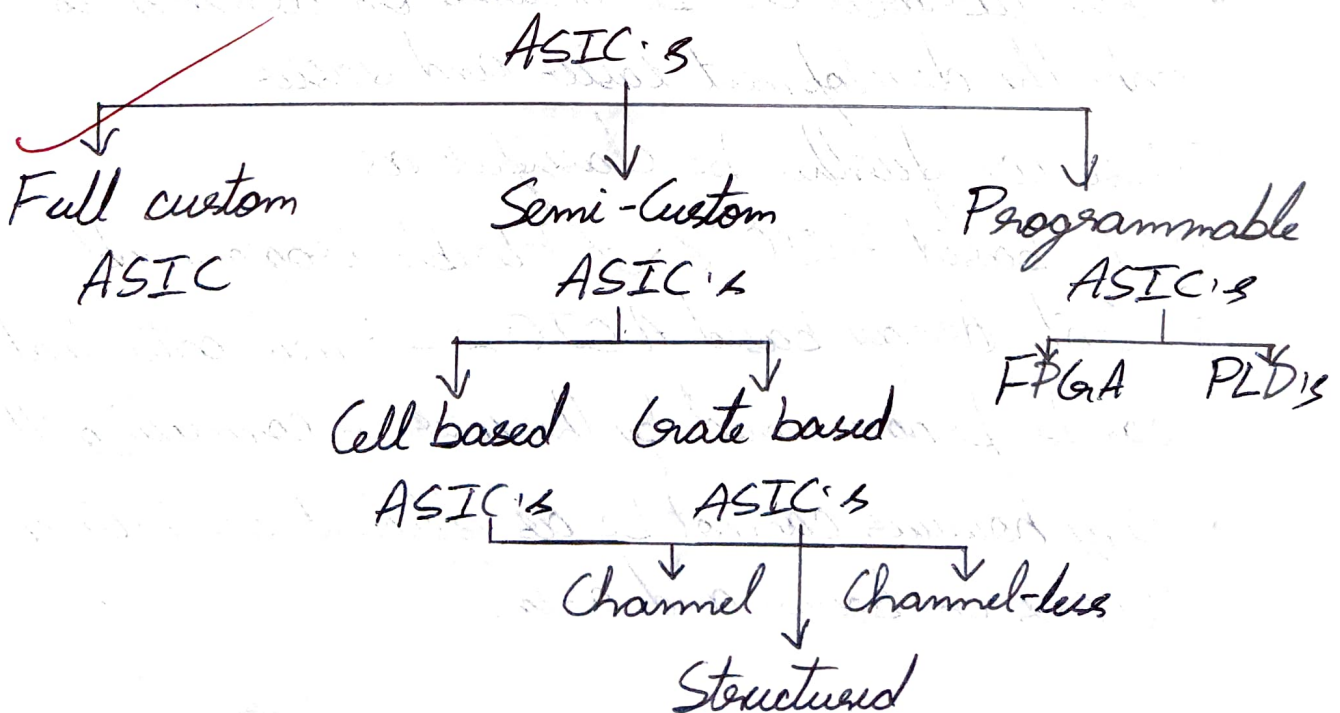1. Application Specific Integrated Circuits (ASIC's) are IC's designed for a specific use-case.
 - They are usually designed for one customer at a time
 - For example, an IC for a bear that talks back, a satellite circuit, for a mobile phone etc...
 - They differ from general purpose Integrated circuits which can be programmed for multiple tasks but cannot be optimised like ASIC's
- ASIC's are classified into 3 types
- i) Full-custom ASIC's
 - ii) Semi-Custom ASIC's
 - iii) Programmable ASIC's



i) Full Custom IC's

- In full custom ASIC's, the designer designs the IC from scratch as per the specifications and requirements.
- The designer squeezes every inch of the IC's to place the units as densely as possible and make it as energy efficient as possible.
- But to do this would take a person who knows CAED software tool well, and a ton of development cost and time.

ii) Semi-Custom ASIC's

- In semi-custom ASIC's there exists predefined libraries such as (basic gates, MUX, Flip Flops etc) which are preverified by the manufacturer.
- These libraries can be invoked on demand to make the development easier and faster.
- These can further be classified as -

i) Cell based ASIC's ✓ Flexible programmable - Cells

ii) Gate Array based ASIC's - Fixed gates that can be programmed by the user in connecting them.


- They however cannot be as efficient as Full custom ASIC's in power and area.

iii) Programmable ASIC's


- These kind of ASIC's can be configured by the user easily and in a short duration.
- These have cells which act as the functional unit.
- They are further classified into
 - i) FPGA - Field programmable Gate Array's
 - ii) PLD's - Programmable Logic Devices

 a) Cell based ASIC's

- In cell based ASIC's there are fundamental arbitration of the logic called cell's.
 - These cell's can be connected in the required manner to obtain the required functions.
 - The cell's contain predefined and pre-verified components like (AND gates, Flip-Flop's and MUX)
- The Cell based ASIC's may further be classified into three kinds
- i) Channeled - Have channels or specified paths for connection of cells.



 ii) Channelless: In this redundant or unused cells are used as contact or connections to transmit the data.



Advantages

- i) They can be flexible to save on space with flexible blocks of cells.
- ii) They have comparatively less congestion as compared to Full custom ASIC's. (Routing paths)
- iii) Easily implementable
- iv) Saves time in programming

Disadvantages.

- i) The cells are pre-programmed and hence the energy consumption is high.
- ii) The unused cells contribute to wasted space and hence lower's density.

2 (b) Gate Array based ASICs

• These type of ASICs have a number of fixed gates (AND (or) OR).

• The connection between these gates are decided by the designer to obtain the required function.

• Advantages

i) They are less flexible energy hungry and consume comparatively less power.

ii) They are easier to work with and program.


iii) They require less time to program.

• Disadvantages.

i) These gates are fixed and hence not properly customisable.

ii) They have higher congestion due to the routing of data.

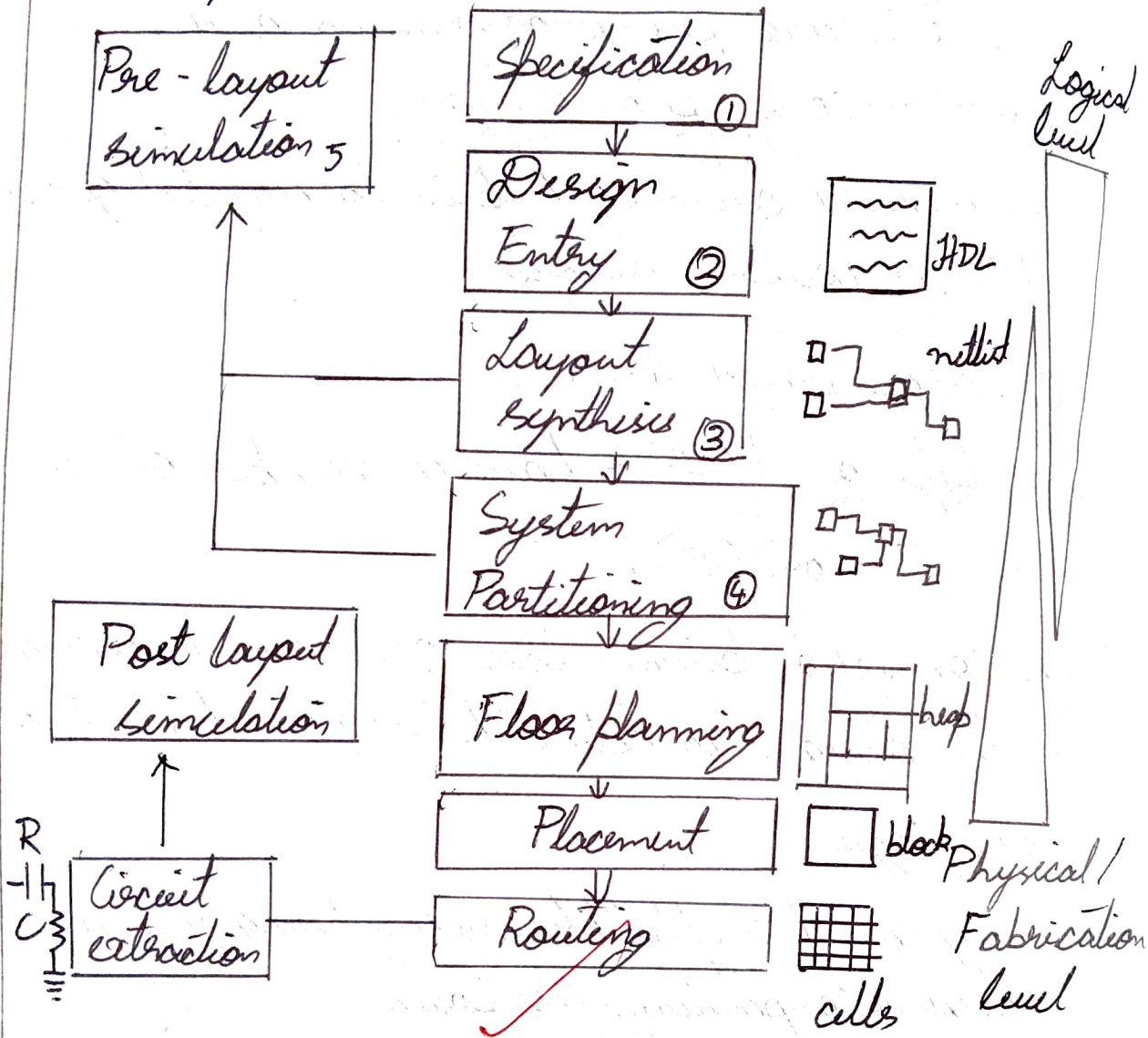3. The steps involved in ASIC design process is



i) **Specification**: The specific application and purpose of the IC's is decided upon with additional usage like power or area constraints if any

ii) **Design Entry**: The design is entered into the design system in the form of a HDL Hardware Definition Language or Verilog

iii) **Layout Synthesis**: The software interprets these

programs in the form of basic components like (basic gates or flip flops.)

iv) The system Partition: The system is made to ~~the~~ shrink / scale down to the size of ASIC's and allow sufficient resources i.e power and area to it.

v) Floor planning: The efficient location of placing blocks are decided.

vi) Placement: The blocks and cells are placed in the appropriate areas to conserve area and power.

vii) Routing: Decides on the routing or paths of connections to be made

viii) Circuit Extraction: The required values of capacitance and resistance is calculated and displayed.

~~ix~~ ix) Pre-layout simulation: The calculation of the code - entered in the software works as required.

x) Post layout simulation: It determines if the ASIC's work as intended after fabrication



4
(a)

PLA

PAL

- It stands for Programmable Logic Array.
- It consists of both programmable AND circuits and OR circuits.
- It is more ~~expensive~~ expensive.
- It requires more power.
- Difficult to programmable the logic comparatively.

  - It stands for Programmable Array Logic.
- It consists of fixed ~~AND~~ OR circuits and programmable AND circuits.
- It is cheaper than PLA.
- It requires less power as compared to PLA.
- Easier to program logic as compared to PLA.



f(x)

4. (b) A 4-bit carry look ahead adder is designed such that it prevents the ripple effect or delay caused by the 4-bit ripple adder.
- Instead of propagating the carry, two terms called ~~carry~~ generate and propagate are calculated.

$$G_i = A_i \cdot B_i$$


$$P_i = A_i \oplus B_i$$

- These terms are then used to calculate the sum

$$C_{i+1} = G_i + (P_i C_i)$$

$$C_2 = G_1 + (P_1 C_1) = G_1 + (P_1 (G_0 + (P_0 C_0)))$$

$$\therefore C_{i+1} = G_i + (P_i C_i)$$

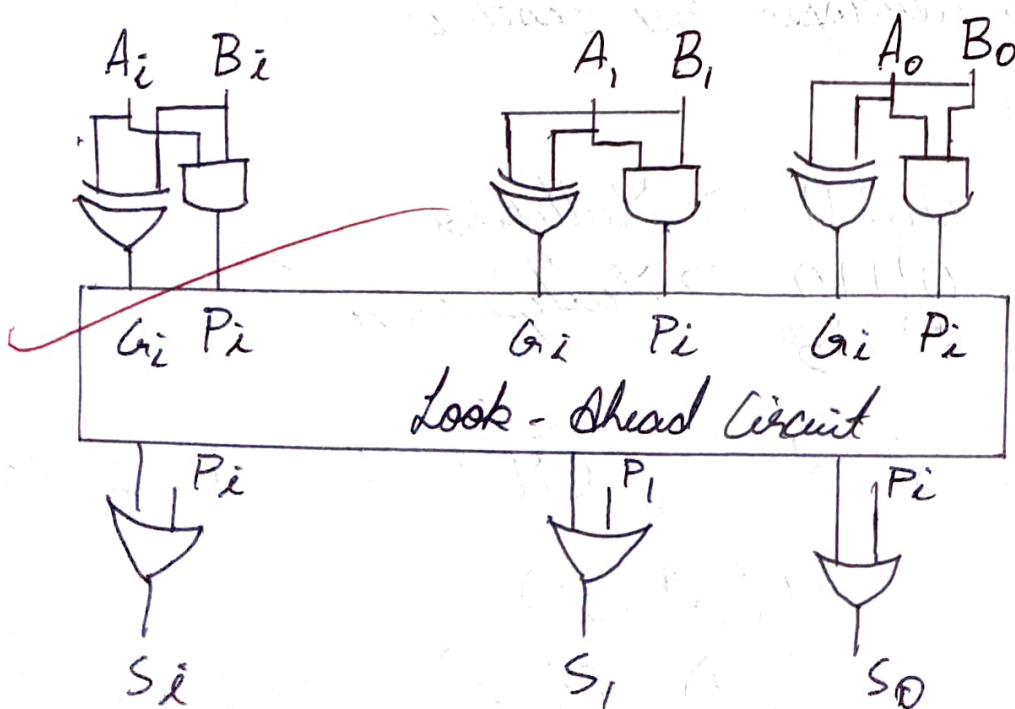

Advantages:

- i) It cuts down on the ripple effect and prevents delay
- ii) It is scalable and can accommodate n bits
- iii) Easy circuit for 4 bits adder look ahead

Disadvantages

- i) It becomes complex as the number of bits increases
- ii) A large number of gates need to be considered or implemented.

5 Booth's Algorithm is a method for multiplying two binary numbers if they have consecutive One's

It was developed by Booth in 1959

Consider

$$(M) = 01011 \rightarrow \text{Multiplier}$$

$$(Q) = 01110 \rightarrow \text{Multiplicand}$$

$$\begin{matrix} & 4 & 3 & 2 & 1 & 0 \\ 2 & 2 & 2 & 2 & 2 & 2 \end{matrix}$$

$$Q = 2^4 - 2^1$$

$$(\overline{M}) = 10101 \text{ (2's complement)}$$

$$M \times Q = M(2^4 - 2^1)$$

$$= 2^4(M) - M(2^1) = 2^4(M) + 2^1(\overline{M})$$

$$2^4(M) = 010110000 \rightarrow 4 \text{ 0's } (2^4)$$

$$2^1(\bar{M}) = 101010 \rightarrow 1 \text{ 0 } (2^1)$$

$$\begin{array}{r}
 2^4(M) = 010110000 \\
 + 2^1(\bar{M}) = \boxed{111101010} \xrightarrow{\text{Pushed to right}} \\
 \hline
 \leftarrow \cancel{201001000} \quad \text{MSB copied} \\
 \times 010011010
 \end{array}$$

\therefore The final answer is 010011010

i) First the number with the consecutive 1's are made the Multiplier

ii) The negative sign is made the 2's complement

The number

$$M = 2^{i+1} - 2^j$$

where i is the position of MSB 1 and j is the position of LSB 1

iii) The power multiplied with M is the number of zeros to be added

iv) The number with the least number of bits is moved to the extreme right or LSB position

- v) The remaining left bits are the MSB of the number copied to all positions
- vi) The final answer is the sum of the two numbers.

Q5

Ans:

a) Simple Programmable Logic Device (SPLDs)


- The IC which has number of logic gates, flipflop which are configured to users to implement function is Programmable IC's
- The connections can be altered using Programming Process.
- Simple Programming Process is to use fuse
- Initially, All device has fuse intact.
- Programming the device by blowing the fuse along the path to be removing for creating connections.
- Simple Programmable device is ROM. Simplest ROM is PROM. An Electrically PROM uses MOS transistors, and changes can be made using high Voltage. It can be erased using another EPROM/ Exposing to UV light.
- Another ROM is Masked ROM which can be implemented on ASIC

SPLD'S


- 1) PROM → Programmable Read only Memory
- 2) PLA → Programmable Logic Array
- 3) PAL → Programmable Array Logic
- 4) GAL → Generic Array Logic


Device	AND AND Gate	OR- Gate
PROM	Fixed	Programmable
PLA	Programmable	Programmable
PAL	Programmable	Fixed
GAL	Programmable	Fixed

PLA


 


PAL

 


 

⇒ Programming Process

  


a) Before Programming

 

b) After Programming

Implement the following using PROM, PLA &

PROM

 

	A	B	C	F ₁
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	1

$$F_1 = \sum m(3, 5, 7)$$

$$F_2 = \sum m(4, 5, 7)$$


PLA

A \ BC	00	01	10	11
0		1		
1	1	1		


$$F_1 = AB + BC$$

A \ BC	00	01	11	10
0				
1	1	1	1	

$$F_2 = \bar{A}B + AC$$

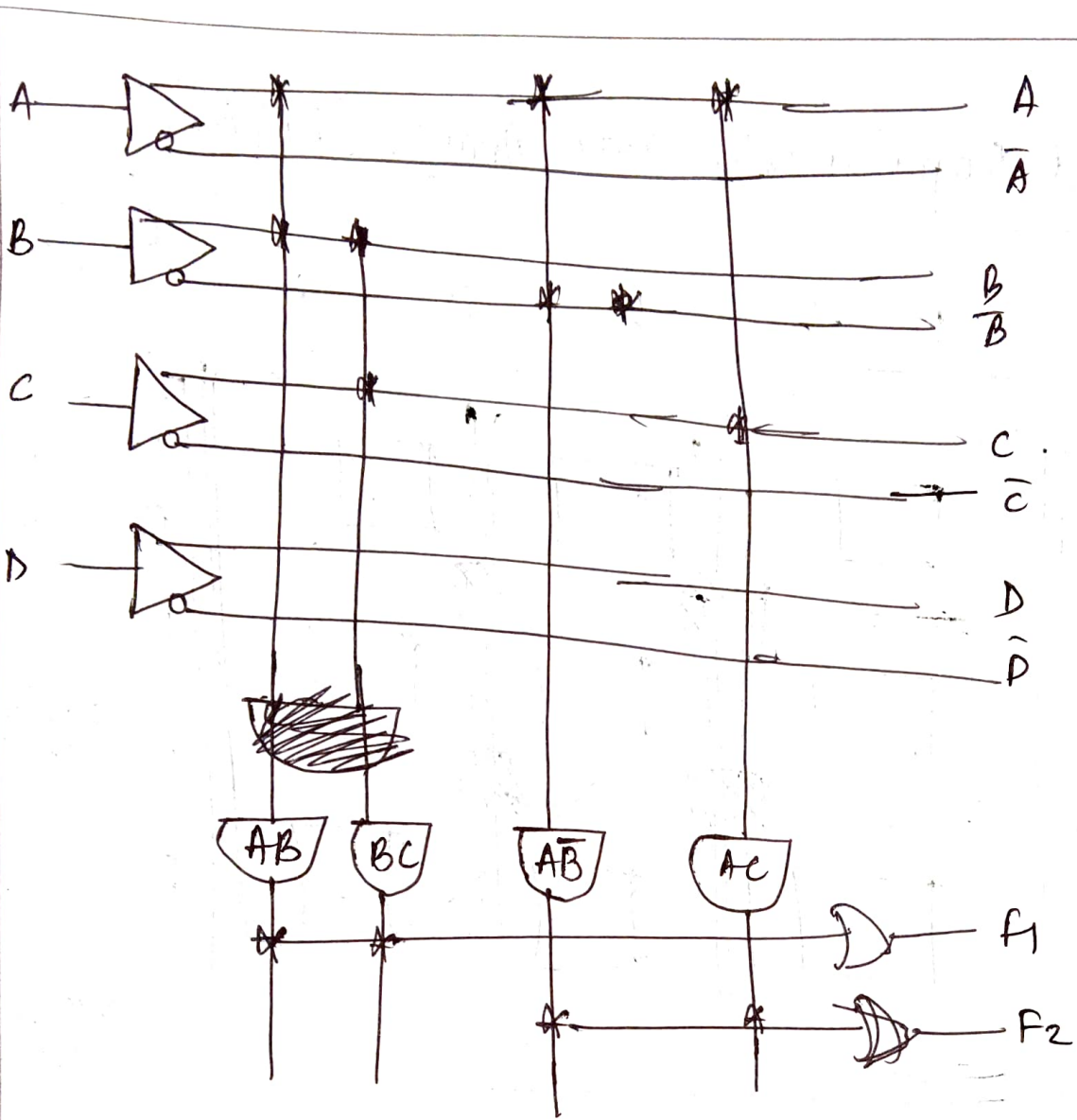


PAL

 

Q6)

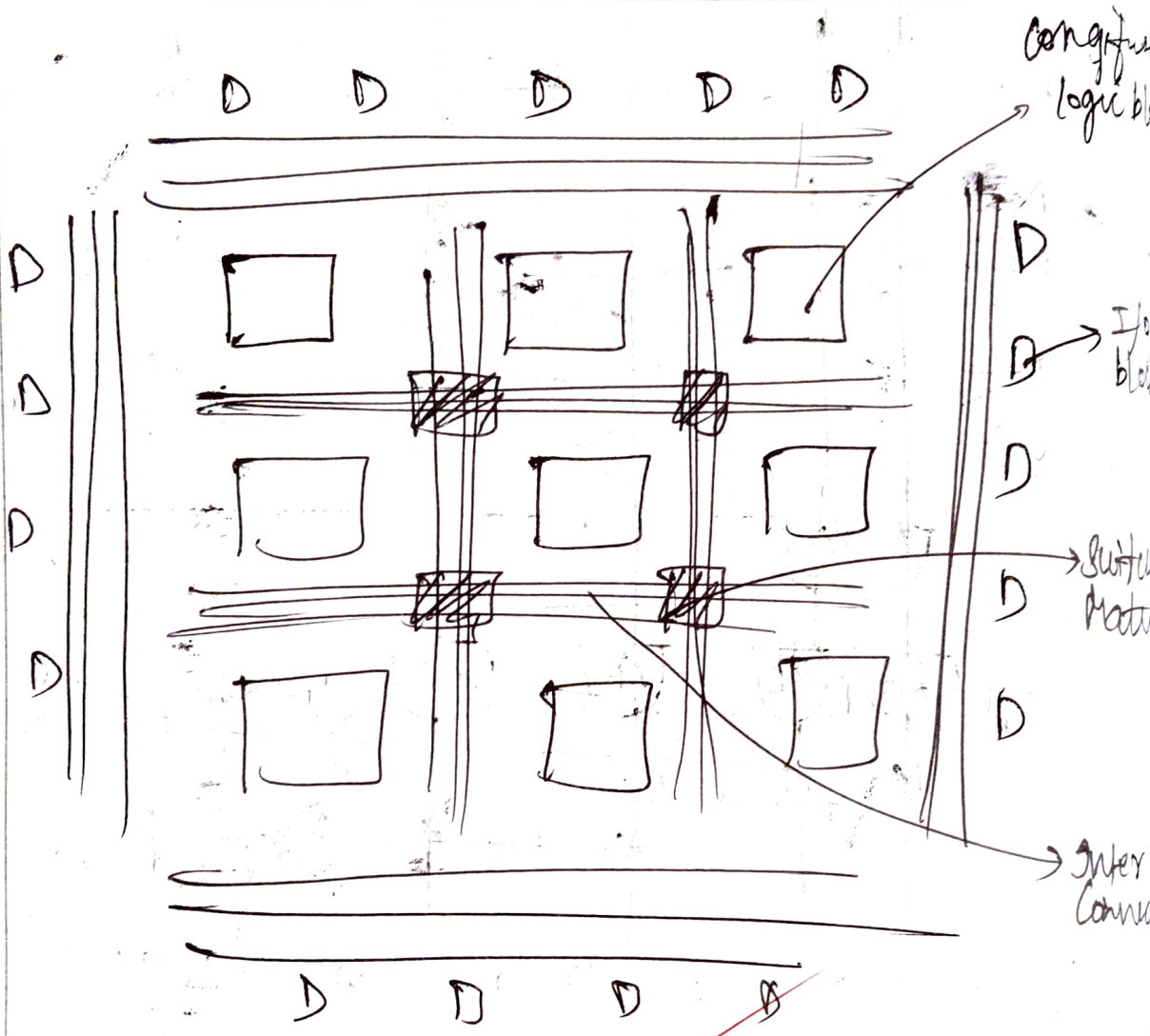b) Field Programmable Gate Arrays (FPGAs)



- FPGA's are 10 thousands to more than millions logic devices with Programmable Interconnect
- Programmable Interconnect provides user with its design the function easily
- Above shown is FPGA - block diagram

It has :

- 1) I/O blocks
- 2) Switch Matrix
- 3) Configurable logic block
- 4) Interconnected

1) I/O Block : It is used to communicate with external device. And for data transfer / or gathering data from external device


2) Switch Matrix : used to make paths with Interconnected

3) Configurable logic block : It is a fundamental block of FPGA and called as 'Heart of FPGA'. Because All the functions are implemented here.

~~It has 3 parts :~~ 1) Look up table

2) D-FF

3) MUX.

 

~~10~~
CLB

- Look-up table: It is a 4-i/p device which functions are implemented based on Truth table.
 - D-FF: It gives delayed version of o/p of LUT.
 - MUX: It selects either the direct o/p or delay o/p of LUT.
- 4) Interconnect: It is used to connect to CLB's, horizontally and vertically. It is spread over entire board for easy transfer of data.