

Design of a Synchronous Mod-6 Counter using

D flip-flops

Step 1 & 2: remains the same.

Step 3: Excitation Table.

Q_n	Q_n^{+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

\Rightarrow Whatever is the next State $Q_{n+1} = D$.

D	Q^+
0	0
0	1
1	0
1	1

Q_n	Q_n^+	D
0	0	0
1	0	1
0	1	0
1	1	1

$$\Phi_A = Q_B Q_C + Q_A Q_C$$

Φ_A

1	0	0	0
0	0	1	0
0	0	1	0
0	1	0	0

QR
QB QC

$$\Phi_B = Q_B Q_C + Q_A Q_B Q_C$$

Φ_B

1	0	0	0
0	0	1	0
0	0	1	0
0	1	0	0

QB
QC

Step 5: K-MAP

1	1	1	1	1	1	1	1
1	1	1	1	1	1	1	1
1	1	1	1	1	1	1	1
1	1	1	1	1	1	1	1
1	1	1	1	1	1	1	1
1	1	1	1	1	1	1	1
1	1	1	1	1	1	1	1
1	1	1	1	1	1	1	1

QA QB QC
QB QC

P.S N.S

Step 4: Transition Table


Q1's of FF

		<u>D_C</u>			
		00	01	11	10
Q _A	0	1	0	0	1
	1	1	0	X	X

$$D_C = \overline{Q_C}$$

Step 6:


Logic Diagram

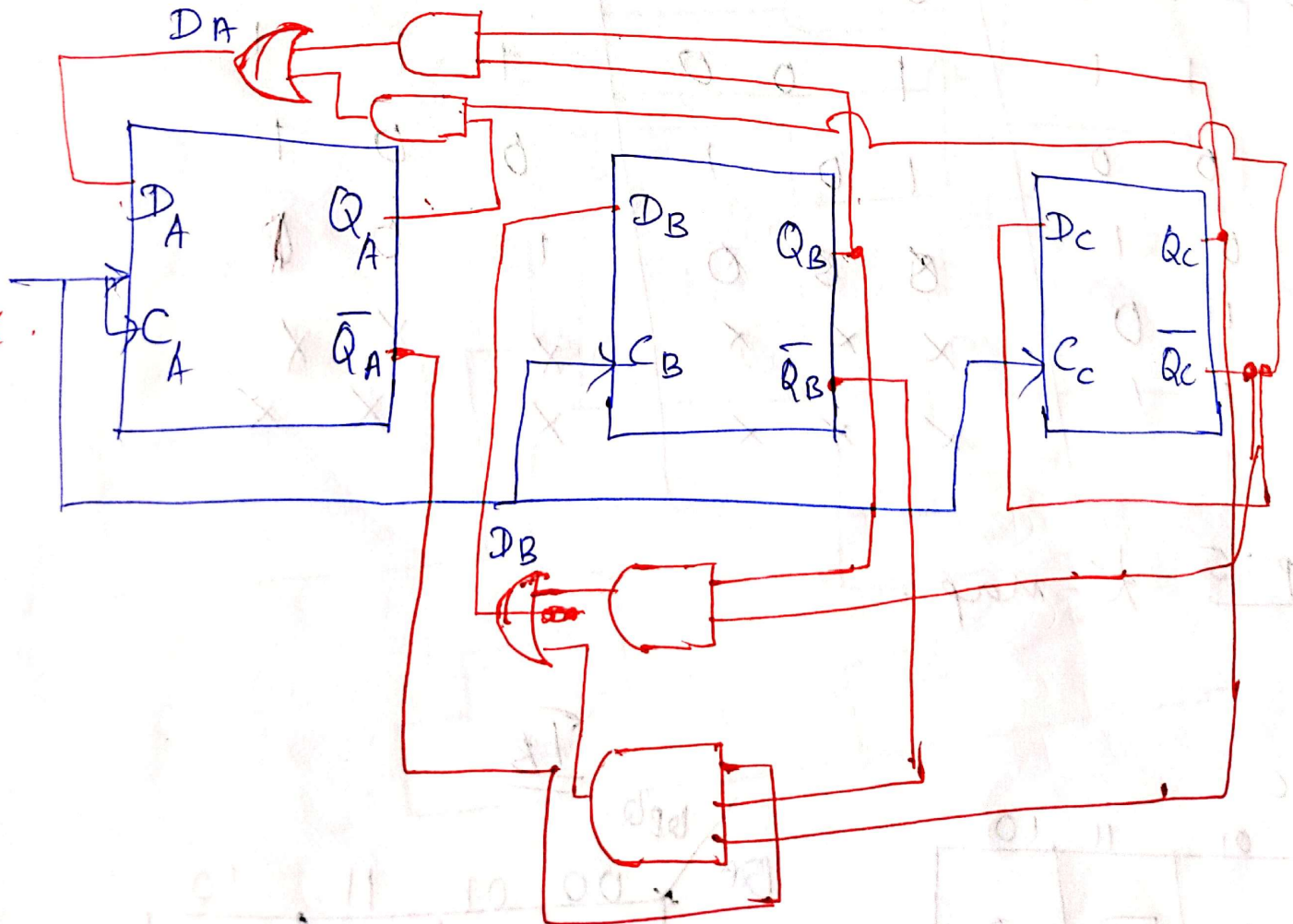

Bidirectional Shift Register :-

- The second general classification of shift registers consists of bidirectional shift register.
- These types of registers are capable of shifting their contents either left or right depending upon the signals present on appropriate control i/p lines.
- This register is also known as universal shift register.
- Depending upon the signal values on the select lines of the multiplexers, i.e. the mode control lines, the register can retain its current state, shift right, shift left or be loaded in parallel.
- These operations are based on the occurrence of a positive edge on the clock line.
- The register is cleared asynchronously if a logic 0 is applied to the line labelled CLEAR.
- When the select lines $S_1 S_0$ of the multiplexers are 01, the register performs shift right operation.


- The IP has the leftmost D flip flop is the signal on the serial-input for shift-right line, the IP is the second leftmost D flip flop is the 0IP of the leftmost D flip-flop, the IP has the third leftmost D flip flop is the 0IP of the second leftmost D flip-flop. The IP to the fourth leftmost D flip flop is the 0IP of the third leftmost D flip-flop.
- Upon the occurrence of the positive-edge signal on the clock line, the register shift its contents one position to the right. (refer fig 6.28, 6.29)

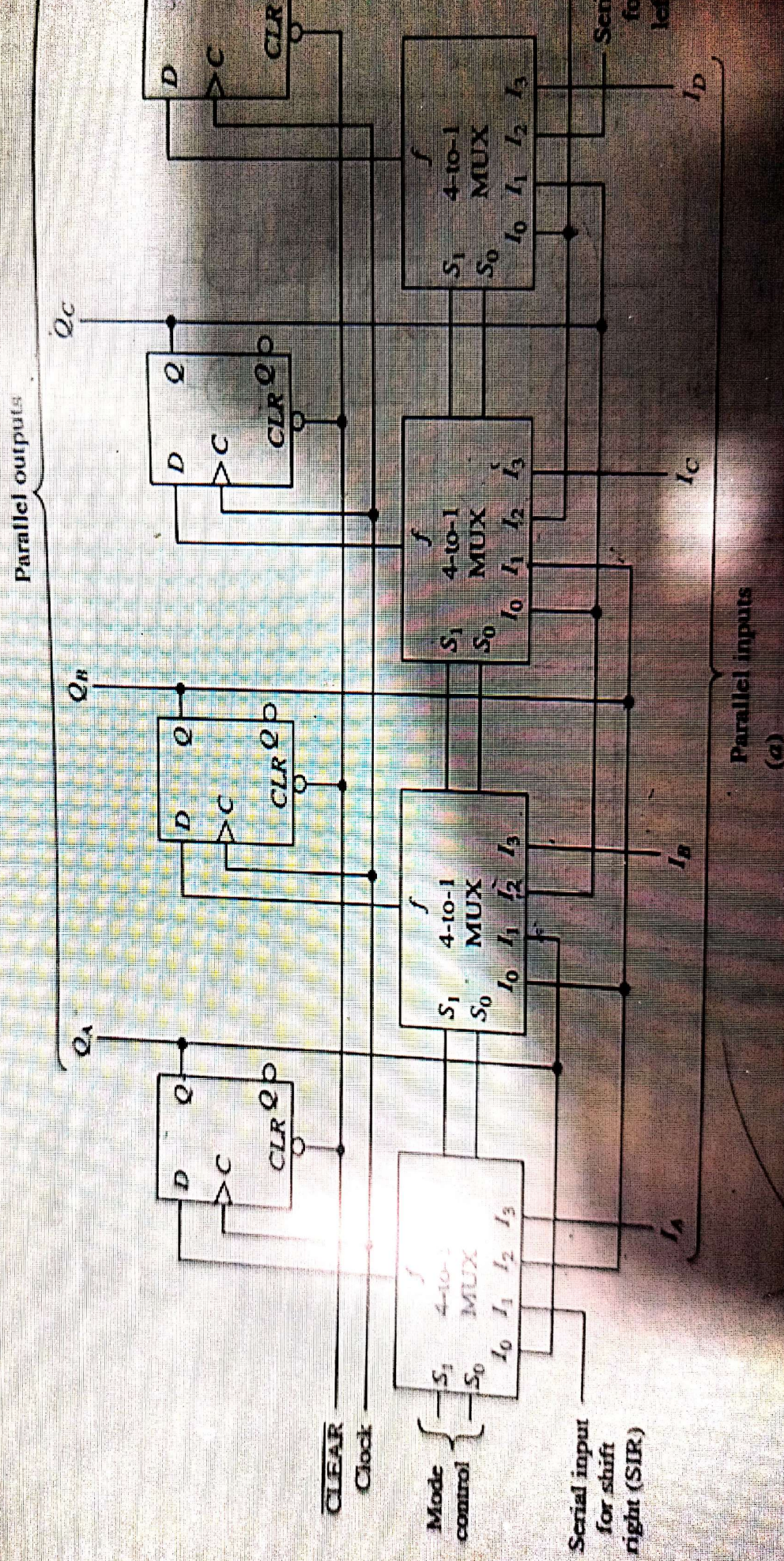

Parallel inputs (a)

Select lines	Register operation
S_1 S_0	
0 0	Hold
0 1	Shift right
1 0	Shift left
1 1	Parallel load

(b)

 

(c)

Figure 6.29 Universal shift register. (a) Logic diagram. (b) Mode control. (c) Symbol

Verilog Data Types

The several data types are nets, registers, vectors, integer, real, parameters and arrays.

Nets:

It is declared by the predefined word wire.

Nets have values that change continuously by the circuits that are driving them.

Verilog Data Types

- Nets:

It is declared by the predefined word **wire**.

It supports 4 values

Value	Definition
0	Logic 0 (false)
1	Logic 1 (true)
X	unknown
z	High impedance

Example:

```
wire sum;
```

```
wire S1 = 1'b0;
```

Verilog Data Types

Registers:

- It store values until they are updated.
- It is a data storage elements.
- It is declared by the predefined word reg.
- It supports 4 values of register.

Value	Definition
0	Logic 0 (false)
1	Logic 1 (true)
X	unknown
z	High impedance

Verilog Data Types

- Vectors:
- Vectors are multiple bits
- Register or net can be declared as a vector.
- Vectors are declared by brackets

Examples:

```
Wire [3:0]a=4'b1010;
```

```
Reg[7:0]total=8'd12;
```

Verilog Data Types

Integers:

- It is defined by a predefined word integer.

Real:

- Real (floating-point) numbers are declared with predefined word `real`.
- Example:

1. 2.4,56.3 and 5×10^{12}

Verilog Data Types

- Vectors:
- Vectors are multiple bits.
- A register or a net can be declared as a vector.
- Vectors are declared by brackets [].
- Example:
 - Wire [3:0] a = 4'b1010
 - Reg [7:0] total = 8'd12;
 - First statement declares the net a. It has 4 bits and the values are 1010

Verilog Data Types

Parameters:

- It represents the global constants.
- It is declared by the predefined word parameter.
- Example:

```
Module compr(X,Y,Xgty,Xlty,Xegy)
```

```
Parameter N=3;
```

```
Input [N:0] X,Y;
```








```
Output Xgty,Xlty,Xegy;
```

```
Wire [N:0] sum, yb;
```

OPERATORS

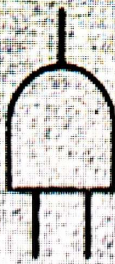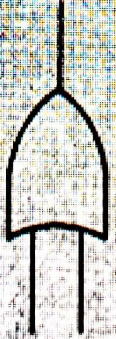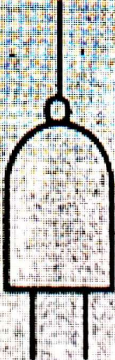- Logical: AND, OR and XOR
- Relational: Express relation between the objects. It includes equality, Inequality, less than, less than or equal, greater than or greater than or equal.
- Arithmetic
- Shift: To move the bits of an object in a certain direction, right or left

Verilog Bitwise Logical Operators

Operator	Equivalent Logic	Operand Type	Result Type
<code>&</code>		Bit	Bit
<code> </code>		Bit	Bit
<code>~(&)</code>		Bit	Bit
<code>~()</code>		Bit	Bit
<code>^</code>		Bit	Bit
<code>~^</code>		Bit	Bit
<code>~</code>		Bit	Bit

Verilog Boolean logical operators

- Operator: &&, ||
- Operation: AND, OR
- Number of operands: two
- These operators operate on two operands and the result is false (0) and true(1)
- !x... ! Negation operator

TABLE 1.4 Verilog Reduction Logical Operators

Operator	Operation	Number of Operands
&	Reduction AND	one
 	Reduction OR	one
~&	Reduction NAND	one
~ 	Reduction NOR	one
^	Reduction XOR	one
~^	Reduction XNOR	one
!	NEGATION	one

Relational Operators

- Compare the values of two objects
- These operators operate on two operands and the result is false (0) and true(1)

Click to add title

TABLE 1.6 Verilog Relational Operators

Operator	Description	Result Type
==	Equality	0,1,x
!=	Inequality	0,1,x
===	Equality inclusive	0,1
!==	Inequality inclusive	0,1
<	Less than	0,1,x
<=	Less than or equal	0,1,x
>	Greater than	0,1,x
>=	Greater than or equal	0,1,x

Verilog Arithmetic Operators

TABLE 1.6 Verilog Arithmetic Operators

Operator	Description	A or B Type	Y Type
+	Addition $A + B$	A numeric B numeric	numeric
-	Subtraction $A - B$	A numeric B numeric	numeric
*	Multiplication $A * B$	A numeric B numeric	numeric
/	Division A / B	A numeric B numeric	numeric
%	Modulus $A \% B$	A numeric, not real B numeric, not real	numeric, not real
**	Exponent $A ** B$	A numeric B numeric	numeric
{,}	Concatenation $\{A, B\}$	A numeric or array B numeric or array	Same as A


Verilog Shift Operators

1.4.4.2 Verilog Shift Operators


Verilog has the basic shift operators. Shift operators are unary operators; they operate on a single operand. To understand the function of these operators, assume operand A is the 4-bit vector 1110. Table 1.10 shows the Verilog shift operators they apply to operand A.

TABLE 1.10 Verilog Shift Operators

Operation	Description	Operand A Before Shift	Operand A After Shift
$A \ll 1$	Shift A one position left logical	1110	110x
$A \ll 2$	Shift A two positions left logical	1110	10xx
$A \gg 1$	Shift A one position right logical	1110	x111
$A \gg 2$	Shift A two positions right logical	1110	xx11

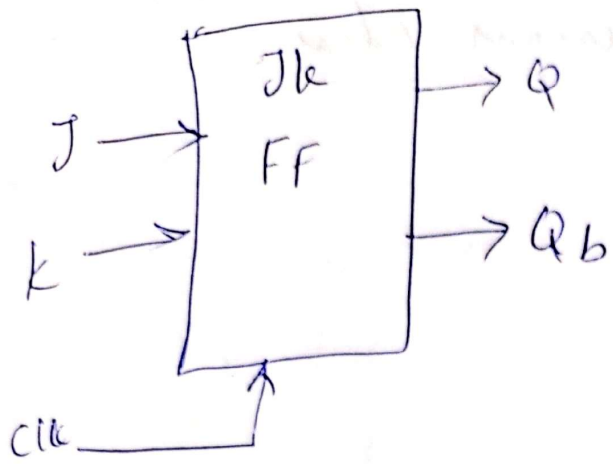

logic Symbol

 

State diagram

Verilog:

```
Module Jk-FF ( J,kJk, clk, q, qb)
```

```
input [1:0] Jk;
```

```
input clk;
```

```
output q, qb;
```

```
reg q, qb;
```

```
always @ (posedge clk)
```

```
begin
```

```
case (Jk)
```

```
2'd0 : q = q;
```

```
2'd1 : q = 0;
```

```
2'd2 : q = 1;
```


```
2'd3 : q = ~q;
```

```
end case
```

Behavioral Description of a 2x1 MUX

With Tri-state o/p

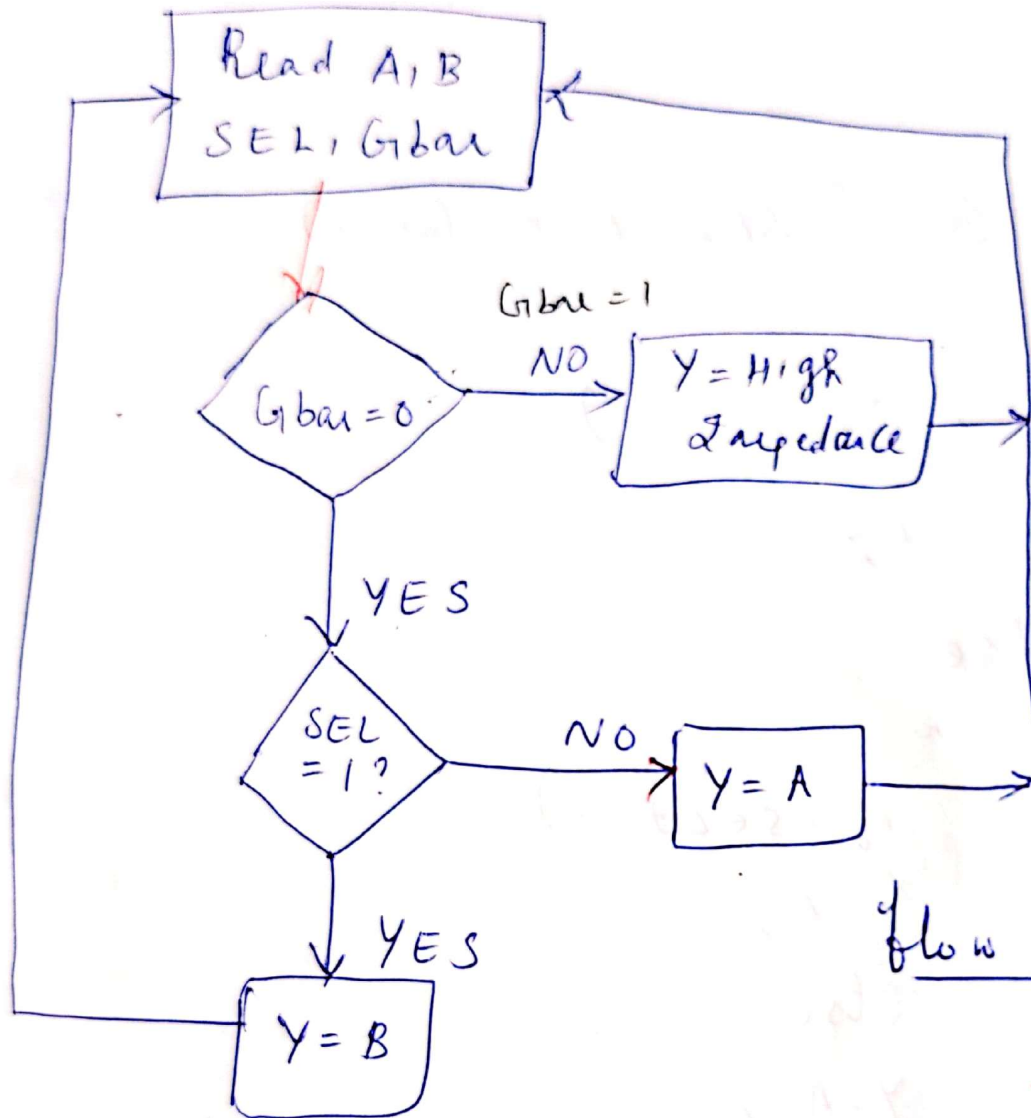
The behaviour is described by the flow chart



NSCAM

Flow chart of 2x1 MUX

Logic Symbol

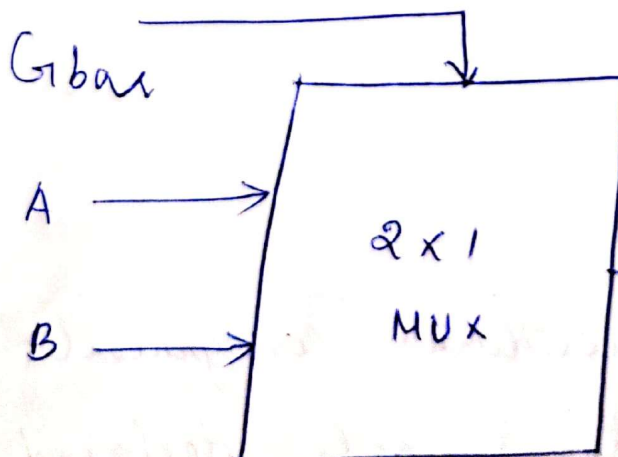

TT		AB	Y
Gbar	sel		
0	1	Z	Z
0	0	B	B
1	0	A	A

Verilog 2x1 MUX using IF-ELSE

```
Module MUX_2x1 (A, B, SEL, Gbar, Y);  
input A, B, SEL, Gbar;  
output Y;  
reg Y;  
always @ (SEL, A, B, Gbar)  
begin  
    if (Gbar == 1)  
        Y = 1'bZ;  
    else  
        begin  
            if (SEL == 1)  
                Y = B;  
            else  
                Y = A;  
        end  
    end  
end  
endmodule
```

Note:- This a procedural assignments, used to

Verilog 2x1 Mux using else-if

```
module MUX2H (A, B, SEL, Gbar, Y);
```

```
input A, B, SEL, Gbar;
```

```
output Y;
```

```
reg Y;
```

```
always @ (SEL, A, B, Gbar)
```

```
begin
```

```
if (Gbar == 0 & SEL == 1)
```

```
begin
```

```
Y = B;
```

```
end
```

```
else if (Gbar == 0 & SEL == 0)
```

```
Y = A;
```

```
else
```

```
Y = 1'bZ; // Y is assigned to high impedance
```

```
end
```

```
endmodule.
```

(Simulation waveforms from textbook).

Verilog Behavioral Description

```
module half_add (I1, I2, O1, O2);  
  input I1, I2;  
  output O1, O2;  
  reg O1, O2;  
  always @ (I1, I2)  
  //The above abatement is always construct  
  //The module consists of always construct  
  begin  
    #10 O1 = I1 ^ I2;  
    #10 O2 = I1 & I2;  
  end  
endmodule
```

Example 2

```
verilog Structural Description  
module system(a, b, sum, cout);  
input a, b;  
output sum, cout;  
xor X1(sum, a, b);  
//The above statement is EXCLUSIVE-OR gate  
and a1(cout, a, b);  
//The above statement is AND gate  
endmodule
```

Example 3

```
Verilog Data-Flow Description  
module halfadder (a, b, s, c);  
input a;  
input b;  
output s;  
output c;  
    assign s = a ^ b;  
    assign c = a & b;  
/* The module has no always, gate  
   tranifo, tran, or tranifo*/  
endmodule
```

Shift Registers

- Registers that are capable of moving information positionwise upon the occurrence of a clock signal is called Shift Registers.
- These registers are normally classified by whether they can move the information one or two directions, i.e. unidirectional or bidirectional.
- The manner in which the informations are entered into and outputted from a register is another way in which they are categorized.
 - There are two basic ways in which these transfers are done:
 - Serially or in parallel.
- When information is transferred in parallel, all the 0-1 symbols that comprise the information are handled simultaneously in a single unit of time. Such information transfer requires as many lines as symbols being transferred.
- The Serial handling of information

Shift Registers

- Registers that are capable of moving information positionwise upon the occurrence of a clock signal is called Shift Registers.

- These registers are normally classified by whether they can move the information in one or two directions, i.e. unidirectional or bidirectional.

- The manner in which the informations are entered into and outputted from a register is another way in which they are categorized.

- There are two basic ways in which these transfers are done:
Serially or in parallel.

- When information is transferred in parallel, all the 0-1 symbols that comprise the information are handled simultaneously in a single unit of time. Such information transfer requires as many lines as symbols being transferred.

- The Serial Handling of information

of the information in a linear sequence. It requires only a single line to perform the transfer.

Thus, there are four possible ways registers can transfer information:

- 1) Serial-in / Serial out.
- 2) Serial-in / Parallel out.
- 3) Parallel-in / Parallel out.
- 4) Parallel-in / Serial out.

Serial-in, Serial-out Unidirectional Shift register

- It is constructed from positive edge-triggered D flip-flops.

- The Q output of each flip flop is connected to the D input of the next flip flop.

- The control inputs of all the flip flops are connected together to a common synchronizing signal called clock.

- Thus, upon the occurrence of a positive edge of the clock signal, the content of each flip flop is shifted one position to the right.

- The content of the left most flip flop the

Signal value on the serial-data-in line and the content of the rightmost flip-flop prior to the clock signal is lost.

- The output from the shift register occurs at the rightmost flip-flop on the serial-data-out line.

 


Figure:- Serial-in, Serial-out Unidirectional Shift Register

- If the initial content of the four flip-flops is 1011 and a logic-0 is applied to the serial-data-in line prior to the positive edge of the clock signal, then the content of the register becomes 0101 after the positive edge of the clock signal.

- The logic 0 becomes available on the serial-data-out line after four clock

- In some applications, the information within a register need be preserved, but only a recirculation is desired.

- To achieve this, serial-data-out line is connected to the serial-data-in-line.

- The content of the register is again shifted one position to the right upon the occurrence of each clock signal, but the state of the leftmost flip-flop is replaced by the state of the rightmost flip-flop.

- Example:-

1011

After Shifting 1101 Circular Shift Register

- Shift registers having this type of connection is called Circular Shift Register.

Note:-

The flip flops of a register are subject to a change in state while they are being interrogated by a next flip flop in the cascade connection.


A flip flop is simultaneously being read into while being read by another flip flop.

71 master-slave flip flop

- Latches are not appropriate, as their o/p's are subject to changes during the entire period in which they are enabled.

Serial-in, Parallel-out Unidirectional Shift Register

- O/p's are provided from each flip-flop.
- Once information is shifted into the register, i.e. Serial in, the information is available as a single entity i.e. parallel out, at the flip-flop O/p terminals.
- Since information is transferred into this register serially and after an appropriate number of shifts made available in parallel, this type of register is called Serial-to-parallel Conversion of information.

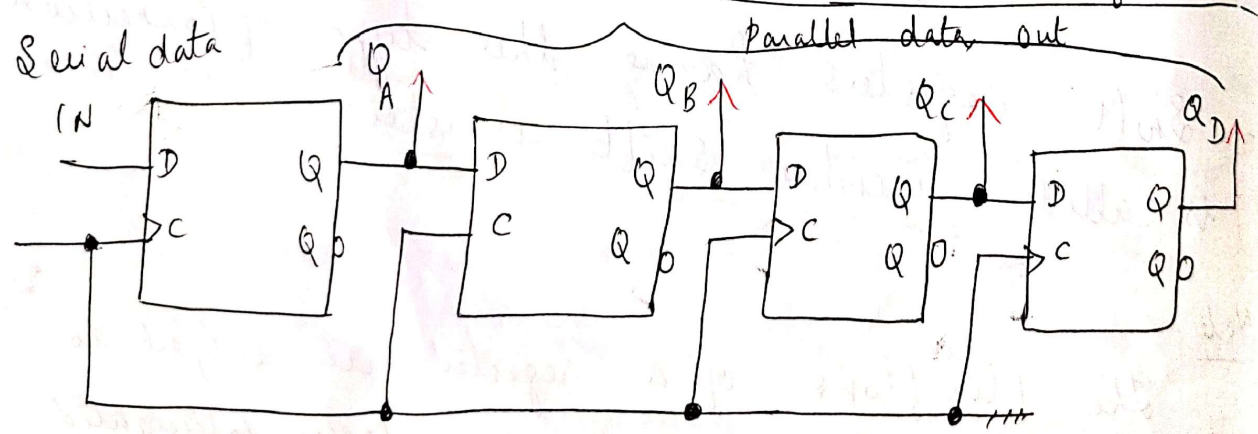

Parallel-in, Serial out Unidirectional Shift Register

- The operation is controlled by the load/Shift line.
- When a logic-0 signal appears on this

$I_A I_B I_C I_D$ are transferred into the register upon the occurrence of positive edge clock signal.


- Then, when logic 1 signal appears on the load/Shift line, the D-flip flop become a cascade connection that functions as a unidirectional shift register providing the serial o/p.
- In this way, it provides parallel-to serial conversion of information. (diagram from book)

Parallel-in, Parallel-out Unidirectional Shift Register

Register :-

- From the same diagram, if o/p's are taken from each individual flip flop, the register functions are parallel-in, parallel-out register.
- The same ckt will work as serial-in, parallel out & serial-in, serial-out register as well.

Parallel-IN, Serial Out : dgm

 



--	--	--	--	--	--	--	--	--	--

USN

Internal Assessment Test 2 – Dec.2024

Sub:	Digital System Design using Verilog			SubCode:	BEC302	Branch:	ECE	
Date:	13-12-2024	Duration:	90 Minutes	MaxMarks:	50	Sem/ Sec:	3/A,B,C,D	
<u>Answer any FIVE FULL Questions</u>								
1	Design a MOD-6 synchronous counter using clocked D flip flop							
2	Explain Universal shift register with neat diagrams.							
3	Illustrate with examples the data types used to define nets, registers, vectors and arrays.							
4	Explain verilog logical operators with examples.							
						MARKS	CO	RBT
						[10]	CO3	L3
						[10]	CO3	L2
						[10]	CO4	L2
						[10]	CO4	L2

X X

5	Write the verilog code for a Positive Edge-Triggered JK flip-flop using the CASE statement with the timing waveform.	[10]	CO3	L2
6	Write the Verilog code for 2*1 multiplexer using If-Else statement and Else-If statement using the below logic (i) when enable is low and selection line is high, the output is equal to input 2 (A) (ii) when enable is low and selection line is low, the output is equal to input 1 (B) (iii) If enable signal is high, the output reaches high impedance state (z)	[10]	CO3	L2
7	Write the Verilog code for the Half Adder using the data-flow description, behavioral and gate level description.	[10]	CO4	L2
8	Explain the different types of shift registers with neat diagram.	[10]	CO3	L2

Praveen Kumar
COURSE INSTRUCTORS

H. Praveen
HOD